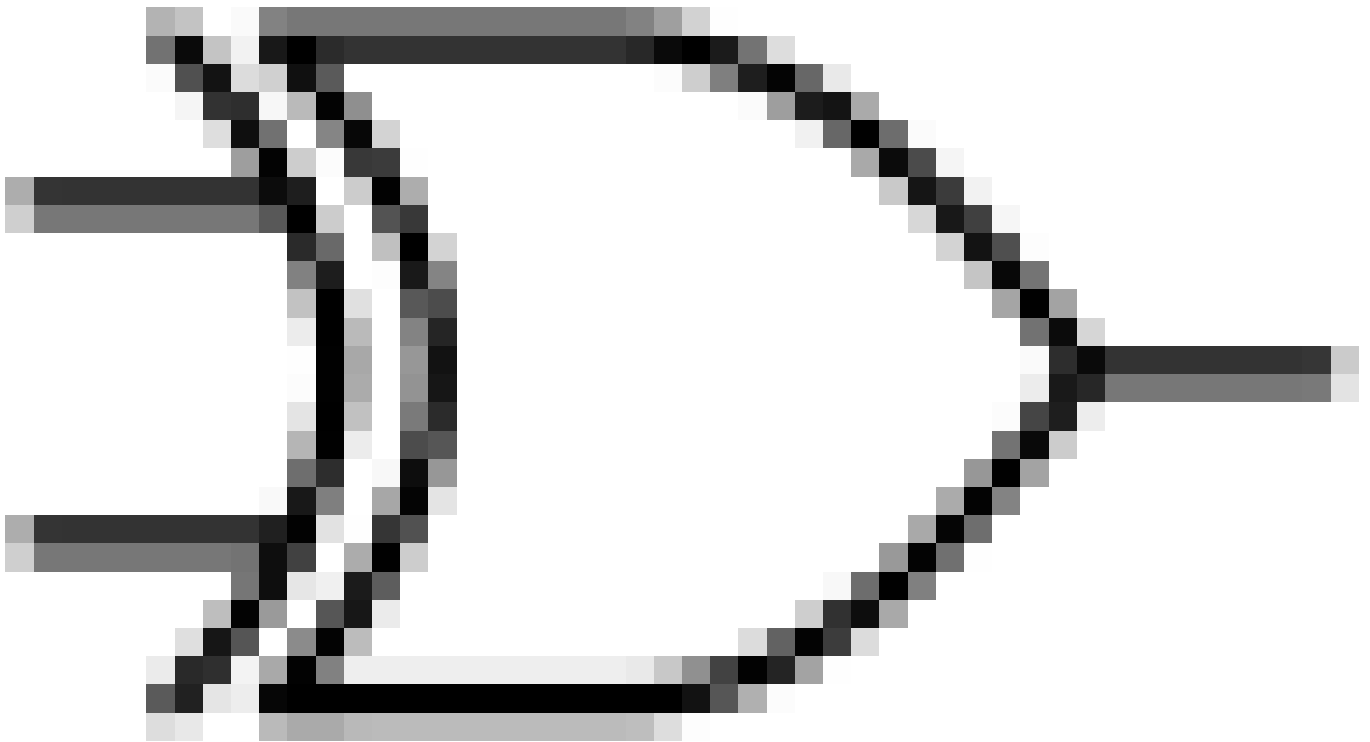


Question 1:

What is the output of the XOR gate with inputs 0, 0?



Options:


1. 0

2. 1

Correct Answer: 0

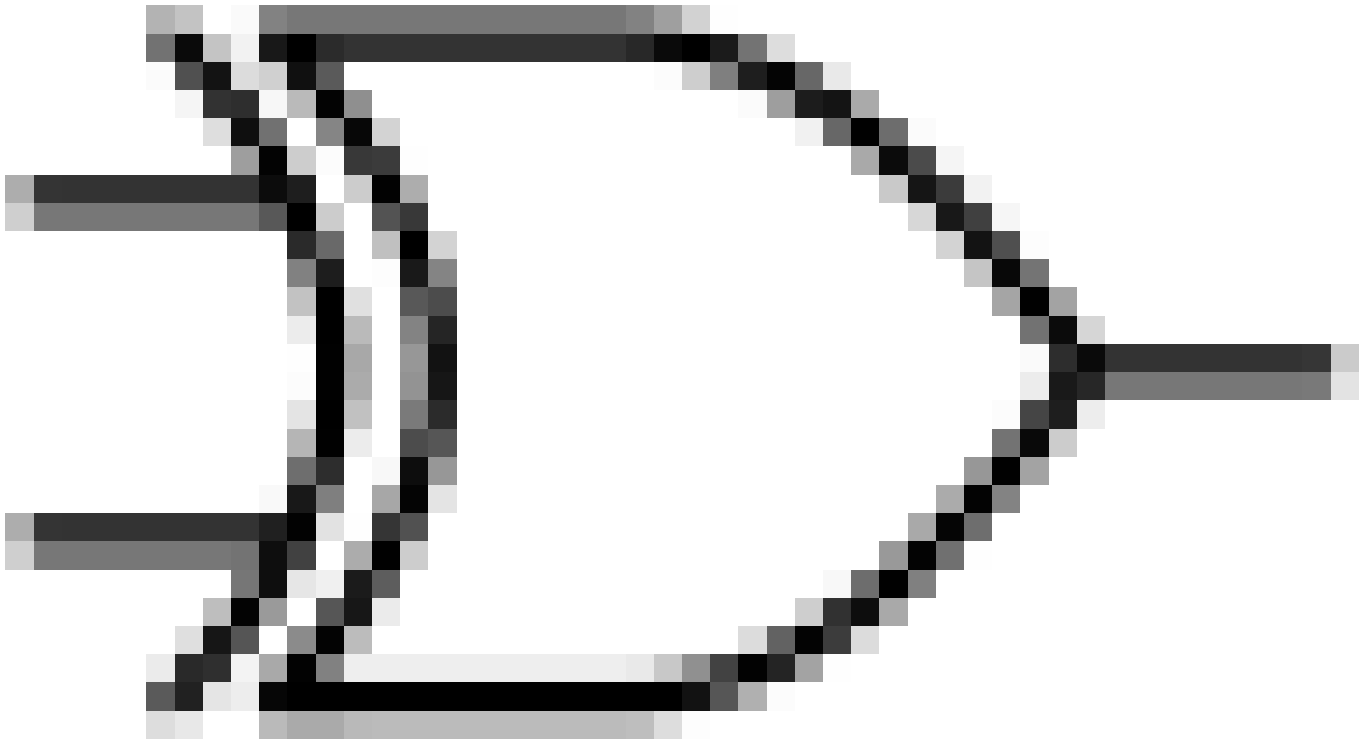Question 2:

What is the output of the XOR gate with inputs 0, 0?



Options:

1. 0

2. 1



Correct Answer: 0

Question 3:

Are these two circuits equivalent?

Expression 1: $(c \text{ nor } b)$

Expression 2: $(c \text{ nor } b)$

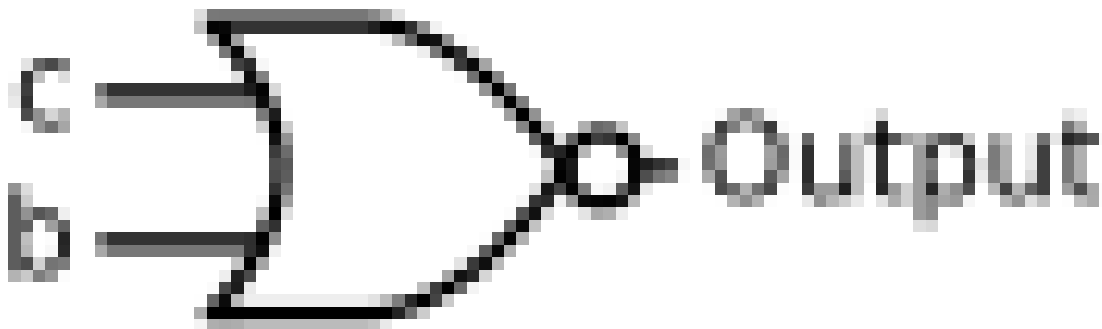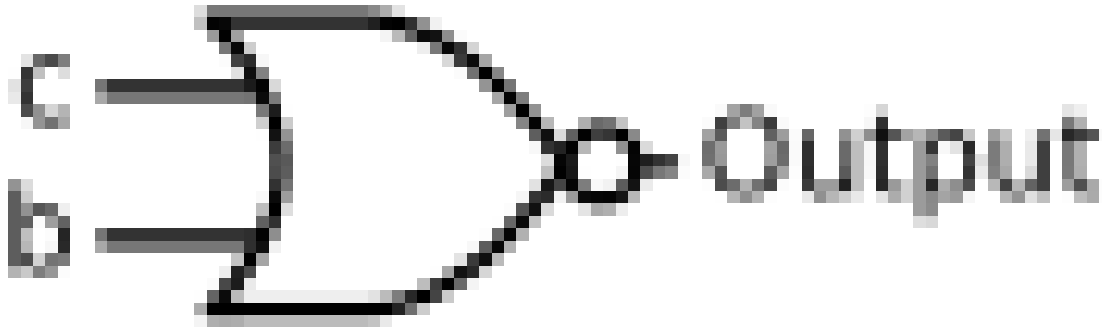

Options:

1. Yes
2. No


Correct Answer: yes

Question 4:

Are these two circuits equivalent?

Expression 1: $(c \text{ nand } b)$

Expression 2: $(c \text{ nand } b)$

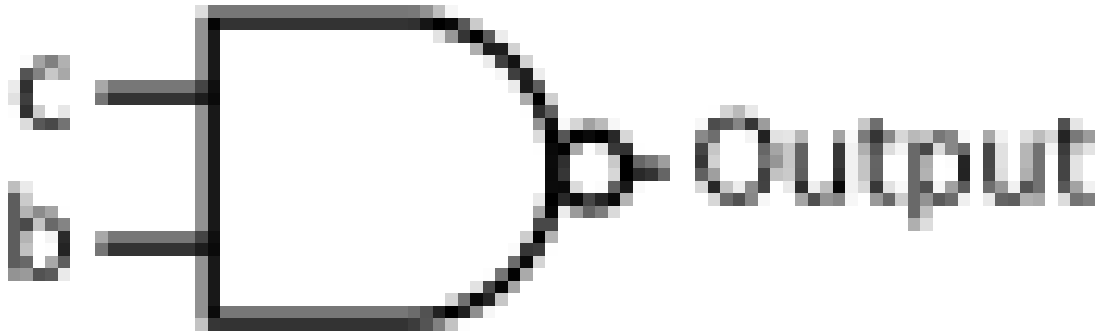

Options:

1. Yes
2. No



Correct Answer: yes

Question 5:

Are these two circuits equivalent?

Expression 1: $(a \text{ nand } c)$

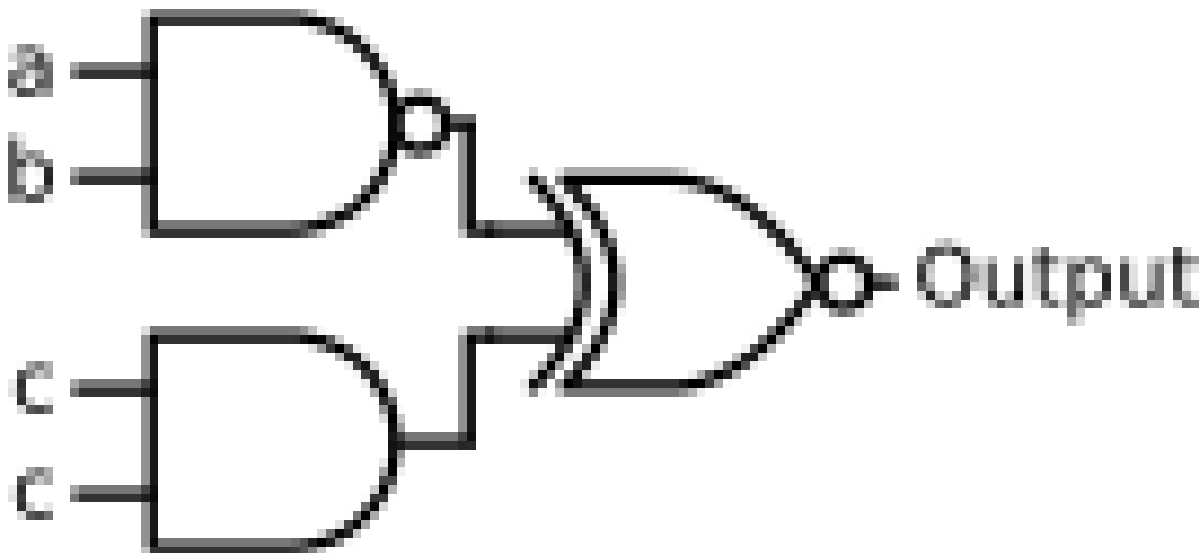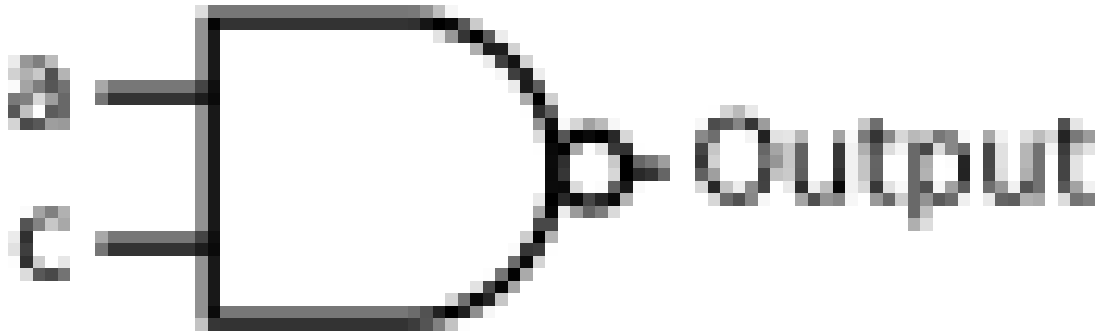Expression 2: $((a \text{ nand } b) \text{ xnor } (c \text{ and } c))$



Options:

1. Yes
2. No



Correct Answer: no

Question 6:

Are these two circuits equivalent?

Expression 1: $(\text{not } (c \text{ xnor } c))$

Expression 2: $(b \text{ xor } c)$

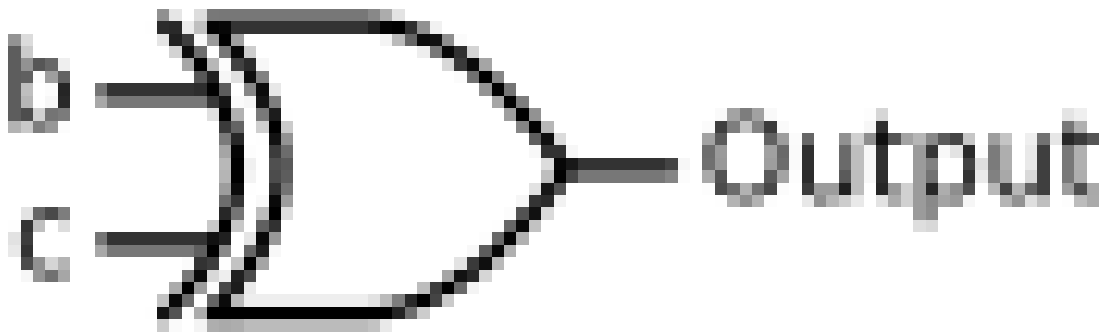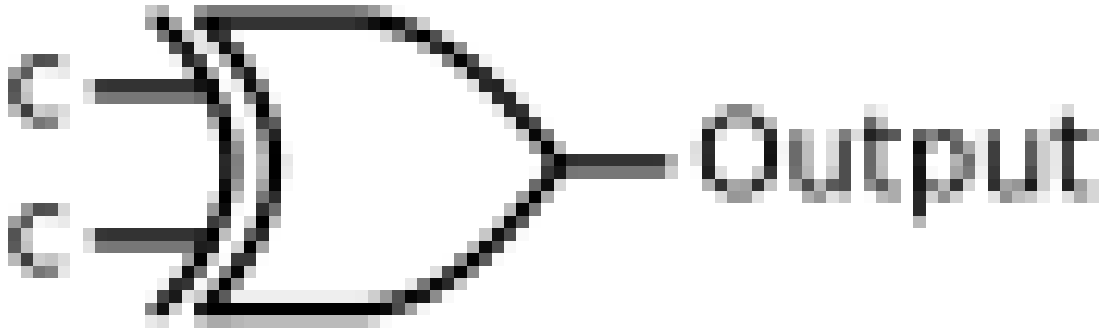

Options:

1. Yes
2. No


Correct Answer: no


Question 7:

Are these two circuits equivalent?

Expression 1: $((c \text{ nand } c) \text{ nand } (c \text{ xnor } a)) \text{ nor } ((b \text{ nand } b) \text{ and } (b \text{ nand } b))$

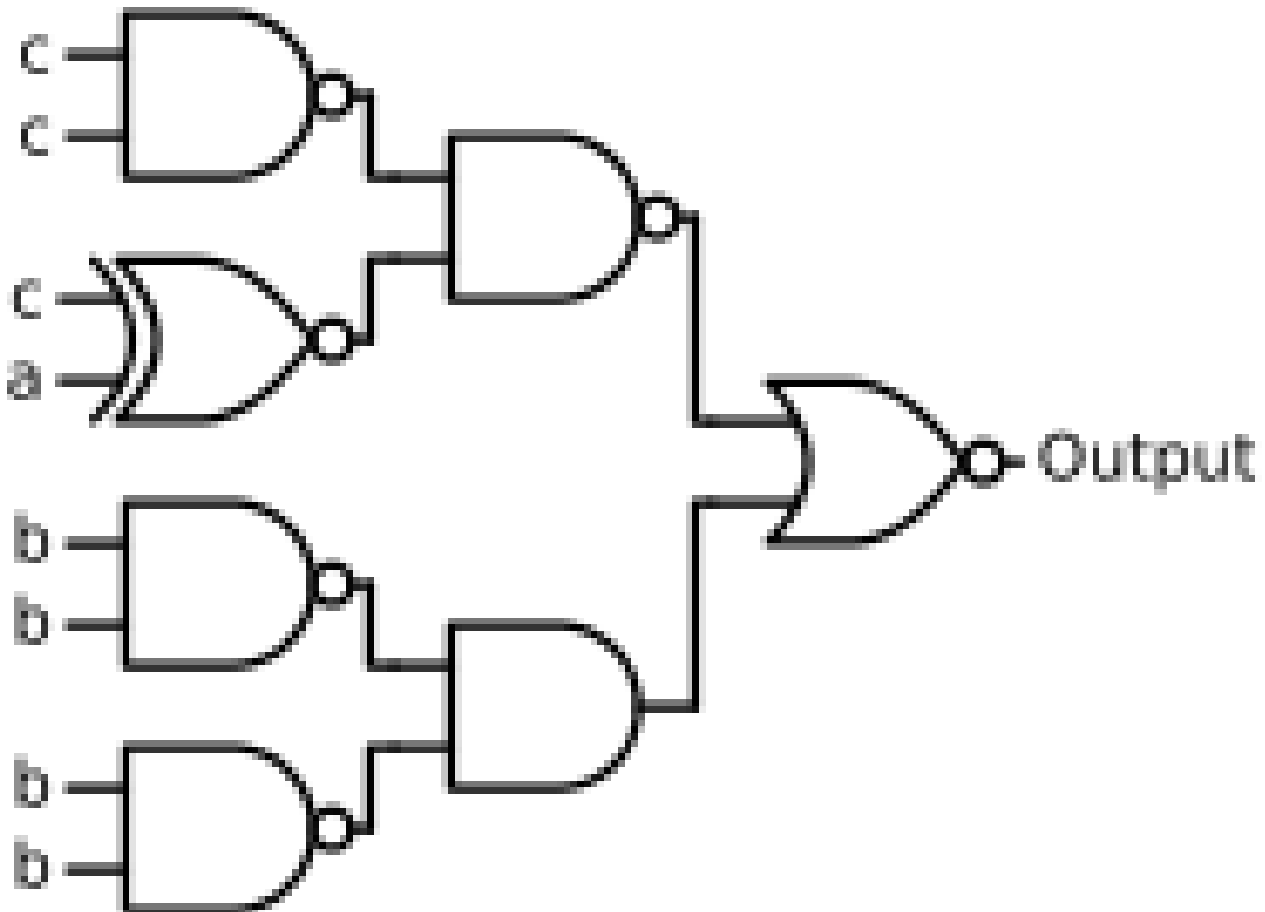Expression 2: $((c \text{ nand } c) \text{ nand } (c \text{ xnor } a)) \text{ nor } ((b \text{ nand } b) \text{ and } (b \text{ nand } b))$



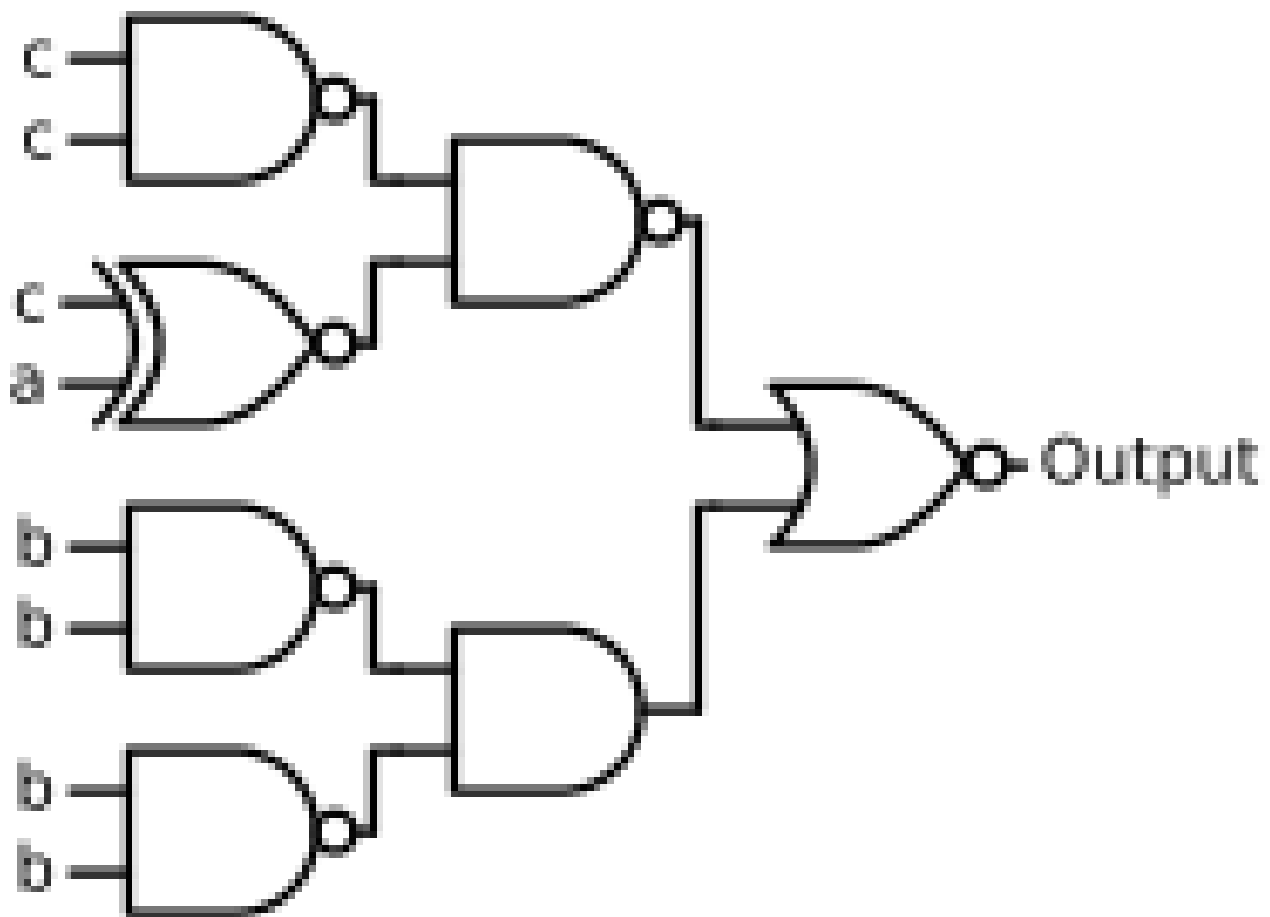

Options:

1. Yes
2. No


Correct Answer: yes


Question 8:

Are these two circuits equivalent?

Expression 1: $((b \text{ xnor } b) \text{ or } (b \text{ xor } a)) \text{ nand } ((c \text{ nor } b) \text{ nor } (c \text{ nand } b))$

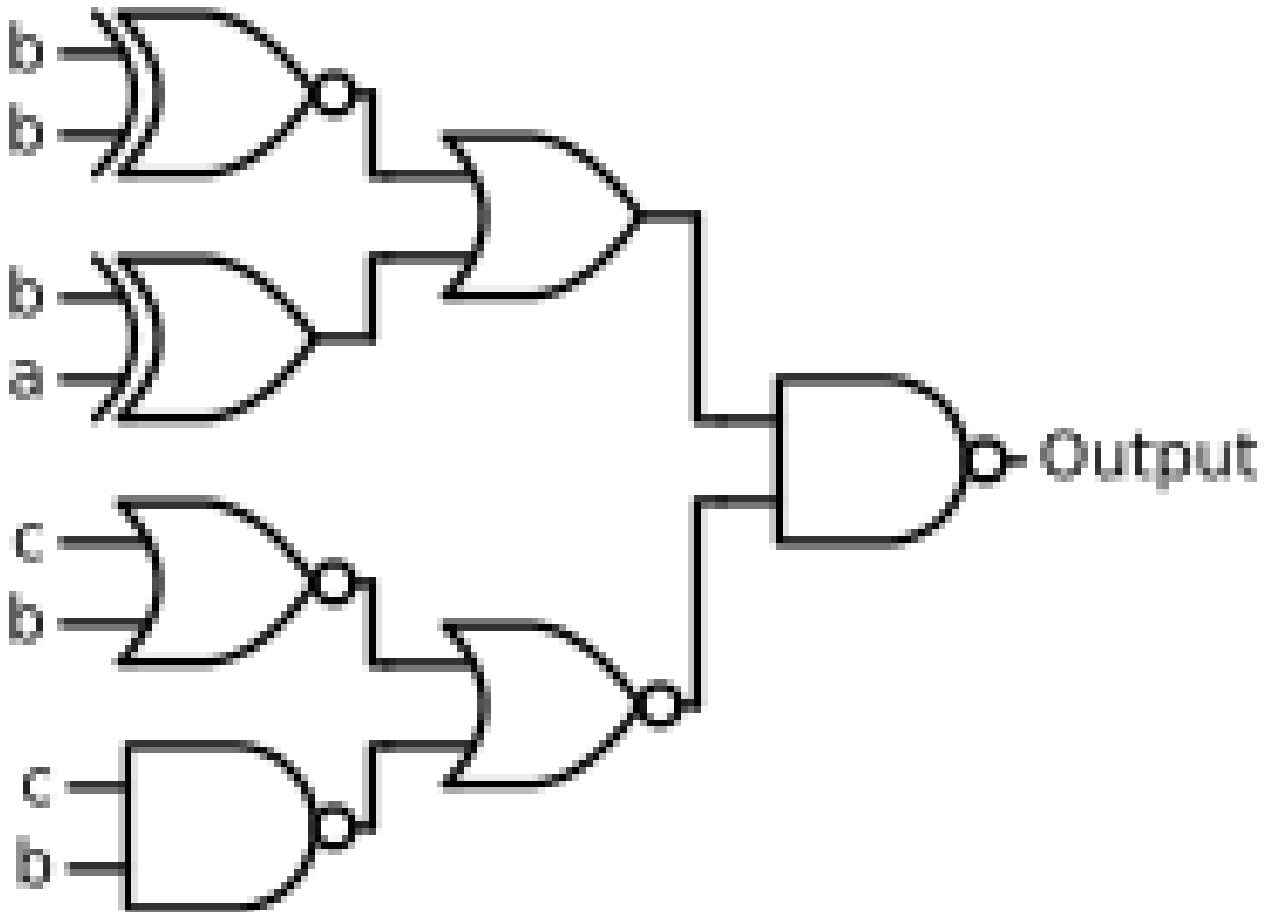Expression 2: $((b \text{ xnor } b) \text{ or } (b \text{ xor } a)) \text{ nand } ((c \text{ nor } b) \text{ nor } (c \text{ nand } b))$



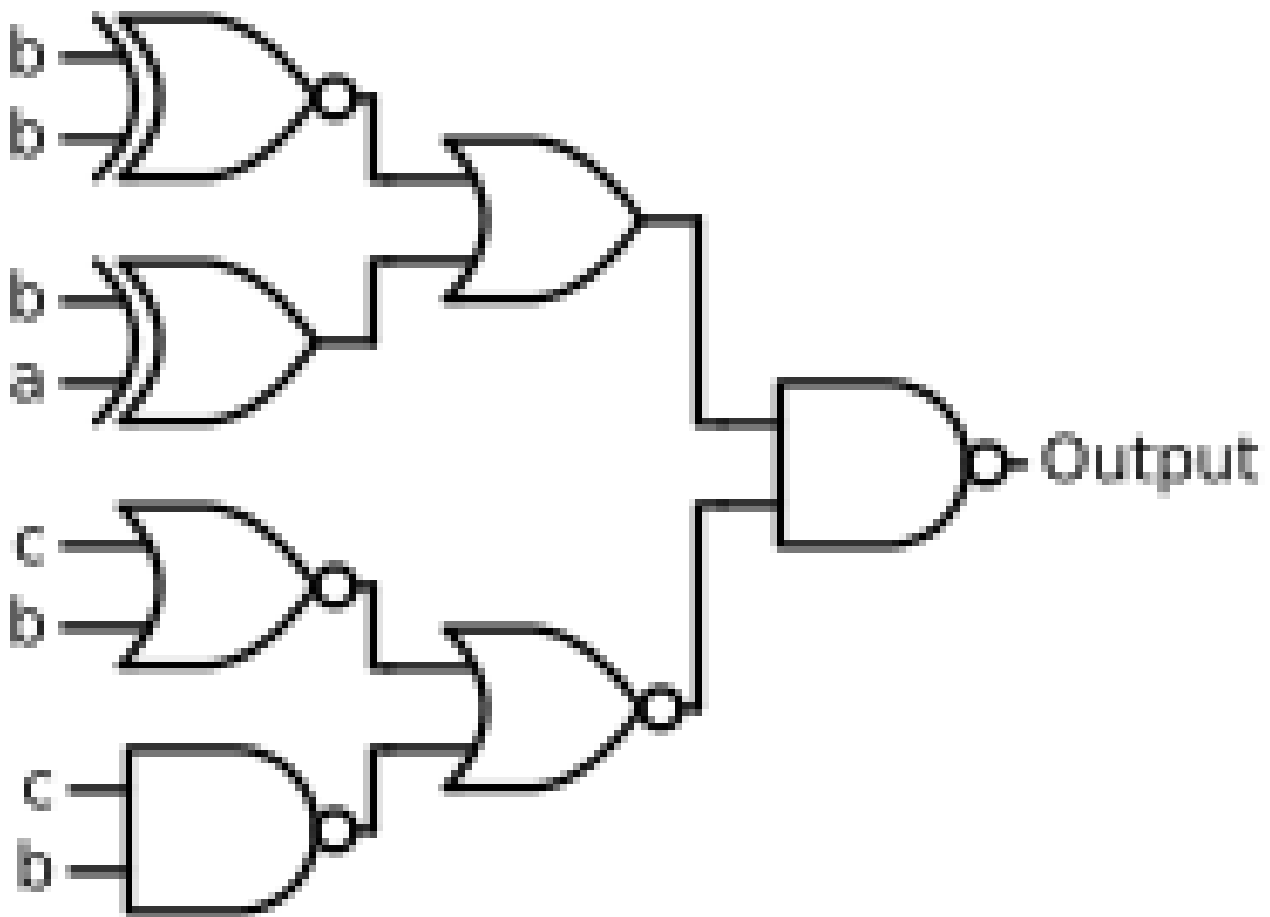


Options:

1. Yes
2. No

Correct Answer: yes

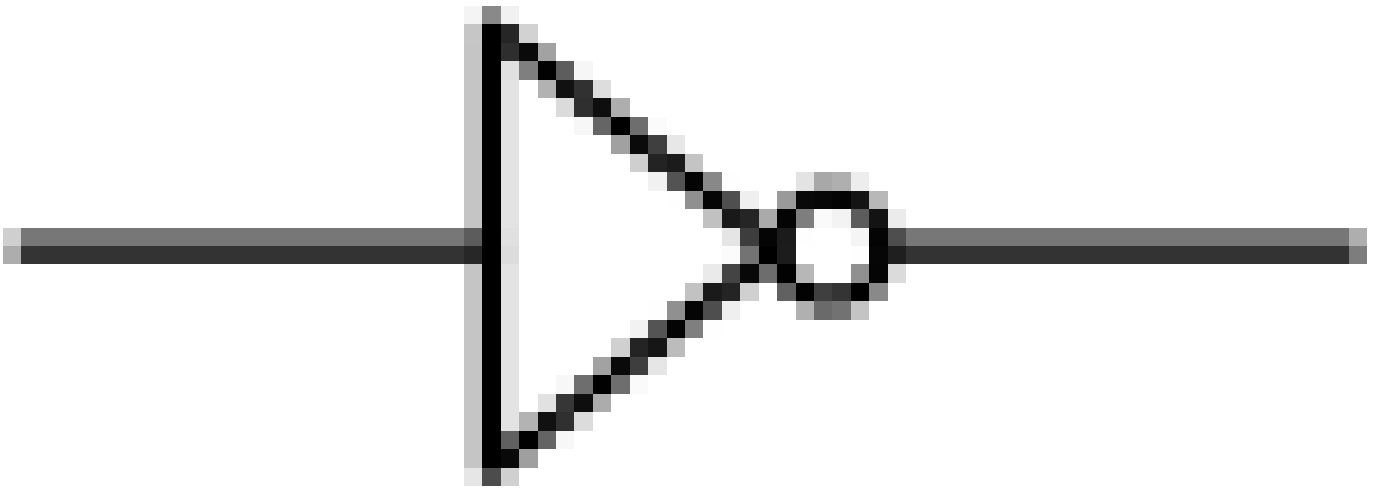Question 9:

What is the output of the NOT gate with input 1?



Options:


1. 1

2. 0

Correct Answer: 0

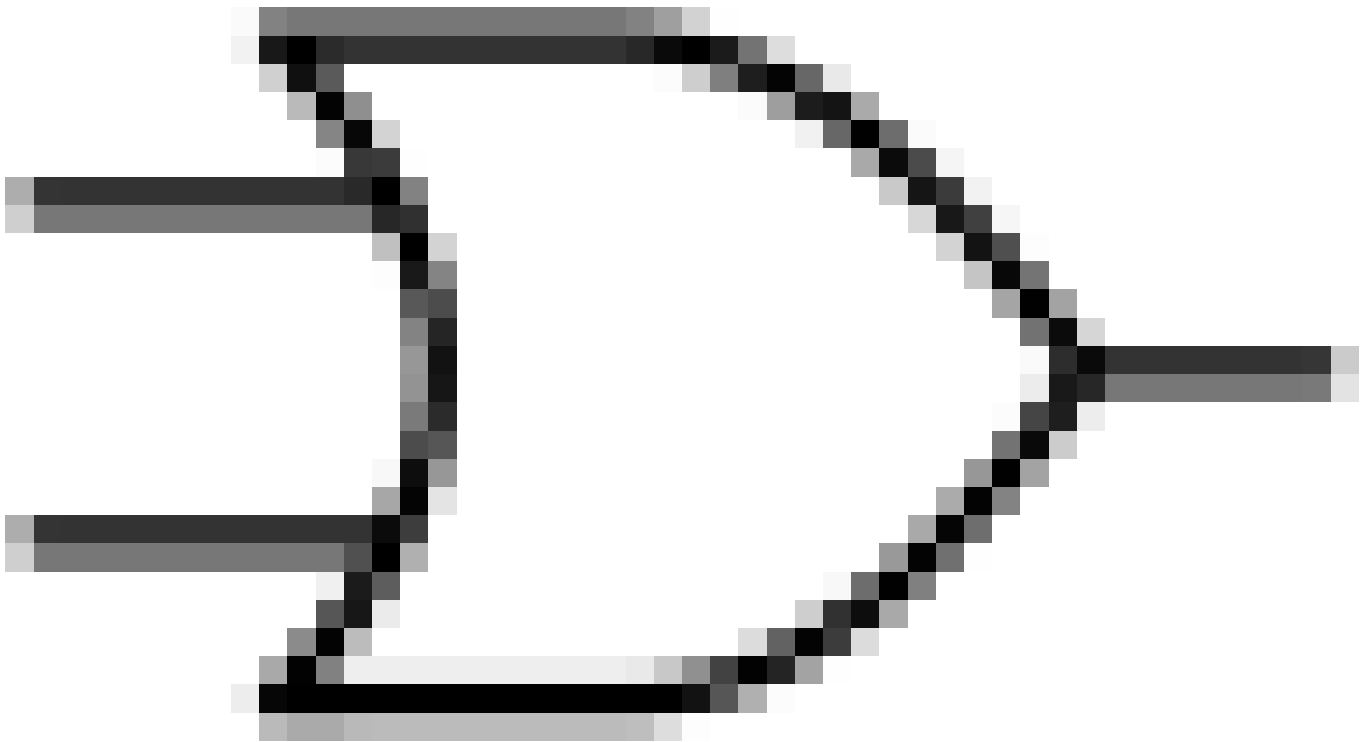Question 10:

What is the output of the OR gate with inputs 0, 1?



Options:

1. 1

2. 0



Correct Answer: 1

Question 11:

Are these two circuits equivalent?

Expression 1: $\neg(a \wedge b)$

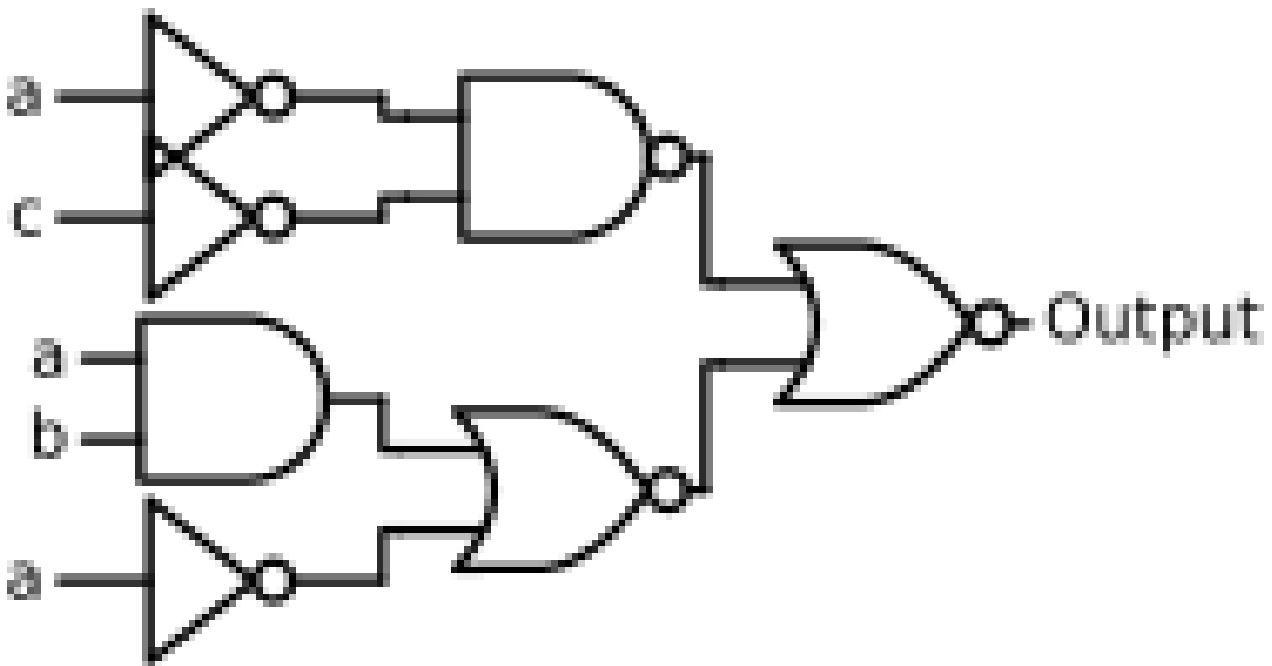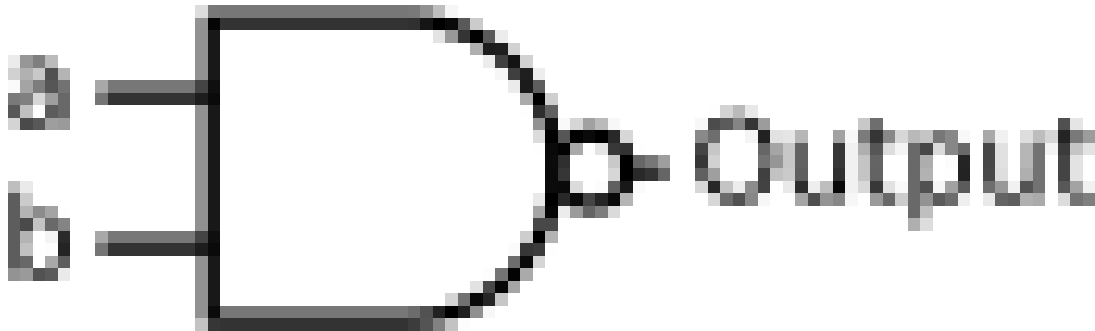Expression 2: $((\neg a \wedge \neg c) \vee ((a \wedge b) \vee \neg a))$



Options:

1. Yes
2. No



Correct Answer: no

Question 12:

Are these two circuits equivalent?

Expression 1: $((a \text{ or } c) \text{ or } (c \text{ xor } b)) \text{ xor } (\text{not } (b \text{ nand } c))$

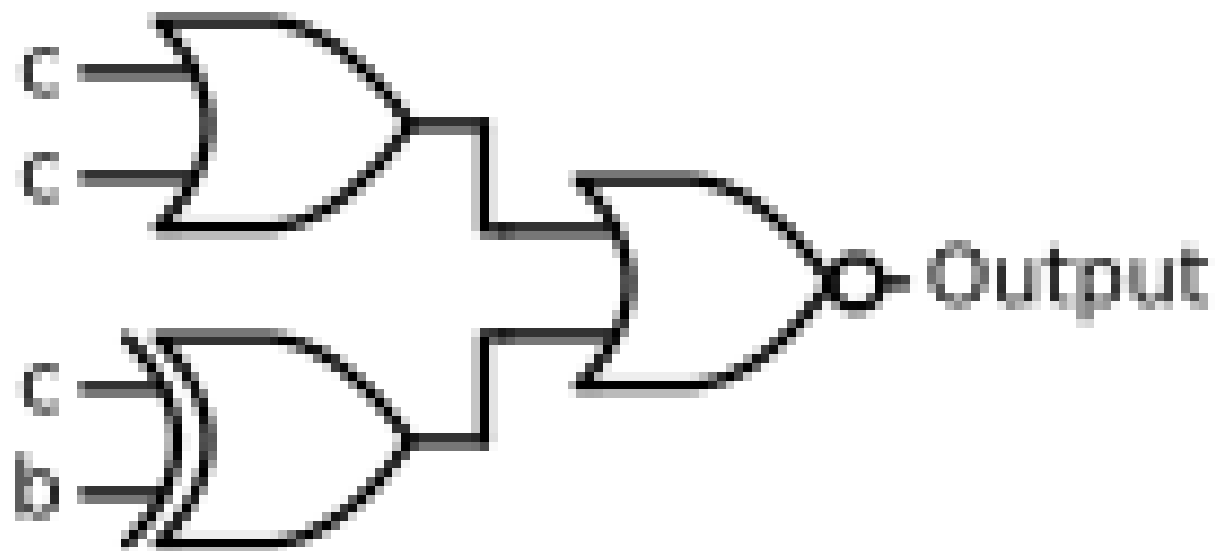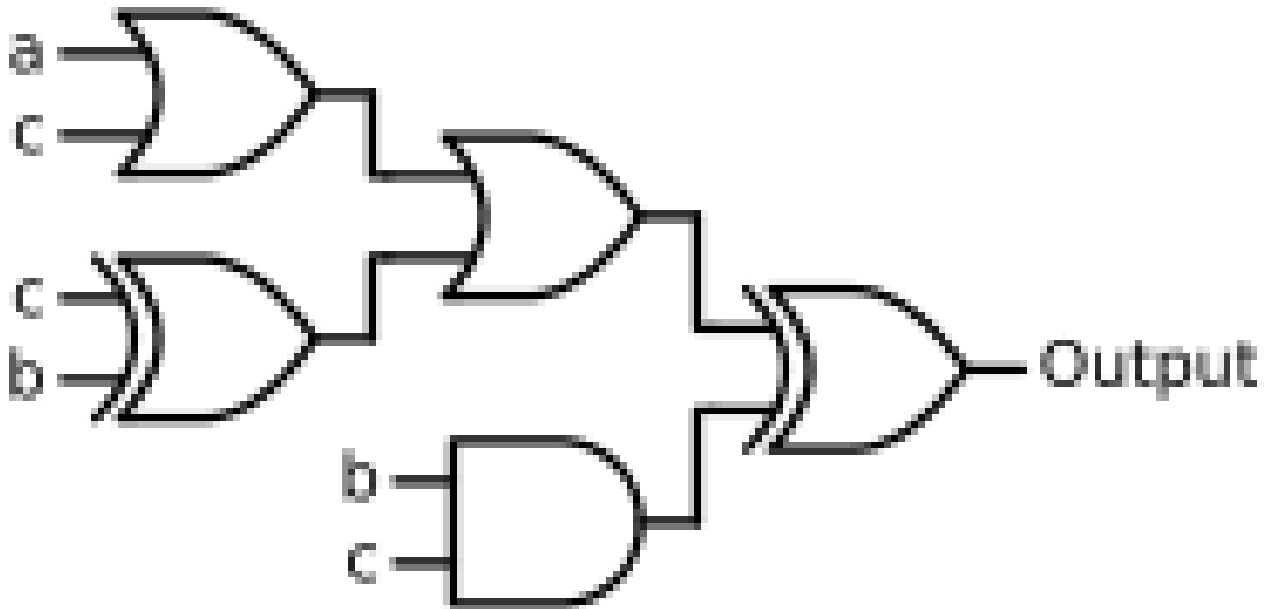Expression 2: $((c \text{ or } c) \text{ nor } (c \text{ xor } b))$




Options:

1. Yes
2. No

Correct Answer: no

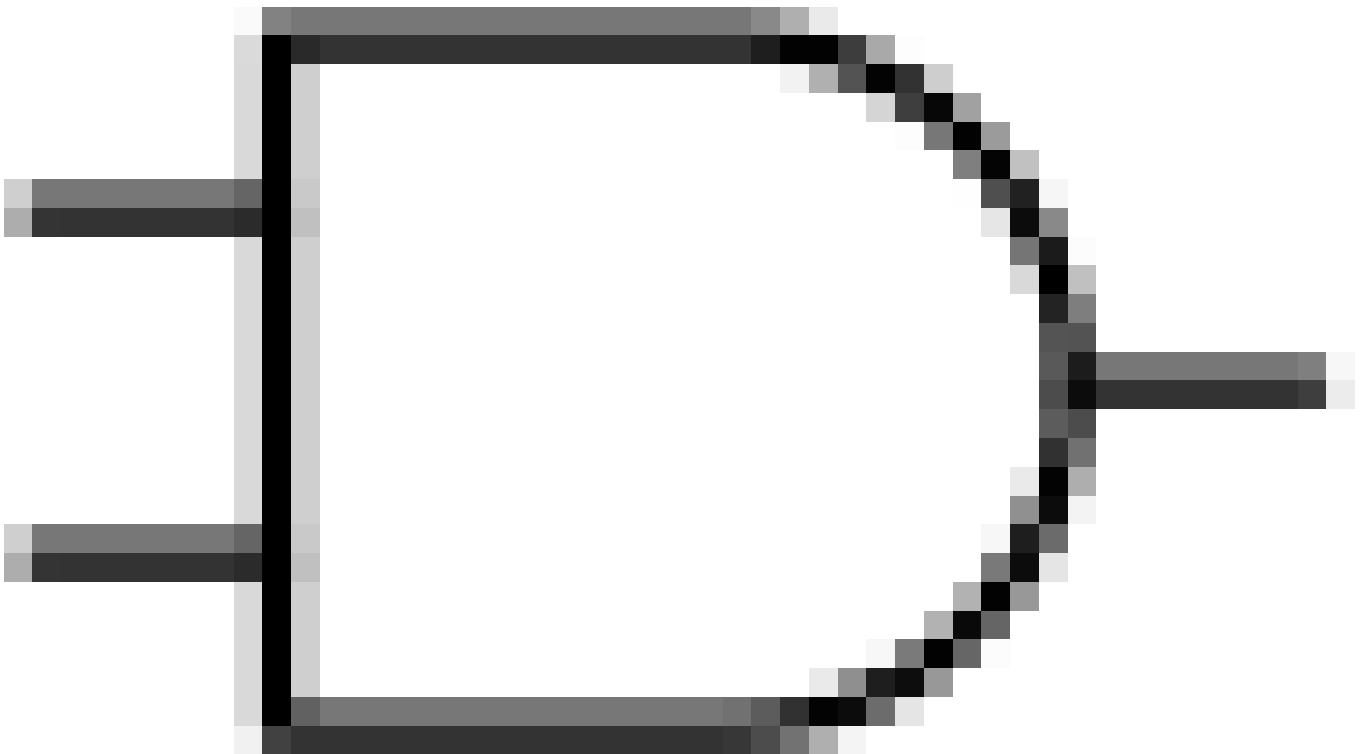Question 13:

What is the output of the AND gate with inputs 1, 1?



Options:

1. 0

2. 1



Correct Answer: 1

Question 14:

Are these two circuits equivalent?

Expression 1: (not b)

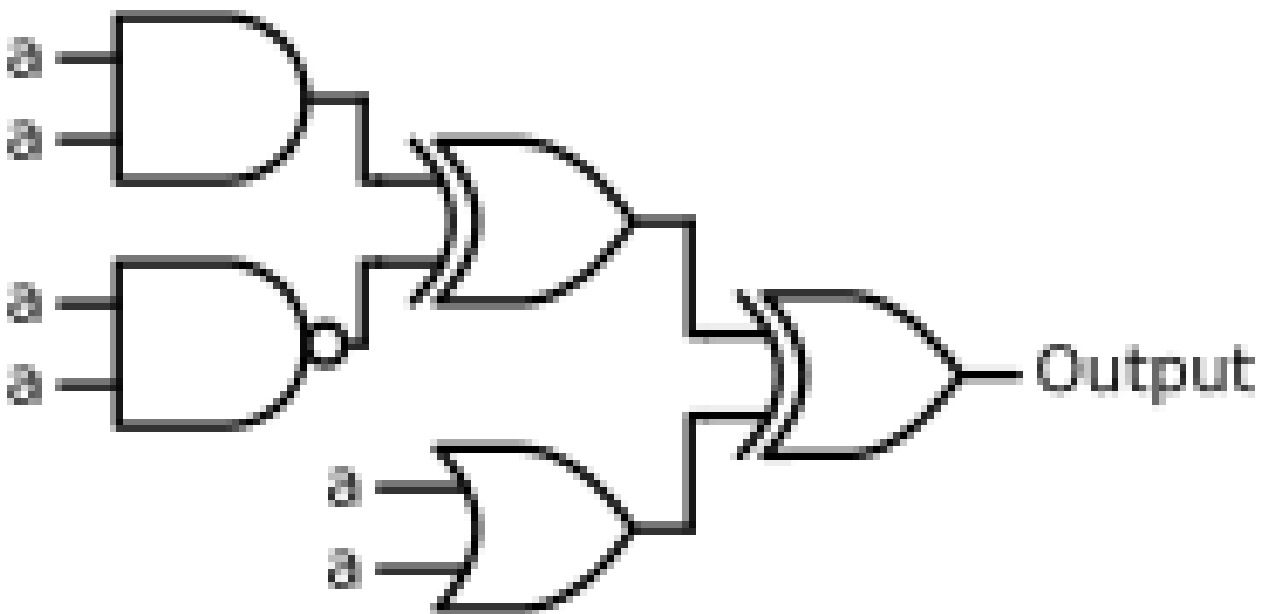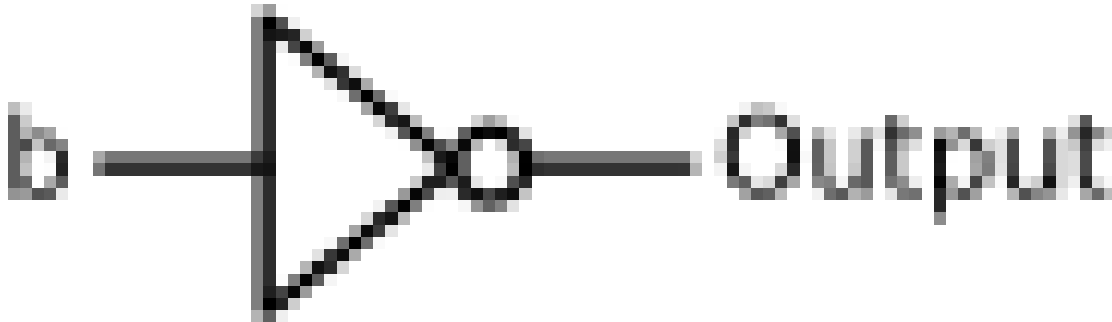Expression 2: (((a and a) xor (a nand a)) xor (not (a nor a)))



Options:

1. Yes
2. No

Correct Answer: no

Question 15:

Are these two circuits equivalent?

Expression 1: $((c \text{ or } b) \text{ xor } (a \text{ xnor } a))$

Expression 2: $((c \text{ or } b) \text{ xor } (a \text{ xnor } a))$



Options:


1. Yes

2. No

Correct Answer: yes

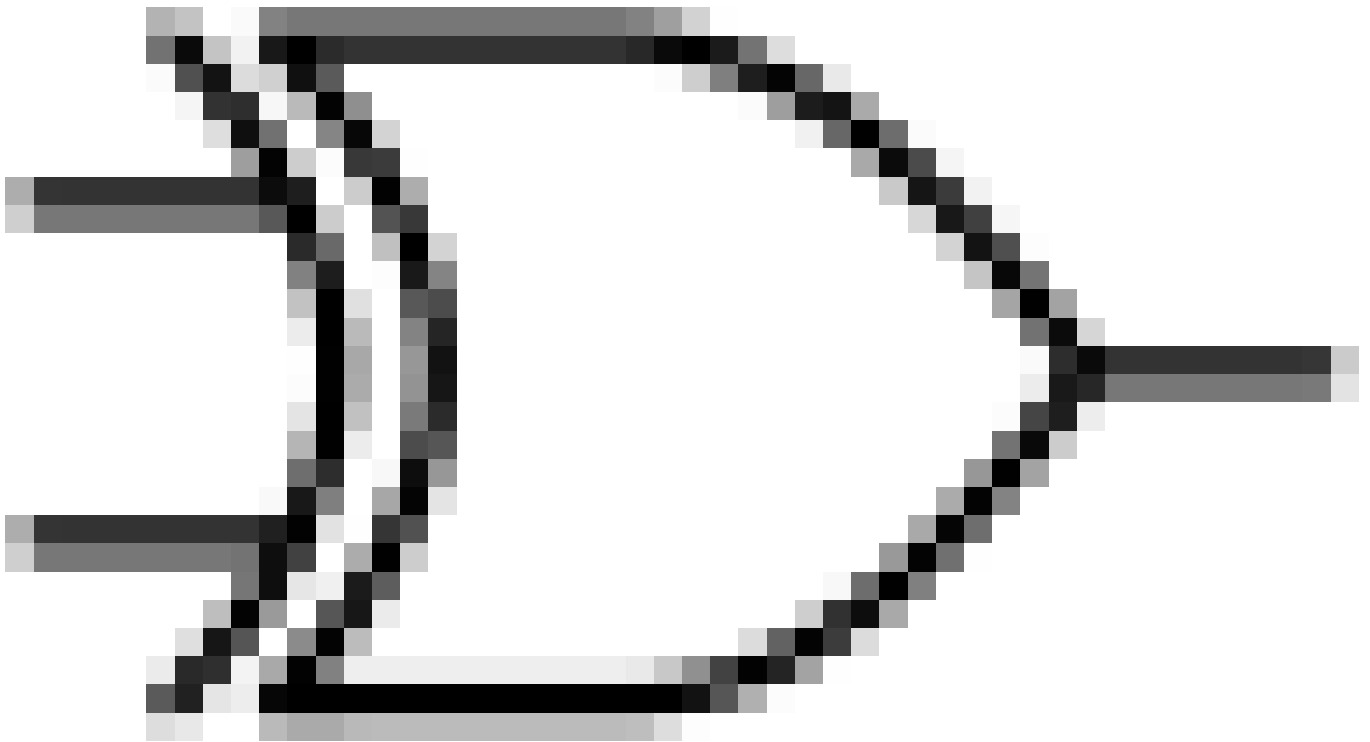Question 16:

What is the output of the XOR gate with inputs 1, 1?



Options:


1. 0

2. 1

Correct Answer: 0

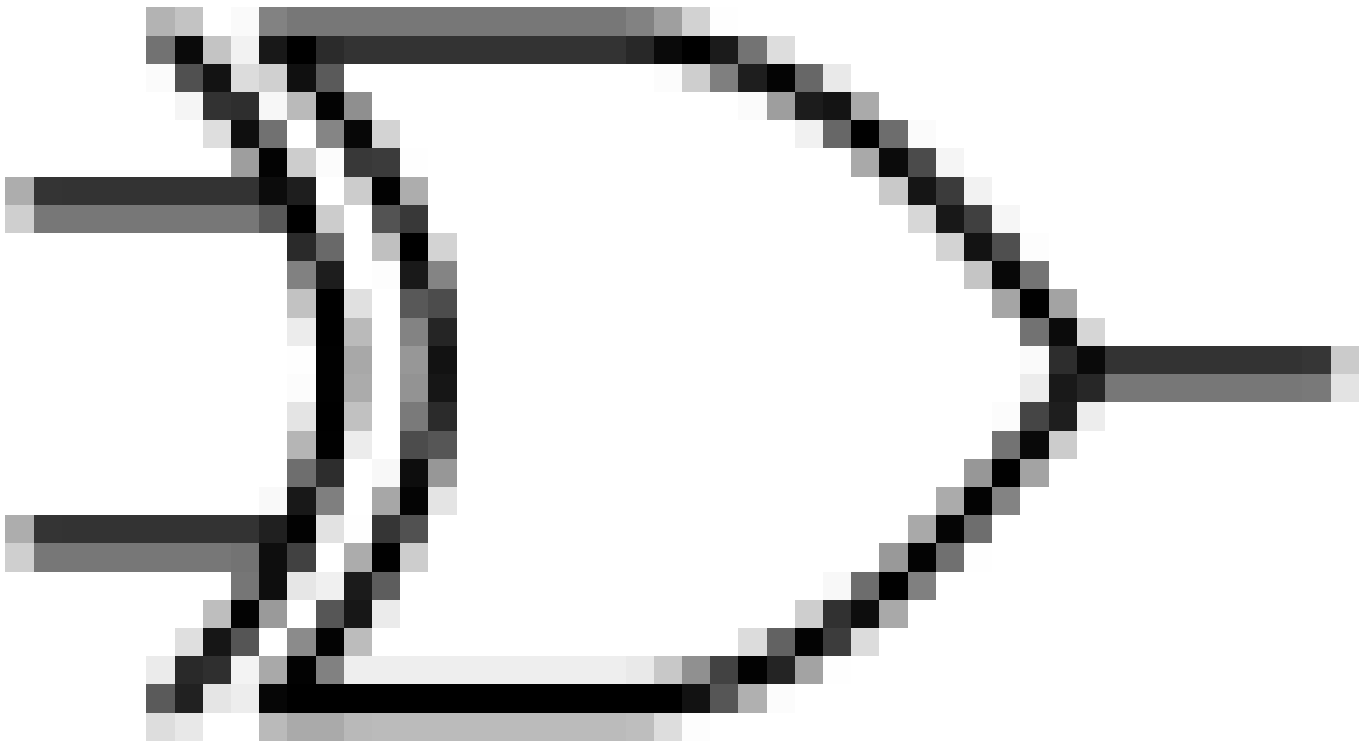Question 17:

What is the output of the XOR gate with inputs 0, 1?



Options:


1. 1

2. 0

Correct Answer: 1

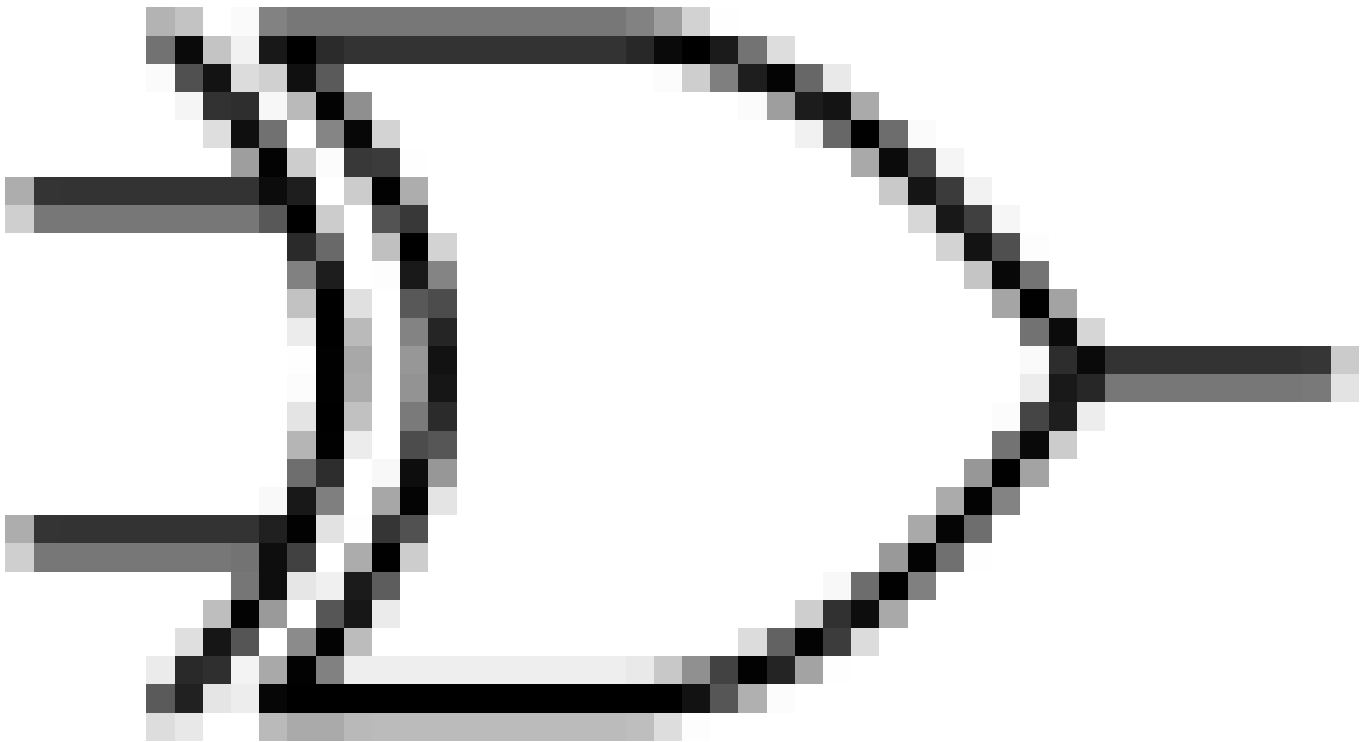Question 18:

What is the output of the XOR gate with inputs 1, 1?



Options:

1. 0

2. 1



Correct Answer: 0

Question 19:

Are these two circuits equivalent?

Expression 1: $((c \text{ and } a) \text{ and } (a \text{ and } c))$

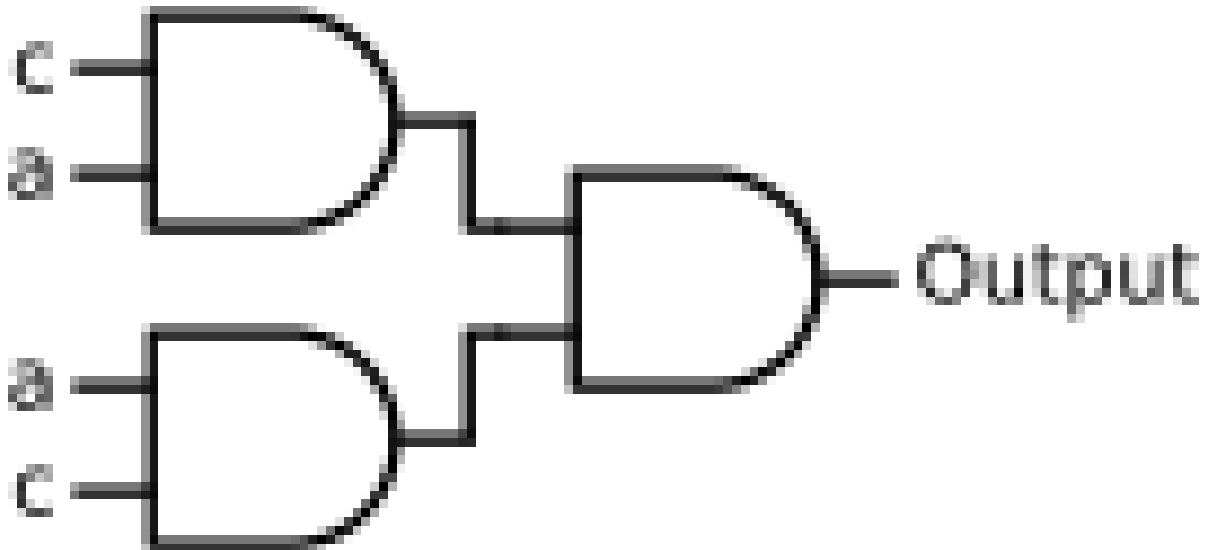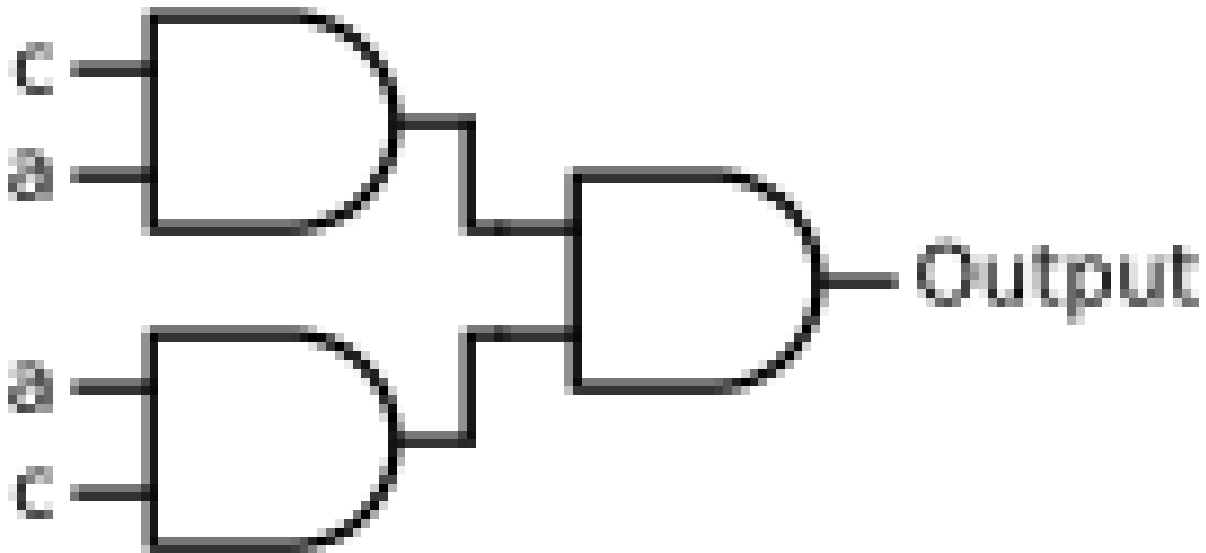Expression 2: $((c \text{ and } a) \text{ and } (a \text{ and } c))$




Options:

1. Yes
2. No

Correct Answer: yes

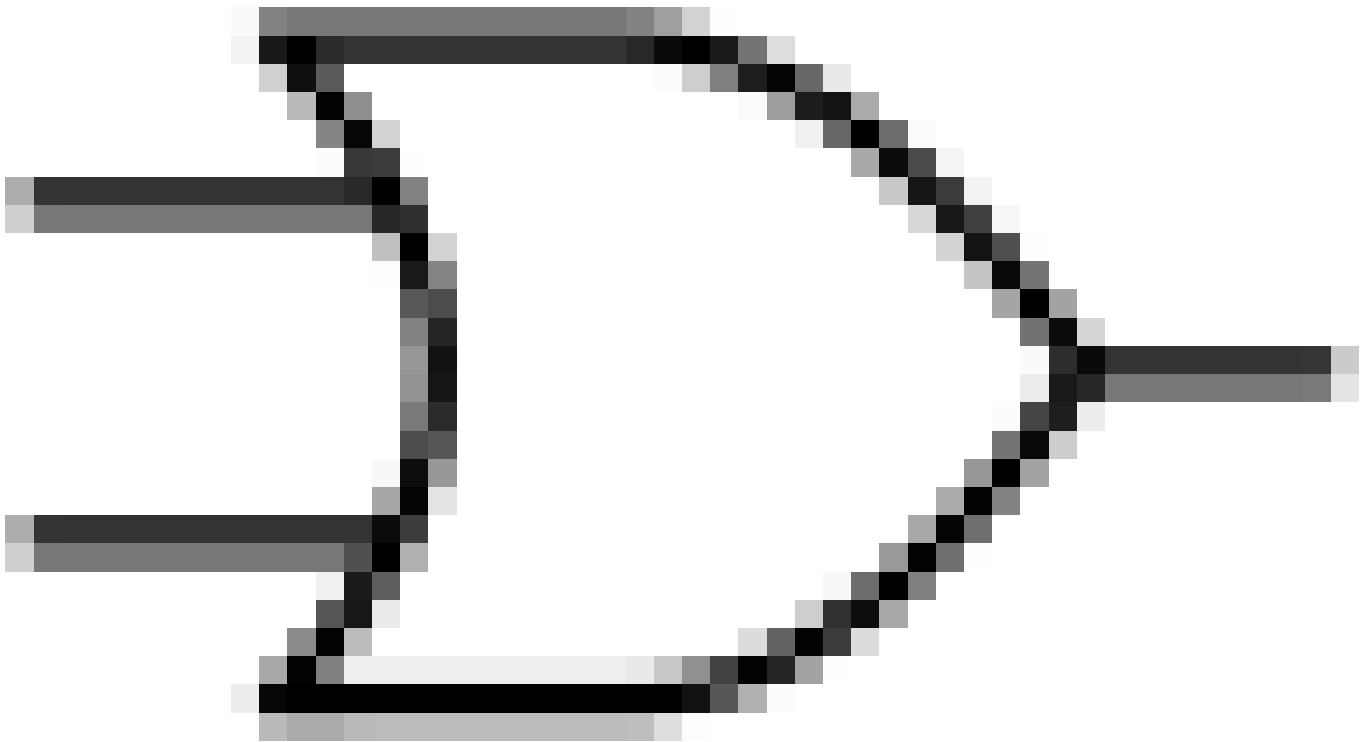Question 20:

What is the output of the OR gate with inputs 0, 1?



Options:

1. 1

2. 0

Correct Answer: 1