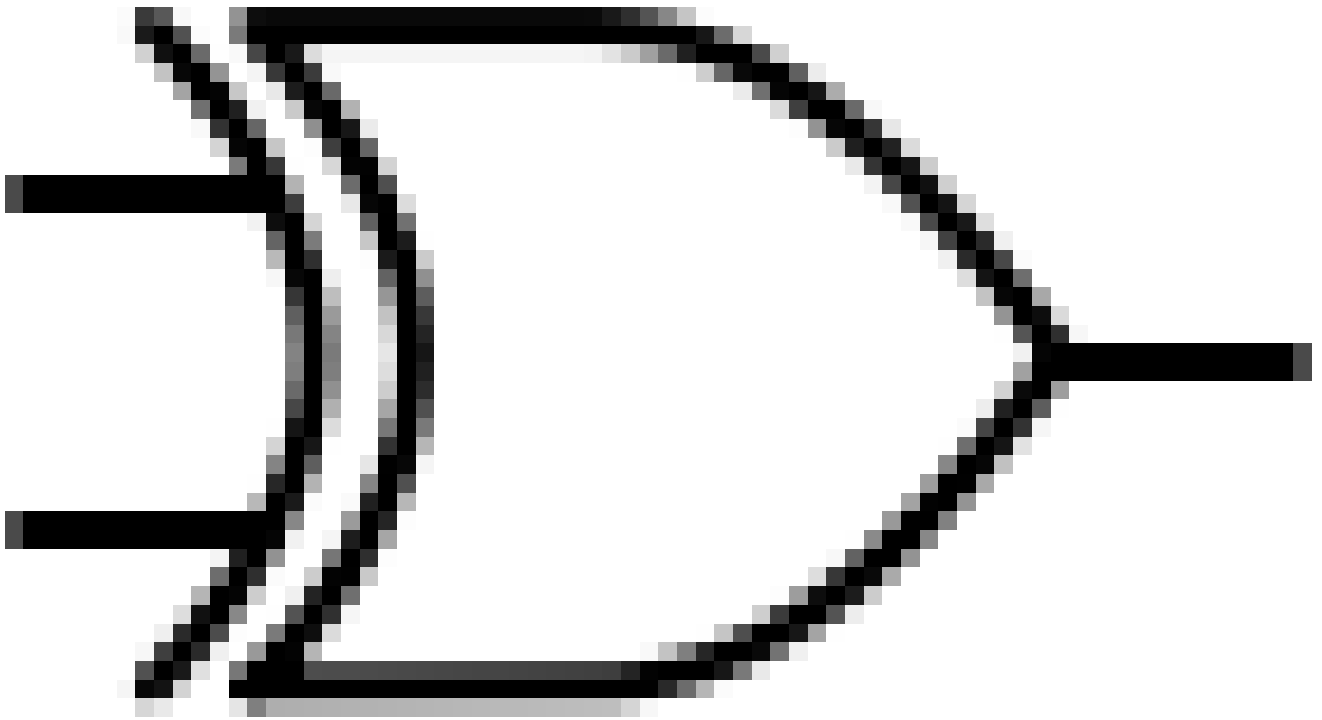


### Question 1:

What is the output of the XOR gate with inputs 1, 1?



Options:


1. 0

2. 1

Correct Answer: 0
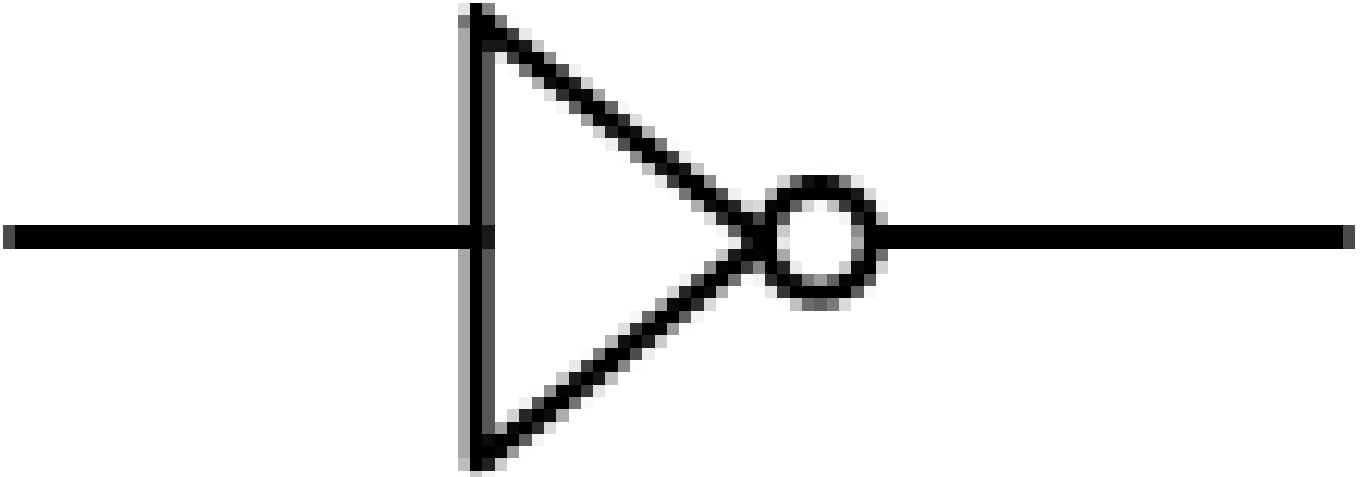
## Question 2:

What is the output of the NOT gate with input 0?



Options:


1. 0

2. 1

Correct Answer: 1
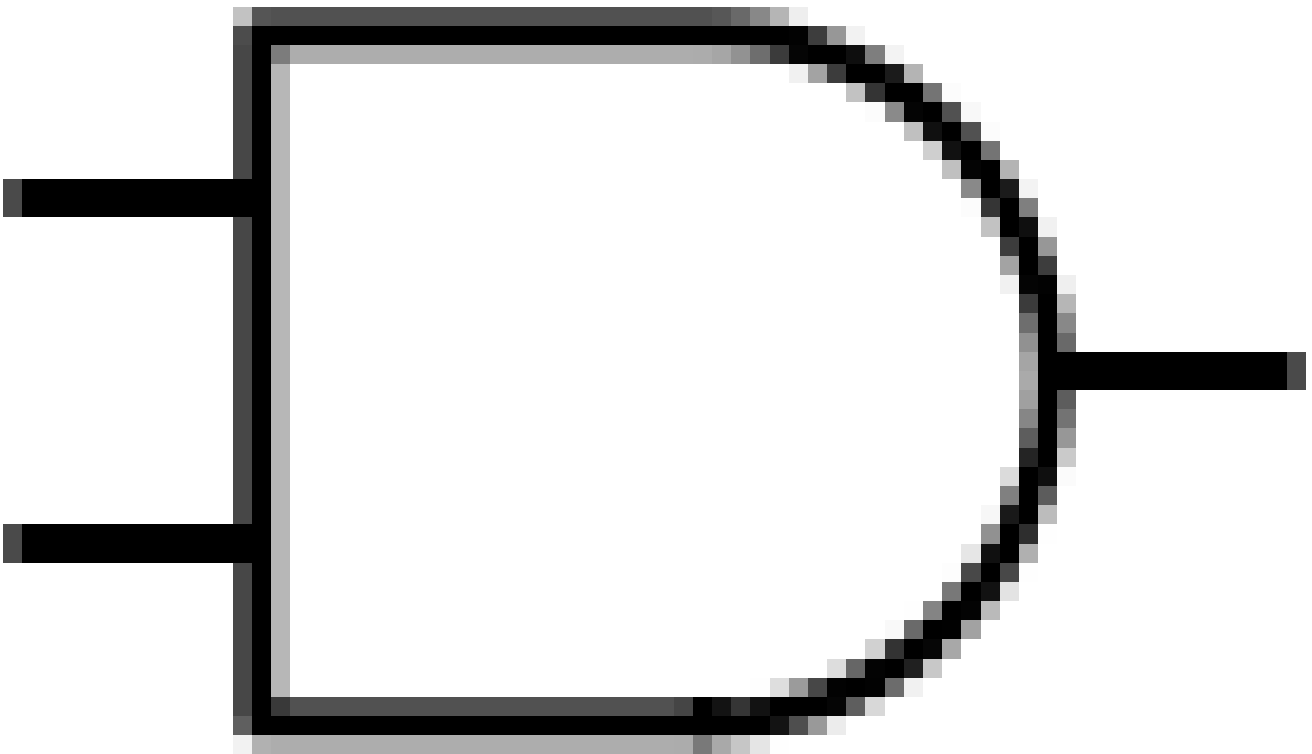
### Question 3:

What is the output of the AND gate with inputs 1, 1?



Options:


1. 0

2. 1

Correct Answer: 1
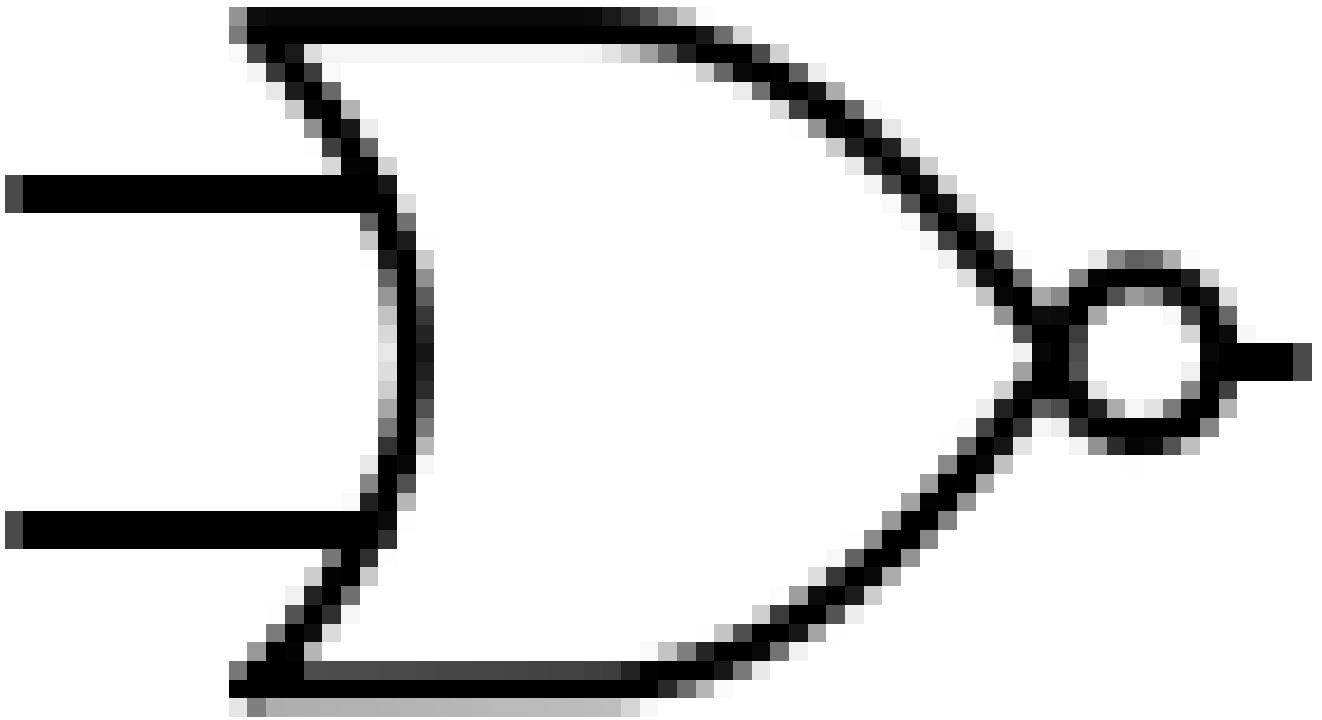
#### Question 4:

What is the output of the NOR gate with inputs 0, 0?



Options:

1. 1

2. 0



Correct Answer: 1

Question 5:

Are these two circuits equivalent?

Expression 1:  $((b \text{ nor } b) \text{ nor } (c \text{ xnor } c)) \text{ xnor } ((c \text{ xor } a) \text{ nand } (b \text{ xor } c))$

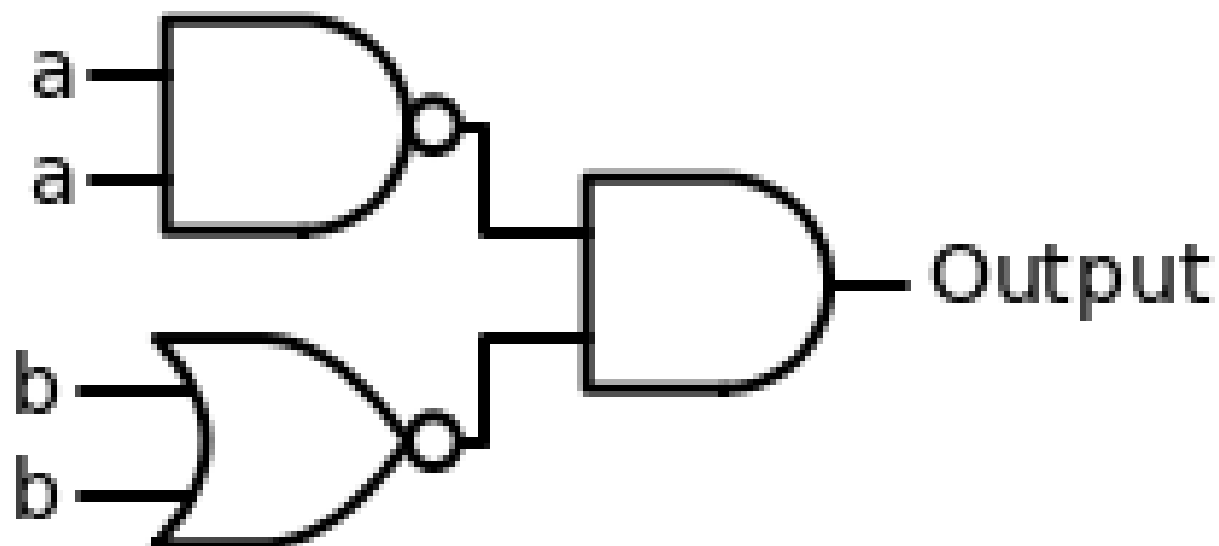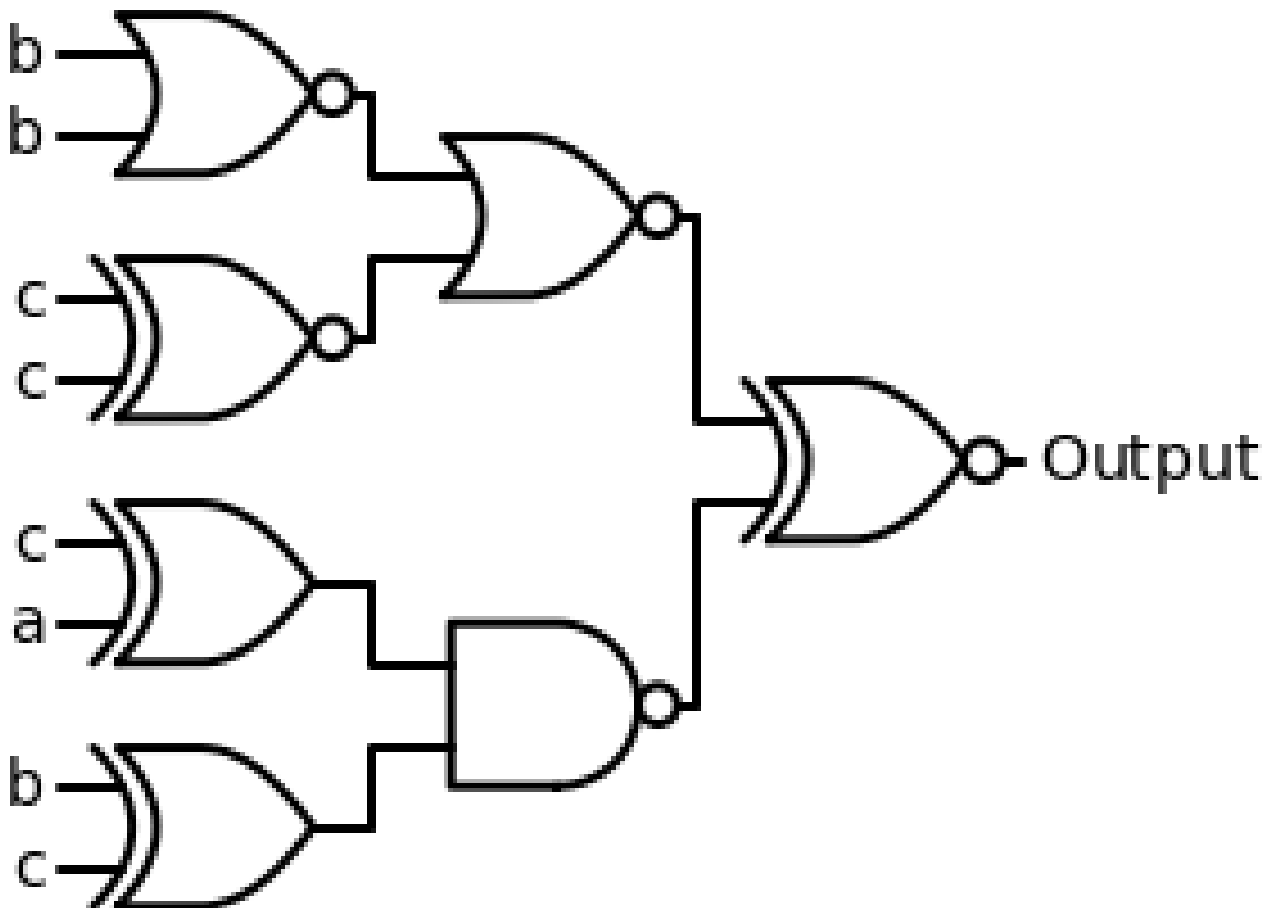Expression 2:  $((\text{not } (a \text{ and } a)) \text{ and } (\text{not } (b \text{ or } b)))$



Options:

1. Yes

2. No



Correct Answer: no

Question 6:

Are these two circuits equivalent?

Expression 1:  $((\text{not } a) \text{ nor } (c \text{ or } a))$

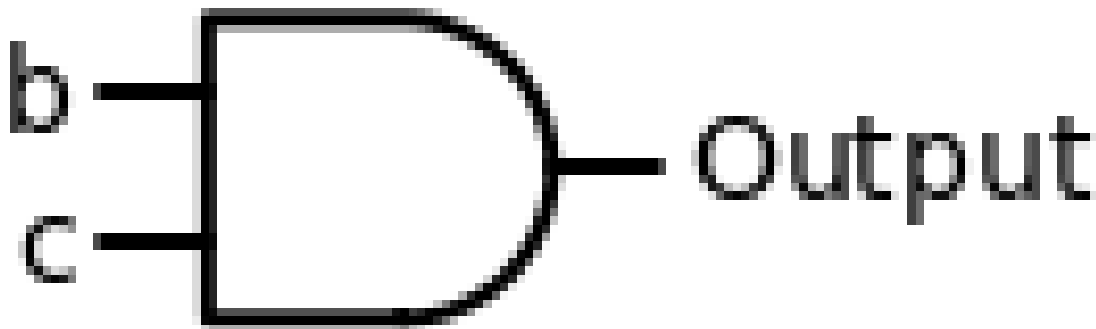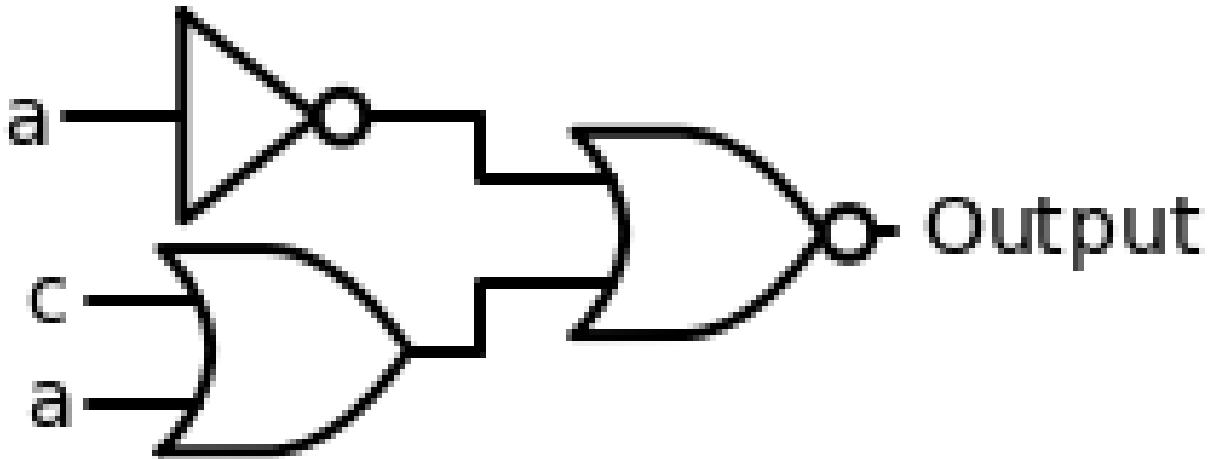Expression 2:  $(\text{not } (b \text{ nand } c))$




Options:

1. Yes
2. No

Correct Answer: no
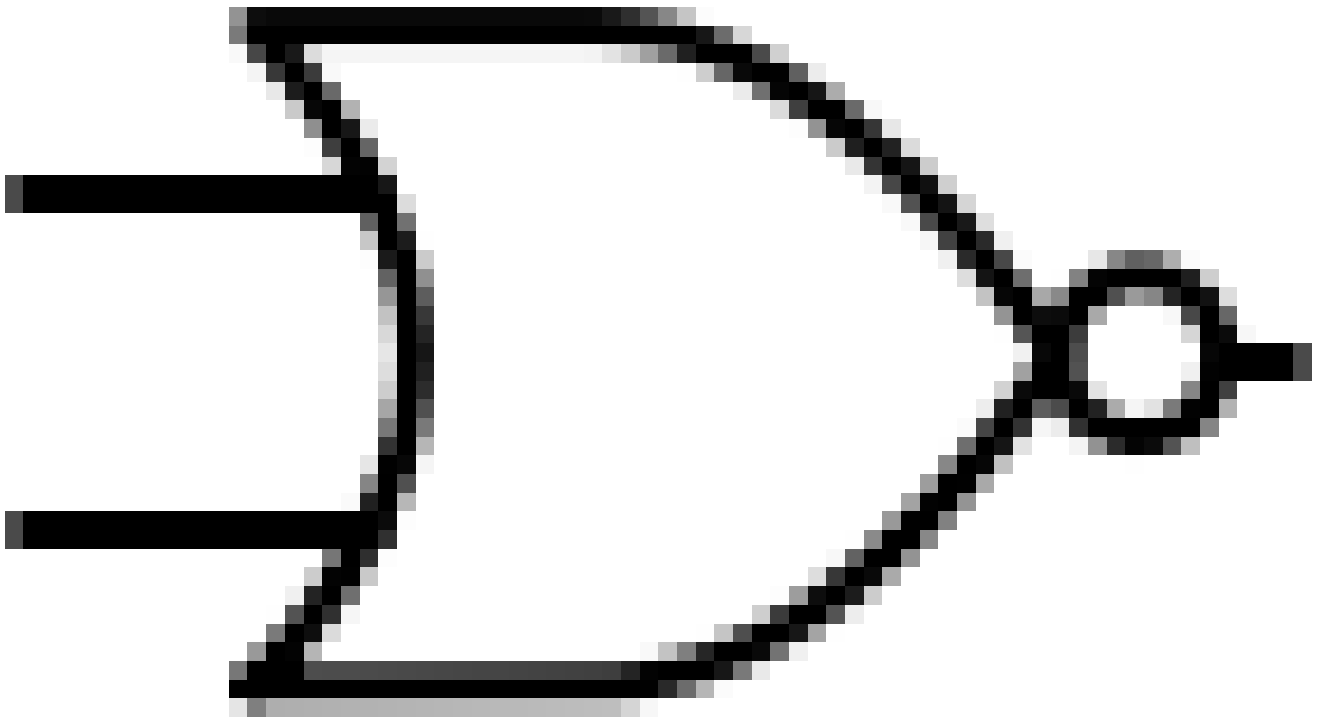
### Question 7:

What is the output of the NOR gate with inputs 1, 0?



Options:

1. 1


2. 0

Correct Answer: 0



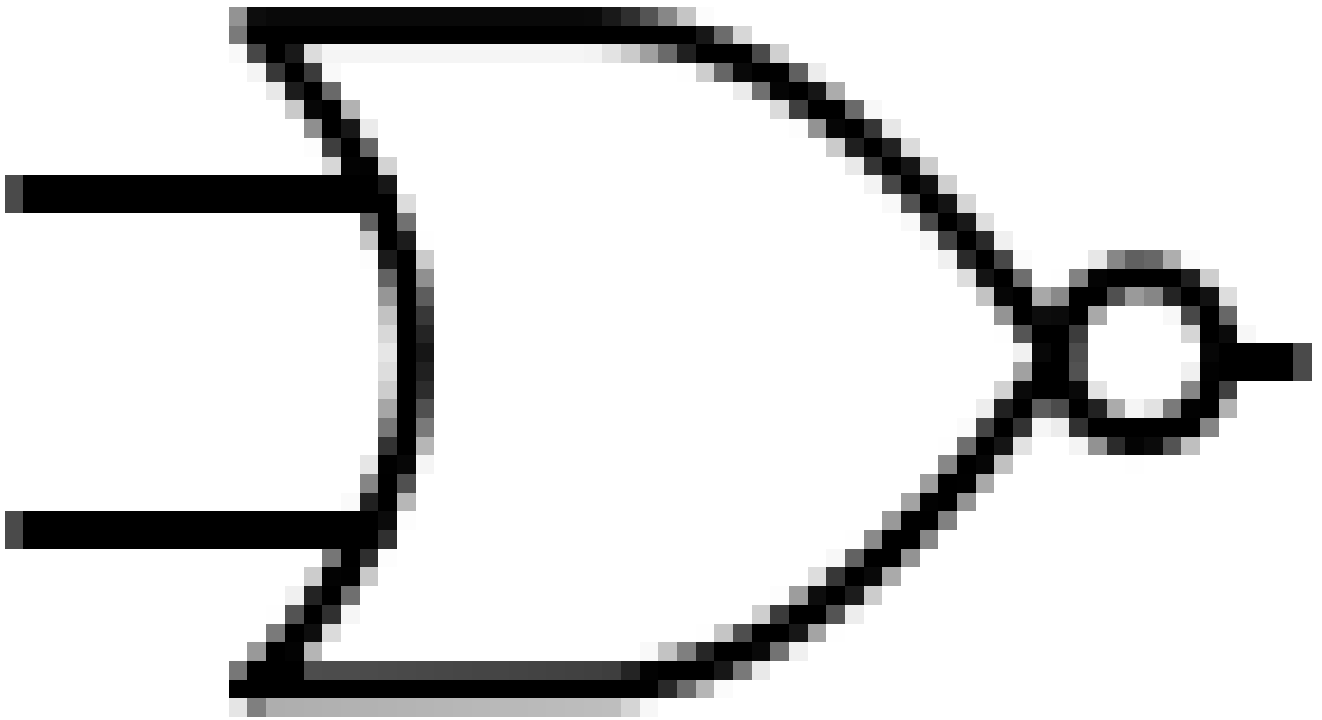Question 8:

What is the output of the NOR gate with inputs 1, 0?



Options:

1. 0

2. 1



Correct Answer: 0

Question 9:

Are these two circuits equivalent?

Expression 1:  $((a \text{ nor } a) \text{ xor } (c \text{ xnor } b))$

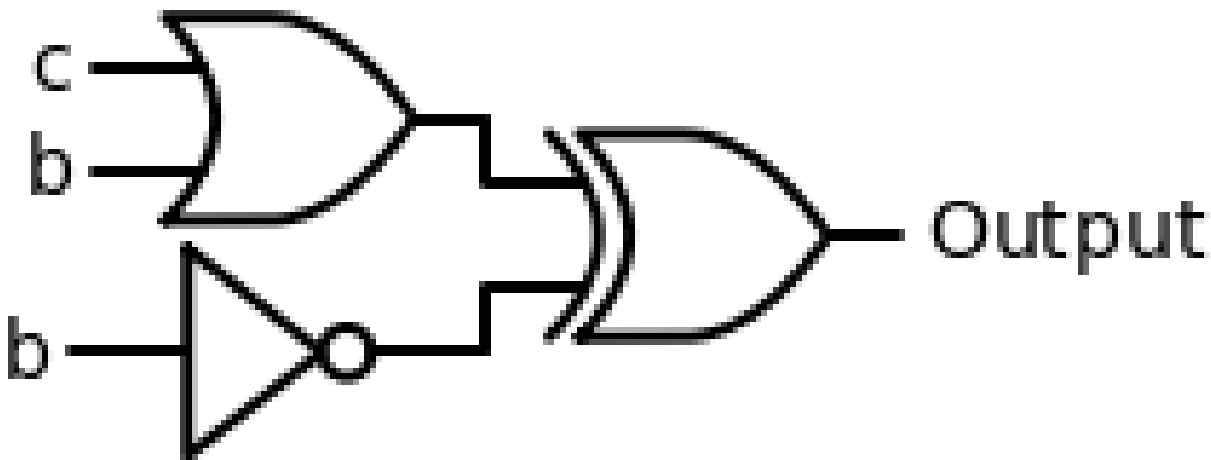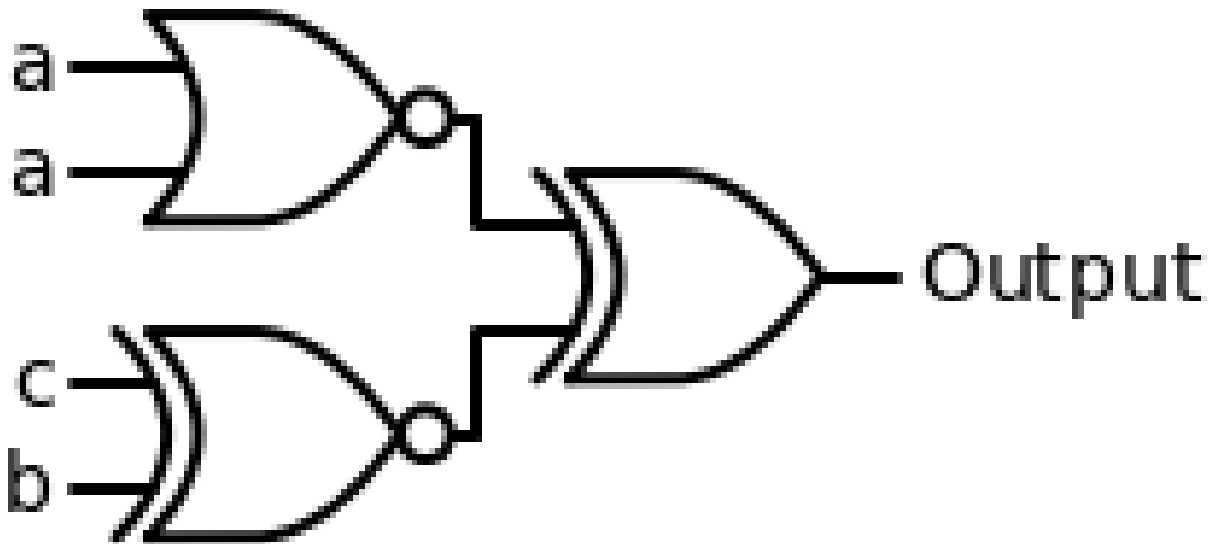Expression 2:  $((c \text{ or } b) \text{ xor } (\text{not } b))$




Options:

1. Yes
2. No

Correct Answer: no

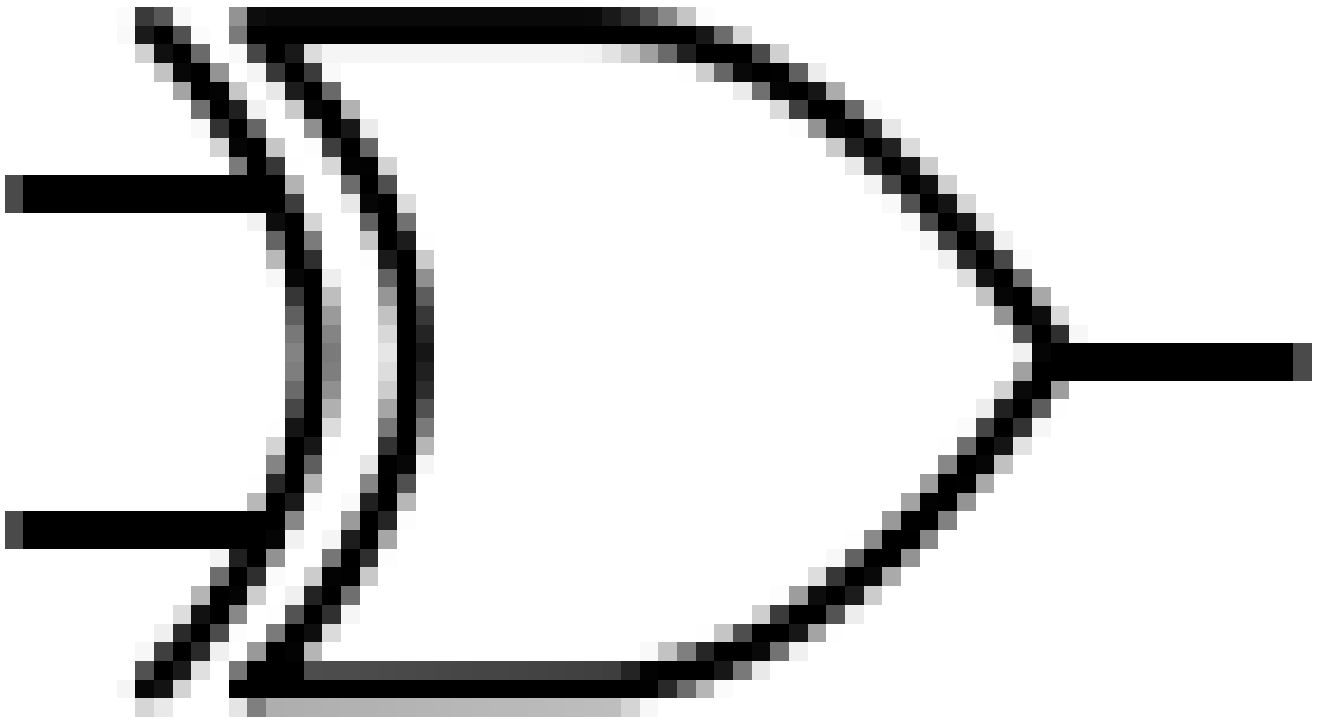Question 10:

What is the output of the XOR gate with inputs 1, 1?



Options:


1. 1

2. 0

Correct Answer: 0

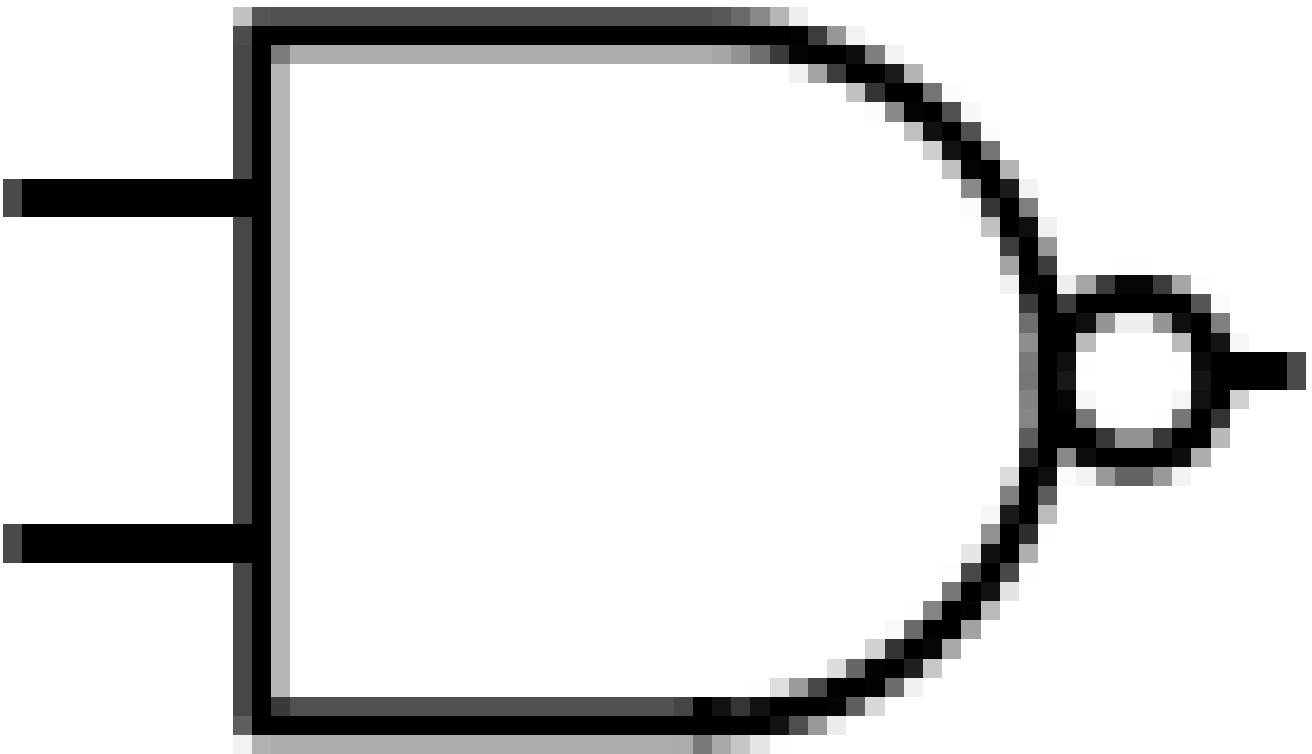Question 11:

What is the output of the NAND gate with inputs 1, 0?



Options:


1. 1

2. 0

Correct Answer: 1

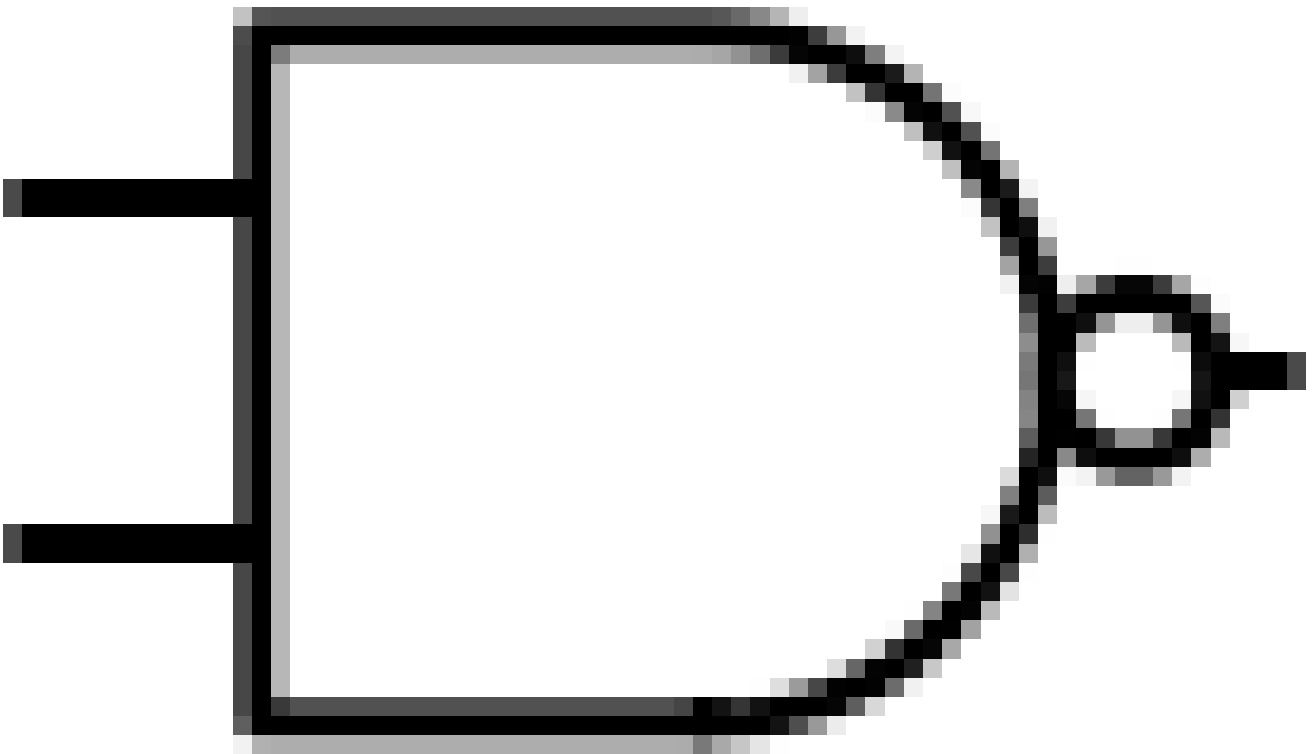Question 12:

What is the output of the NAND gate with inputs 0, 0?



Options:


1. 0

2. 1

Correct Answer: 1

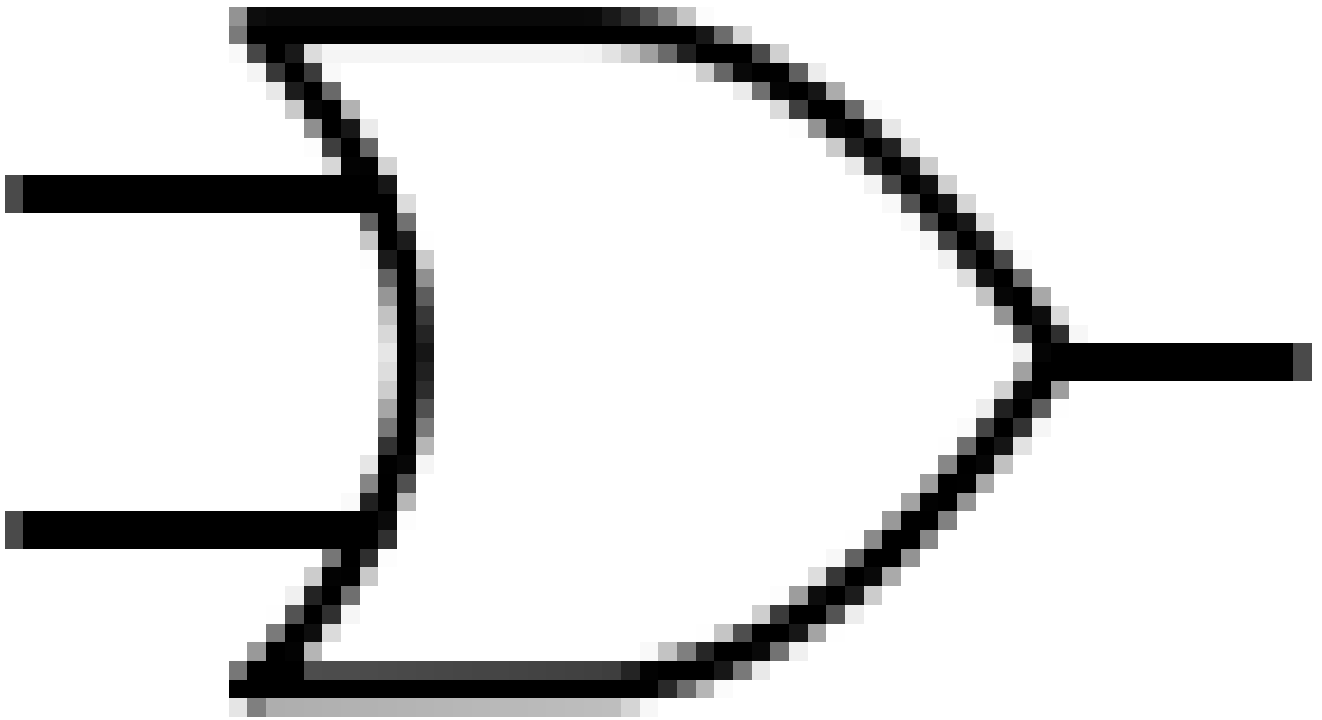Question 13:

What is the output of the OR gate with inputs 0, 1?



Options:

1. 1

2. 0


Correct Answer: 1

Question 14:

Are these two circuits equivalent?

Expression 1:  $((a \text{ xor } a) \text{ nand } (b \text{ and } b))$

Expression 2:  $(\text{not } a)$

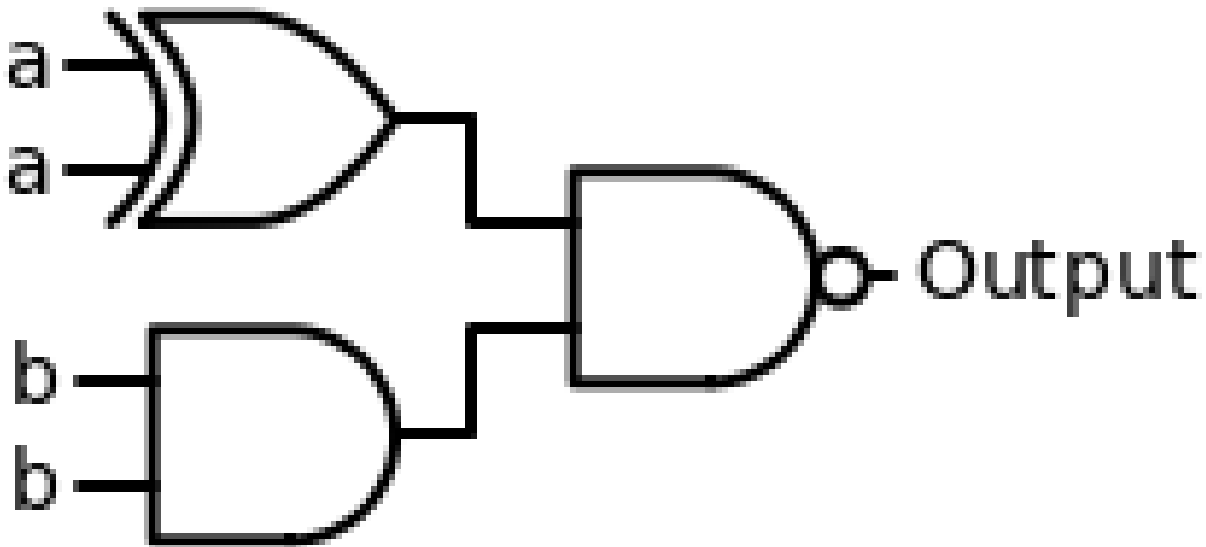

Options:

1. Yes
2. No



Correct Answer: no

Question 15:

Are these two circuits equivalent?

Expression 1:  $((c \text{ nand } b) \text{ nor } (b \text{ xnor } b))$

Expression 2:  $(c \text{ xor } b)$

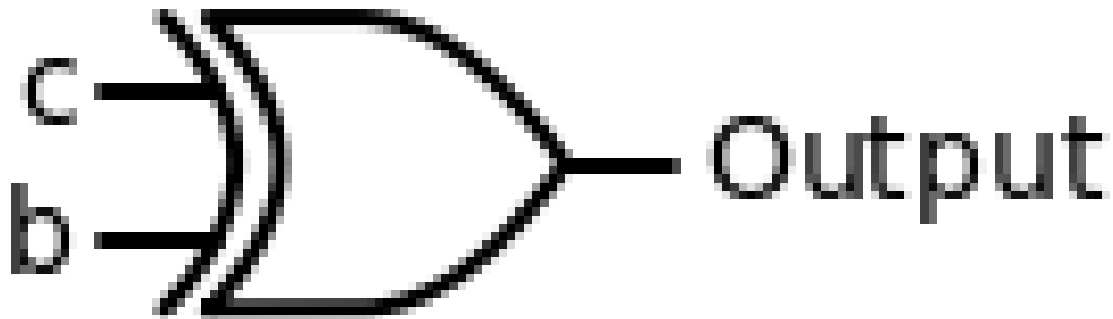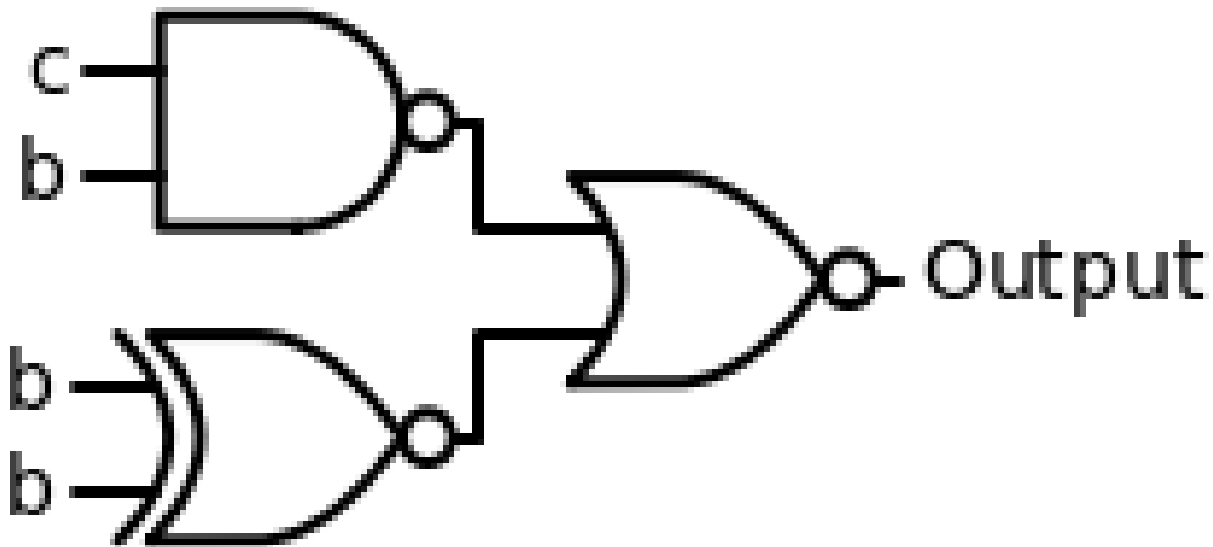

Options:


1. Yes
2. No

Correct Answer: no



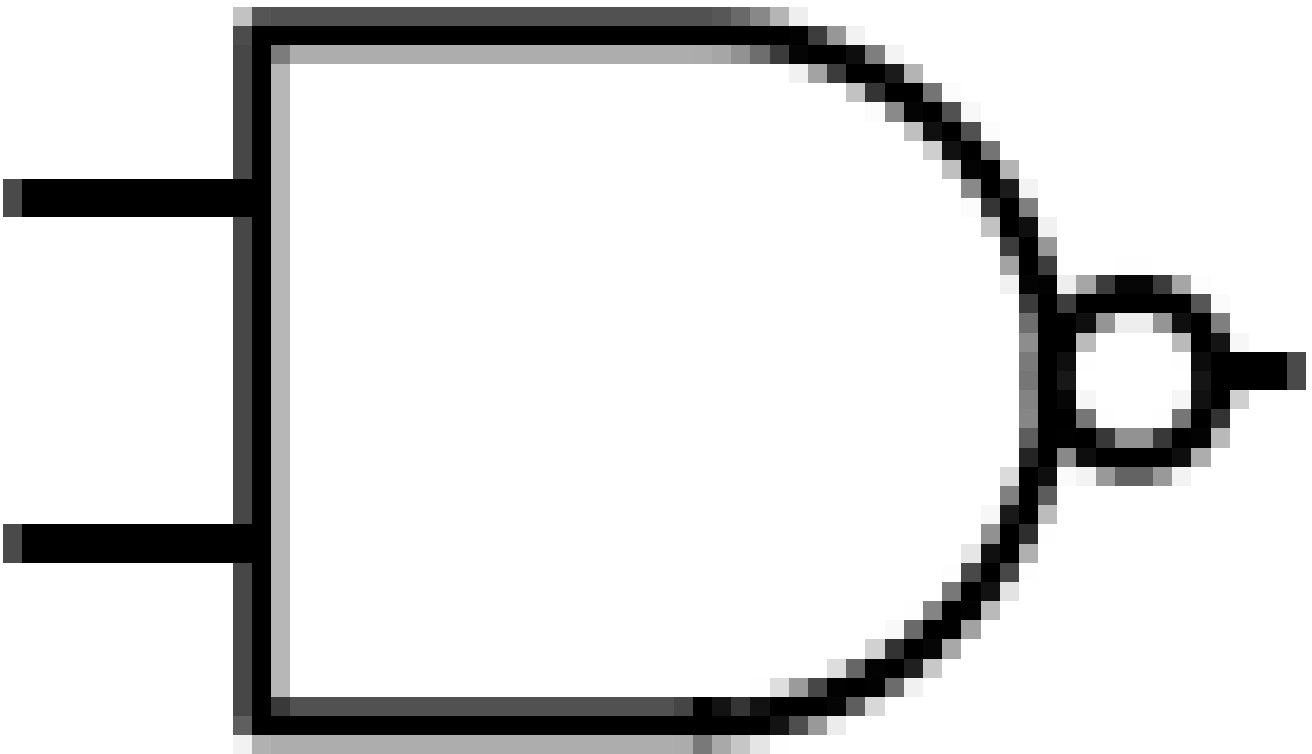Question 16:

What is the output of the NAND gate with inputs 0, 0?



Options:


1. 1

2. 0

Correct Answer: 1

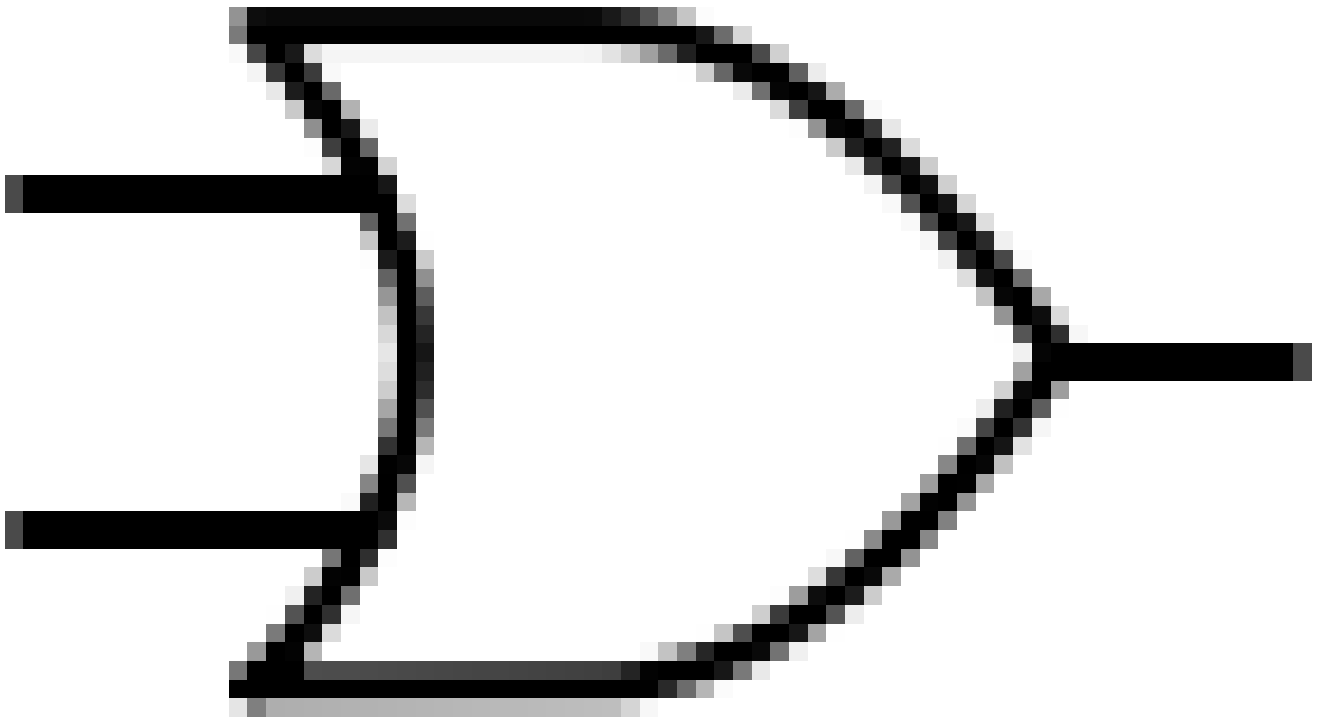Question 17:

What is the output of the OR gate with inputs 0, 1?



Options:

1. 1

2. 0



Correct Answer: 1

Question 18:

Are these two circuits equivalent?

Expression 1: (b or a)

Expression 2: (b or a)

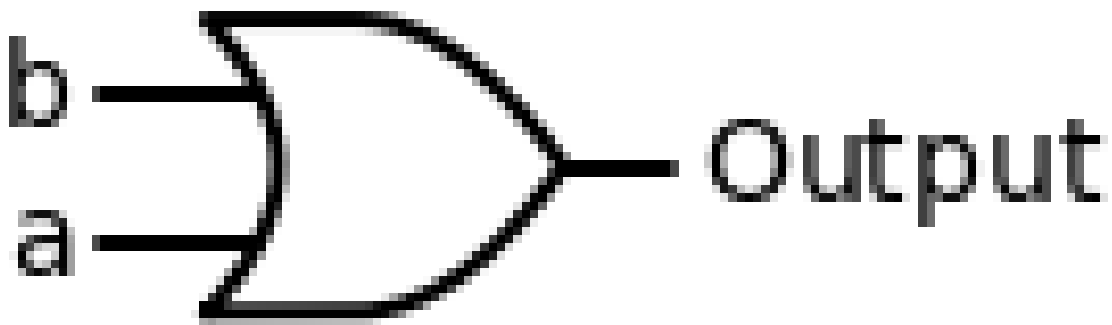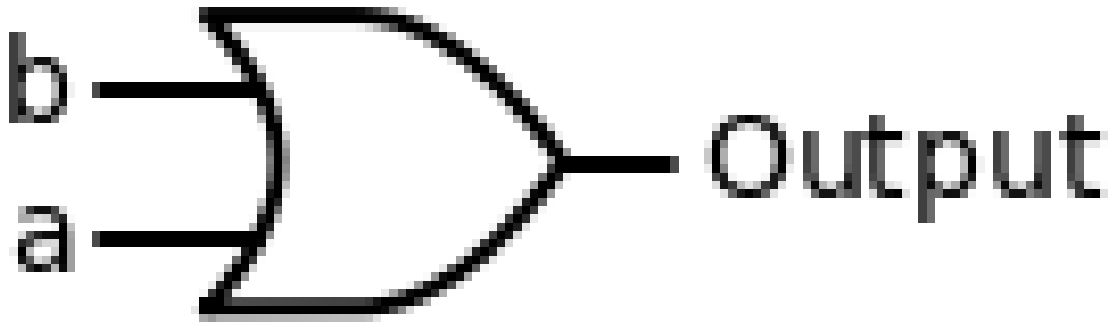

Options:

1. Yes
2. No


Correct Answer: yes

Question 19:

Are these two circuits equivalent?

Expression 1:  $((\text{not } b) \text{ nor } (b \text{ nor } a)) \text{ or } ((\text{not } b) \text{ nand } (\text{not } c))$

Expression 2:  $(a \text{ nor } a)$

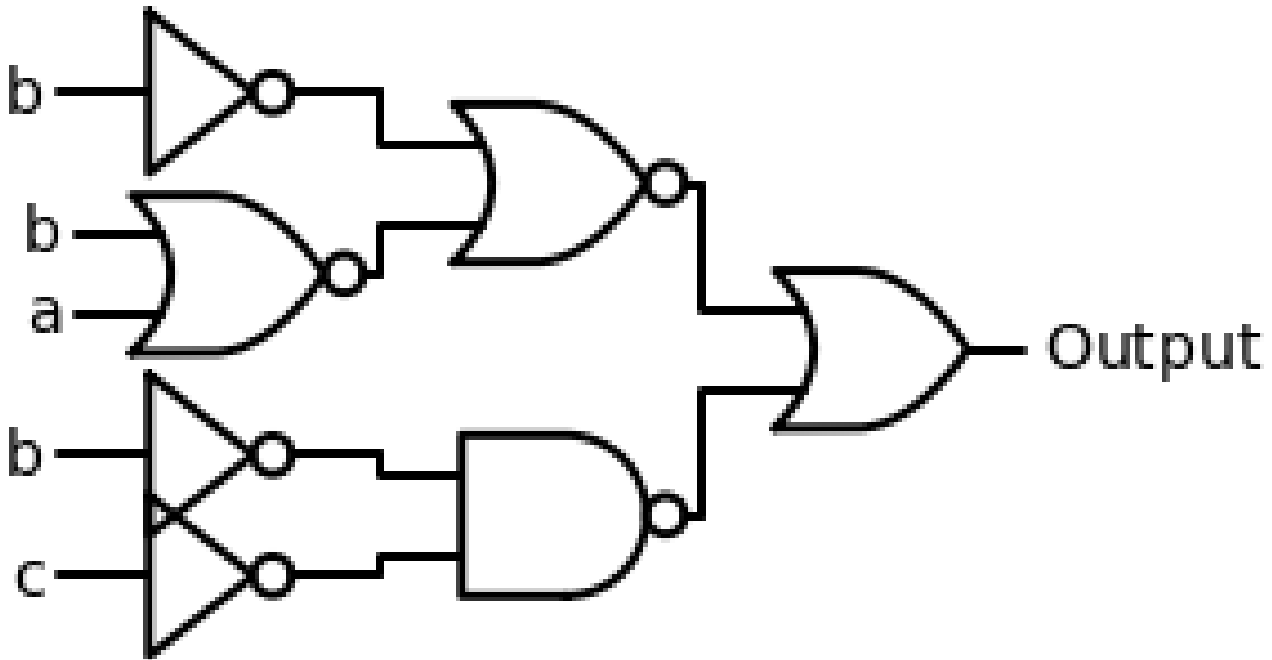

Options:

1. Yes
2. No



Correct Answer: no

Question 20:

Are these two circuits equivalent?

Expression 1: (c or a)

Expression 2: ((c or c) nand (a nor c))

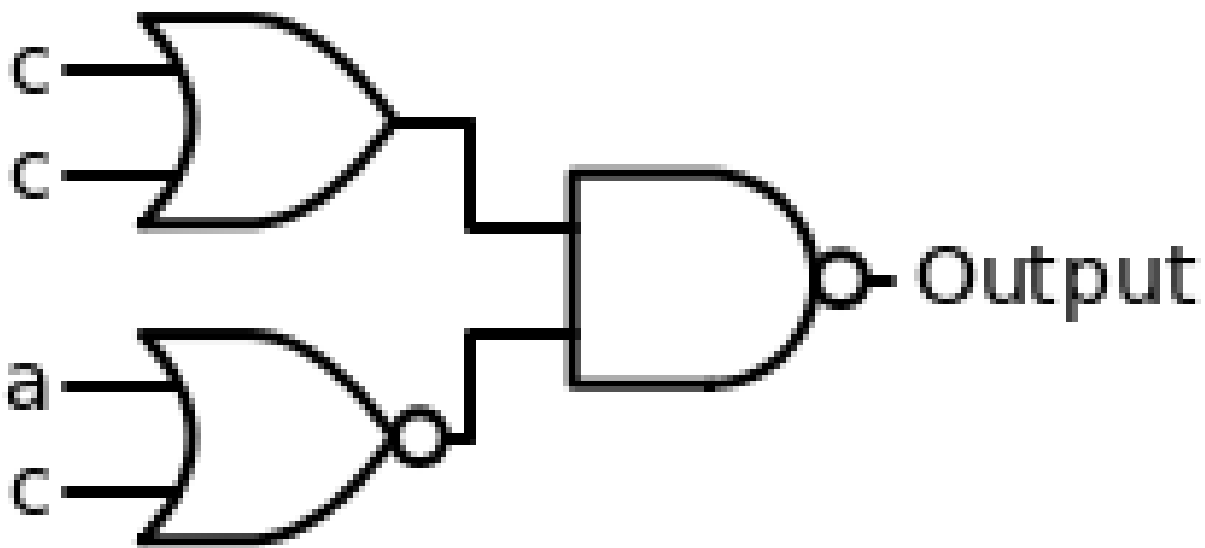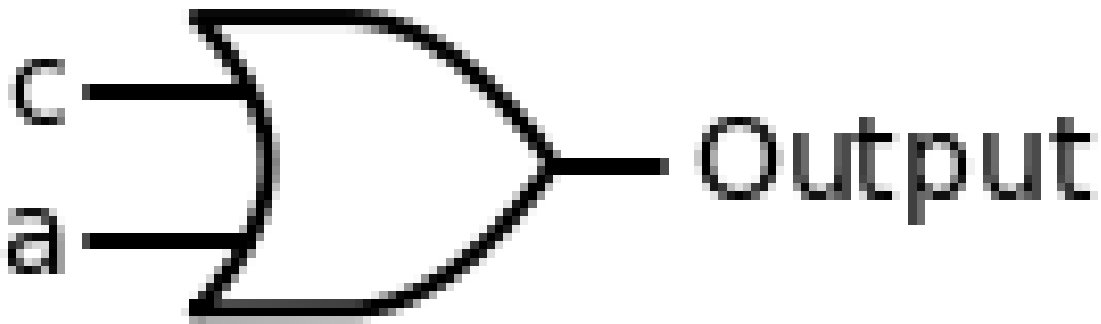


Options:

1. Yes
2. No

Correct Answer: no

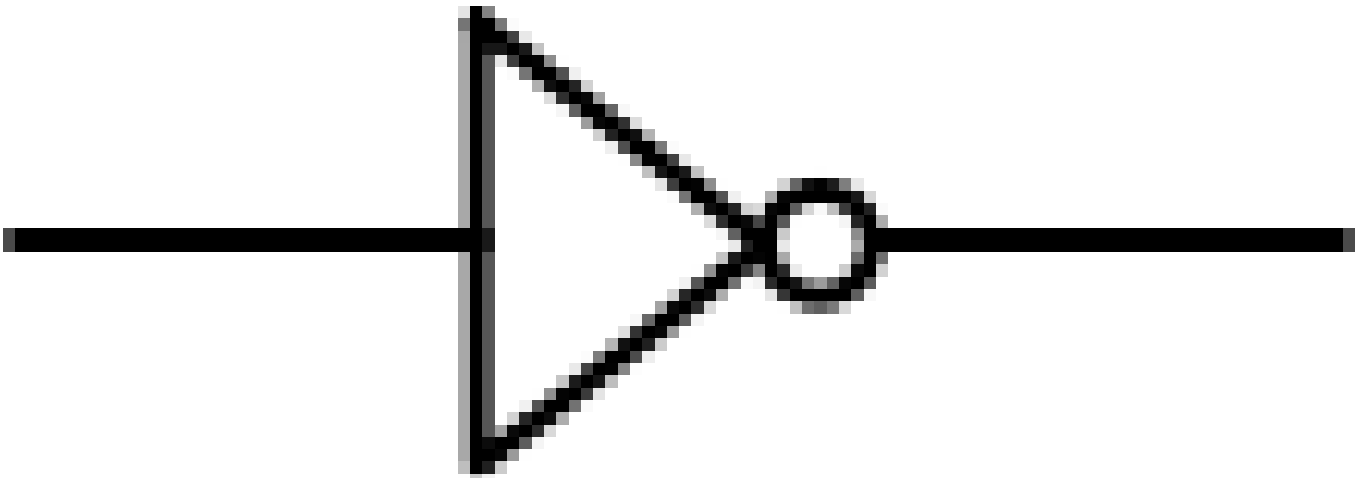Question 21:

What is the output of the NOT gate with input 0?



Options:

1. 0

2. 1



Correct Answer: 1

Question 22:

Are these two circuits equivalent?

Expression 1:  $((b \text{ xnor } b) \text{ xor } (\text{not } b)) \text{ xor } ((\text{not } c) \text{ xor } (a \text{ or } b))$

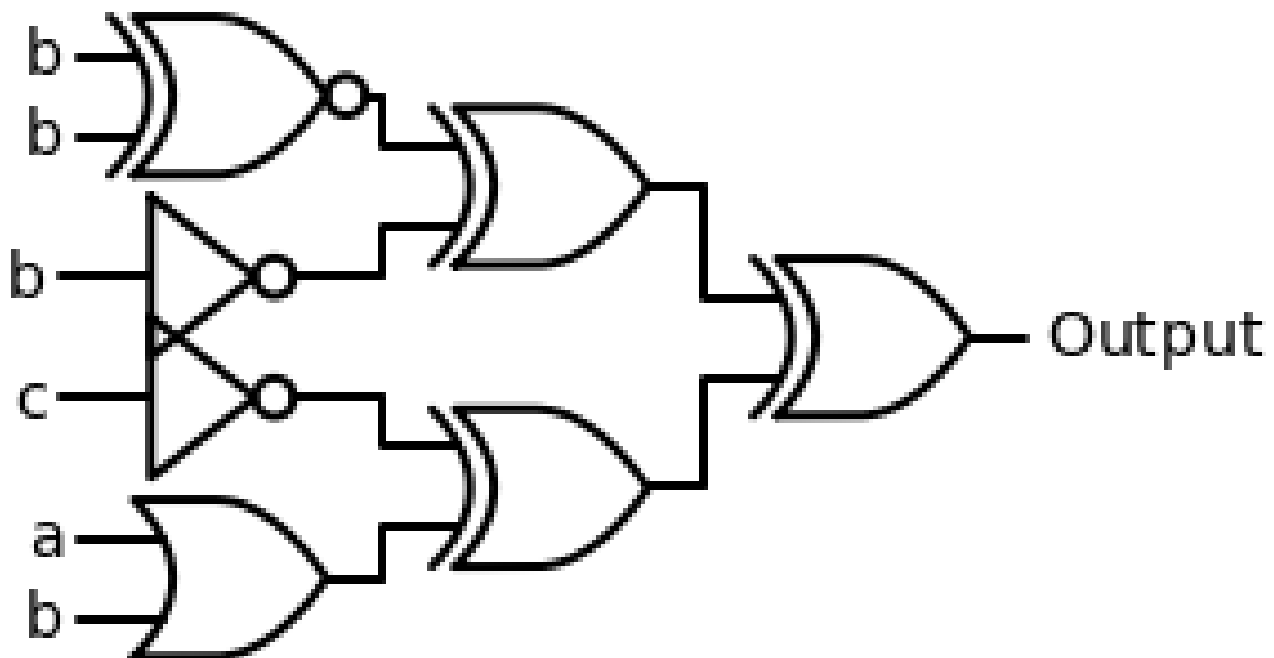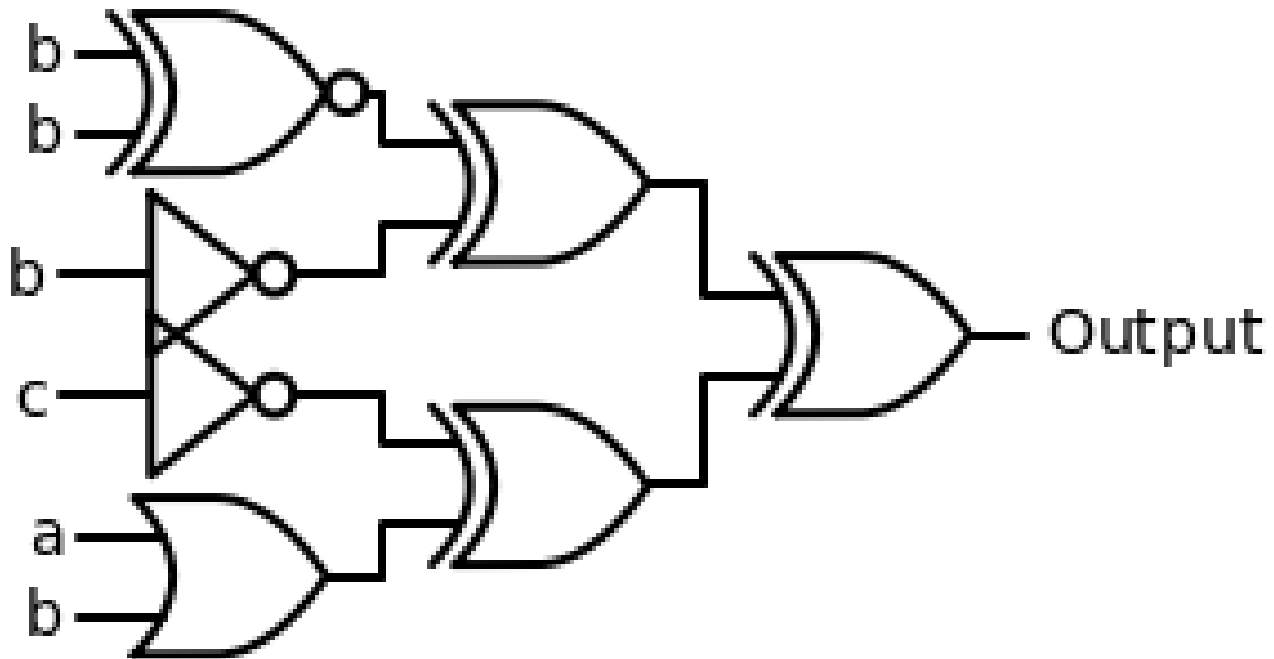Expression 2:  $((b \text{ xnor } b) \text{ xor } (\text{not } b)) \text{ xor } ((\text{not } c) \text{ xor } (a \text{ or } b))$



Options:

1. Yes


2. No

Correct Answer: yes



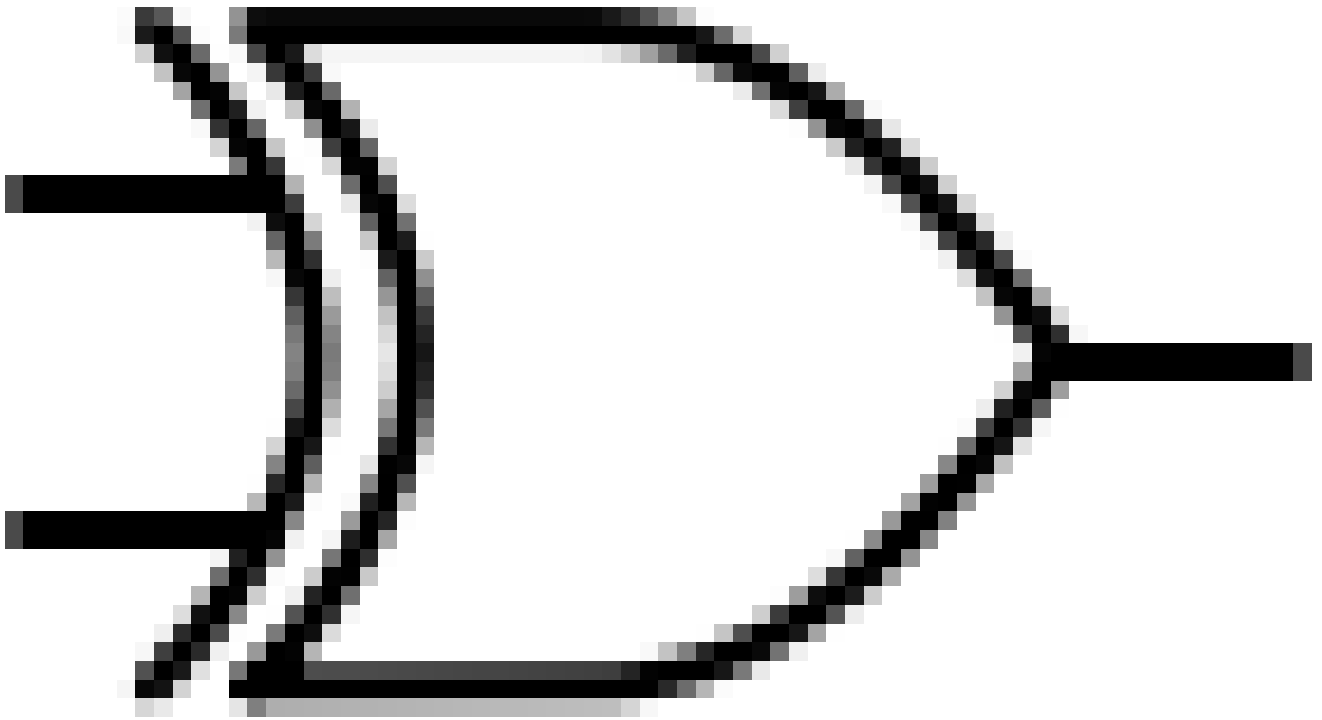Question 23:

What is the output of the XOR gate with inputs 1, 0?



Options:


1. 1

2. 0

Correct Answer: 1

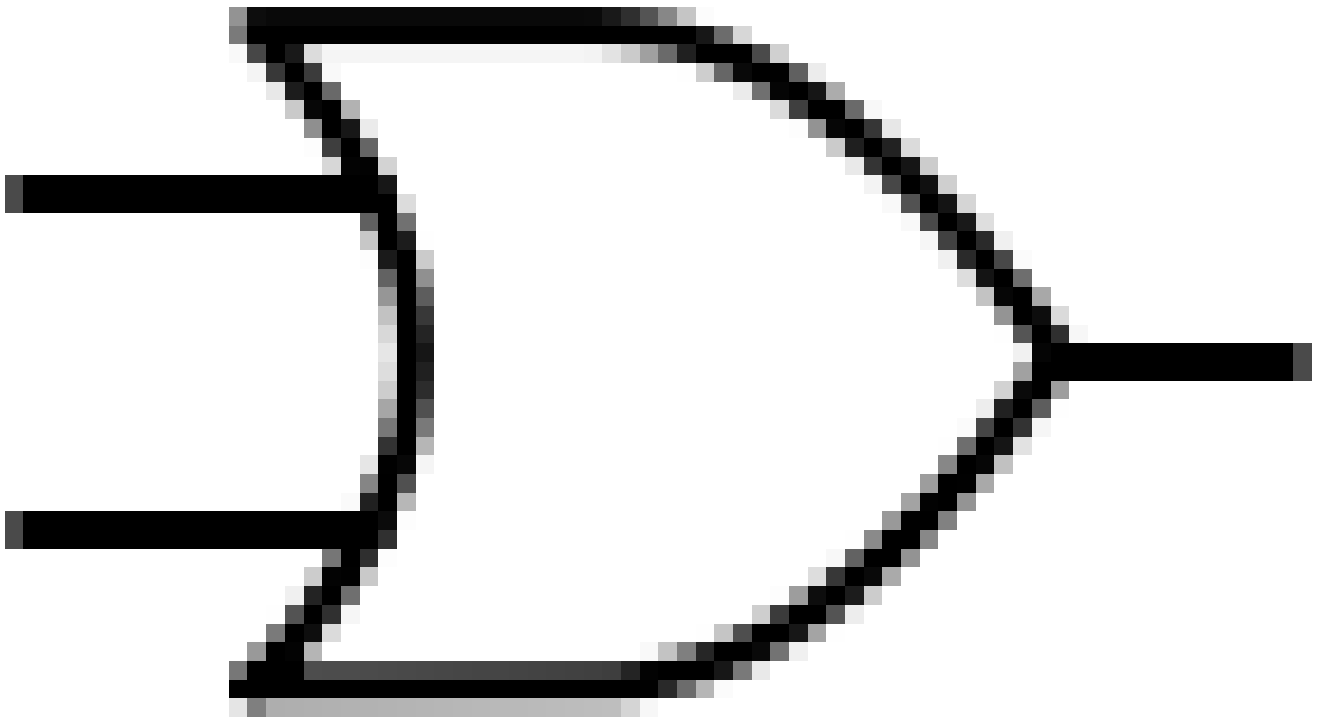Question 24:

What is the output of the OR gate with inputs 1, 0?



Options:

1. 0

2. 1



Correct Answer: 1

Question 25:

Are these two circuits equivalent?

Expression 1:  $((a \oplus b) \oplus (c \wedge a)) \oplus ((\neg c) \vee (\neg a))$

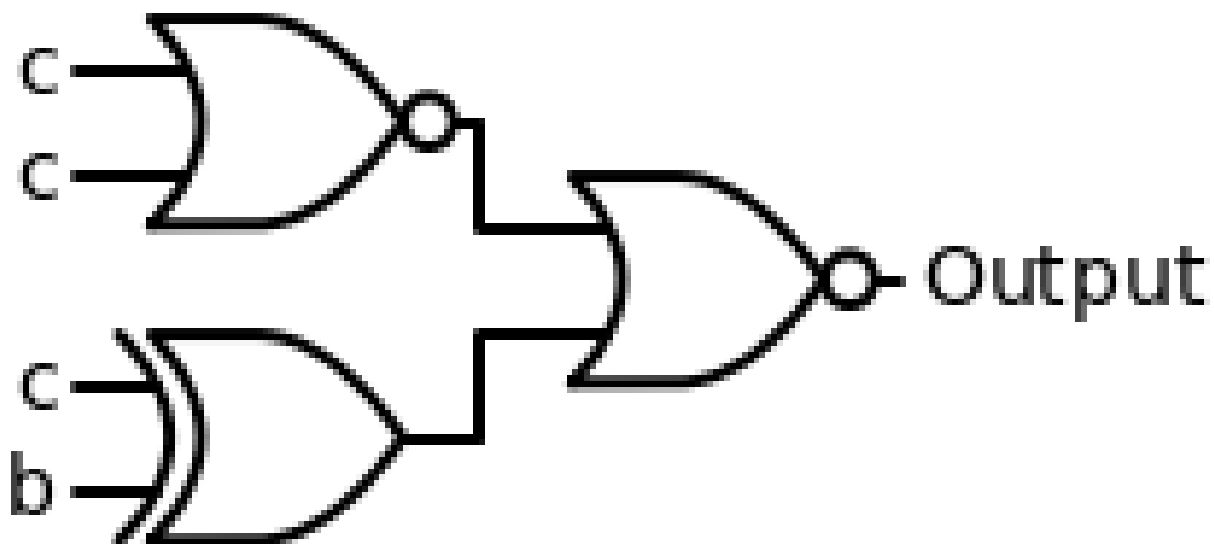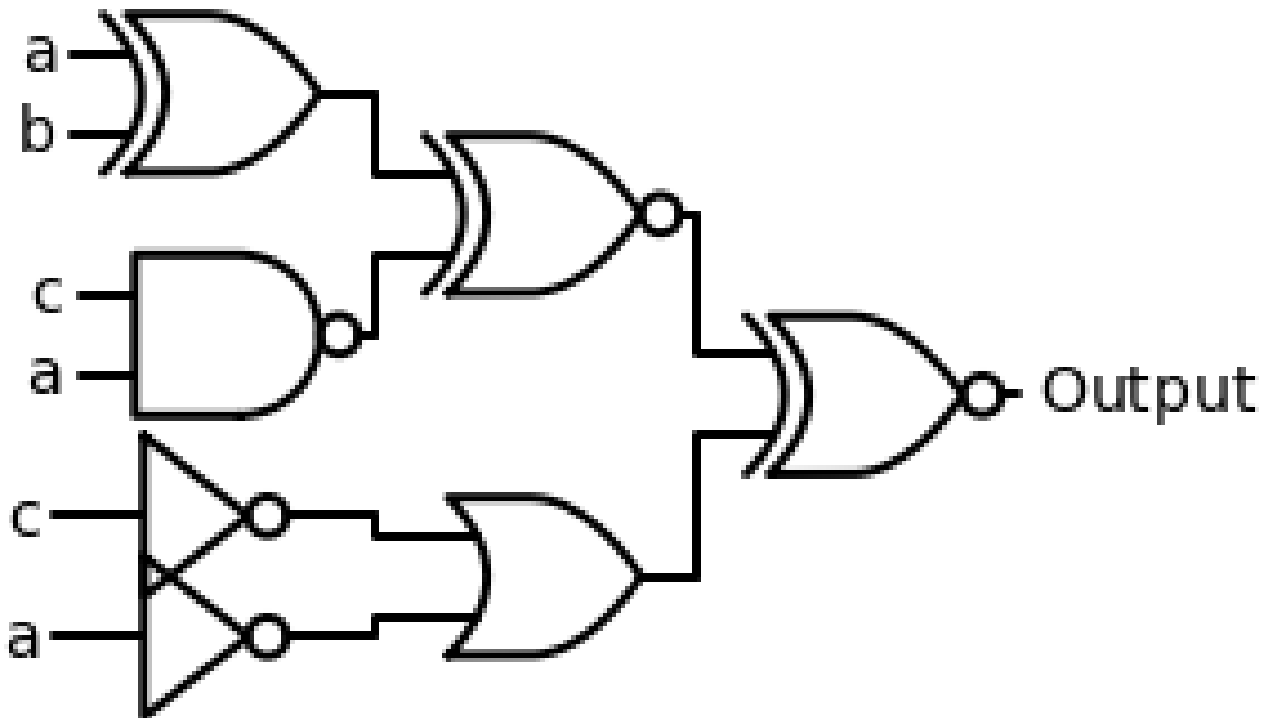Expression 2:  $((c \text{ nor } c) \text{ nor } (c \oplus b))$



Options:


1. Yes

2. No

Correct Answer: no

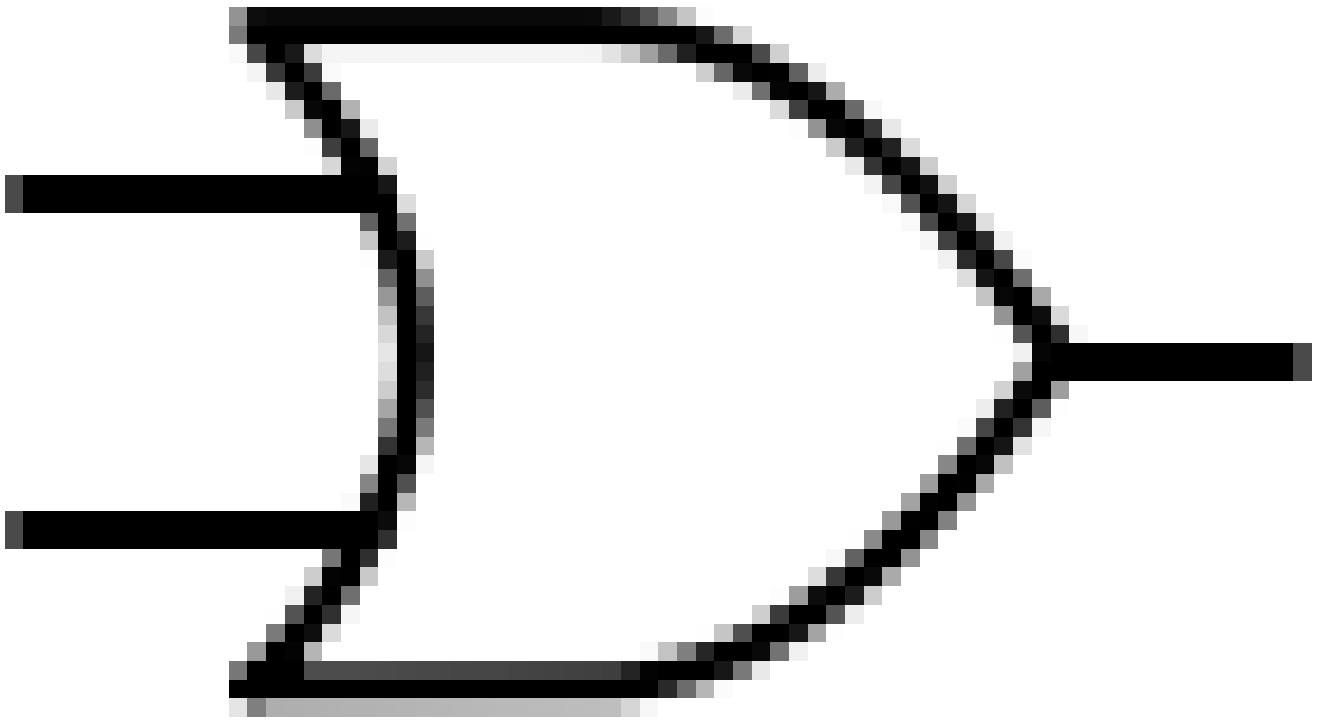Question 26:

What is the output of the OR gate with inputs 1, 0?



Options:

1. 1

2. 0



Correct Answer: 1

Question 27:

Are these two circuits equivalent?

Expression 1: (not c)

Expression 2: (not c)

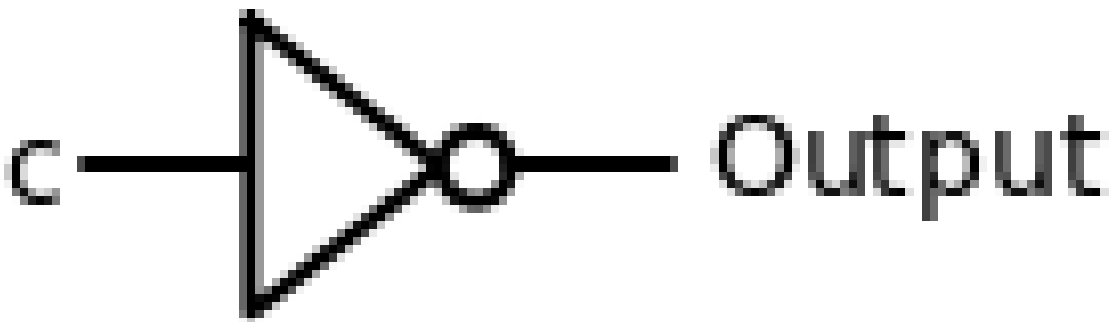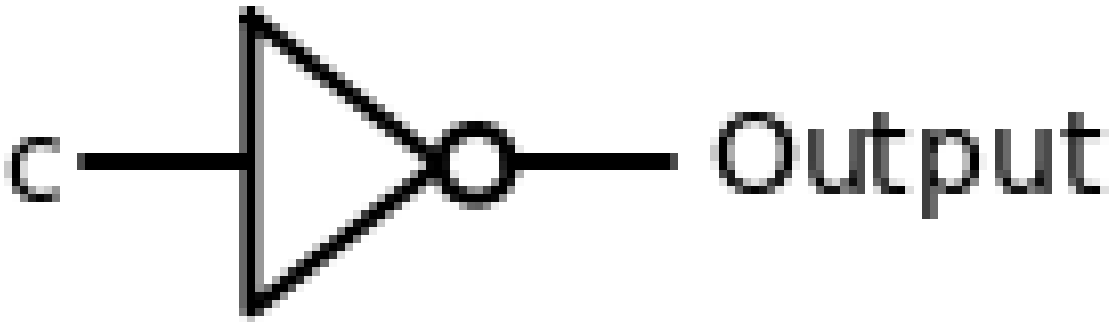


Options:

1. Yes
2. No

Correct Answer: yes

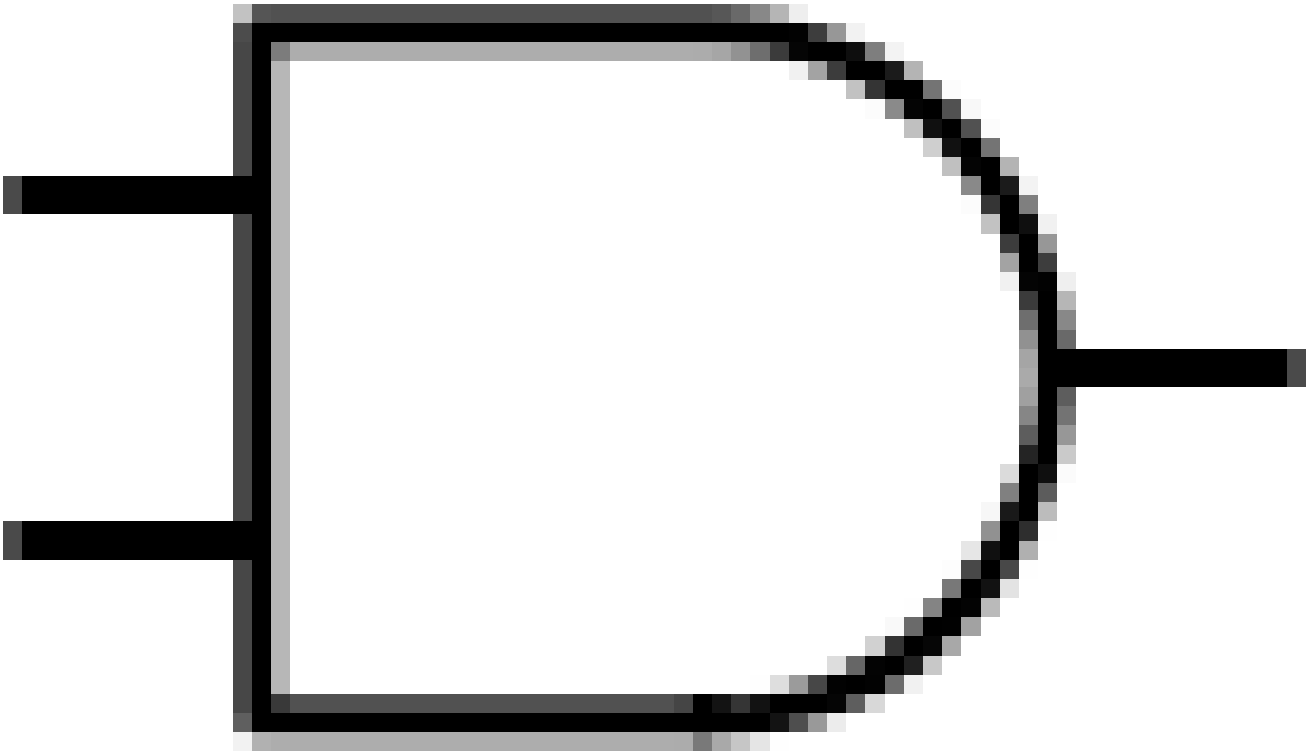Question 28:

What is the output of the AND gate with inputs 1, 0?



Options:


1. 1

2. 0

Correct Answer: 0

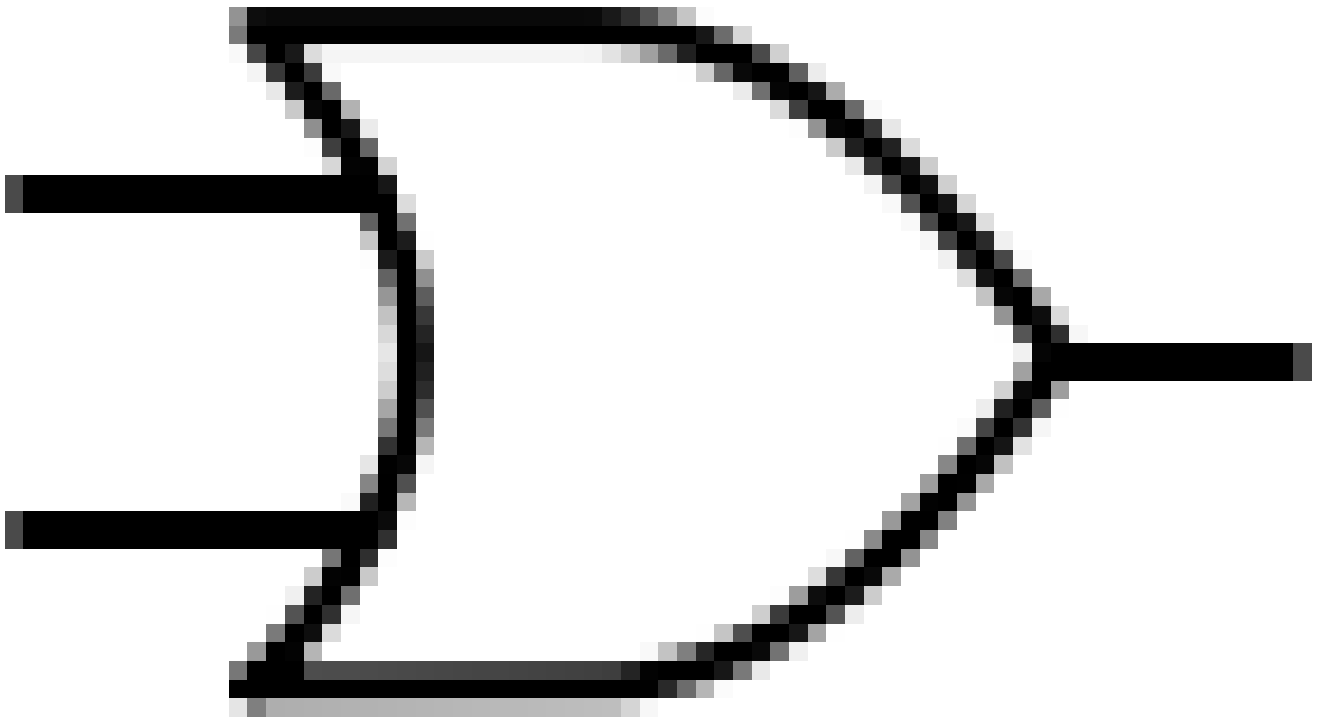Question 29:

What is the output of the OR gate with inputs 0, 0?



Options:

1. 0

2. 1

Correct Answer: 0





Question 30:

Are these two circuits equivalent?

Expression 1: (not b)

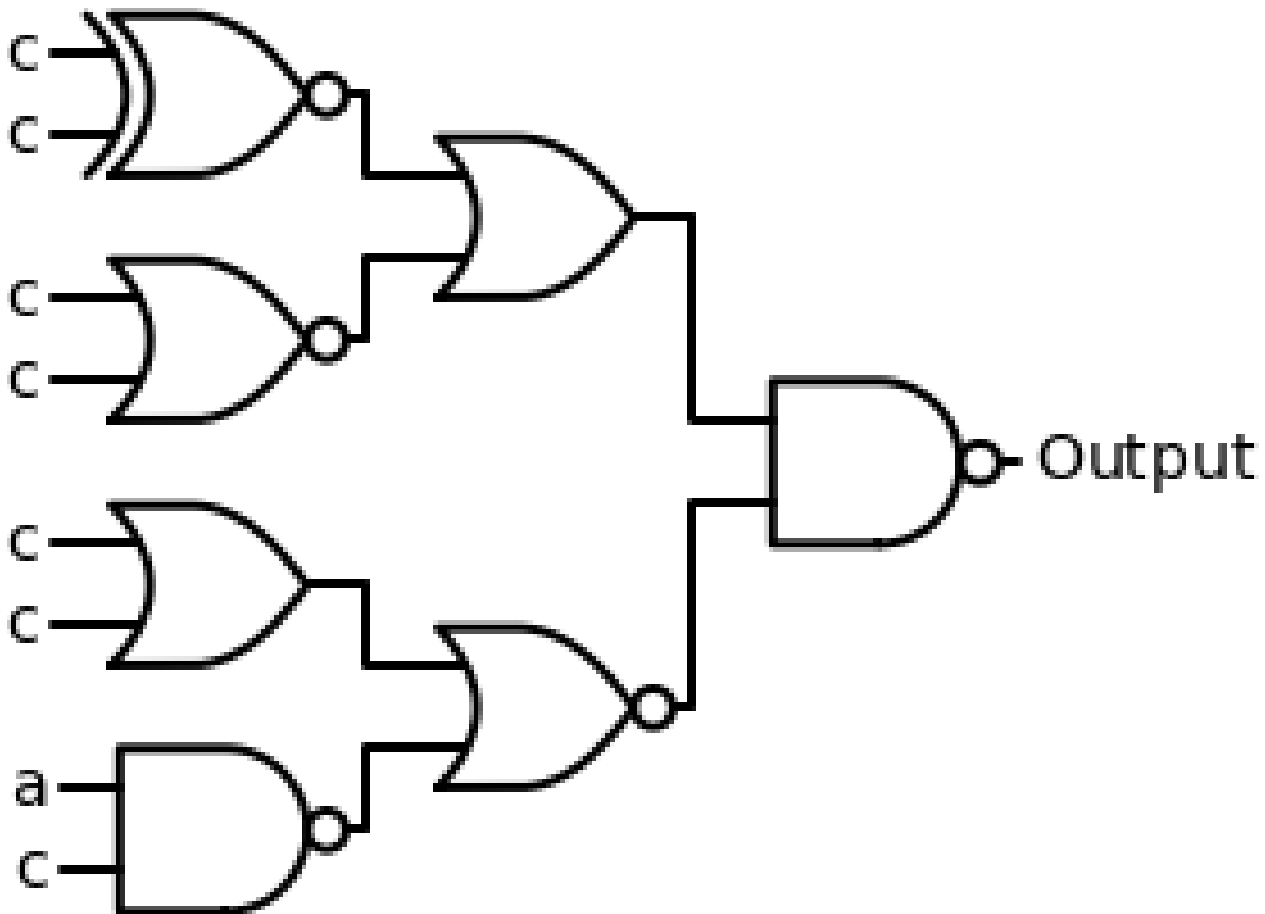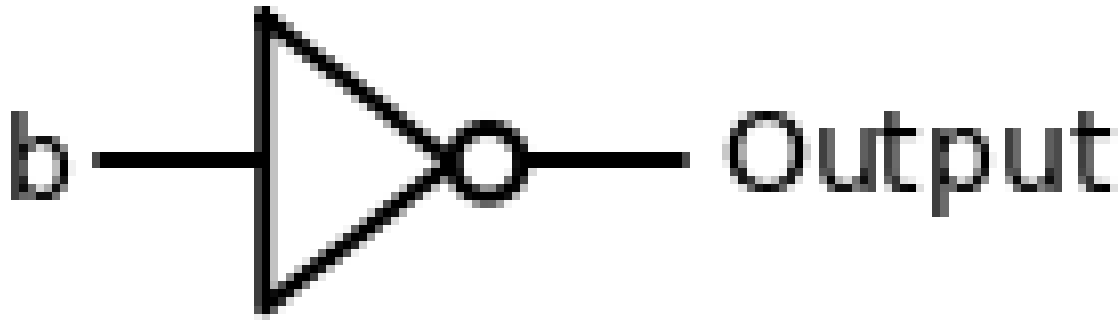Expression 2: (((c xnor c) or (c nor c)) nand ((c or c) nor (a nand c)))



Options:

1. Yes

2. No

Correct Answer: no