

Question 1:

Construct the truth table for the following logic circuit with 2 inputs.

Input 1	Input 2	Output
0	0	0
1	0	1
0	1	1
1	1	1

Question 2:

Construct the truth table for the following logic circuit with 2 inputs.

Input 1	Input 2	Output
0	0	0
1	0	1
0	1	1
1	1	1