


### Question 1:

What is the output of the AND gate with inputs 0, 1?

Options:

1. 1

2. 0

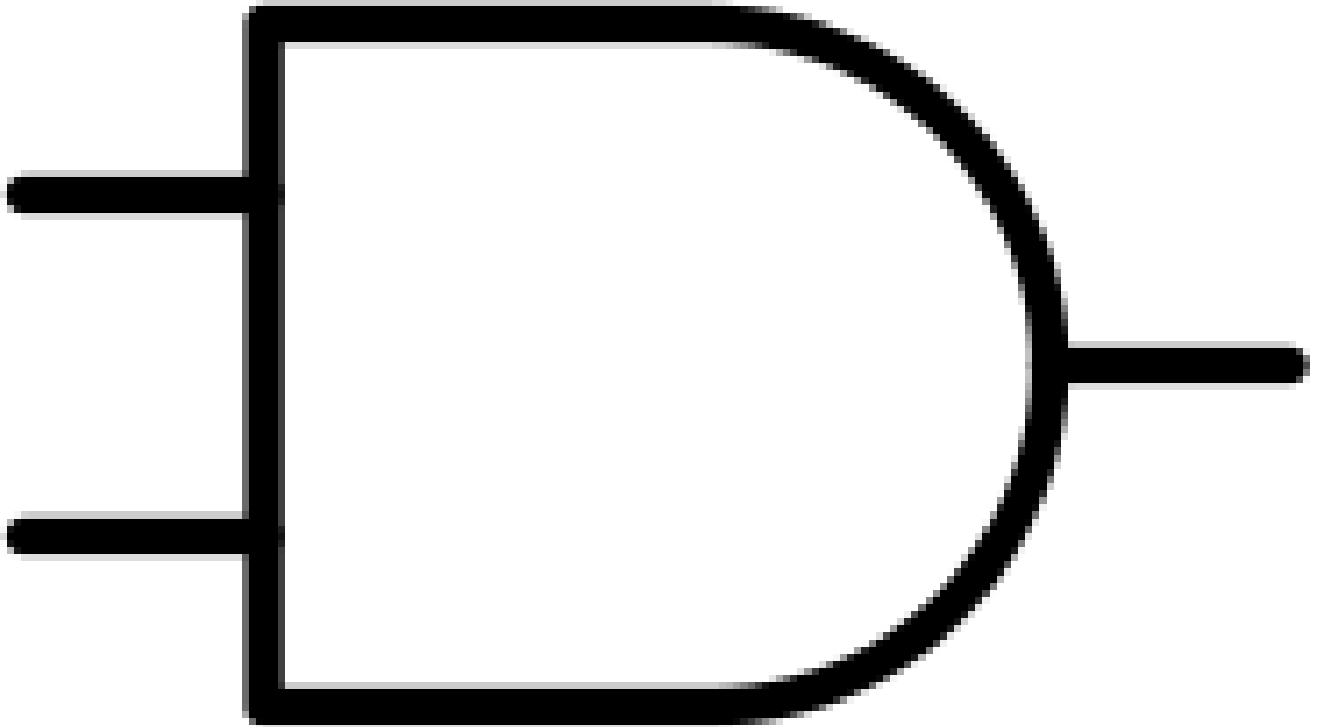

Correct Answer: 0

Question 2:

Are these two circuits equivalent?



Expression 1:  $(\text{not } ((\text{not } c) \text{ nand } (\text{not } a)))$

Expression 2:  $(\text{not } ((\text{not } c) \text{ nand } (\text{not } a)))$

Options:

1. Yes

2. No

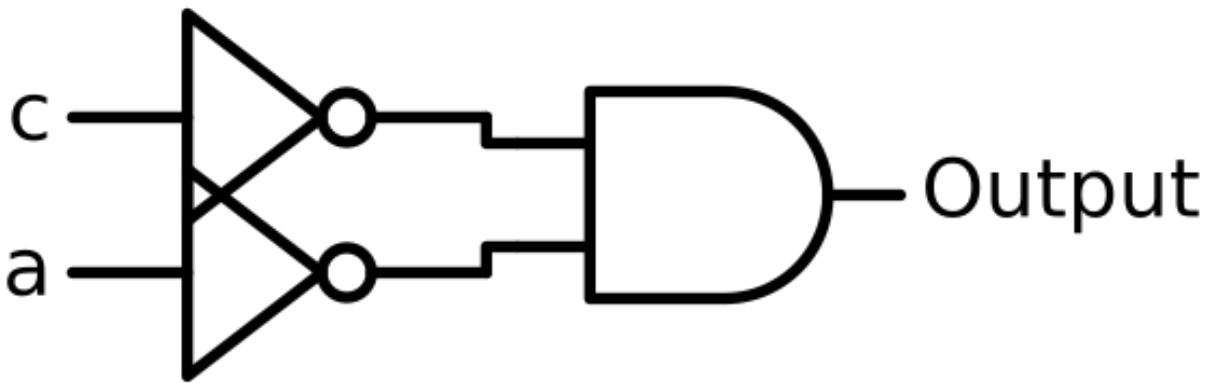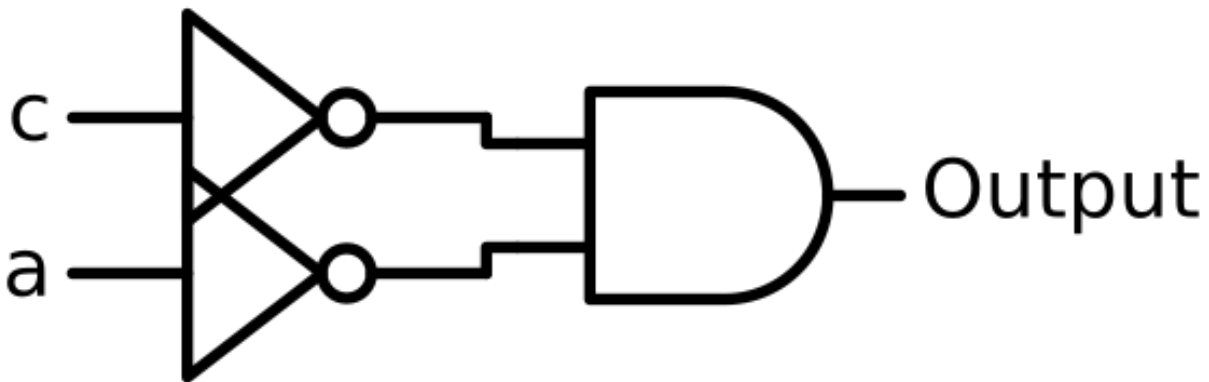

Correct Answer: yes

Question 3:



Are these two circuits equivalent?

Expression 1:  $(a \text{ nand } c)$

Expression 2:  $(a \text{ nand } c)$

Options:

1. Yes
2. No

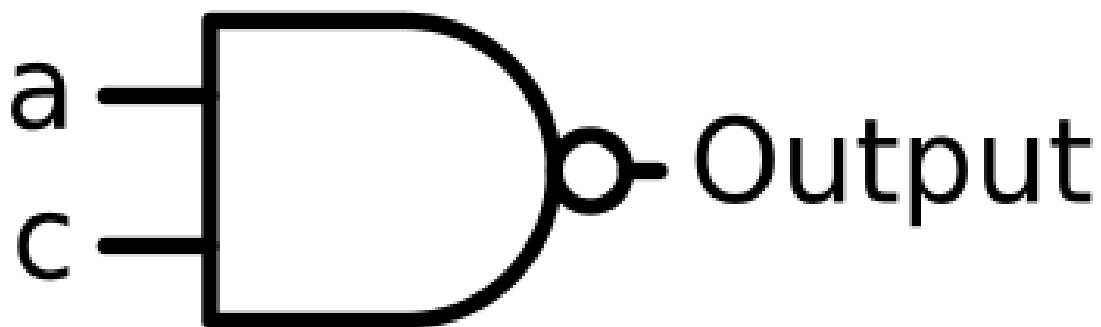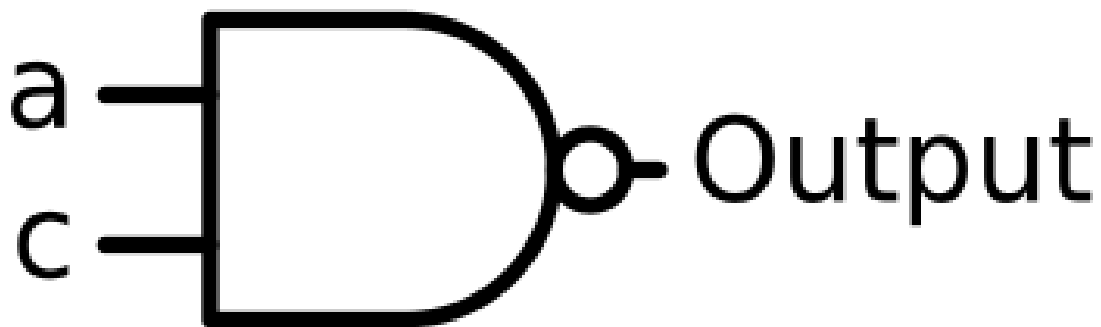

Correct Answer: yes


Question 4:

What is the output of the XOR gate with inputs 1, 1?

Options:

1. 0

2. 1

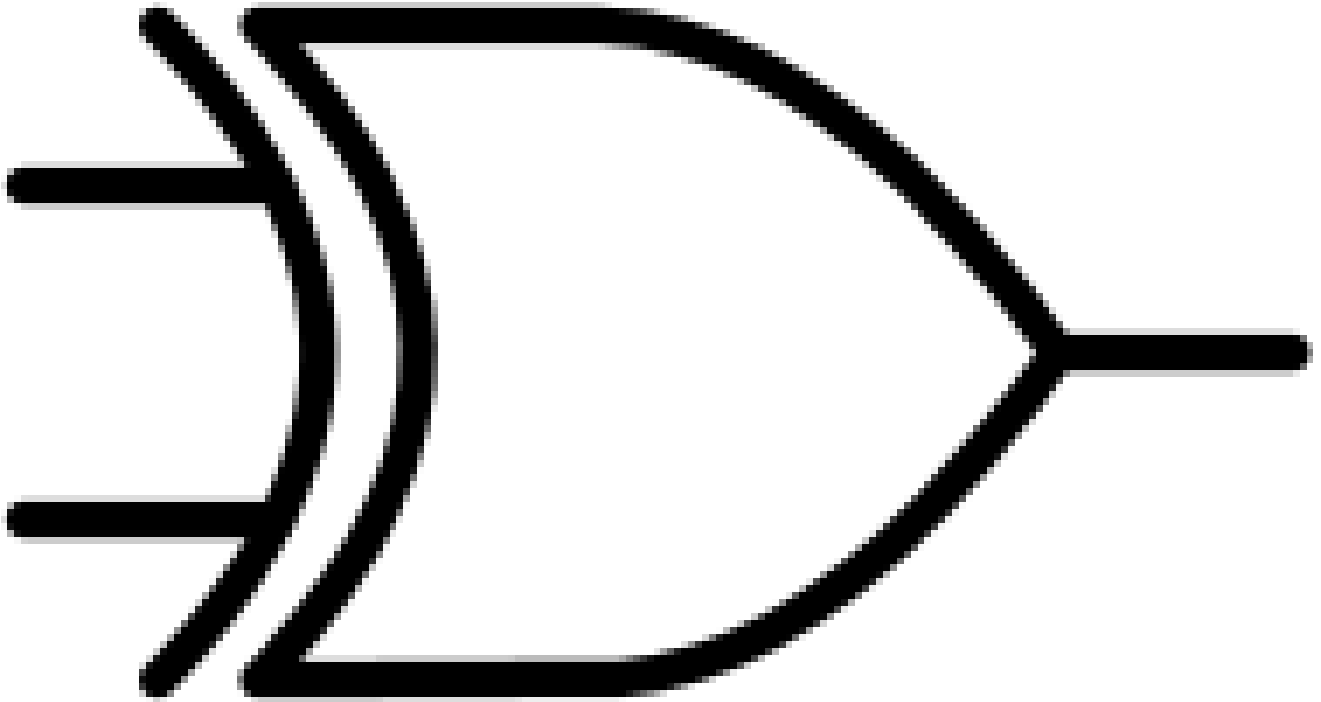

Correct Answer: 0


Question 5:

What is the output of the NOT gate with input 0?

Options:

1. 1

2. 0

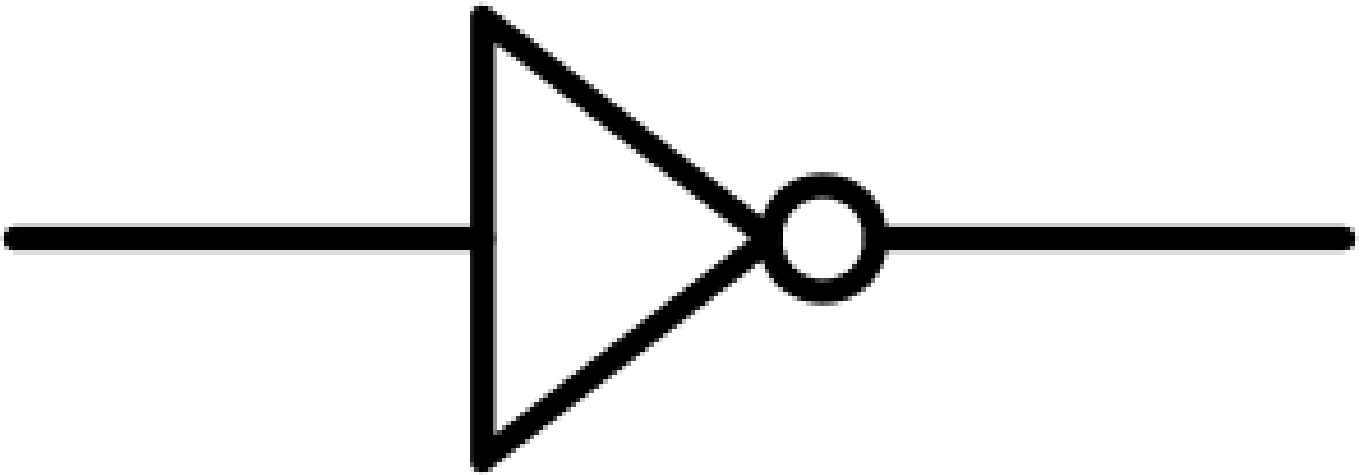

Correct Answer: 1


Question 6:

What is the output of the NOT gate with input 1?

Options:

1. 1

2. 0

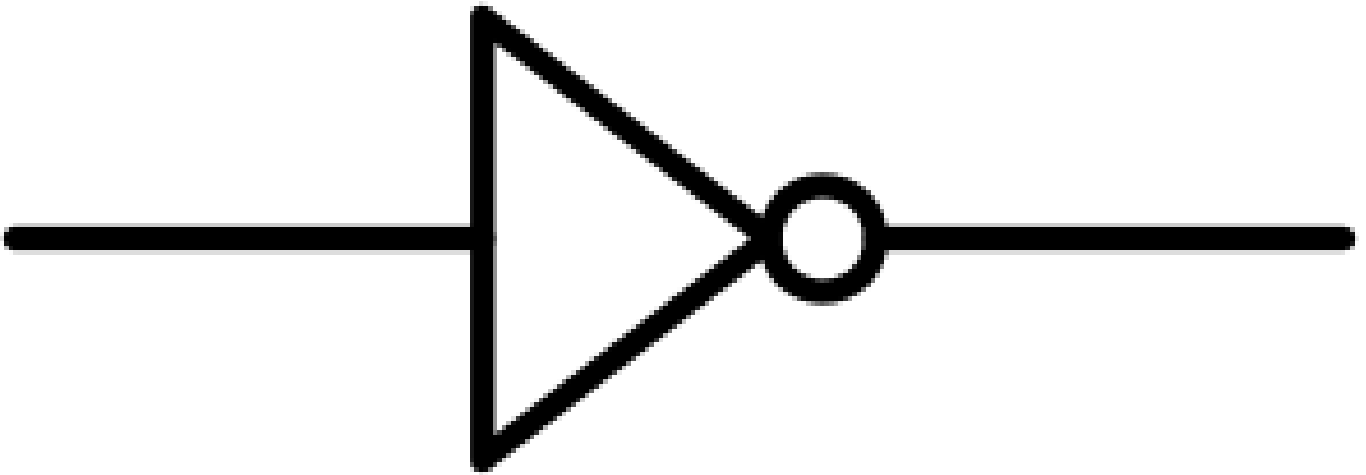

Correct Answer: 0

### Question 7:


Are these two circuits equivalent?


Expression 1:  $((c \text{ nand } c) \text{ and } (a \text{ nand } b)) \text{ nor } ((c \text{ nand } c) \text{ xnor } (c \text{ nand } a))$

Expression 2:  $((c \text{ nand } c) \text{ and } (a \text{ nand } b)) \text{ nor } ((c \text{ nand } c) \text{ xnor } (c \text{ nand } a))$

Options:

1. Yes
2. No

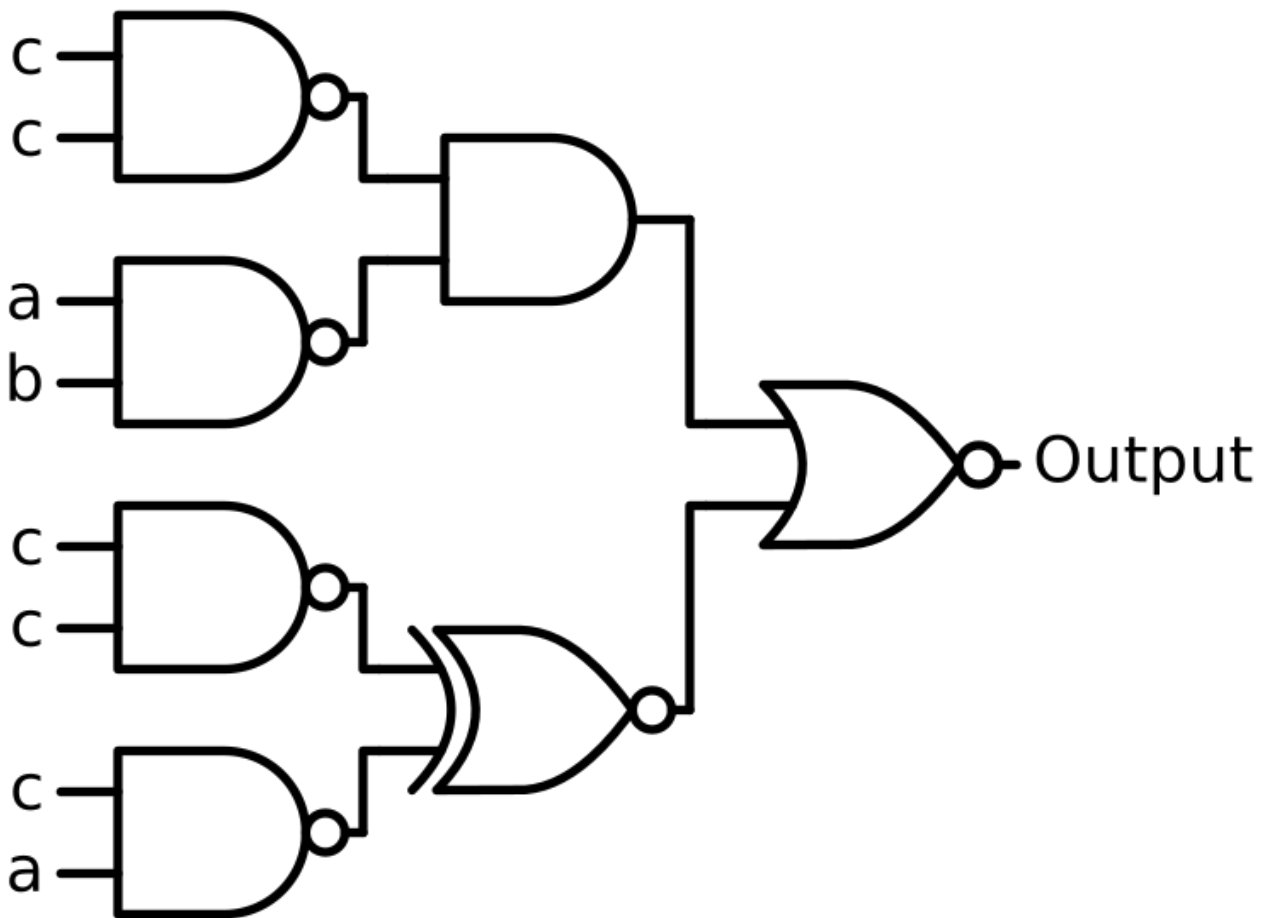

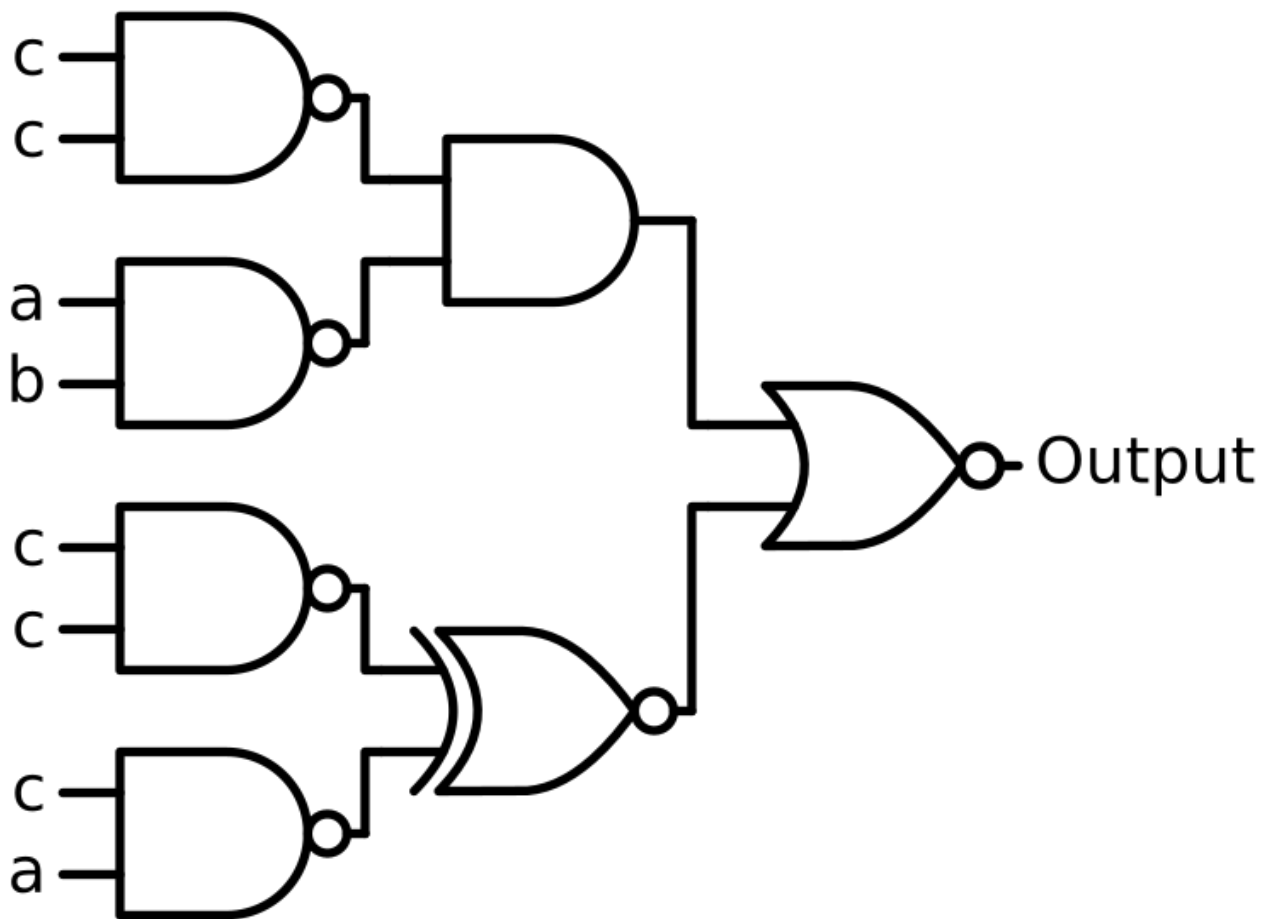

Correct Answer: yes




Question 8:

What is the output of the NOT gate with input 1?

Options:

1. 0

2. 1

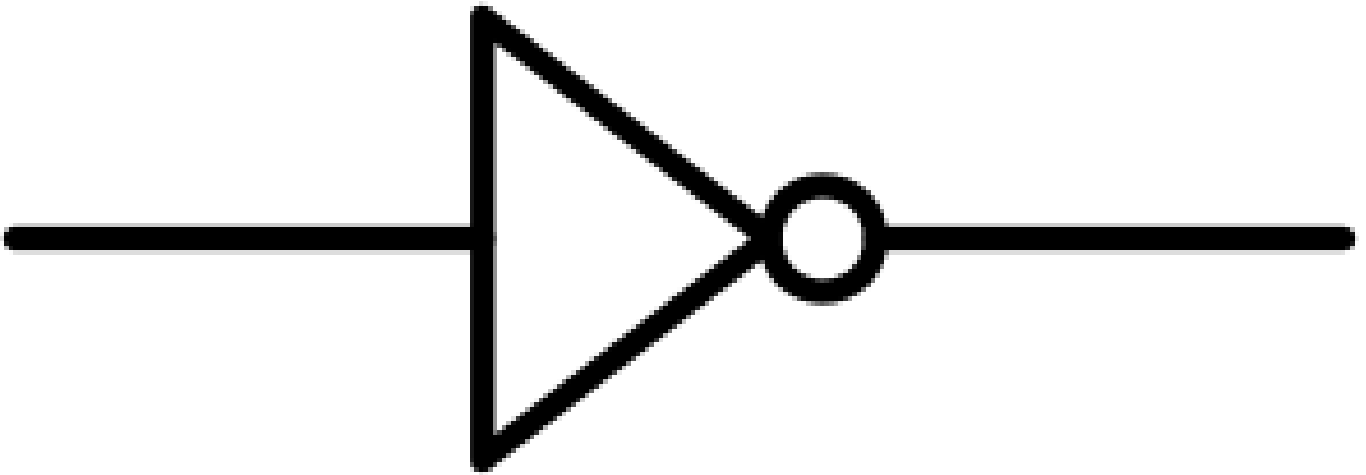

Correct Answer: 0


Question 9:

What is the output of the NOT gate with input 1?

Options:

1. 0

2. 1

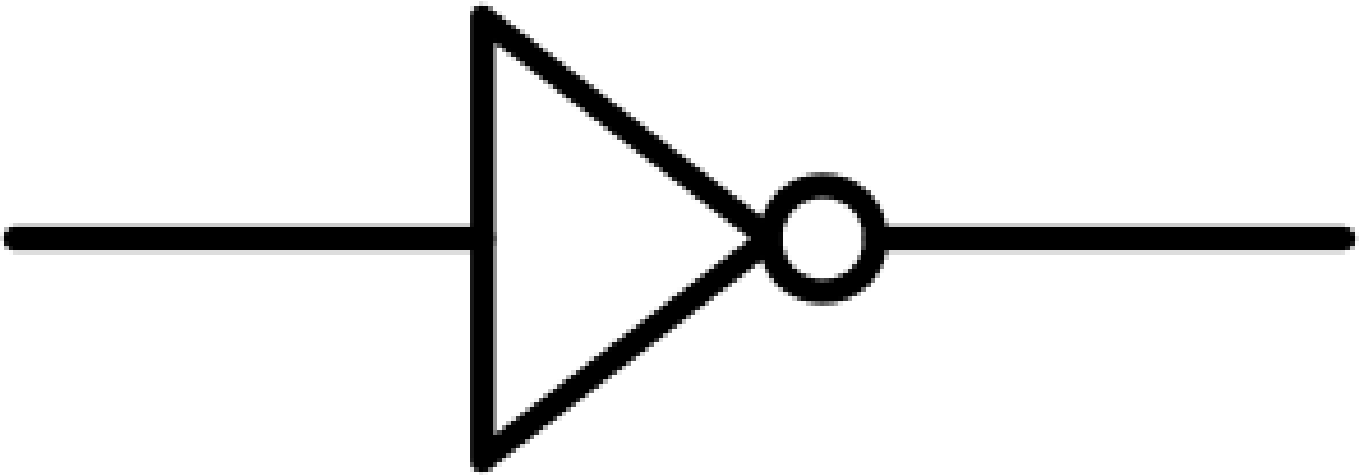

Correct Answer: 0

Question 10:



Are these two circuits equivalent?

Expression 1: (not c)

Expression 2: (((b nor c) and (a xnor a)) or ((c xor c) or (c xnor c)))

Options:

1. Yes
2. No

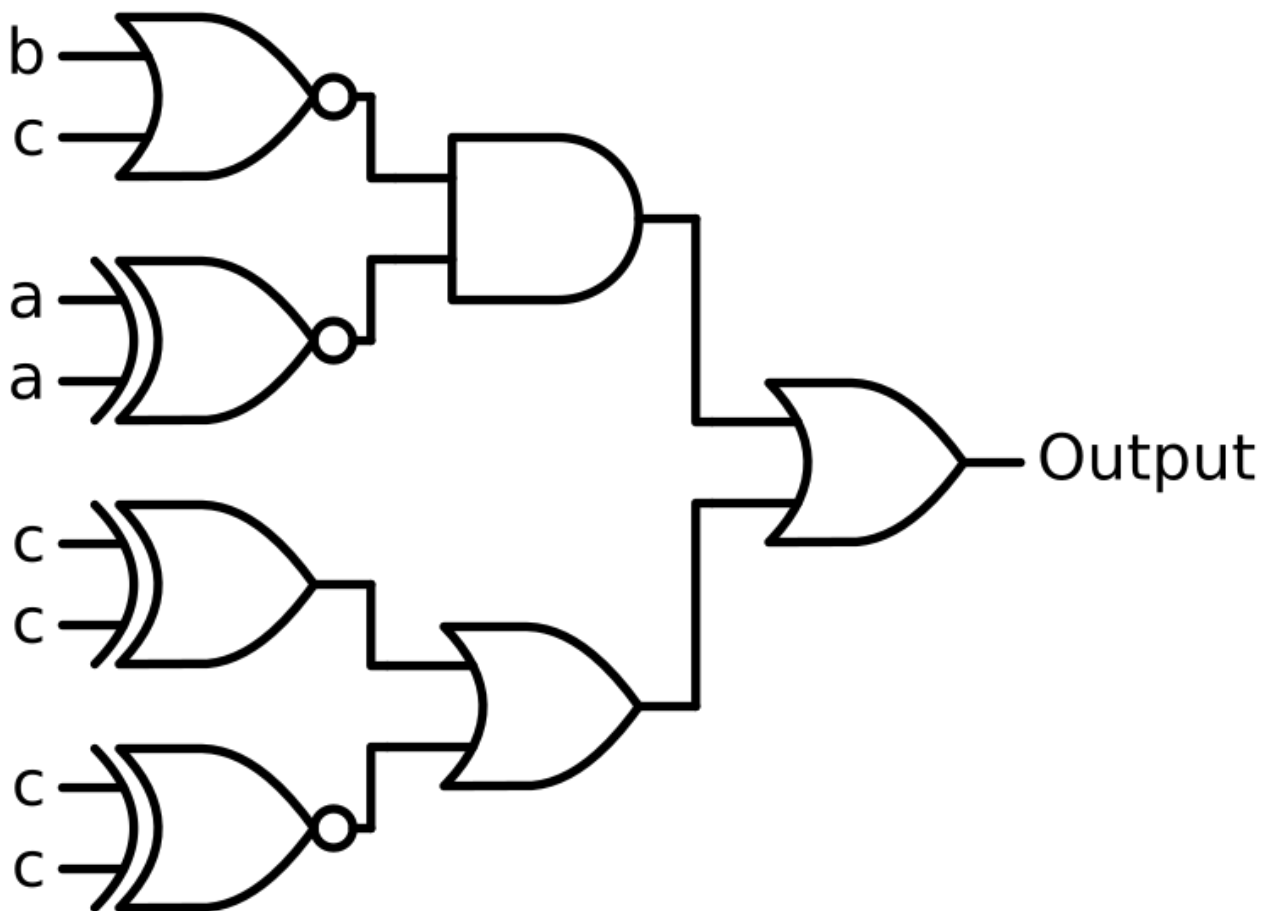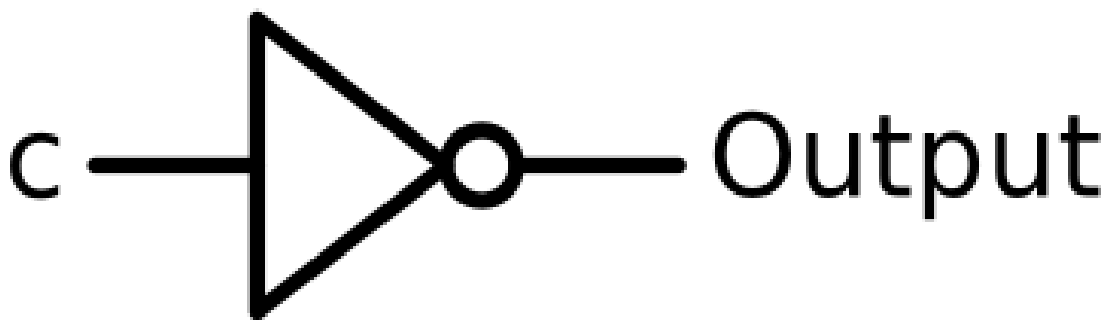

Correct Answer: no


Question 11:

What is the output of the NOR gate with inputs 0, 1?

Options:

1. 0

2. 1

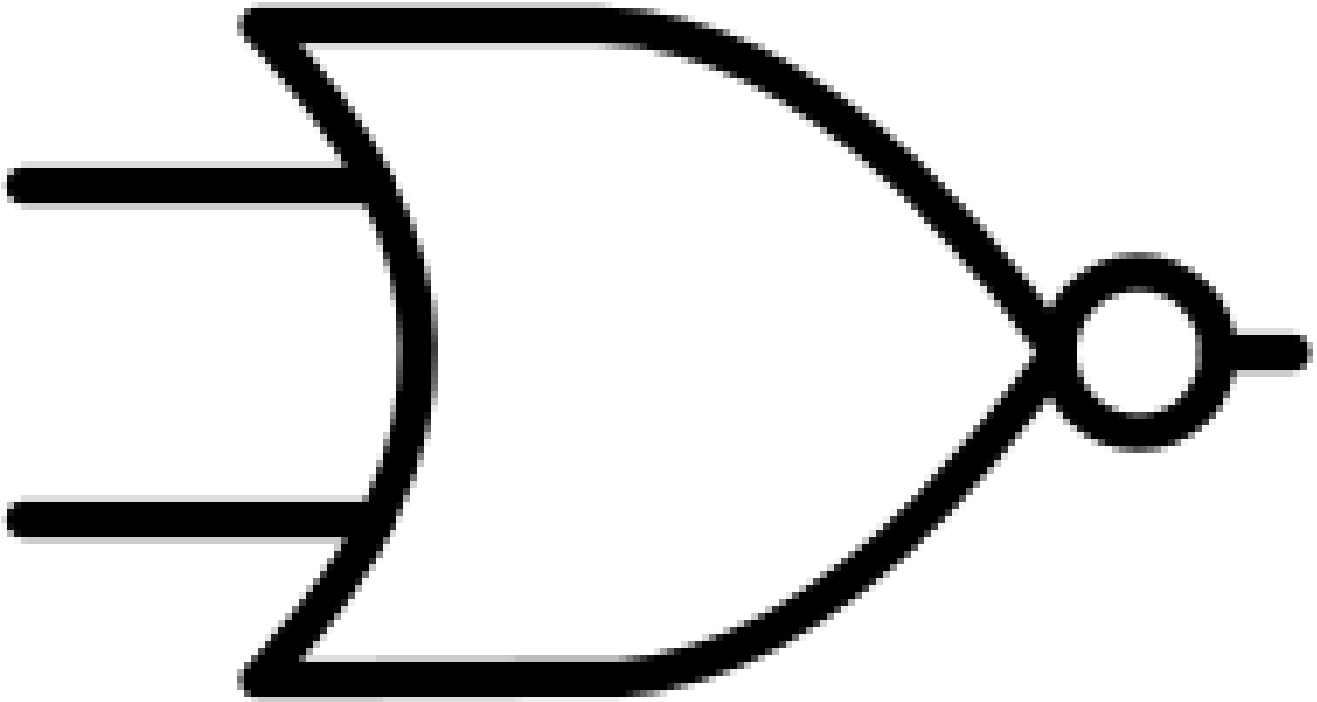

Correct Answer: 0


Question 12:

What is the output of the AND gate with inputs 1, 0?

Options:

1. 1

2. 0

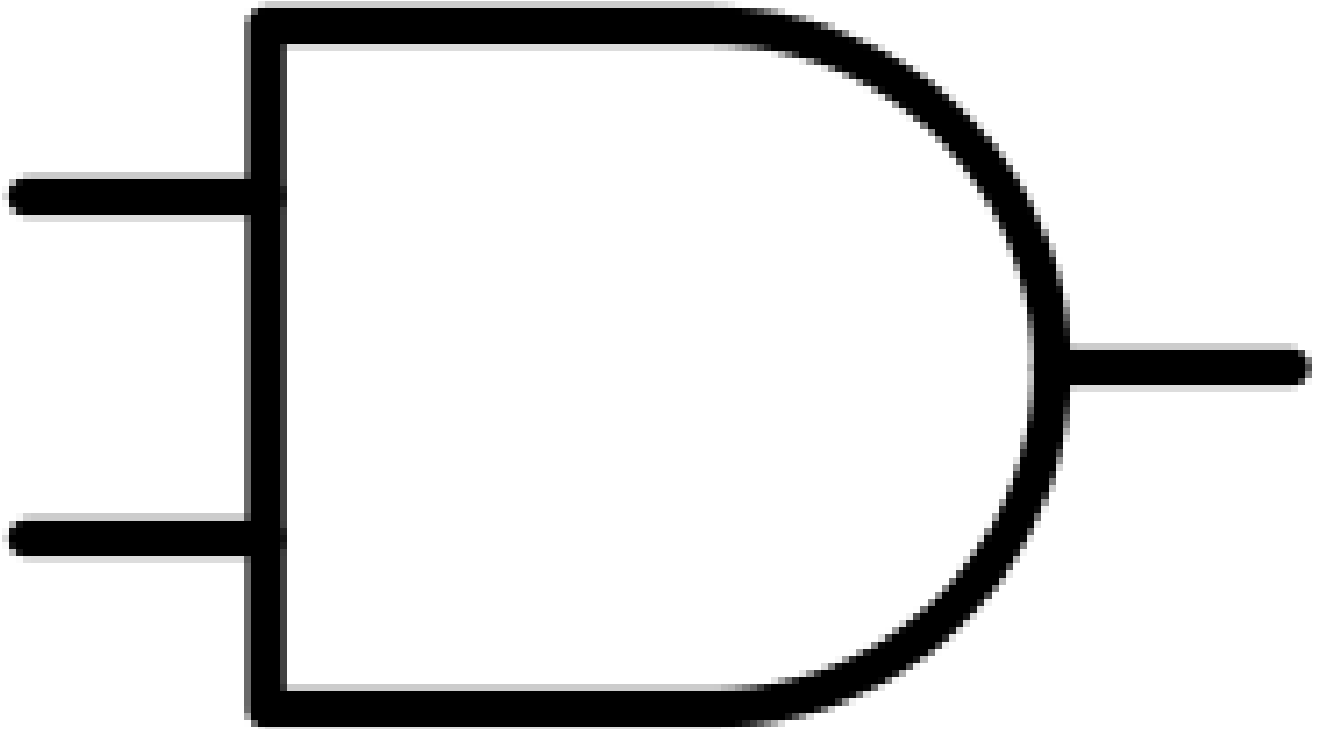

Correct Answer: 0

Question 13:

Are these two circuits equivalent?


Expression 1:  $((b \text{ xor } b) \text{ nor } (c \text{ and } b))$

Expression 2:  $((a \text{ or } a) \text{ or } (a \text{ xor } b))$

Options:

1. Yes

2. No

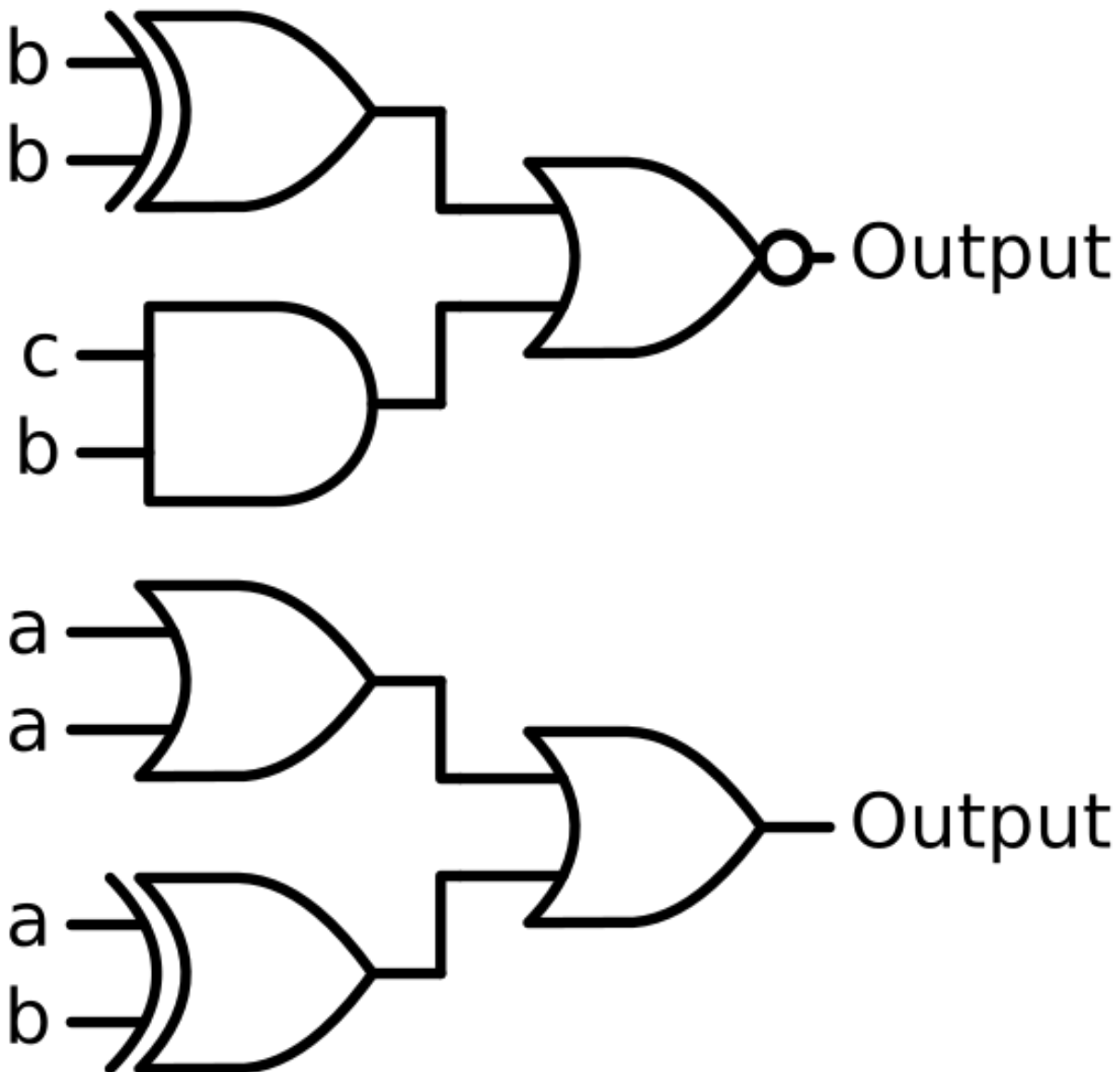

Correct Answer: no


Question 14:

What is the output of the NAND gate with inputs 1, 1?

Options:

1. 0

2. 1

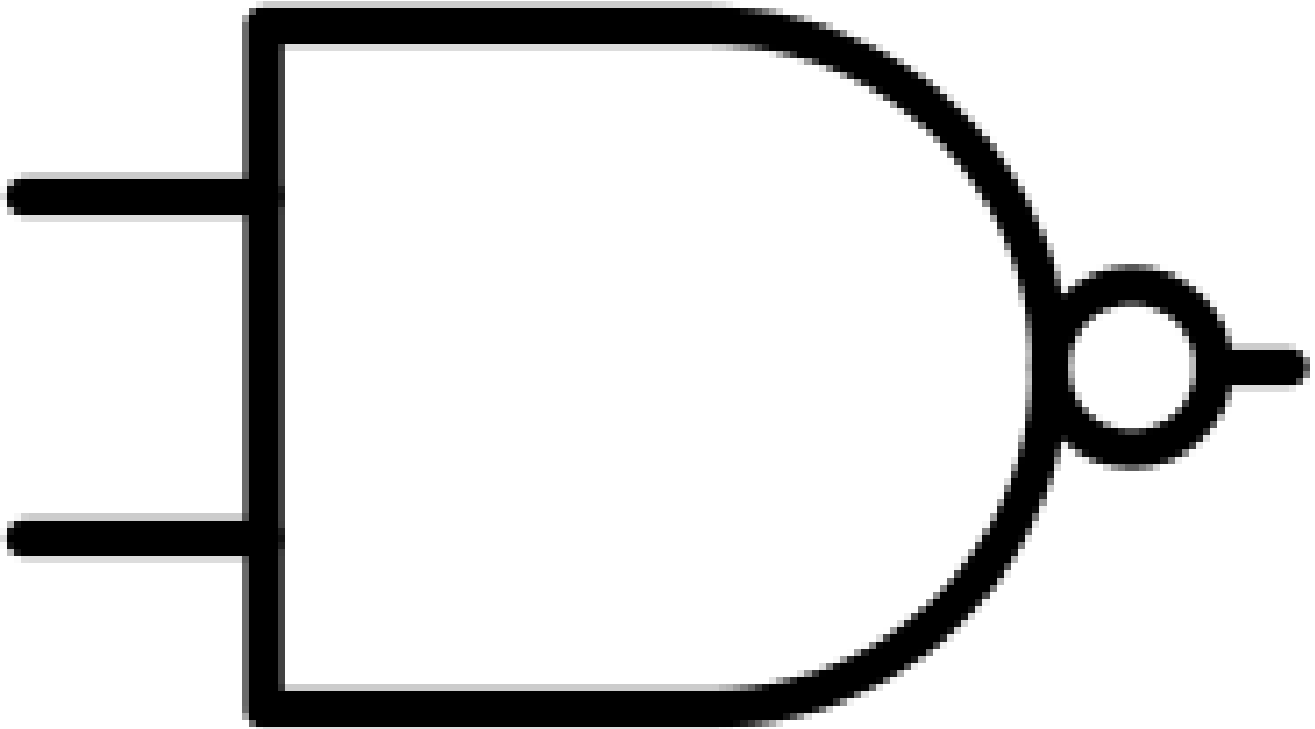

Correct Answer: 0


Question 15:

What is the output of the OR gate with inputs 1, 1?

Options:

1. 1

2. 0

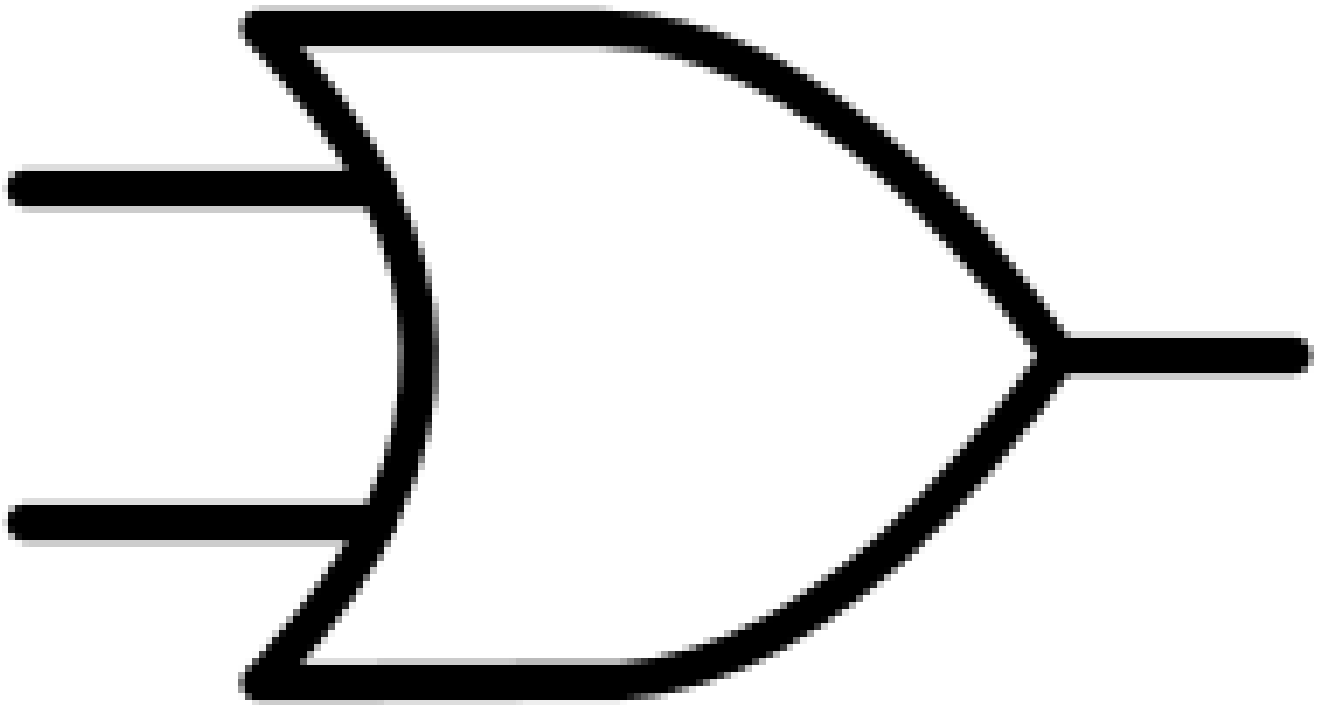

Correct Answer: 1




Question 16:

What is the output of the NAND gate with inputs 0, 0?

Options:

1. 0

2. 1

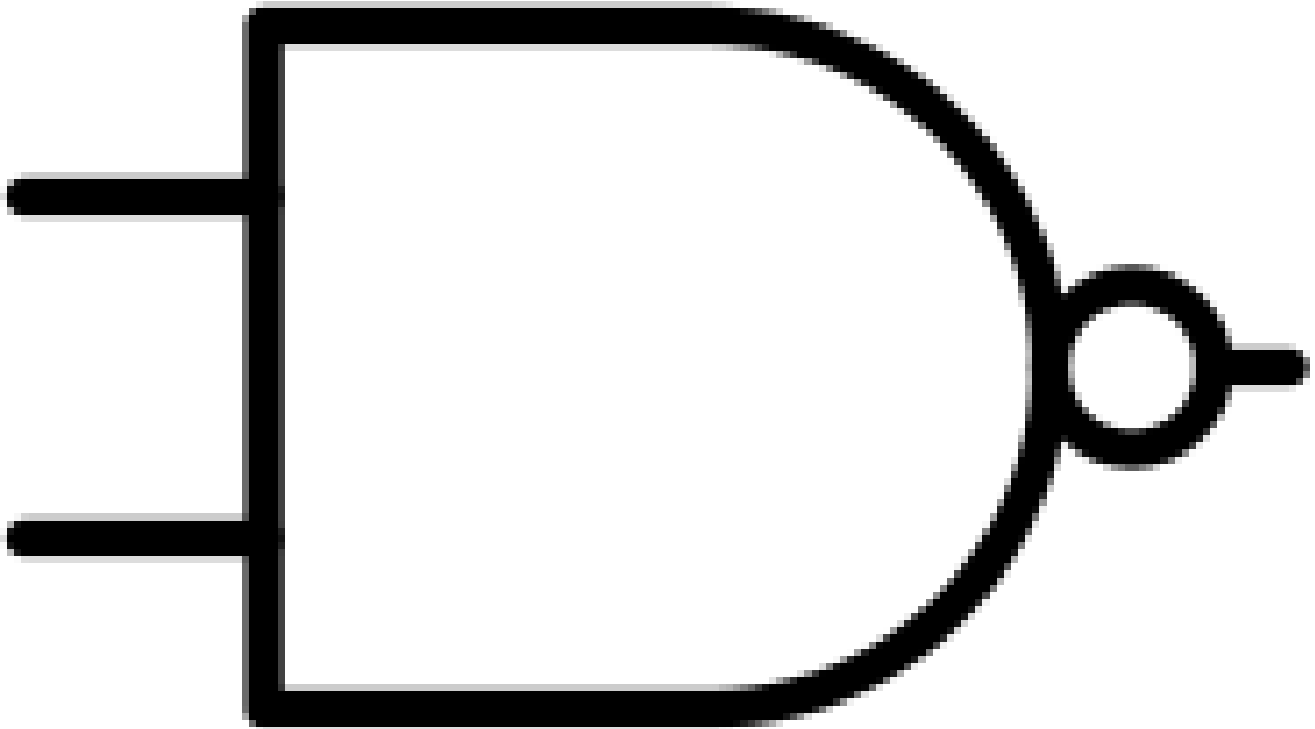

Correct Answer: 1


Question 17:

What is the output of the XOR gate with inputs 0, 0?

Options:

1. 0

2. 1

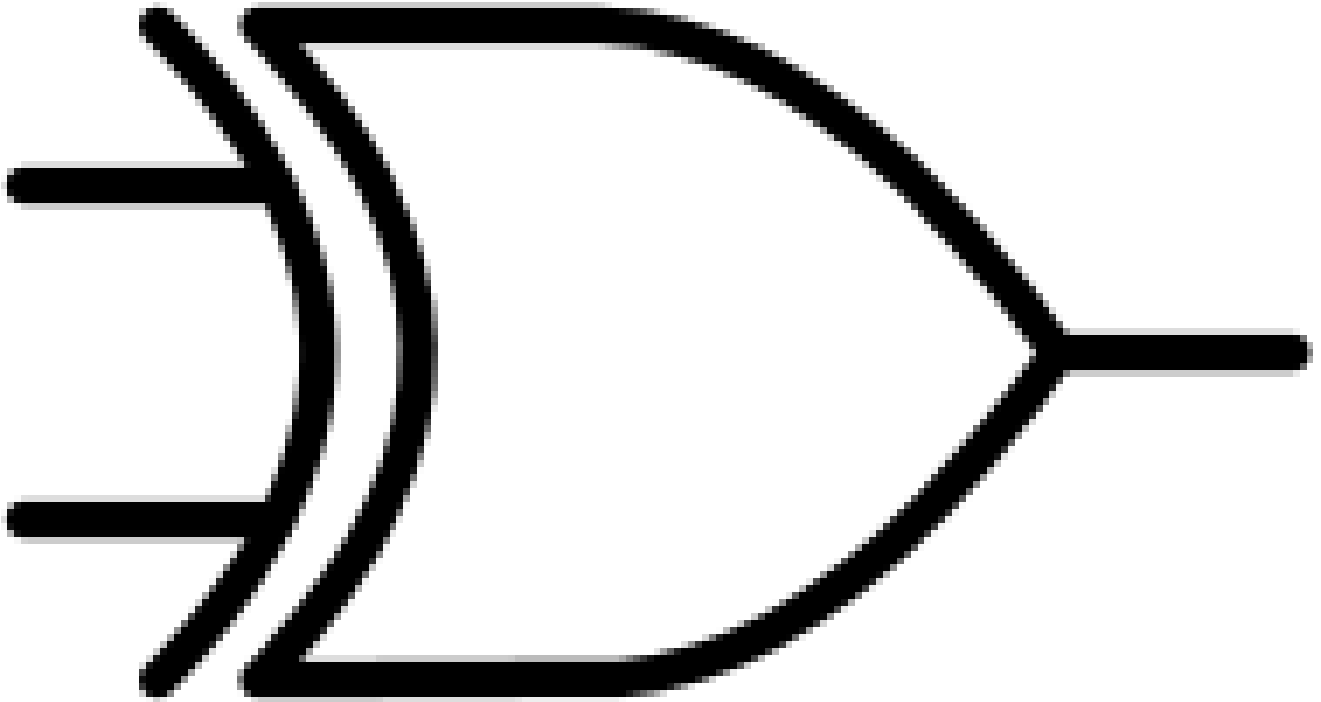

Correct Answer: 0

Question 18:

Are these two circuits equivalent?


Expression 1:  $(\text{not } ((a \text{ xnor } c) \text{ xor } (c \text{ nor } c)))$

Expression 2:  $(\text{not } ((a \text{ xnor } c) \text{ xor } (c \text{ nor } c)))$

Options:

1. Yes

2. No

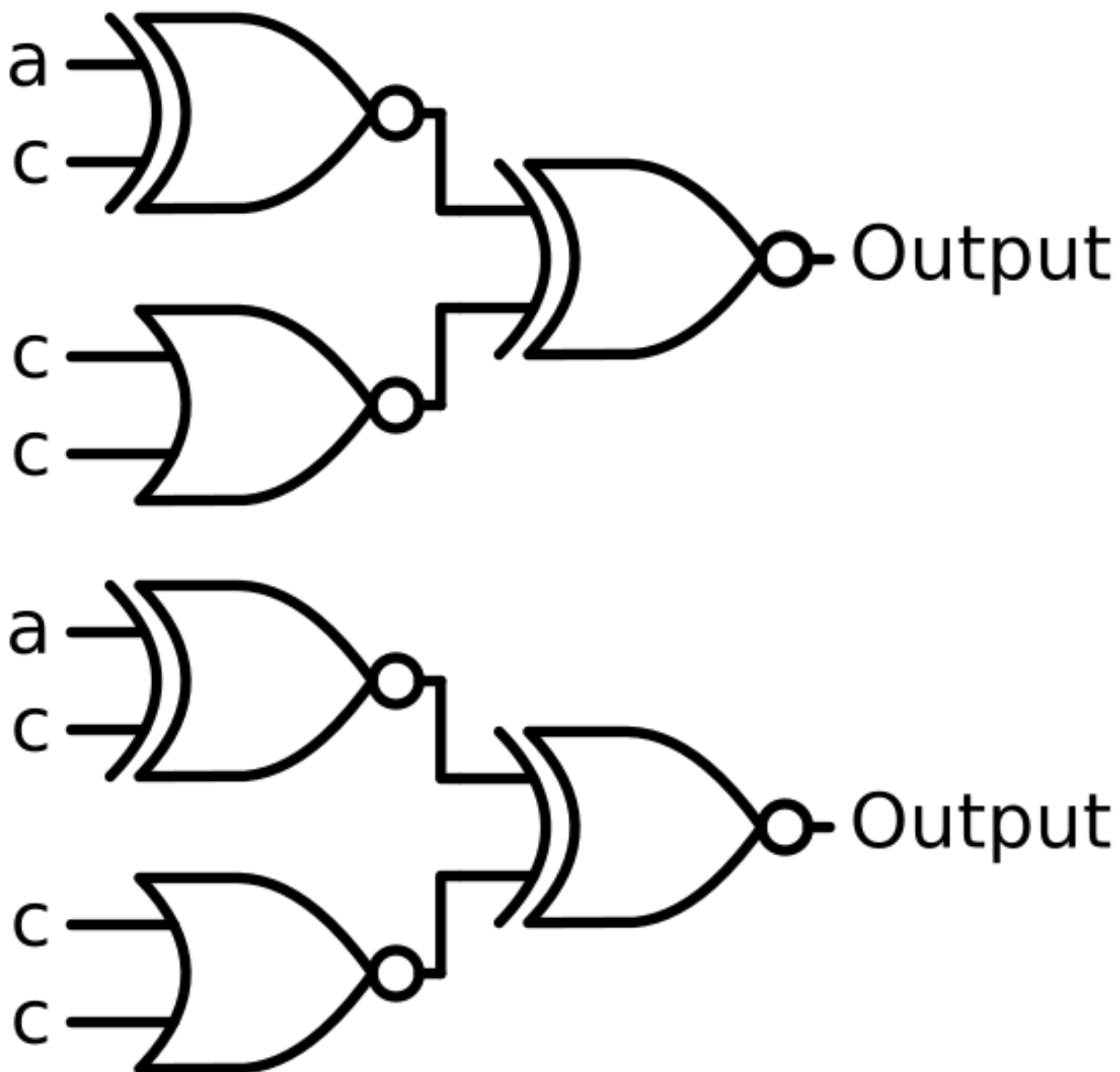

Correct Answer: yes


Question 19:

What is the output of the NOT gate with input 0?

Options:

1. 1

2. 0

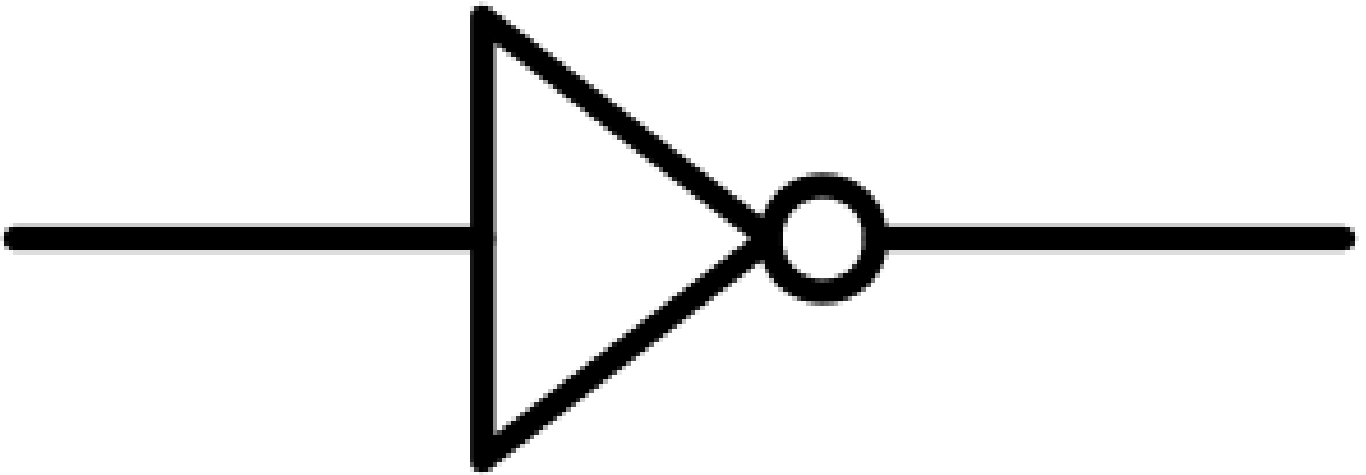

Correct Answer: 1


Question 20:

What is the output of the NOR gate with inputs 0, 0?

Options:

1. 1

2. 0

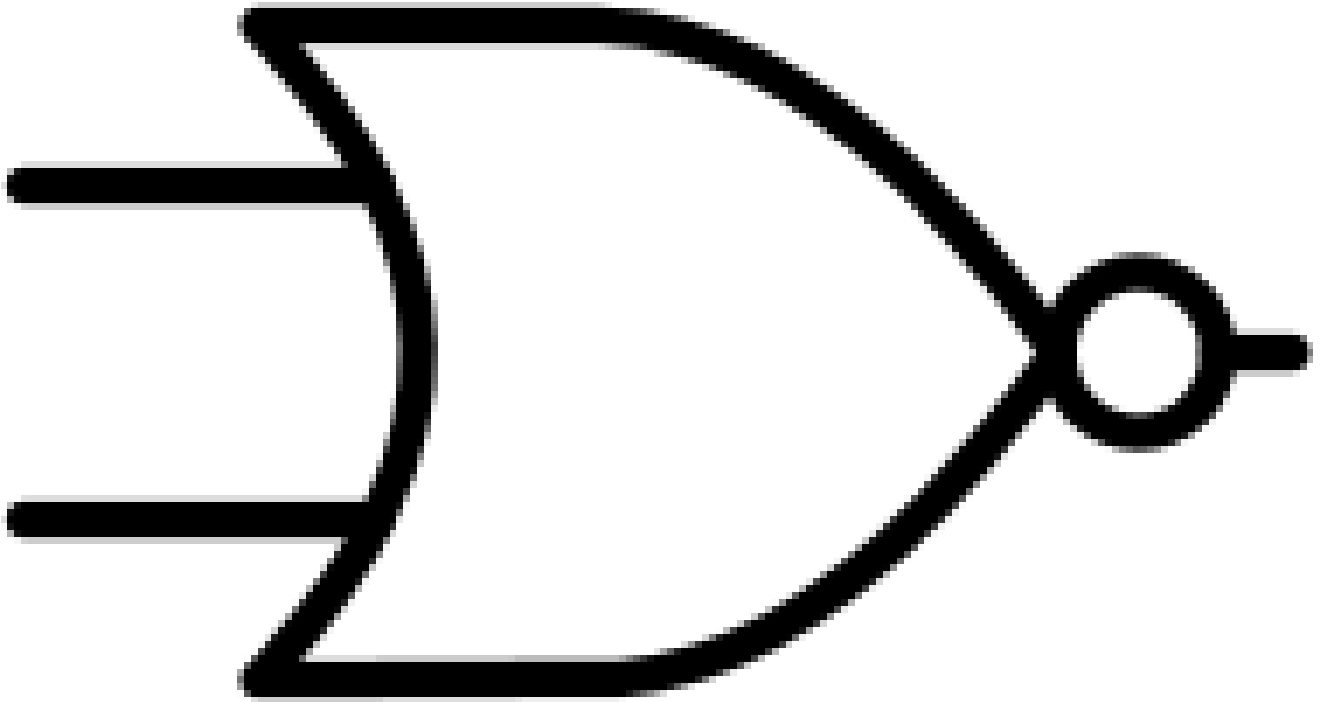

Correct Answer: 1


Question 21:

What is the output of the AND gate with inputs 0, 1?

Options:

1. 0

2. 1

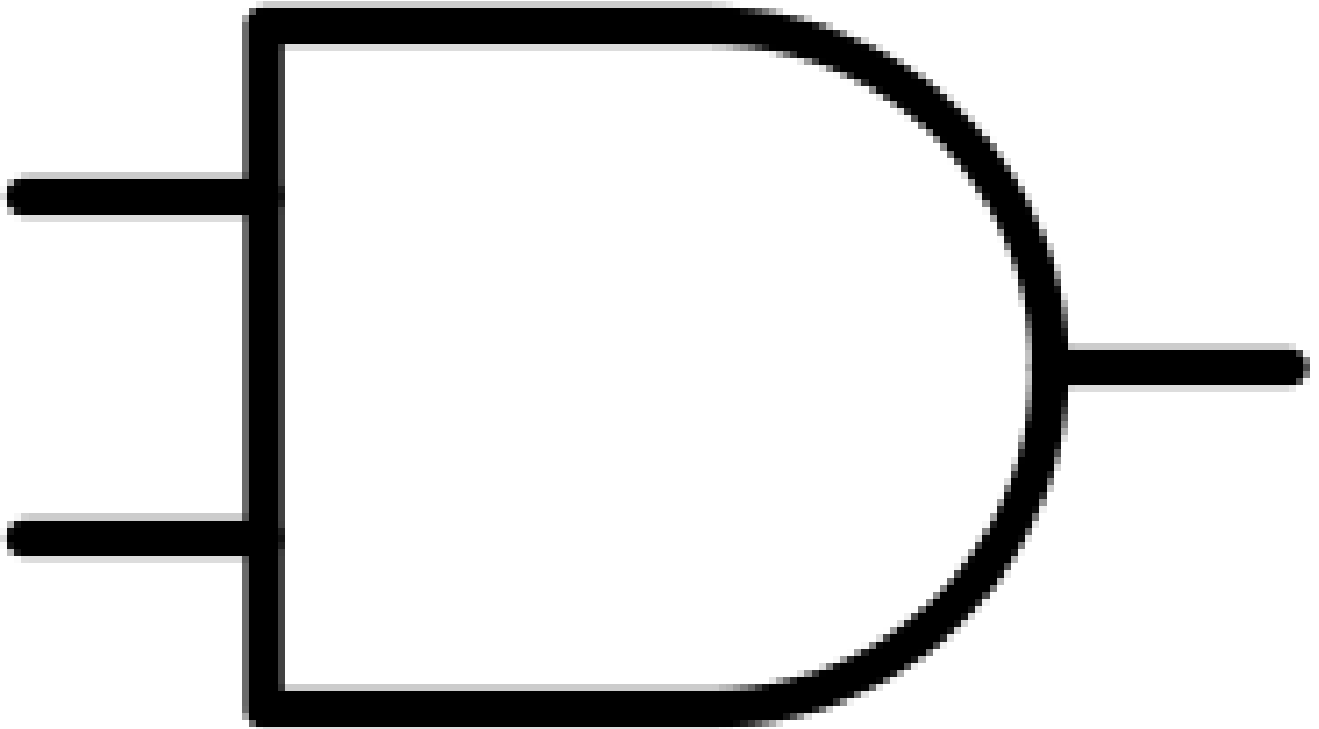

Correct Answer: 0


Question 22:

What is the output of the NAND gate with inputs 1, 0?

Options:

1. 0

2. 1

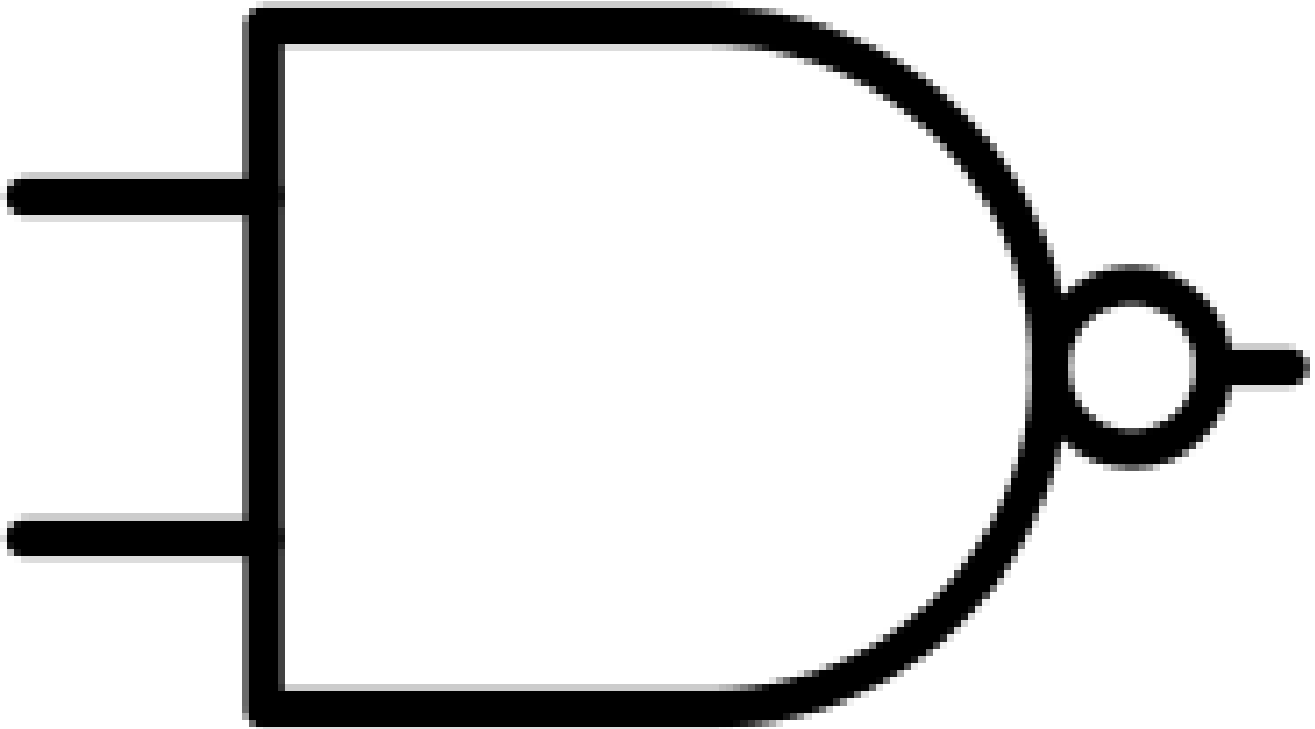

Correct Answer: 1

Question 23:

Are these two circuits equivalent?



Expression 1: (not a)

Expression 2: (not a)

Options:

1. Yes

2. No

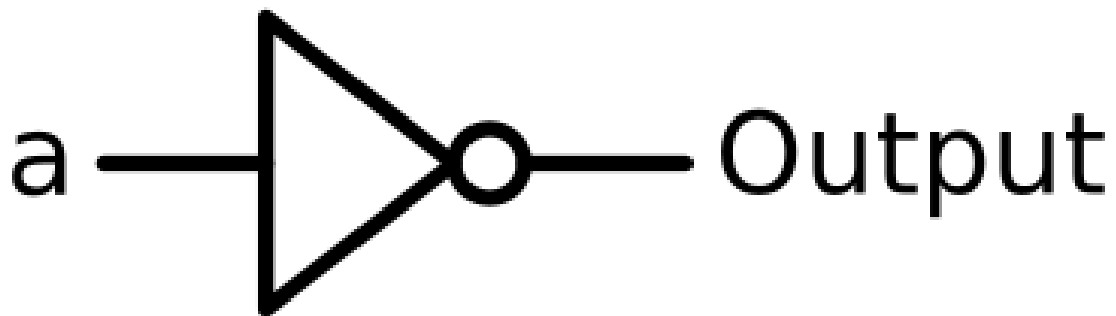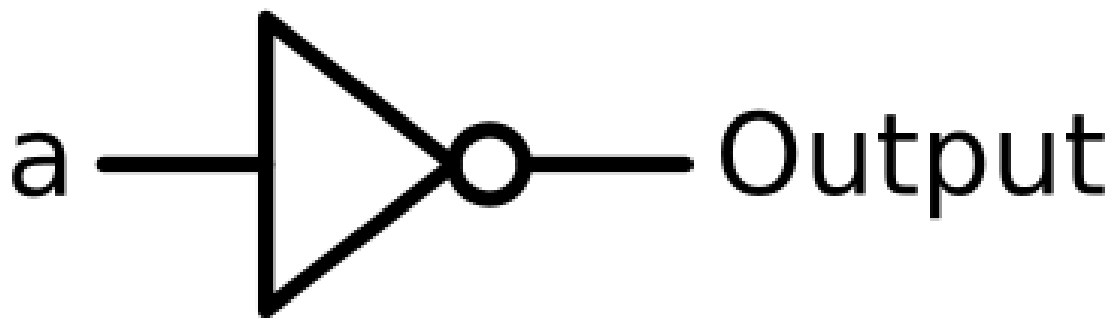

Correct Answer: yes



Question 24:


Are these two circuits equivalent?

Expression 1:  $((c \text{ or } c) \text{ or } (b \text{ nand } c))$

Expression 2:  $((c \text{ or } c) \text{ or } (b \text{ nand } c))$

Options:

1. Yes
2. No

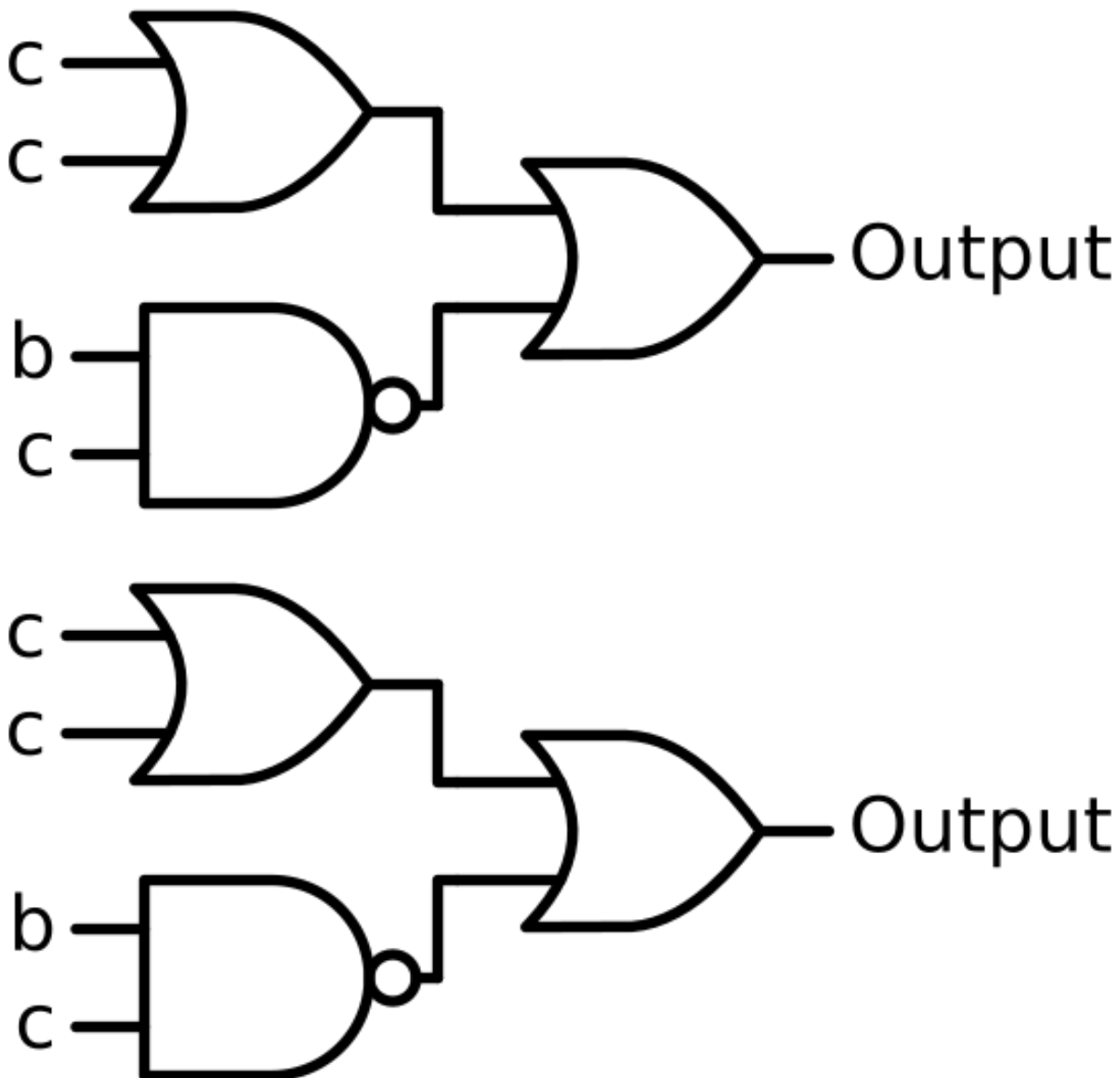

Correct Answer: yes


Question 25:

What is the output of the OR gate with inputs 0, 1?

Options:

1. 0

2. 1

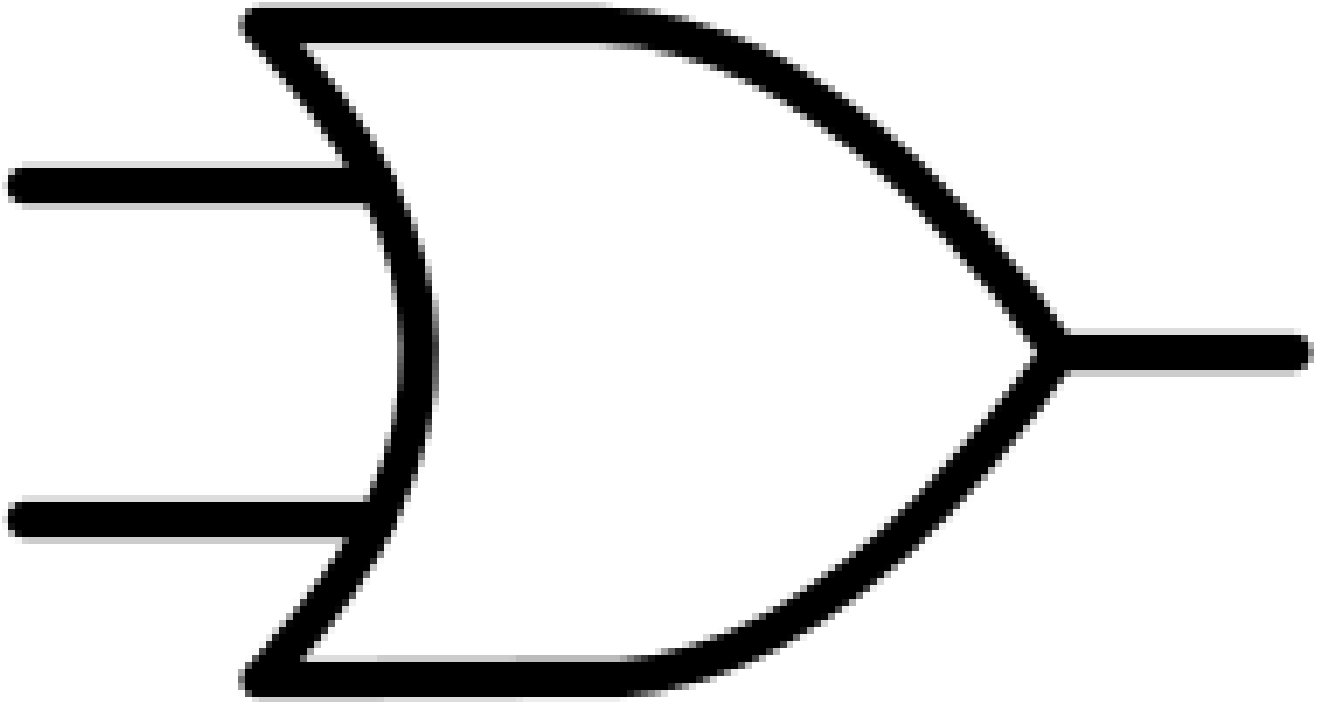

Correct Answer: 1


Question 26:

What is the output of the OR gate with inputs 1, 1?

Options:

1. 0

2. 1

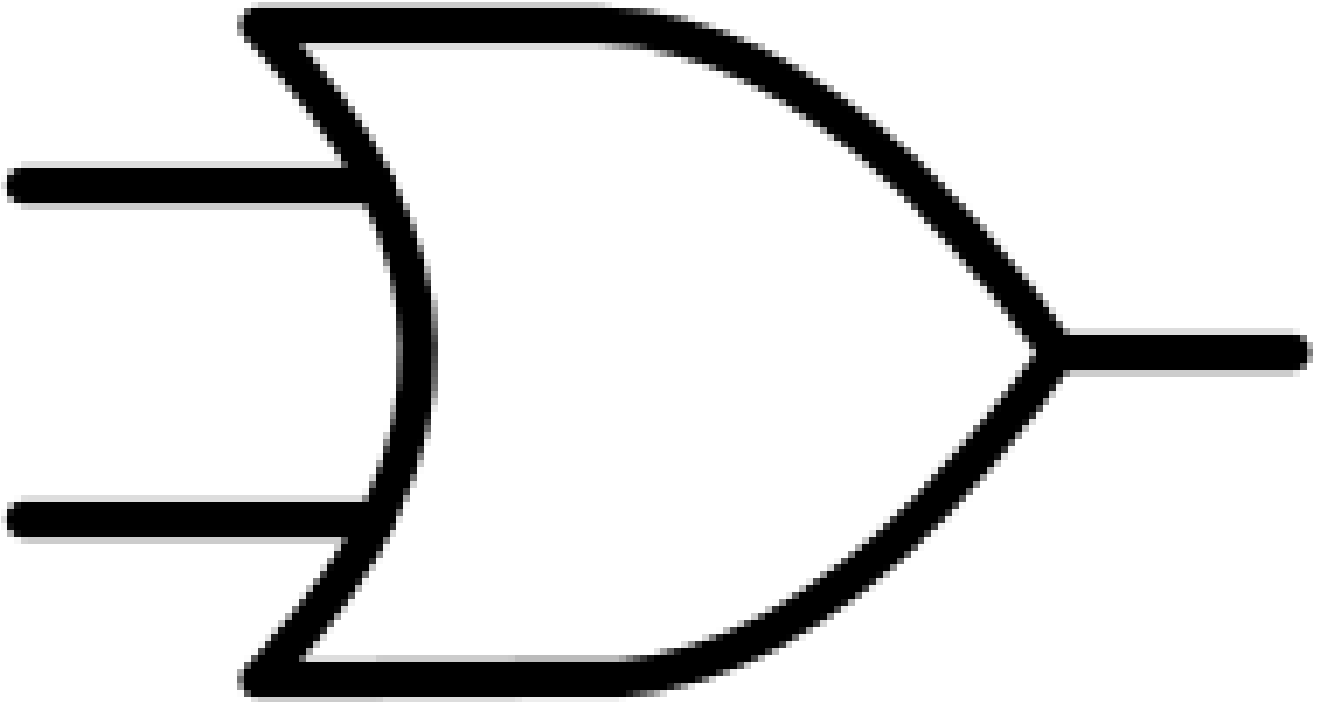

Correct Answer: 1


Question 27:

What is the output of the NAND gate with inputs 0, 1?

Options:

1. 0

2. 1

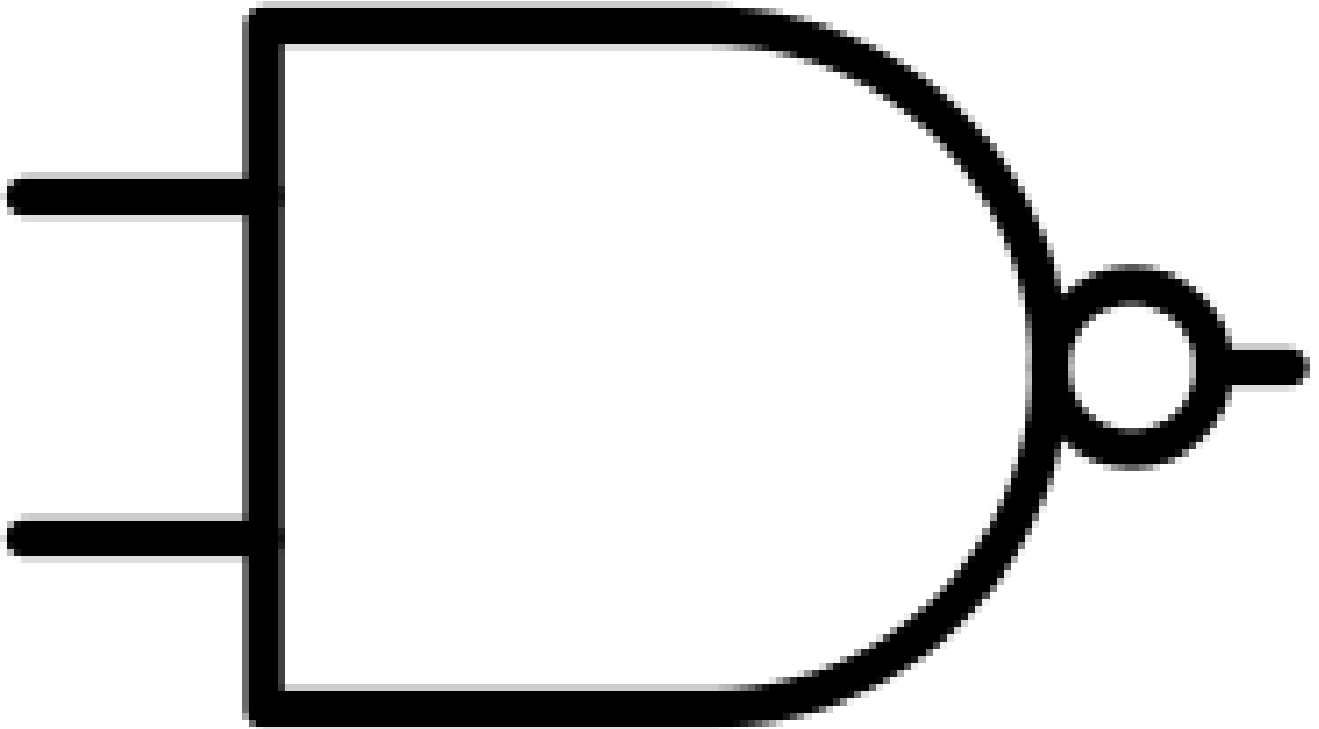

Correct Answer: 1


Question 28:

What is the output of the NAND gate with inputs 1, 1?

Options:

1. 0

2. 1

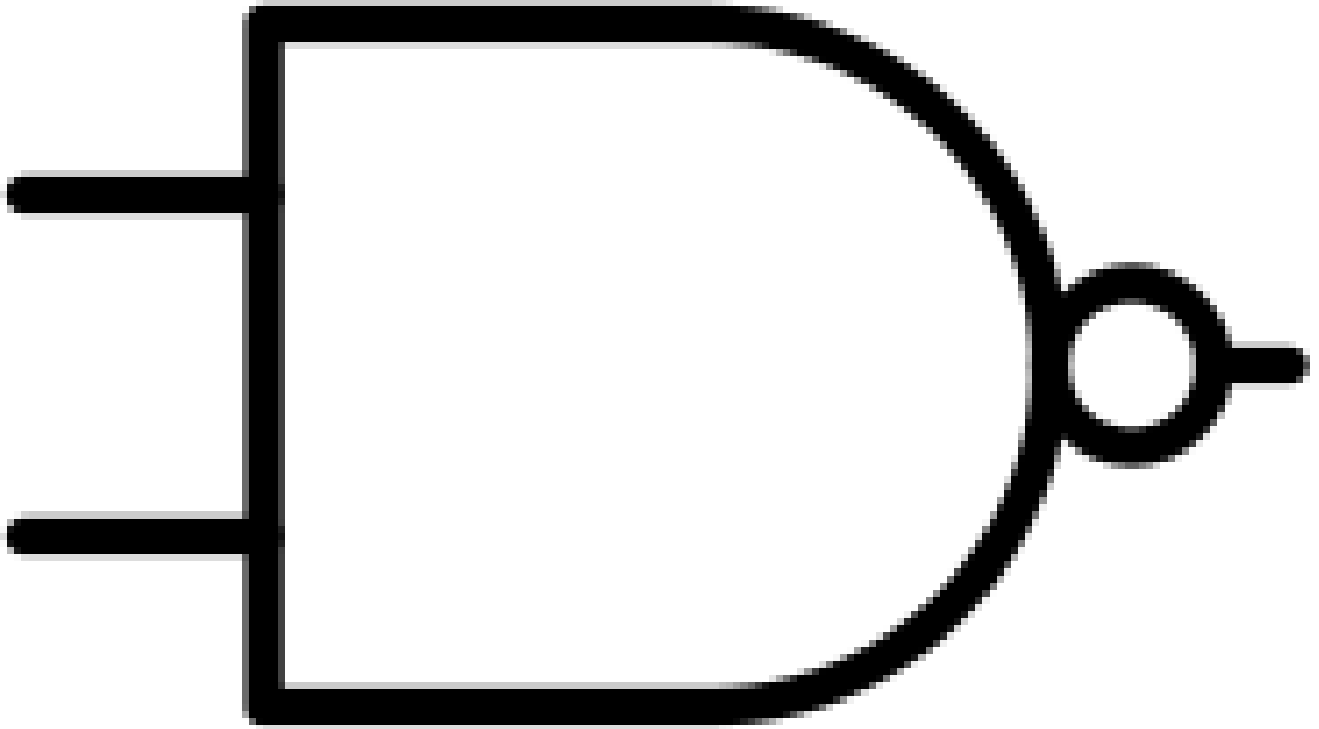

Correct Answer: 0


Question 29:

What is the output of the NAND gate with inputs 1, 0?

Options:

1. 1

2. 0

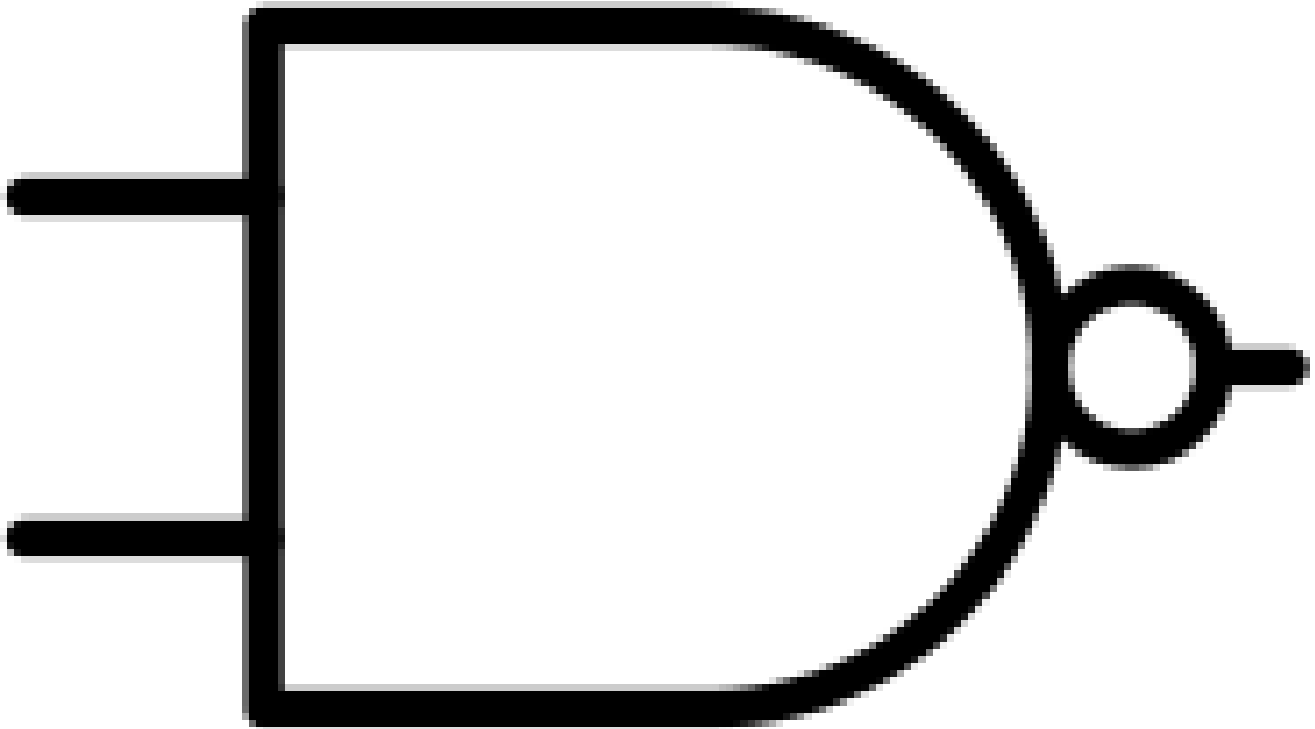

Correct Answer: 1

Question 30:

Are these two circuits equivalent?


Expression 1:  $((b \text{ or } a) \text{ or } (b \text{ or } a))$

Expression 2:  $((b \text{ or } a) \text{ or } (b \text{ or } a))$

Options:

1. Yes

2. No

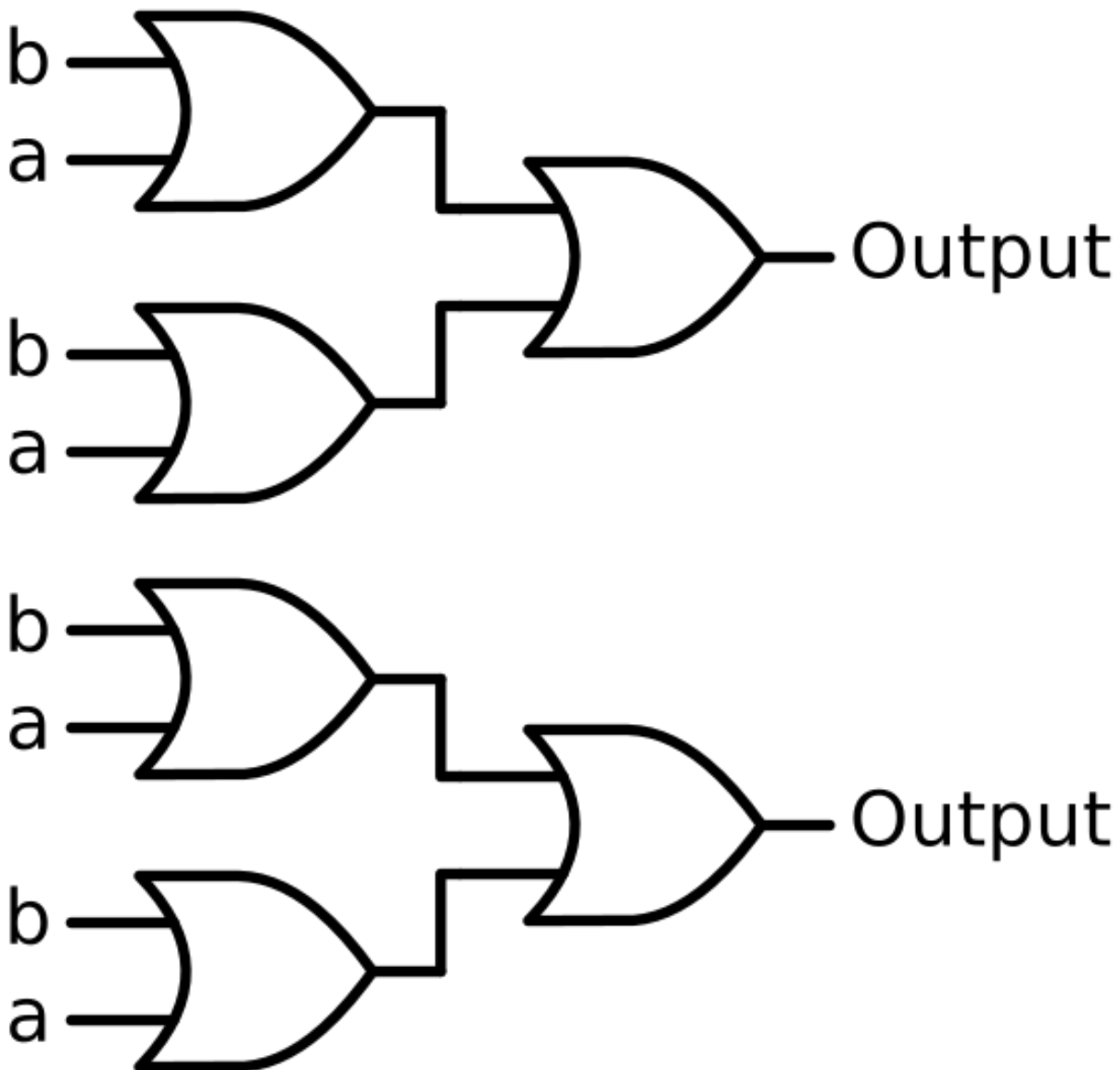

Correct Answer: yes


Question 31:

What is the output of the XOR gate with inputs 0, 0?

Options:

1. 0

2. 1

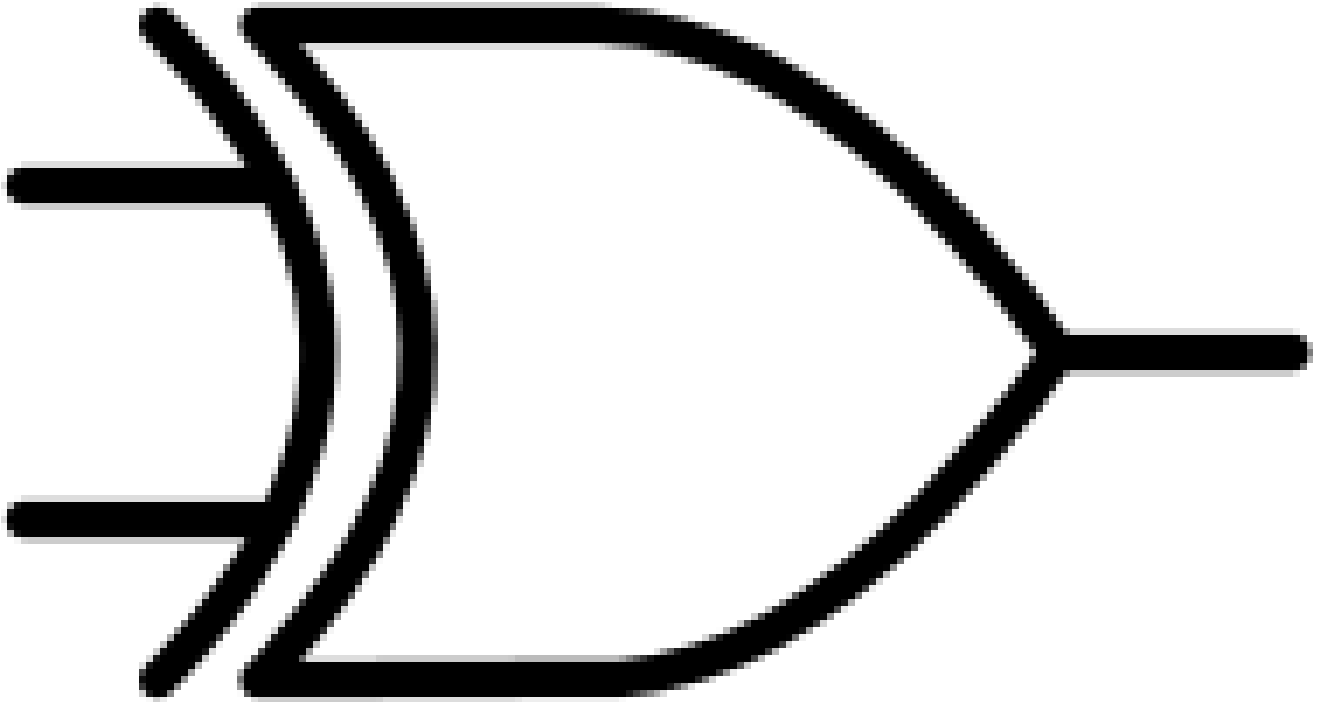

Correct Answer: 0



Question 32:



Are these two circuits equivalent?

Expression 1:  $(b \text{ nor } a)$

Expression 2:  $(b \text{ nor } a)$

Options:

1. Yes
2. No

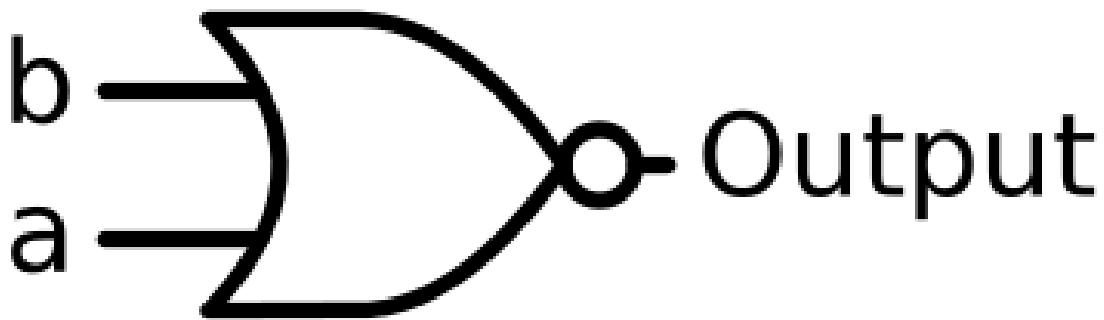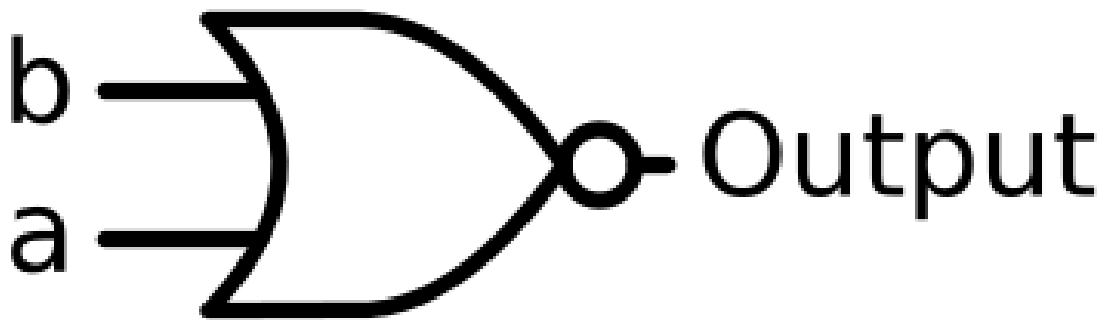

Correct Answer: yes

Question 33:


Are these two circuits equivalent?

Expression 1:  $((a \text{ or } b) \text{ and } (a \text{ xnor } c))$

Expression 2:  $((a \text{ or } b) \text{ and } (a \text{ xnor } c))$

Options:

1. Yes
2. No

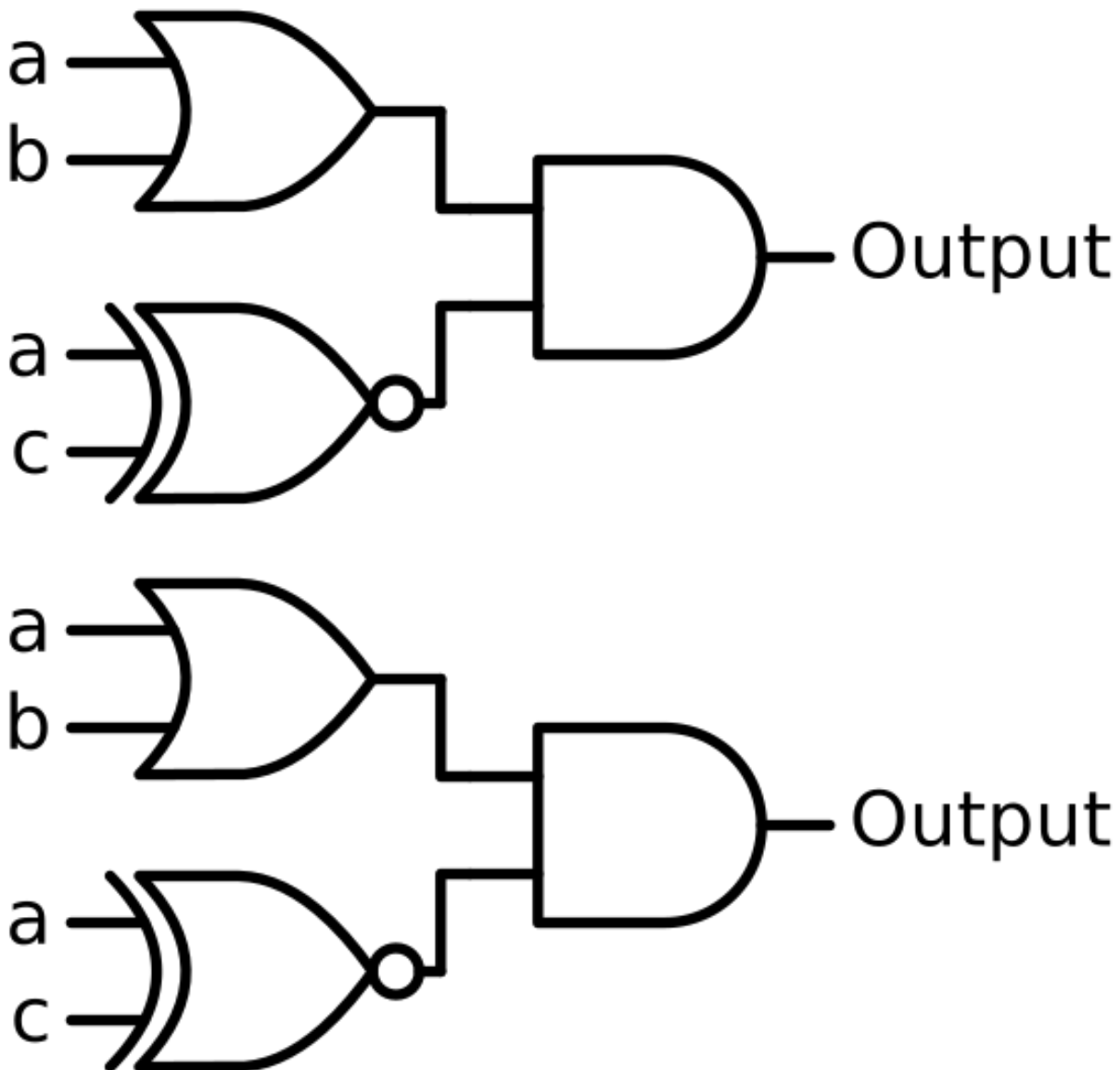

Correct Answer: yes


Question 34:

What is the output of the NOT gate with input 0?

Options:

1. 1

2. 0

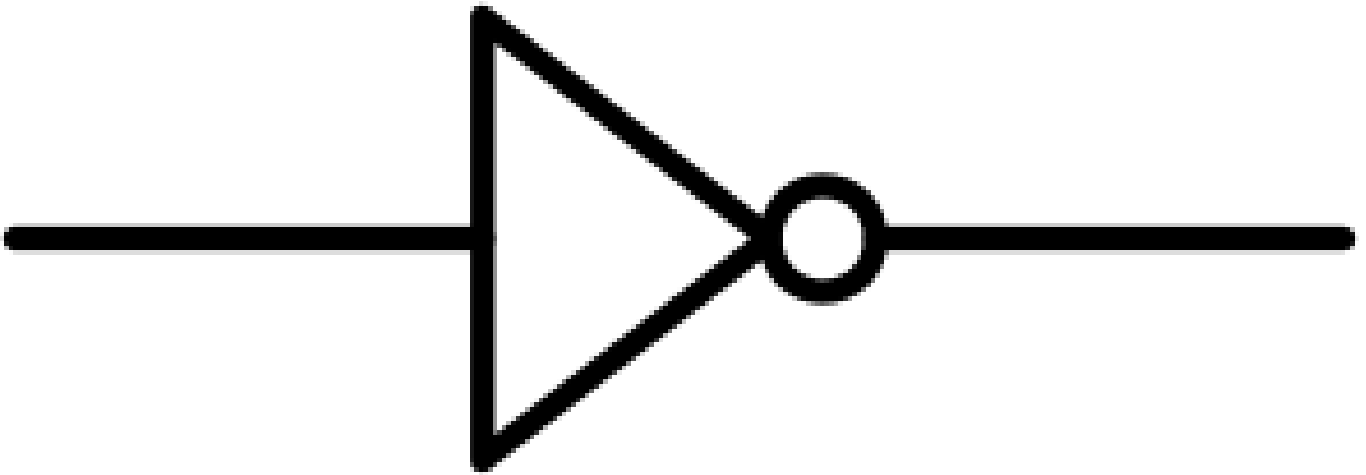

Correct Answer: 1

Question 35:



Are these two circuits equivalent?

Expression 1: (not (b or c))

Expression 2: (not (b or c))

Options:

1. Yes
2. No

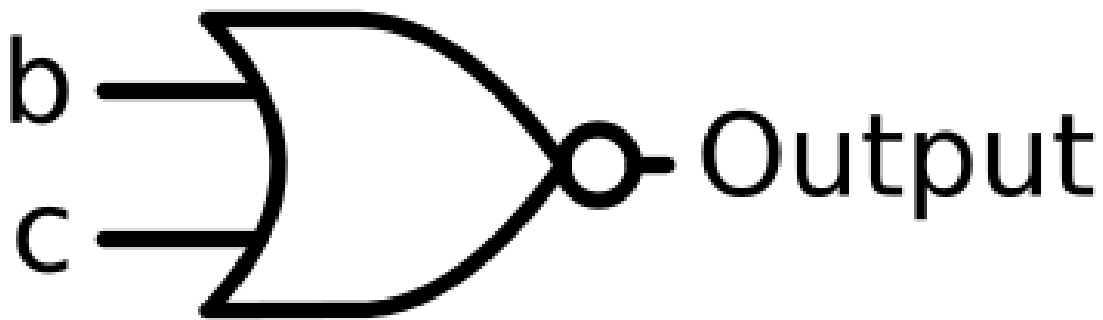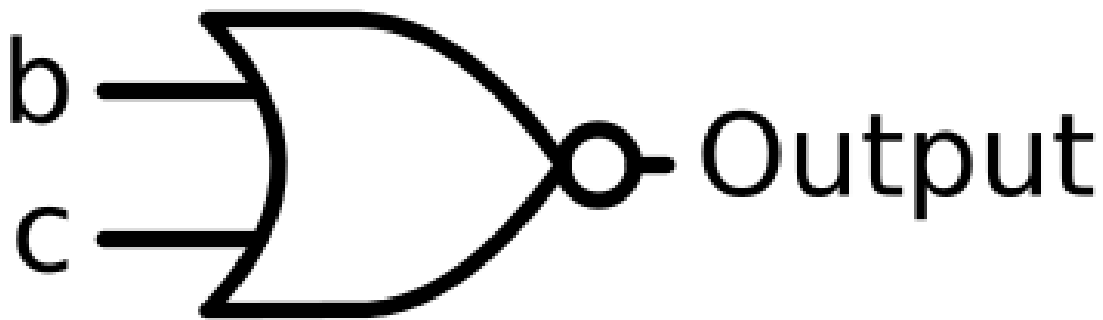

Correct Answer: yes

Question 36:


Are these two circuits equivalent?

Expression 1:  $(a \text{ nand } a)$

Expression 2:  $(b \text{ nor } b)$

Options:

1. Yes
2. No

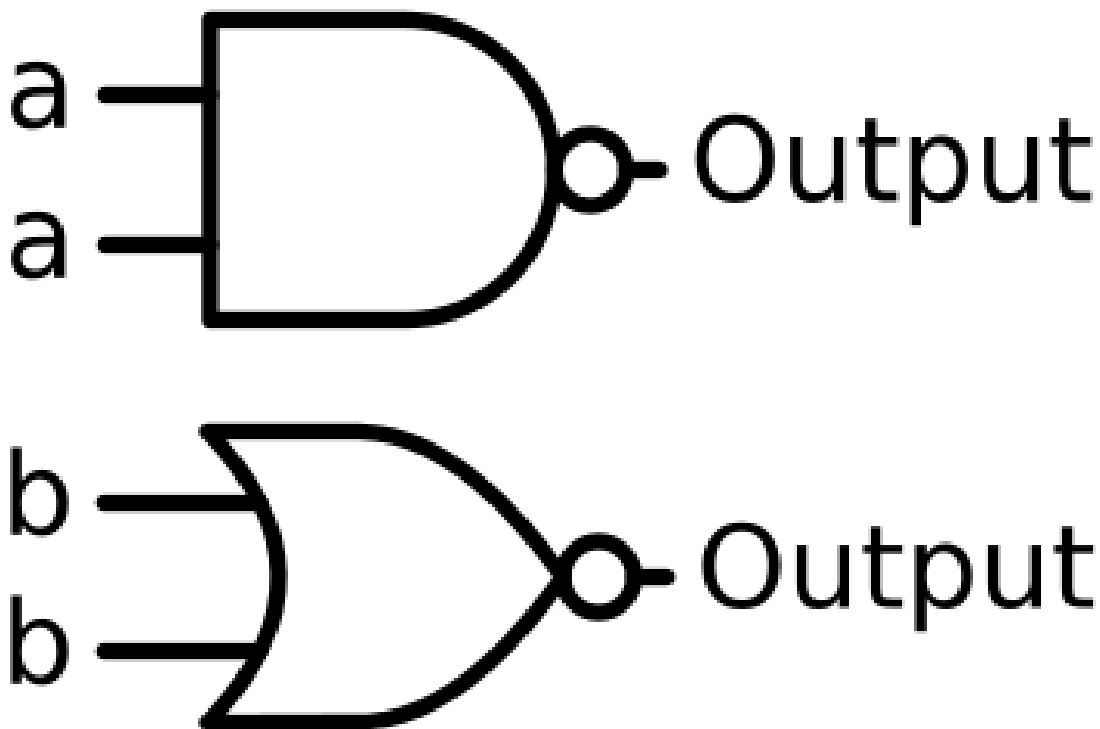

Correct Answer: no


Question 37:

What is the output of the NAND gate with inputs 1, 1?

Options:

1. 1

2. 0

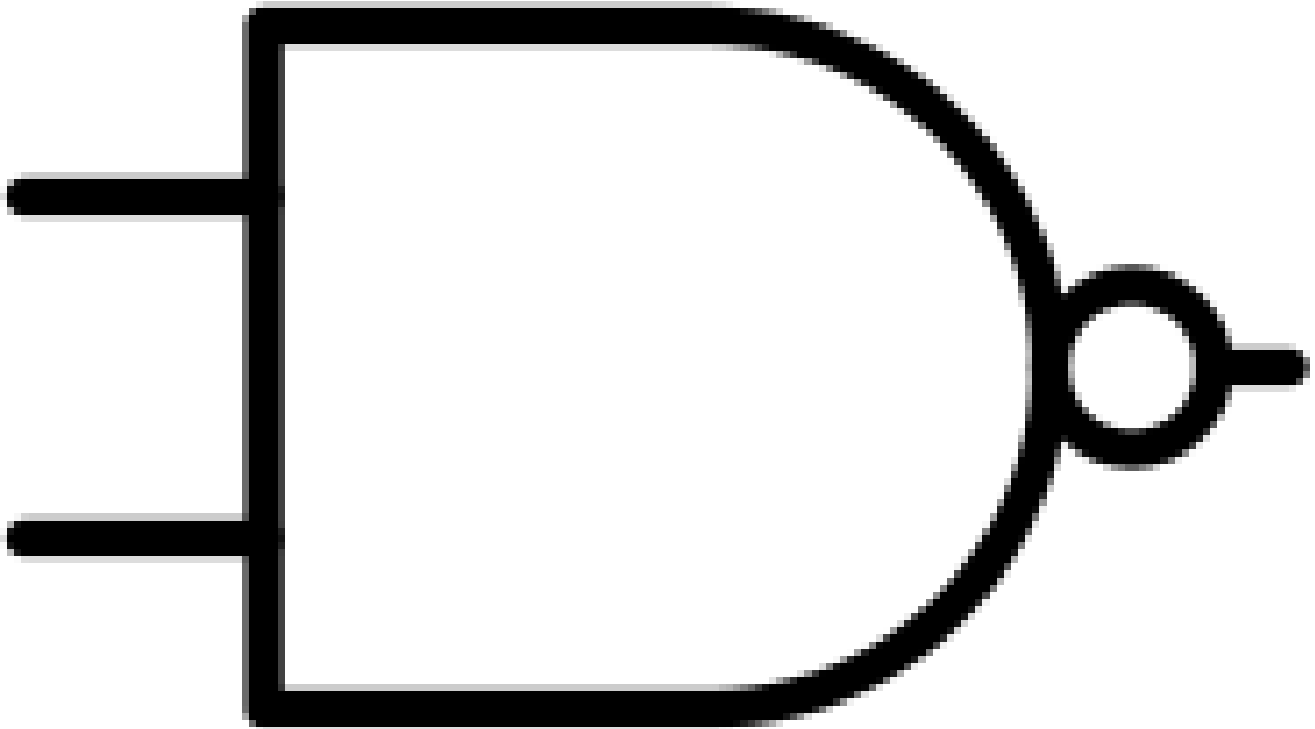

Correct Answer: 0

Question 38:

Are these two circuits equivalent?


Expression 1: (not (not c))

Expression 2: (not (not c))

Options:

1. Yes

2. No

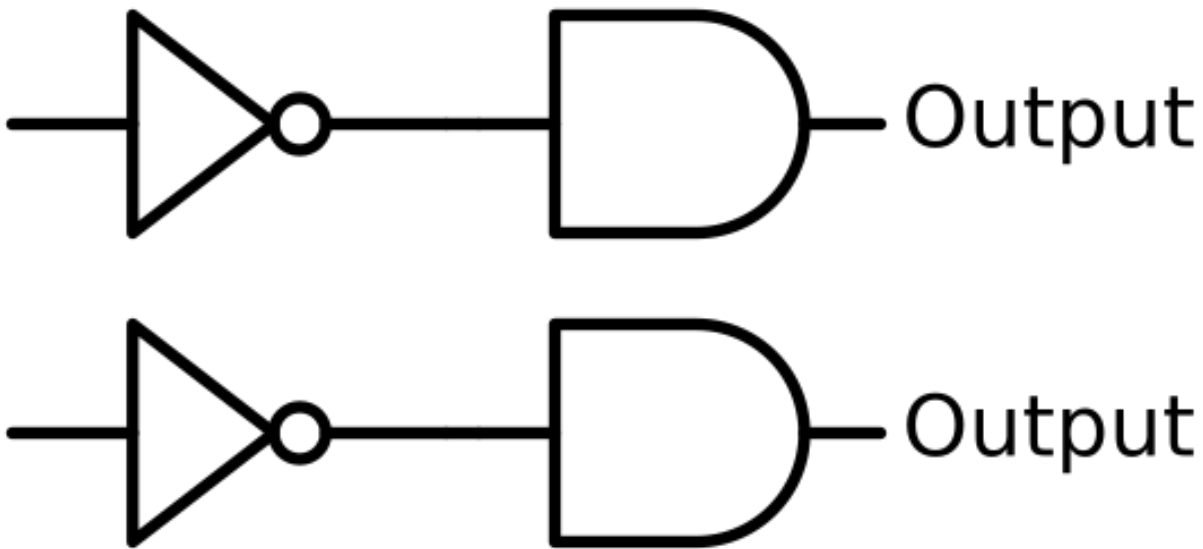

Correct Answer: yes

Question 39:


Are these two circuits equivalent?

Expression 1:  $(\text{not } ((b \text{ nor } c) \text{ xnor } (b \text{ nand } c)))$

Expression 2:  $(b \text{ or } b)$

Options:

1. Yes
2. No

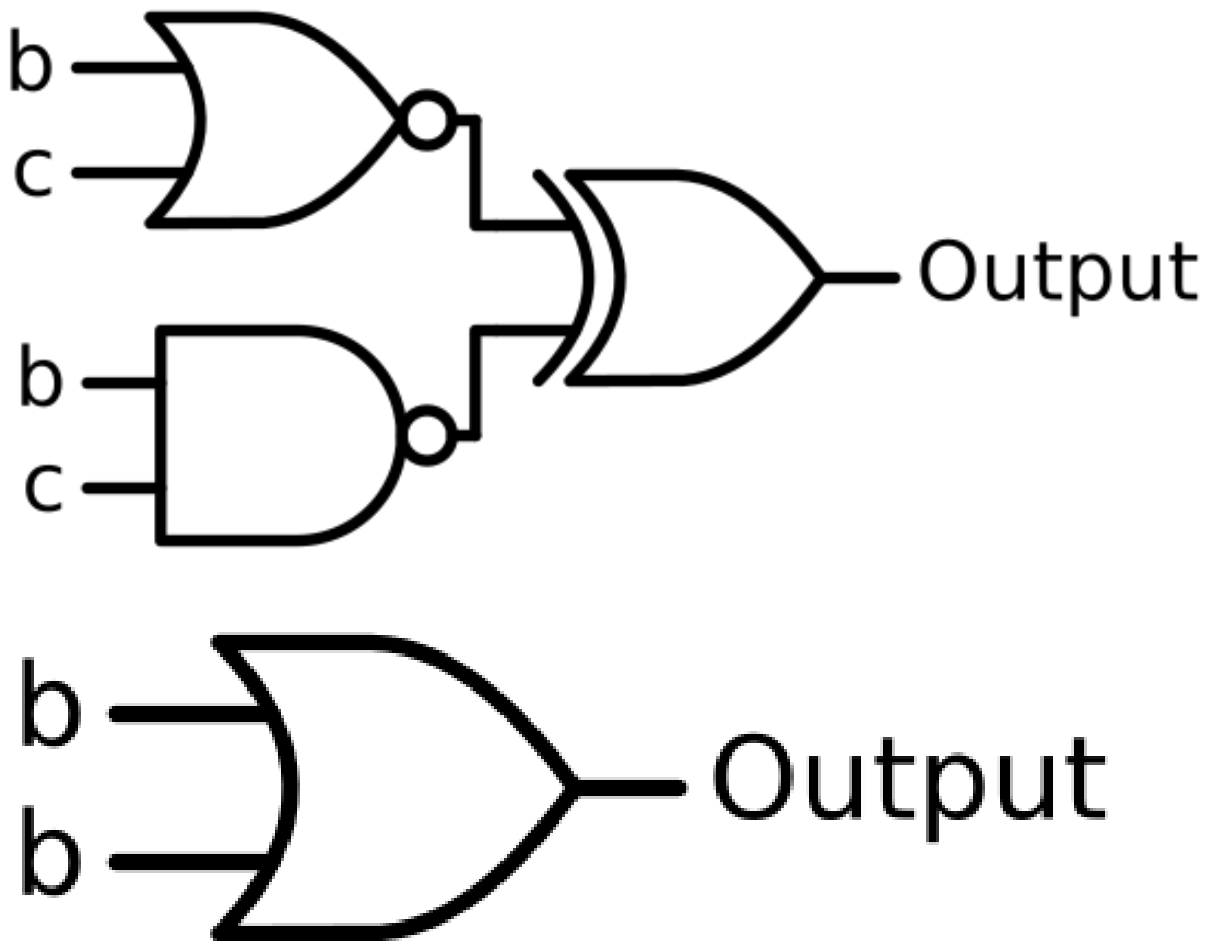

Correct Answer: no




Question 40:

What is the output of the NOR gate with inputs 0, 0?

Options:

1. 0

2. 1

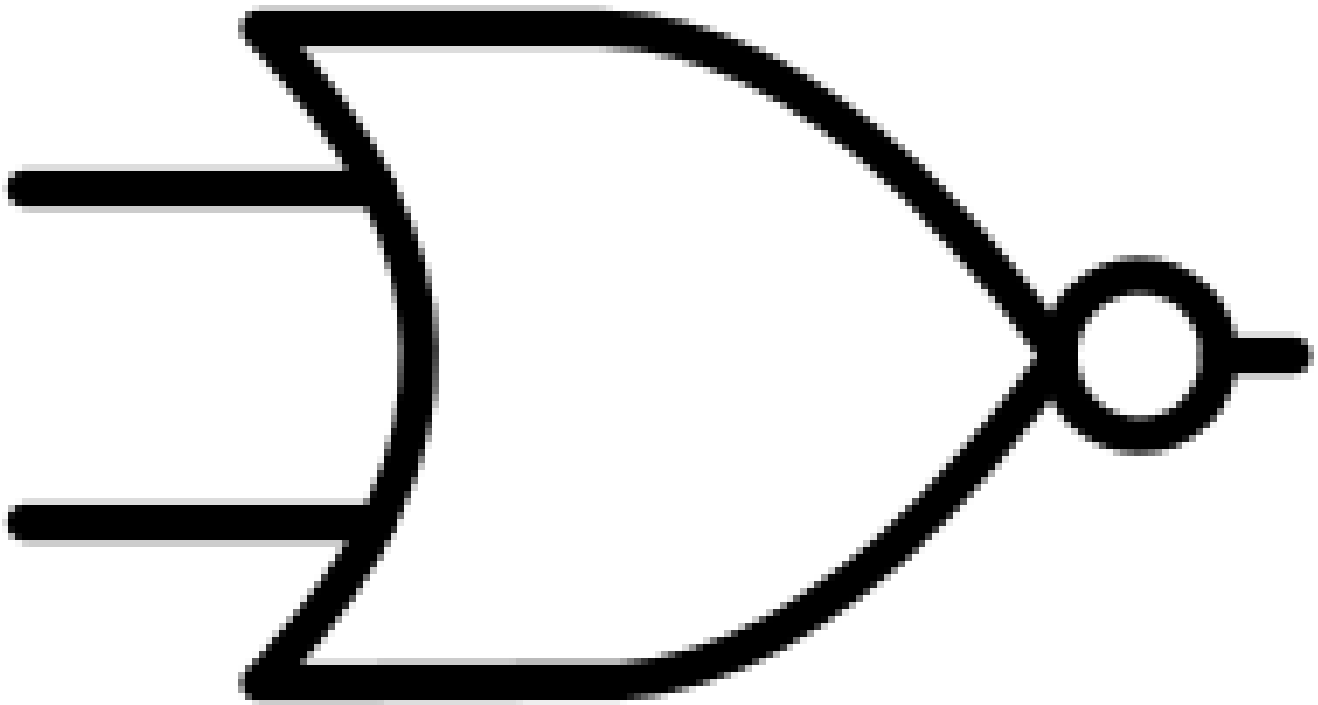

Correct Answer: 1


Question 41:

What is the output of the OR gate with inputs 0, 1?

Options:

1. 1

2. 0

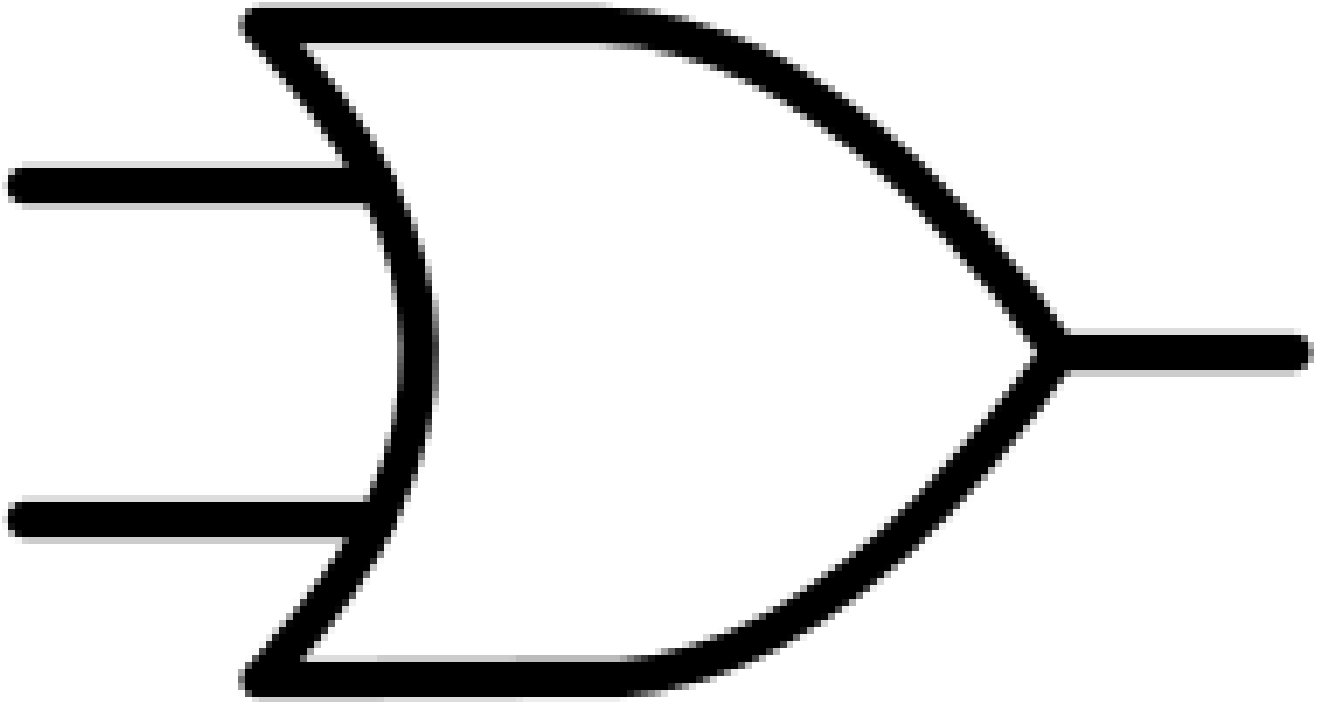

Correct Answer: 1

Question 42:

Are these two circuits equivalent?



Expression 1: (not b)

Expression 2: (not b)

Options:

1. Yes

2. No

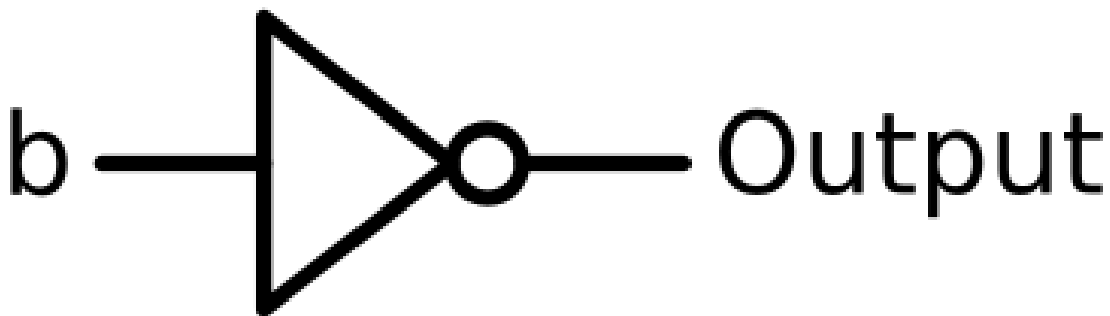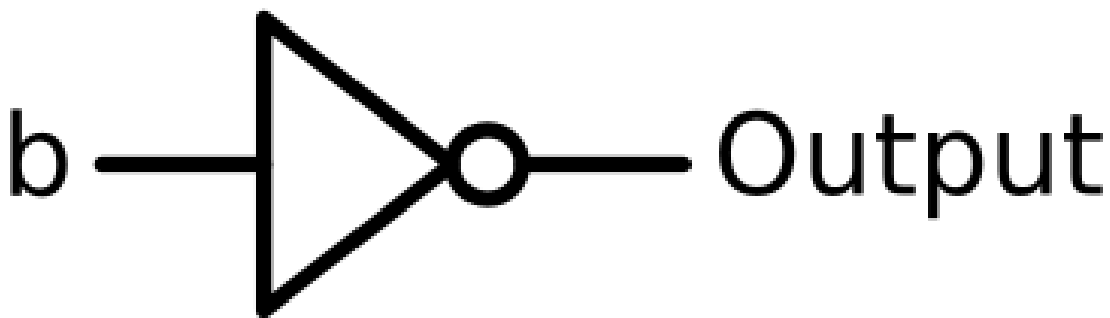

Correct Answer: yes


Question 43:

What is the output of the NOT gate with input 0?

Options:

1. 0

2. 1

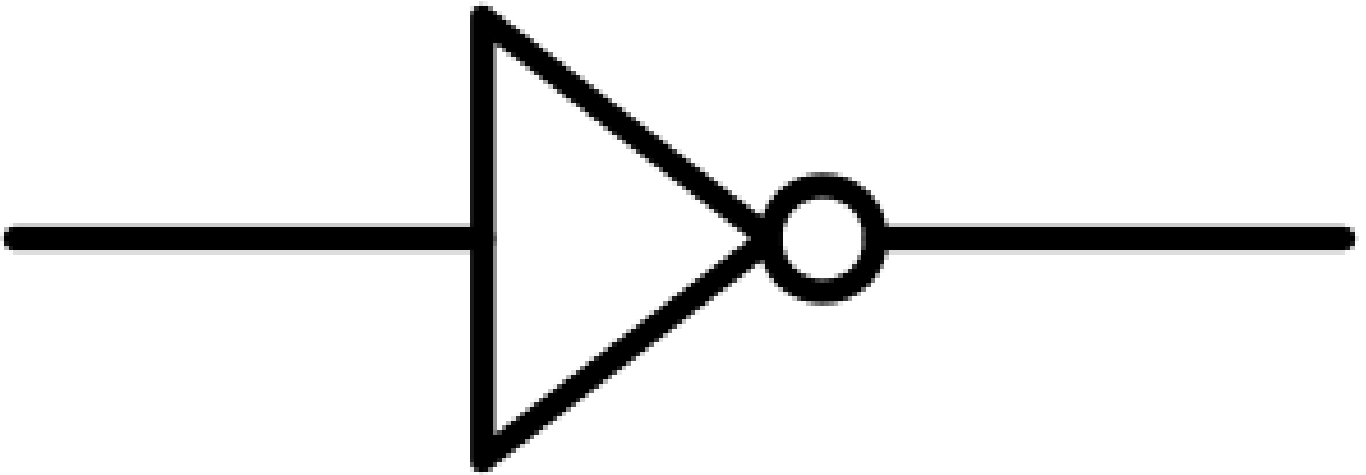

Correct Answer: 1

Question 44:



Are these two circuits equivalent?

Expression 1:  $((\text{not } (b \text{ xor } b)) \text{ or } ((c \text{ and } a) \text{ nand } (b \text{ nand } b)))$

Expression 2:  $(c \text{ xnor } a)$

Options:

1. Yes
2. No

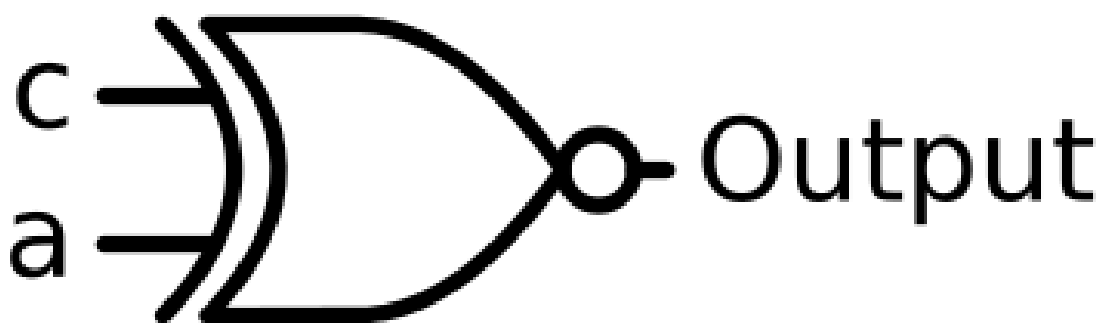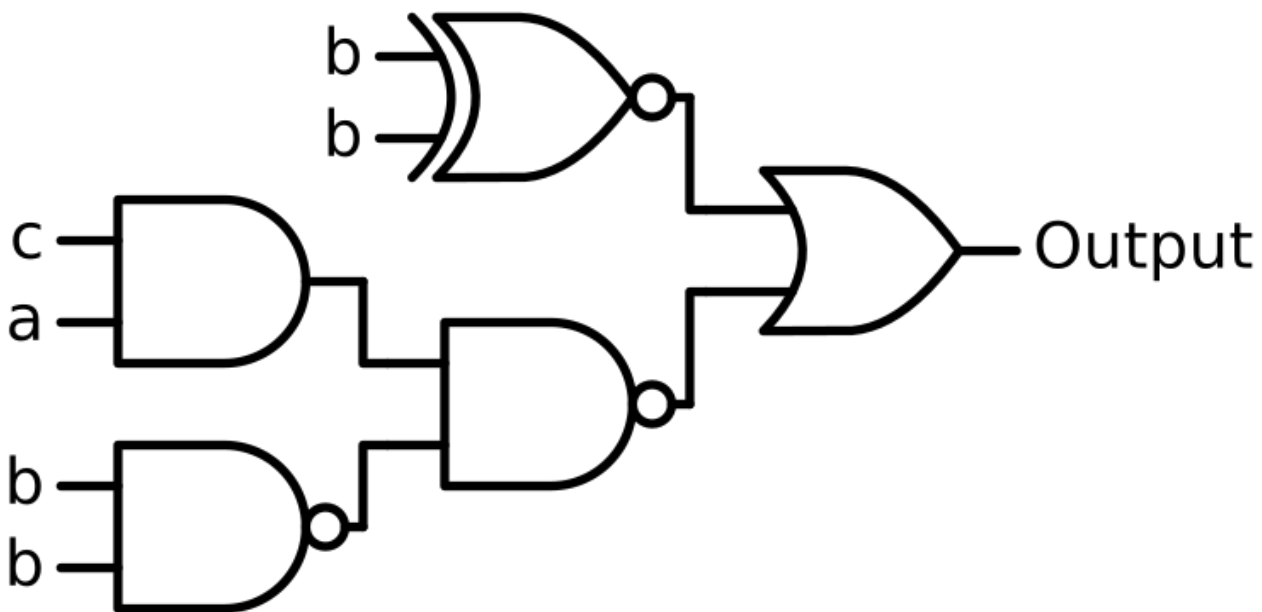

Correct Answer: no

Question 45:


Are these two circuits equivalent?


Expression 1:  $((c \text{ and } c) \text{ or } (b \text{ or } b)) \text{ nor } ((a \text{ nand } a) \text{ nand } (\text{not } a))$

Expression 2:  $((b \text{ xnor } c) \text{ nor } (\text{not } a)) \text{ xor } ((\text{not } a) \text{ or } (a \text{ nand } a))$

Options:

1. Yes
2. No

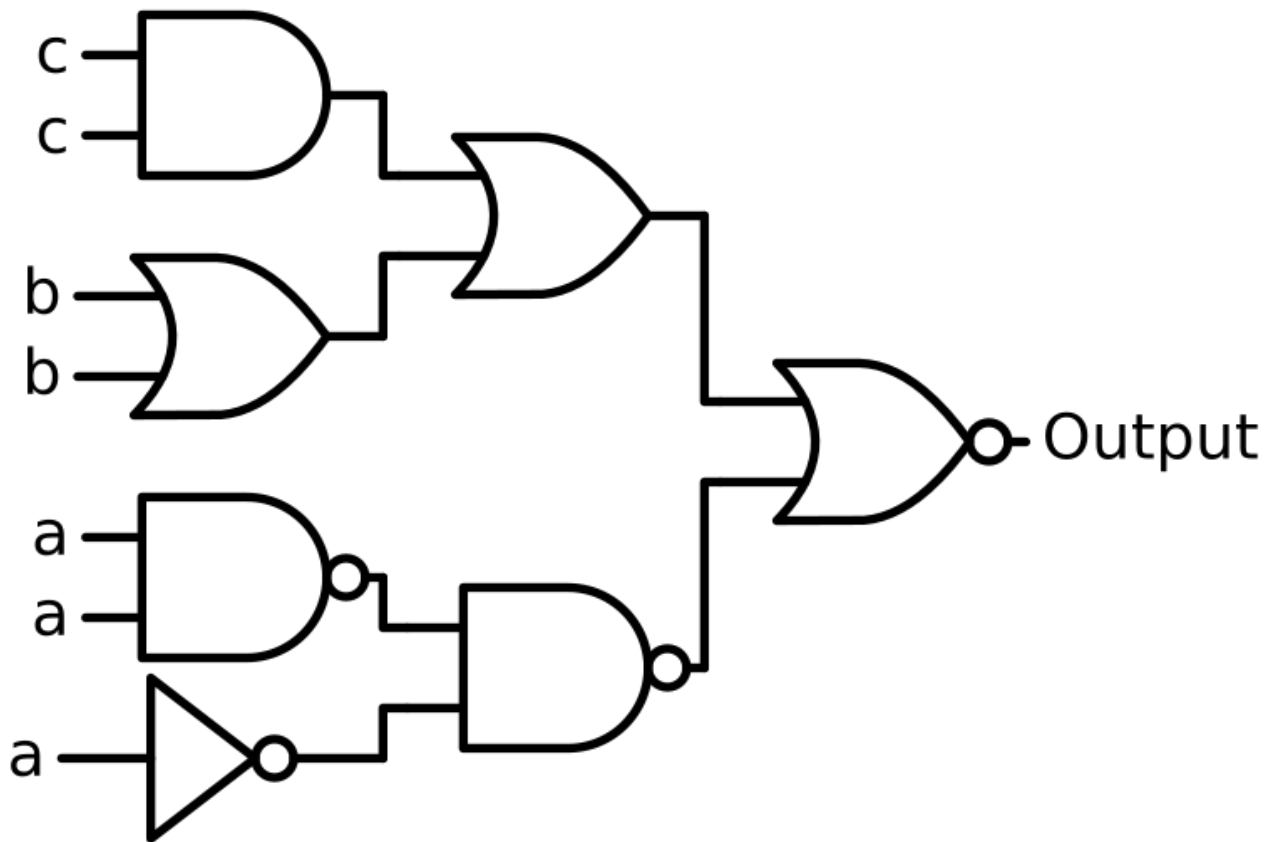

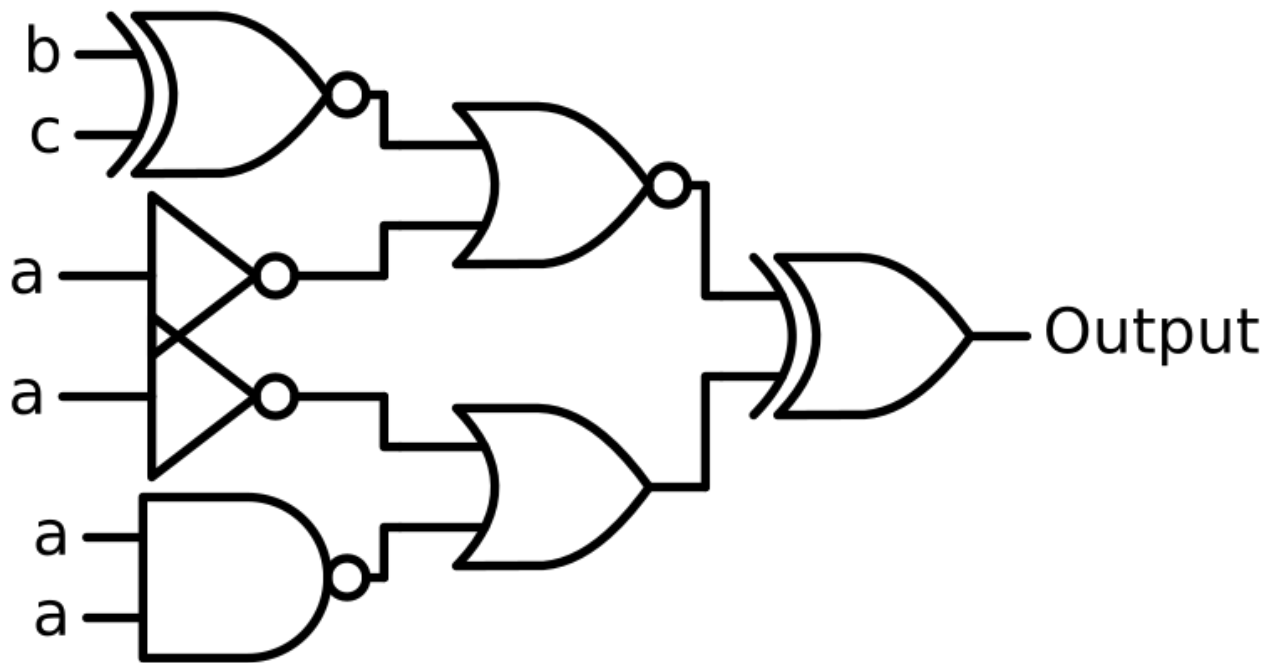

Correct Answer: no

Question 46:


Are these two circuits equivalent?

Expression 1:  $((a \text{ or } c) \text{ xnor } (c \text{ or } a))$

Expression 2:  $((a \text{ or } c) \text{ xnor } (c \text{ or } a))$

Options:

1. Yes
2. No

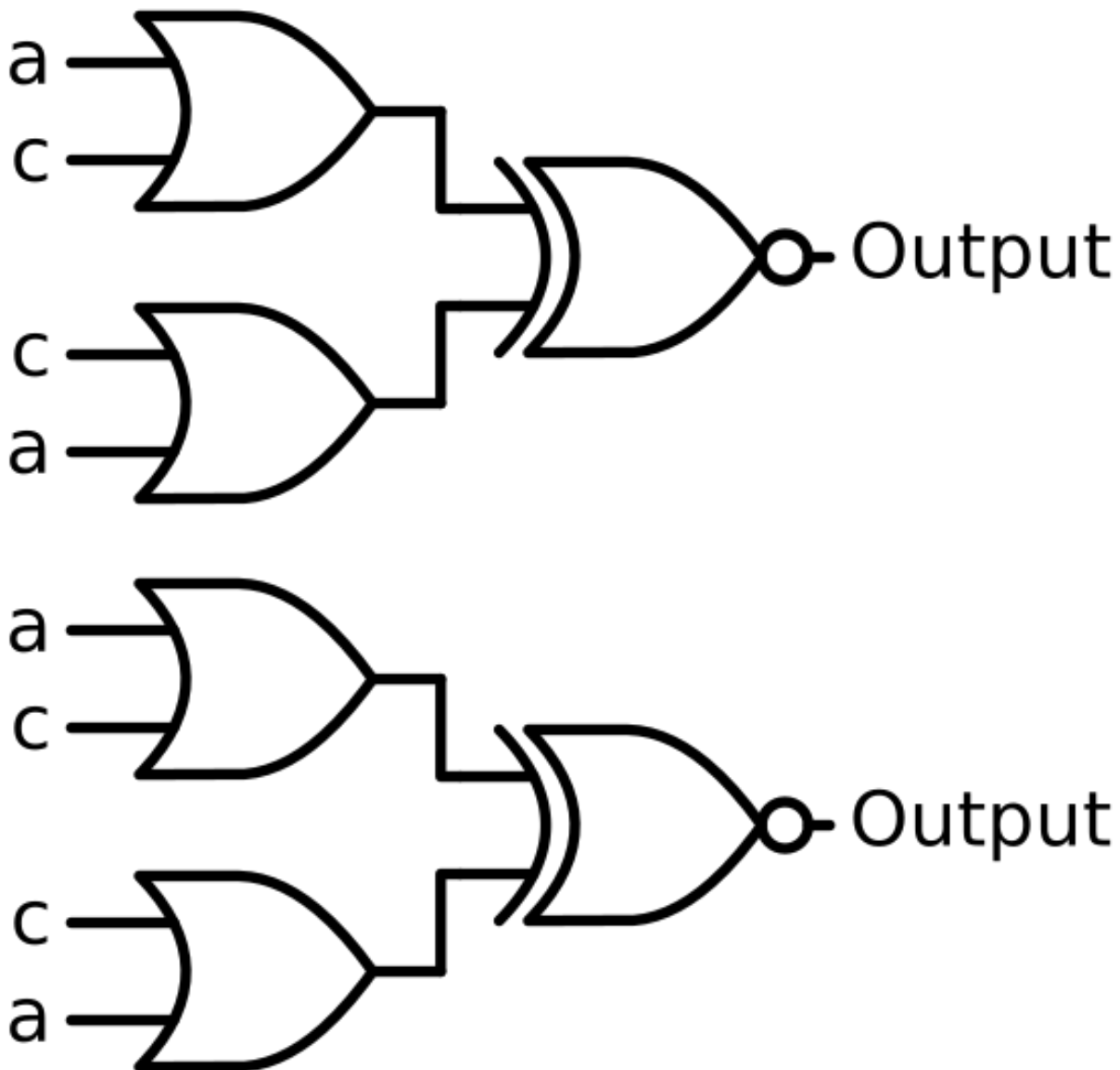

Correct Answer: yes



Question 47:

Are these two circuits equivalent?



Expression 1:  $(\text{not } ((a \text{ or } c) \text{ xnor } (b \text{ nor } b)))$

Expression 2:  $(\text{not } ((a \text{ or } c) \text{ xnor } (b \text{ nor } b)))$

Options:

1. Yes

2. No

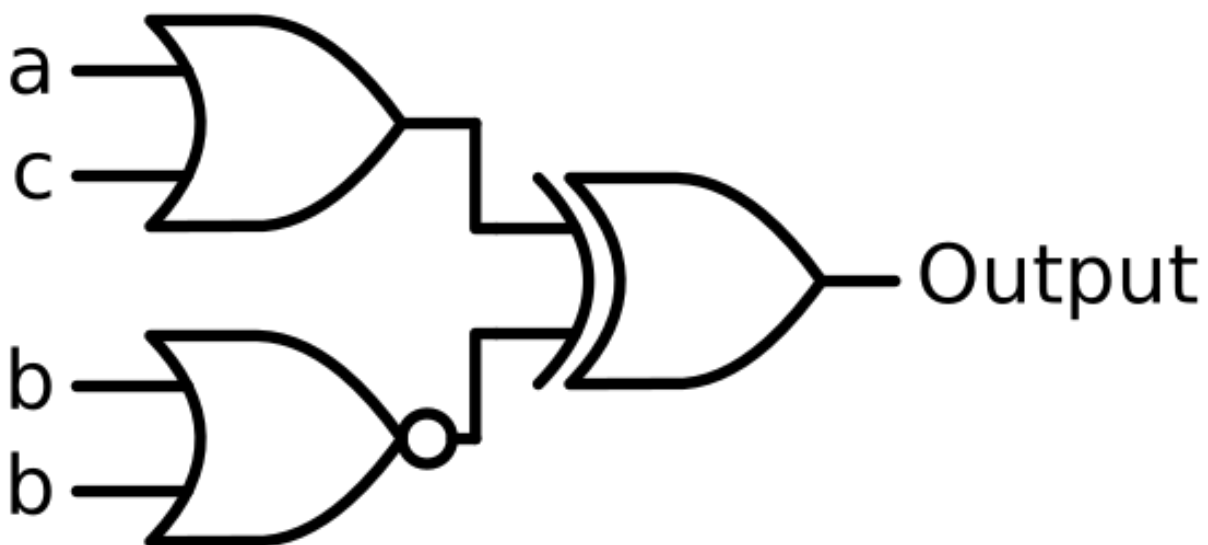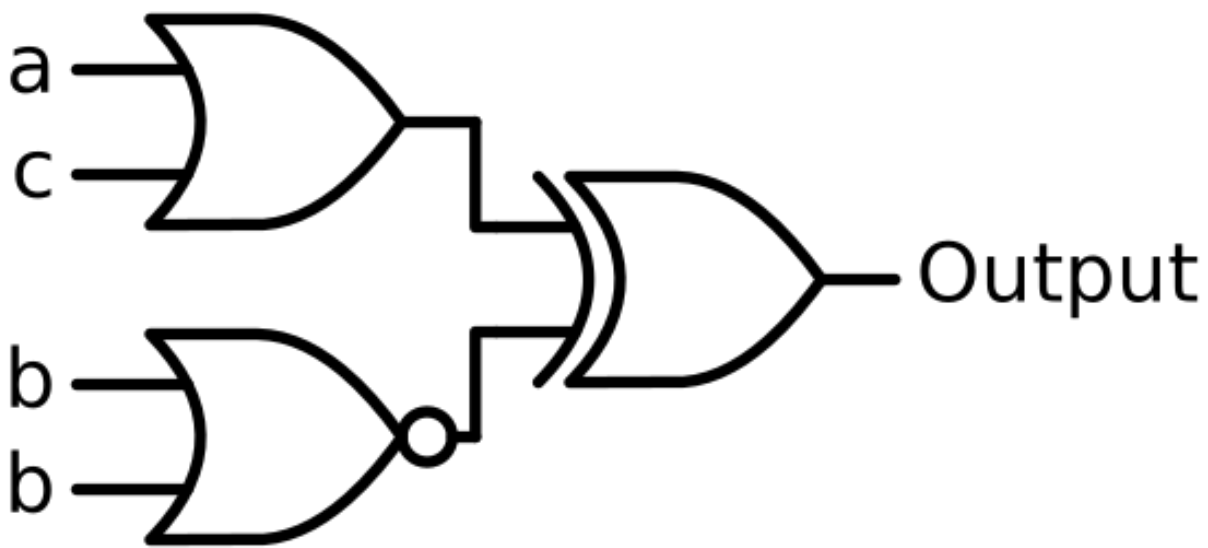

Correct Answer: yes

Question 48:



Are these two circuits equivalent?

Expression 1:  $(b \text{ nand } c)$

Expression 2:  $((c \text{ xnor } b) \text{ nor } (c \text{ and } a))$

Options:

1. Yes
2. No

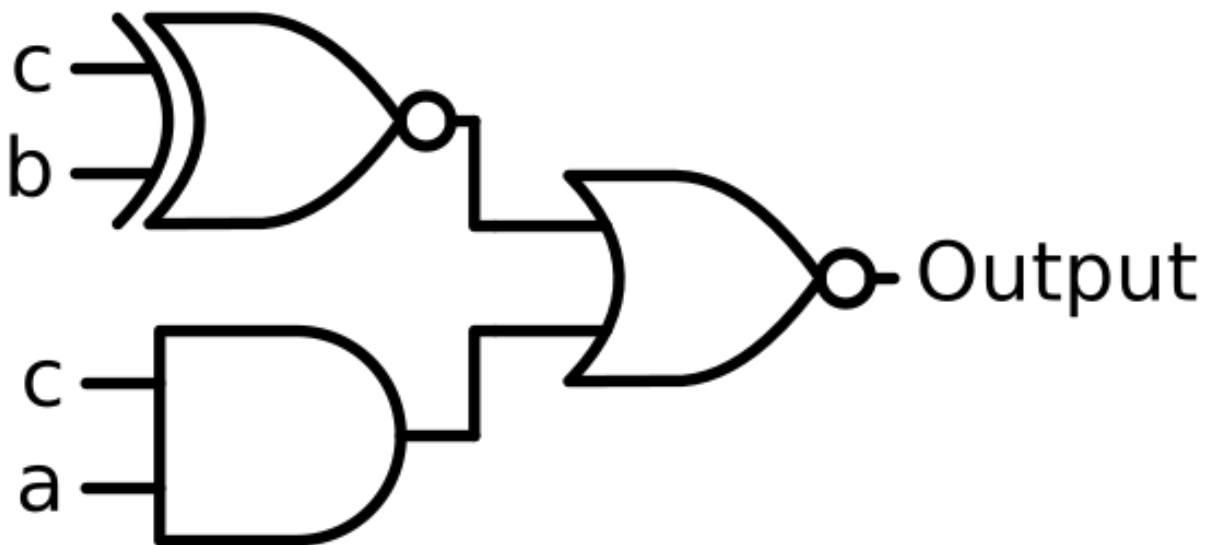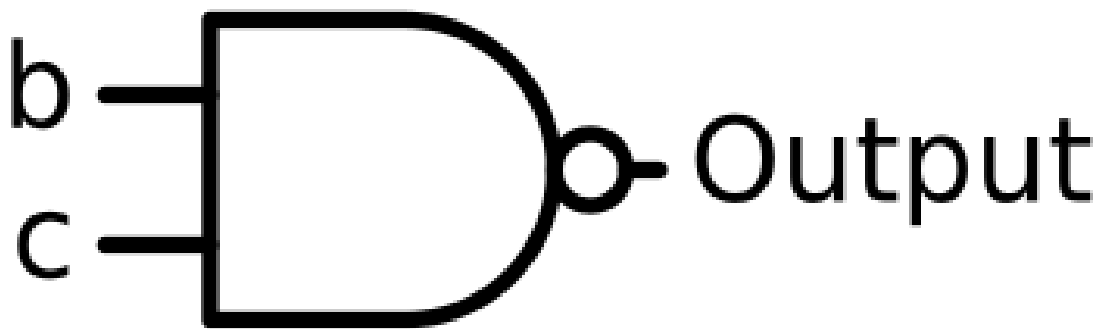

Correct Answer: no

Question 49:



Are these two circuits equivalent?

Expression 1:  $(a \text{ nand } c)$

Expression 2:  $(a \text{ nand } c)$

Options:

1. Yes
2. No

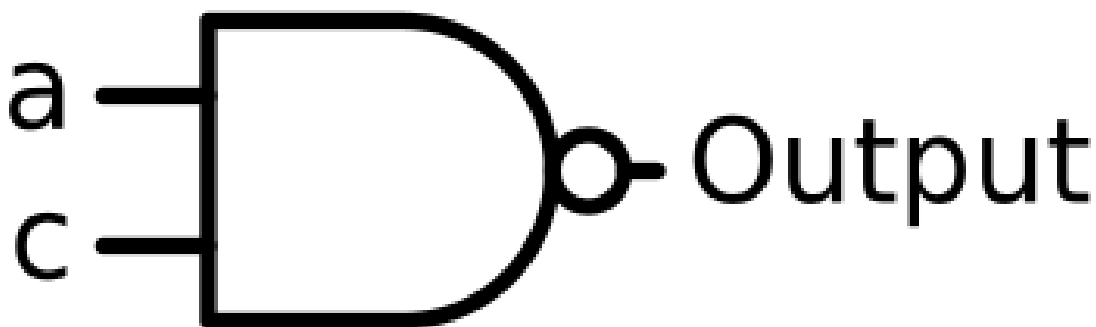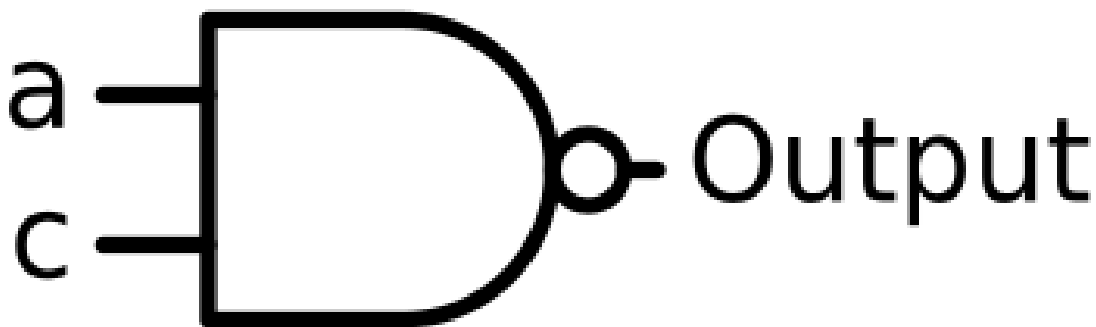

Correct Answer: yes

Question 50:



Are these two circuits equivalent?

Expression 1:  $(a \text{ xnor } c)$

Expression 2:  $((a \text{ xor } c) \text{ nor } (c \text{ or } c)) \text{ xnor } ((c \text{ nor } c) \text{ xor } (a \text{ nor } c))$

Options:

1. Yes
2. No

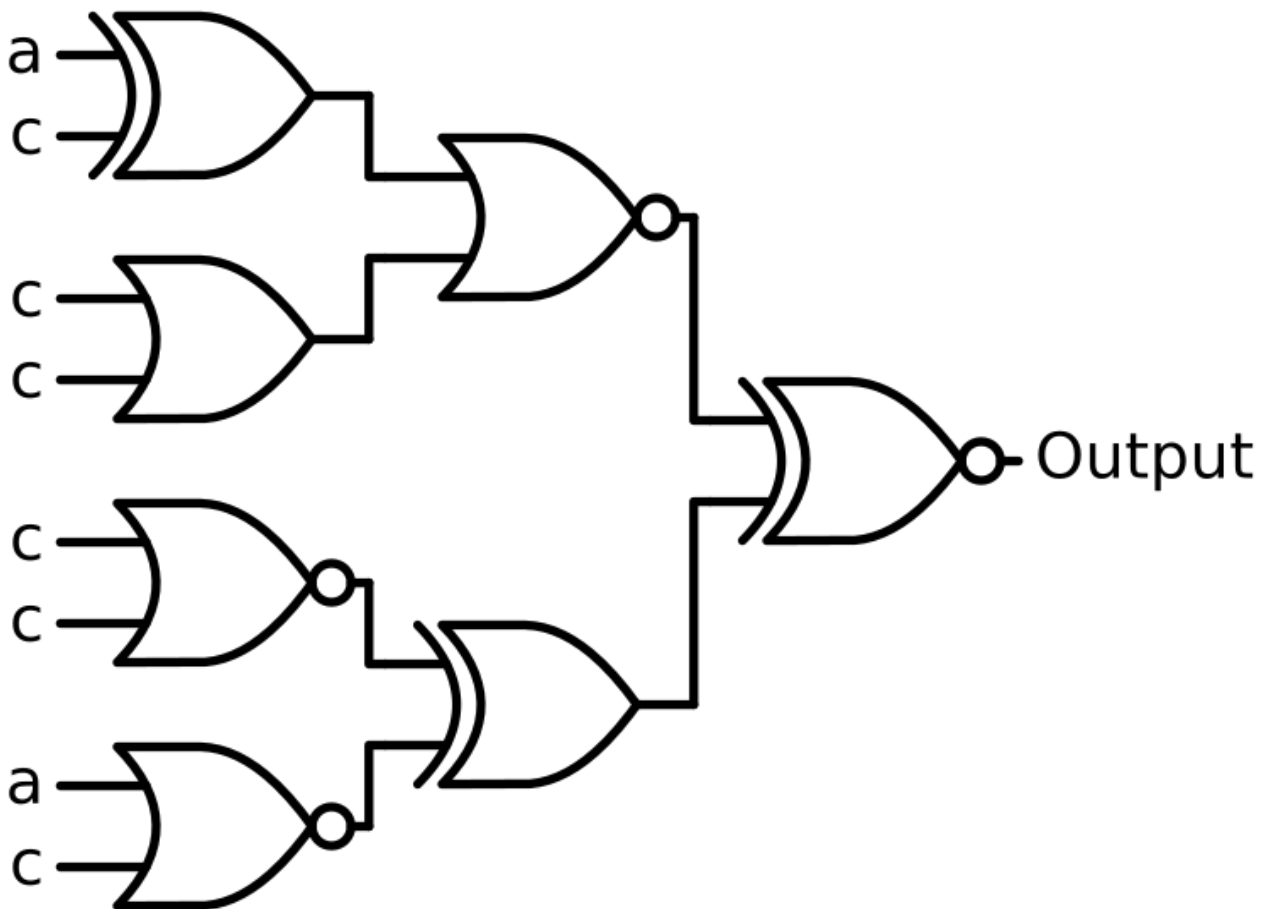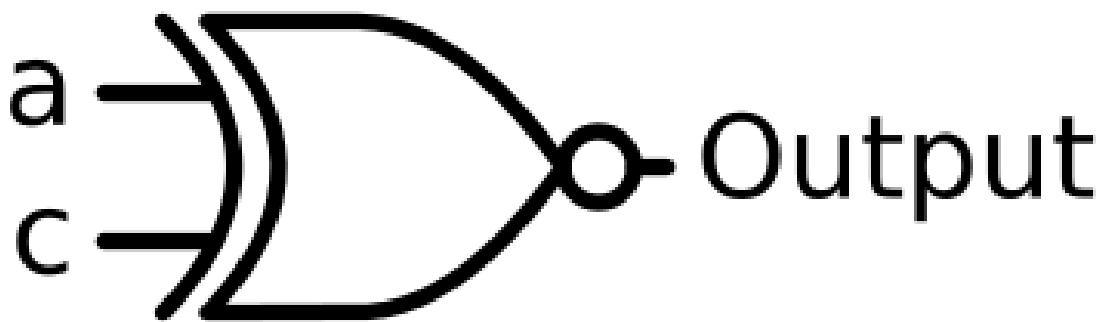

Correct Answer: no