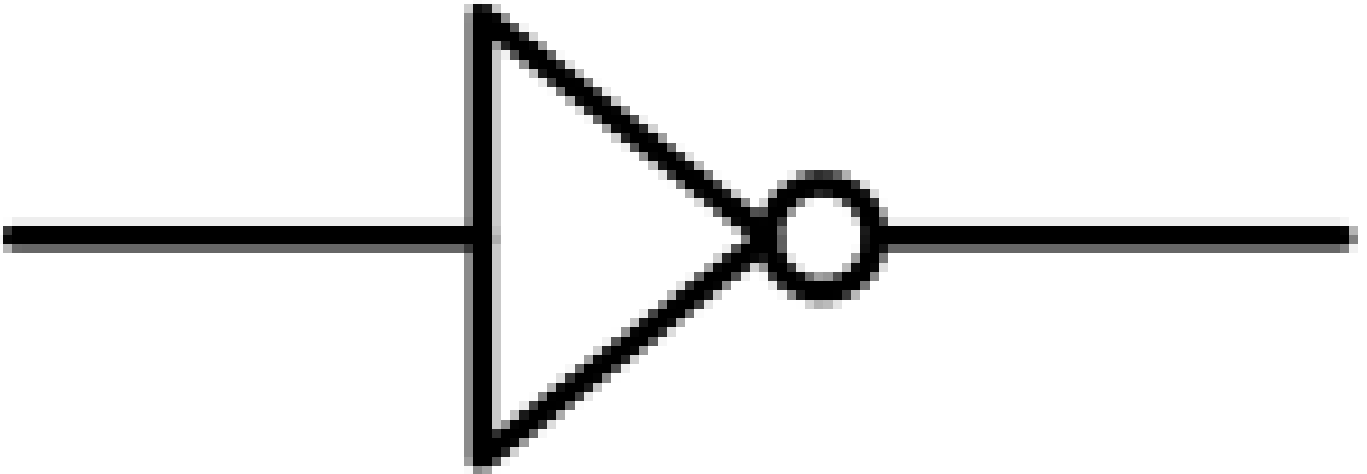


Question 1:

What is the output of the NOT gate with input 1?



Options:

1. 0


2. 1

Correct Answer: 0

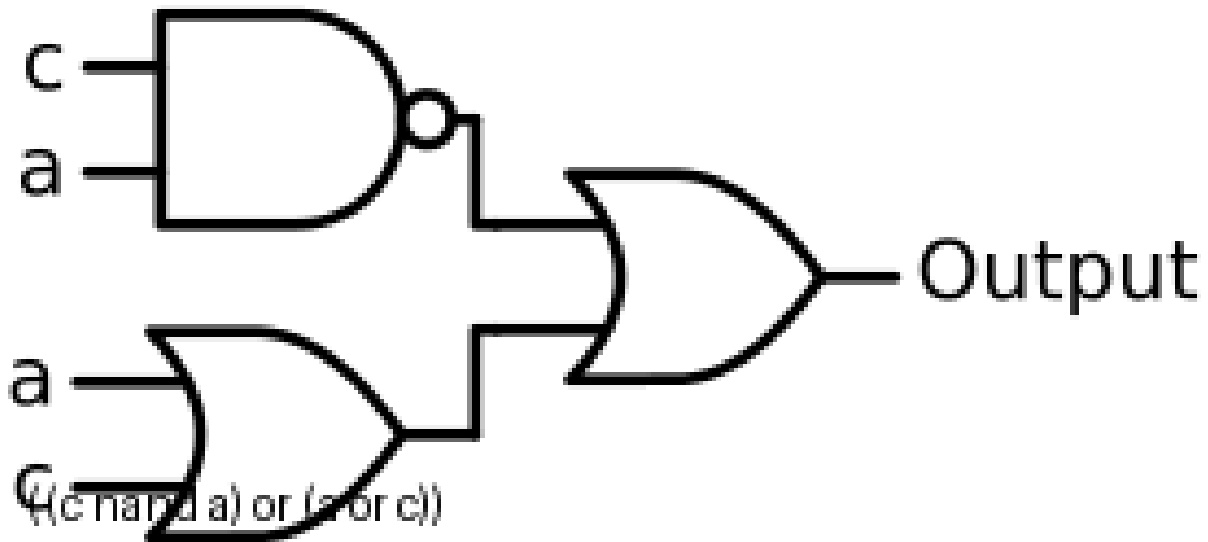Question 2:

What is the simplified form of the logic expression?

$((c \text{ nand } a) \text{ or } (a \text{ or } c))$




Correct Answer:  $((c \text{ nand } a) \text{ or } (a \text{ or } c))$

Question 3:

What is the simplified form of the logic expression?


(not b)

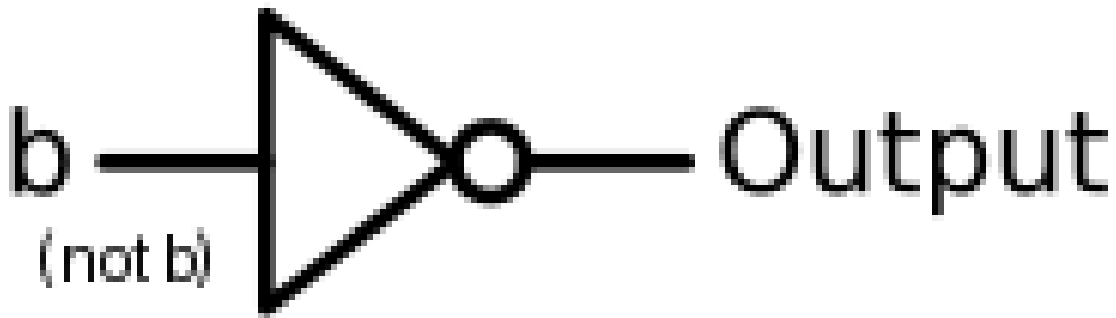

Correct Answer: (not b)
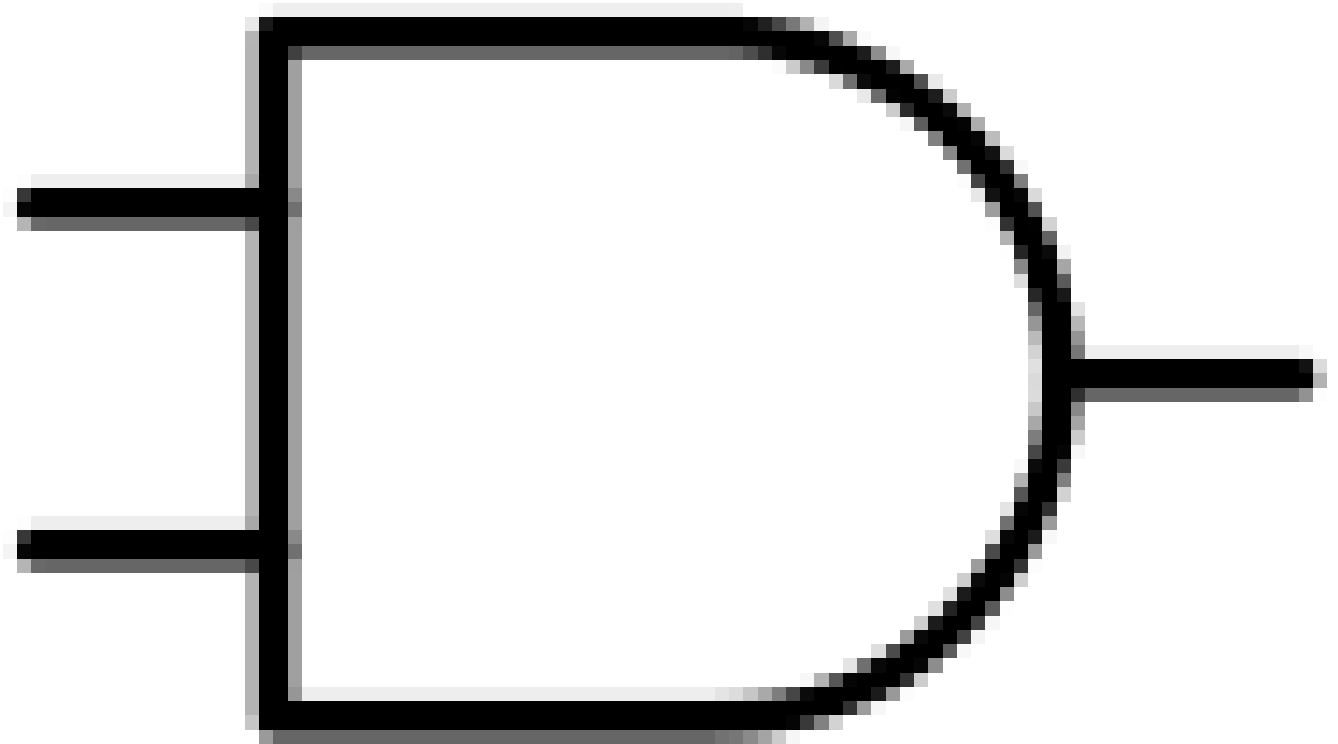
#### Question 4:

What is the output of the AND gate with inputs 0, 1?




Options:

1. 1
2. 0

Correct Answer: 0

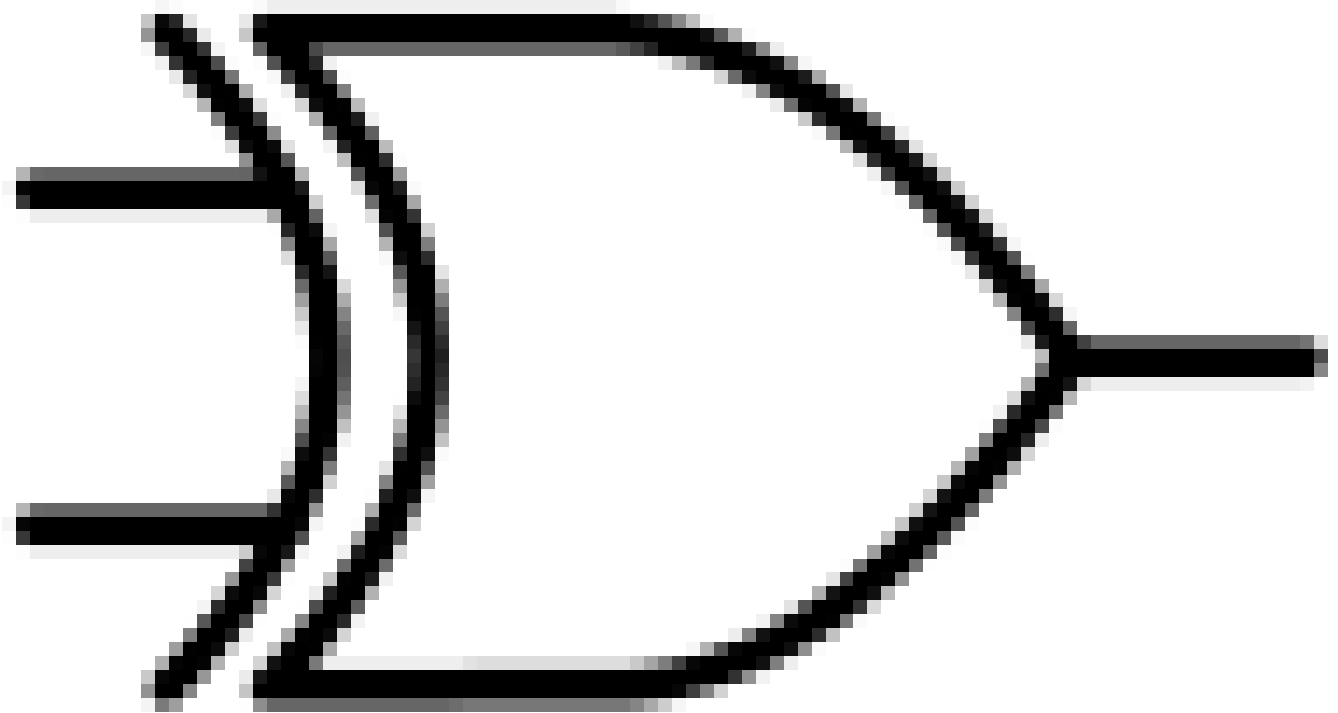Question 5:

What is the output of the XOR gate with inputs 1, 0?



Options:

1. 1


2. 0

Correct Answer: 1

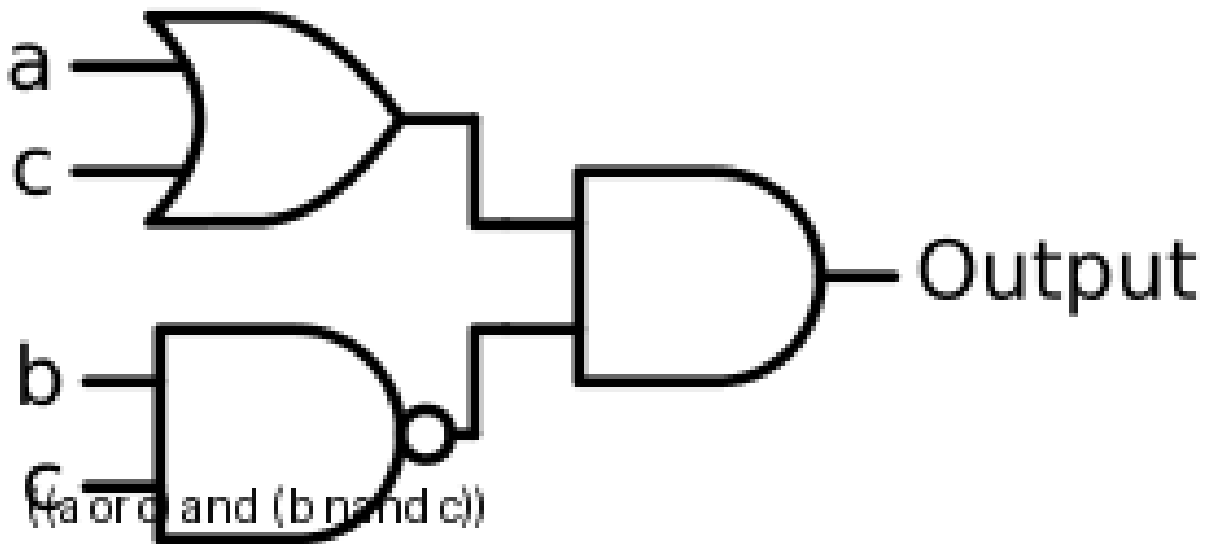Question 6:

What is the simplified form of the logic expression?


$((a \text{ or } c) \text{ and } (b \text{ nand } c))$



Correct Answer:  $((a \text{ or } c) \text{ and } (b \text{ nand } c))$

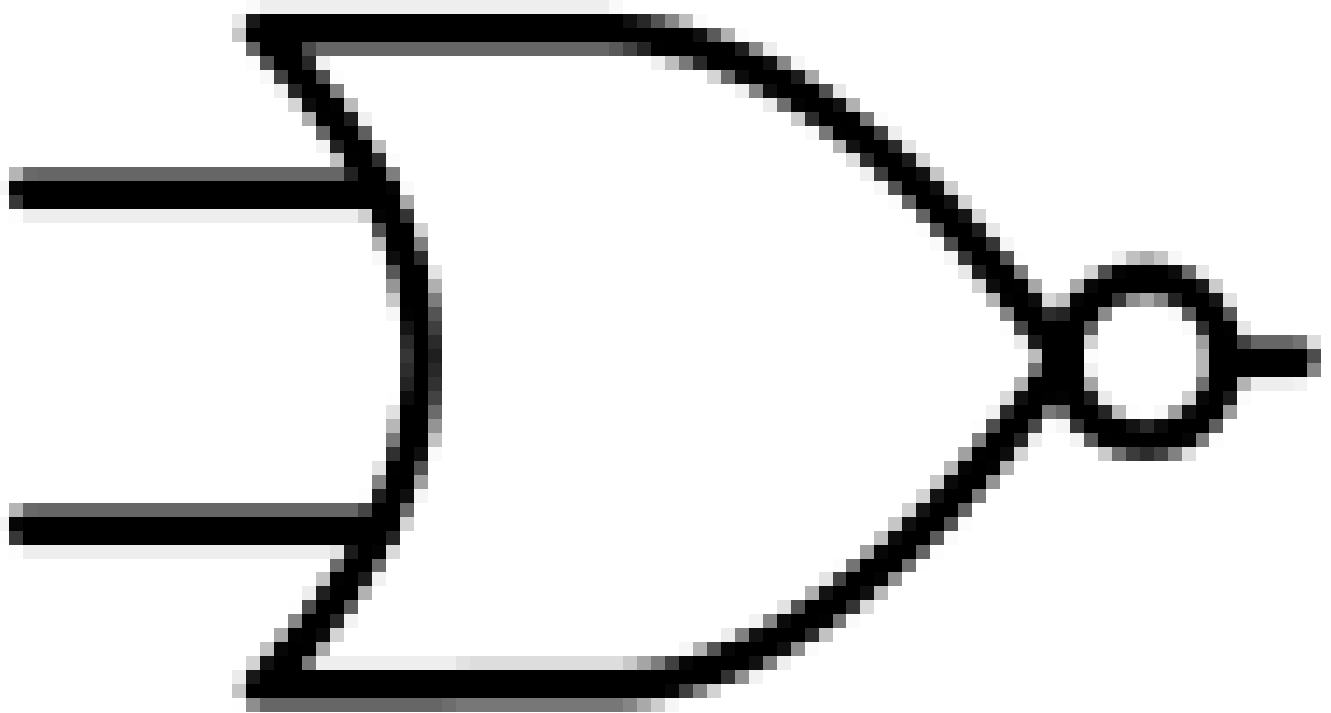Question 7:

What is the output of the NOR gate with inputs 0, 1?



Options:

1. 1


2. 0

Correct Answer: 0

Question 8:

What is the simplified form of the logic expression?

(c or b)

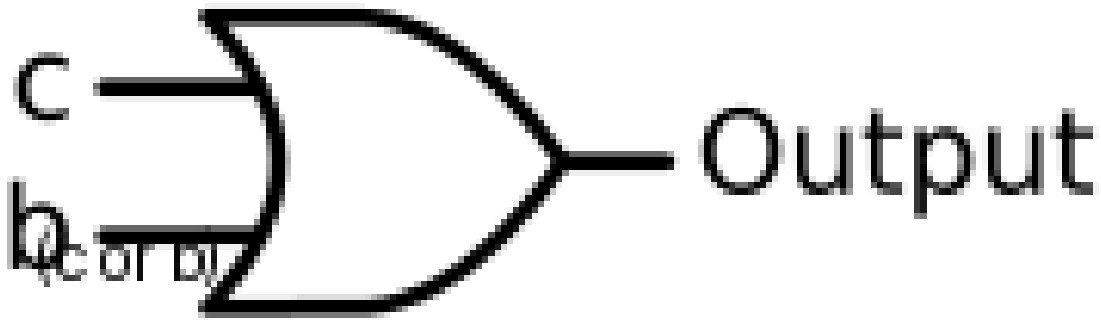


Correct Answer: (c or b)



Question 9:

What is the simplified form of the logic expression?


(c xor b)

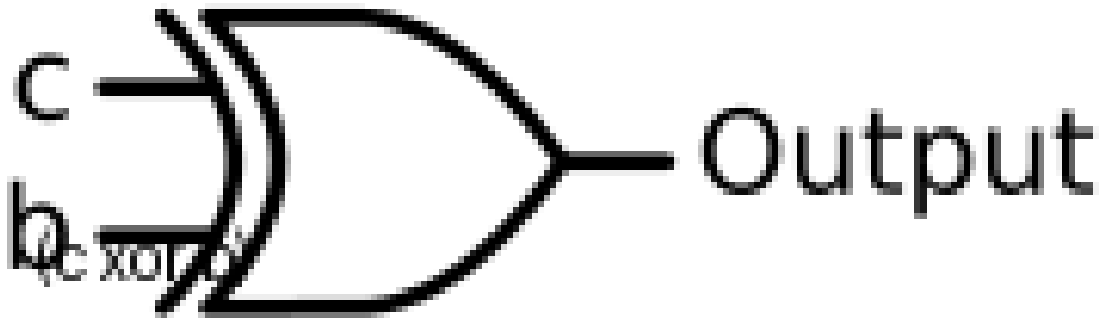

Correct Answer: (c xor b)

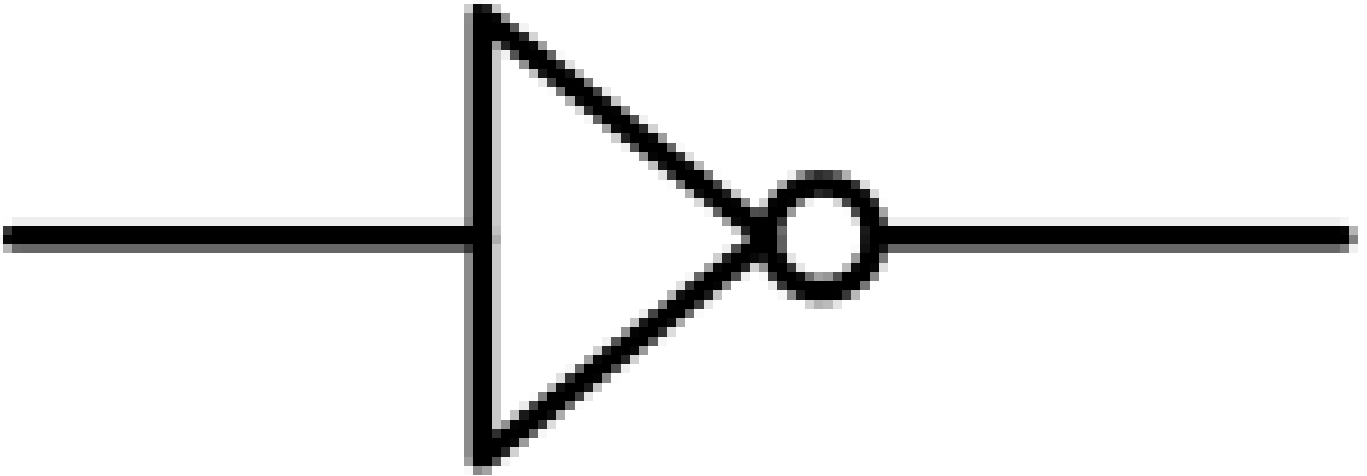Question 10:

What is the output of the NOT gate with input 0?



Options:

1. 0


2. 1

Correct Answer: 1

Question 11:

What is the simplified form of the logic expression?

(not c)

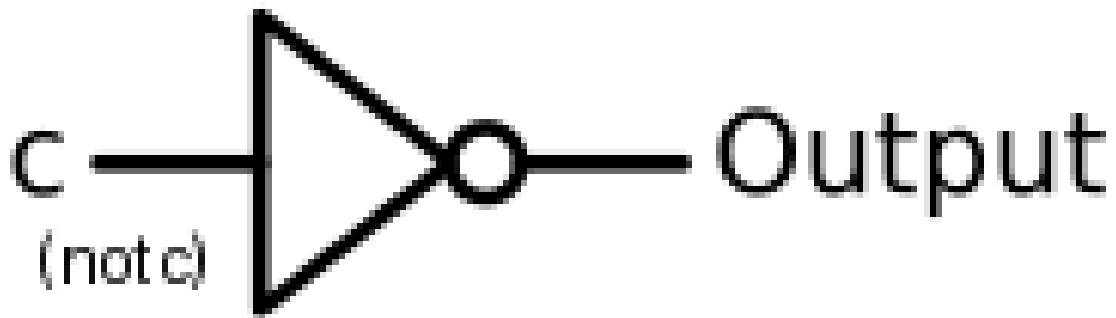


Correct Answer: (not c)

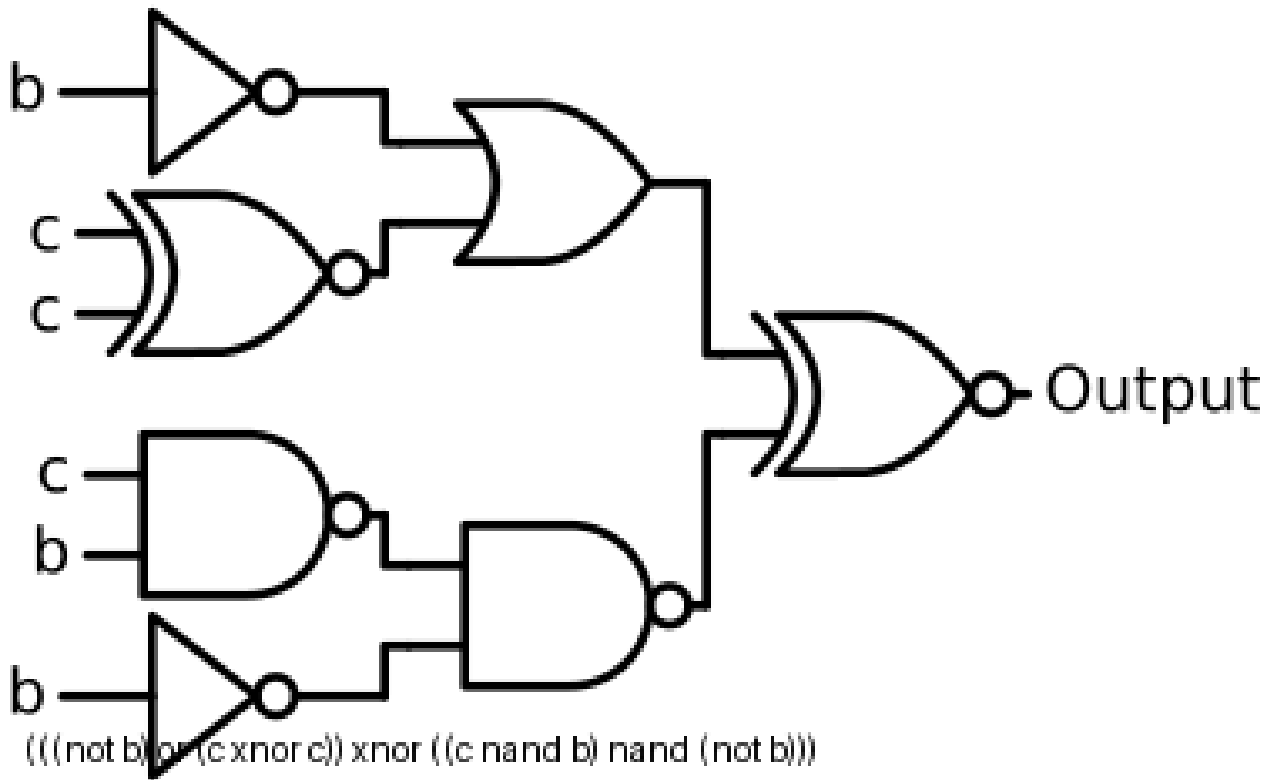Question 12:

What is the simplified form of the logic expression?

$((\text{not } b) \text{ or } (c \text{ xnor } c)) \text{ xnor } ((c \text{ nand } b) \text{ nand } (\text{not } b))$



Correct Answer:  $((\text{not } b) \text{ or } (c \text{ xnor } c)) \text{ xnor } ((c \text{ nand } b) \text{ nand } (\text{not } b))$