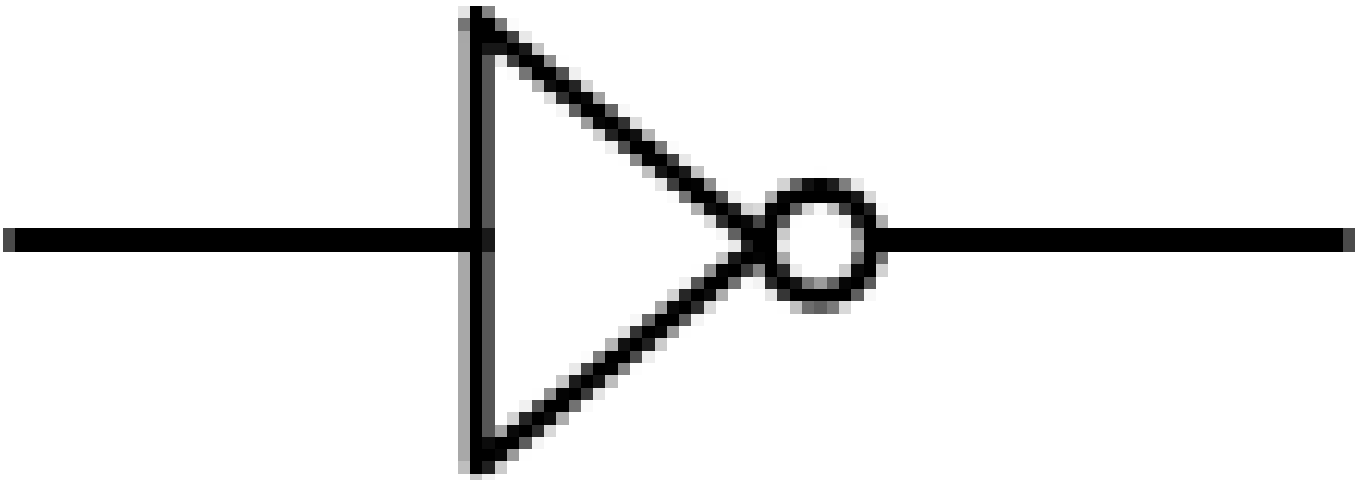


Question 1:

What is the output of the NOT gate with input 0?



Options:

1. 1

2. 0



Correct Answer: 1

Question 2:

Are these two circuits equivalent?

Expression 1: $((a \text{ xor } b) \text{ nand } (c \text{ xnor } a))$

Expression 2: $(a \text{ xor } a)$

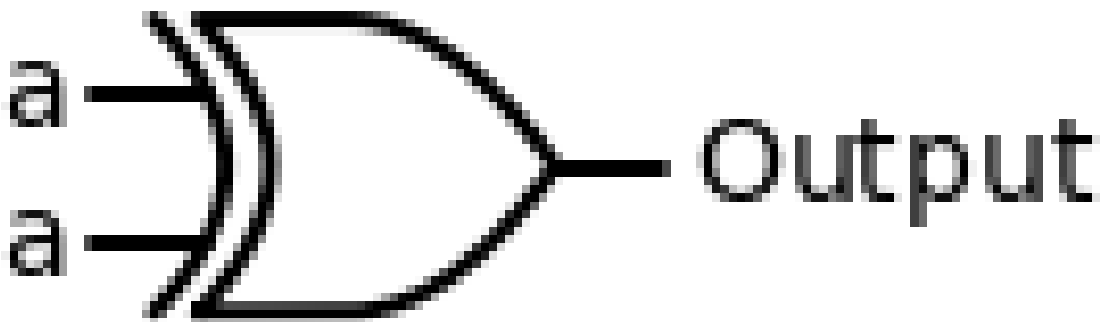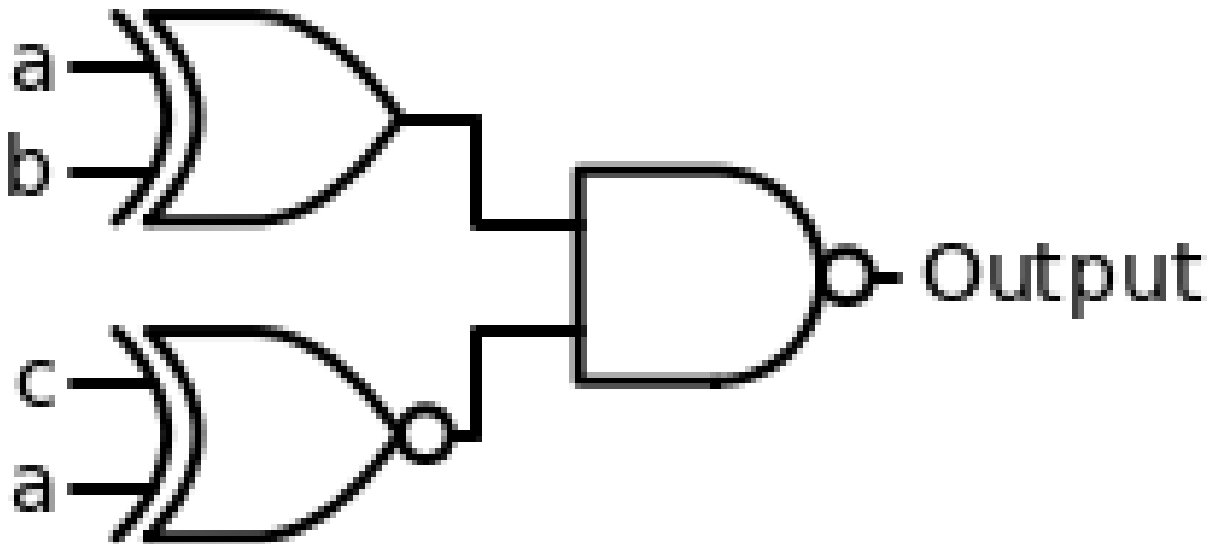


Options:

1. Yes
2. No

Correct Answer: no

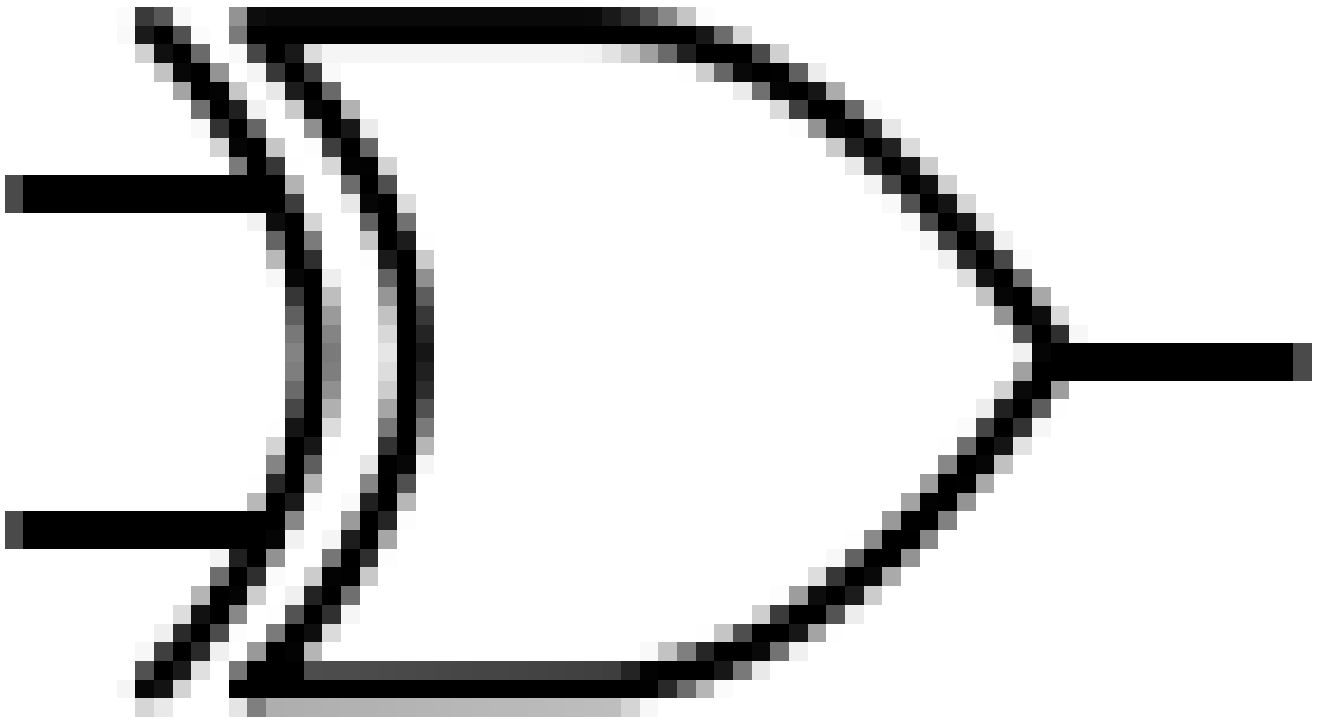Question 3:

What is the output of the XOR gate with inputs 0, 1?



Options:


1. 1

2. 0

Correct Answer: 1

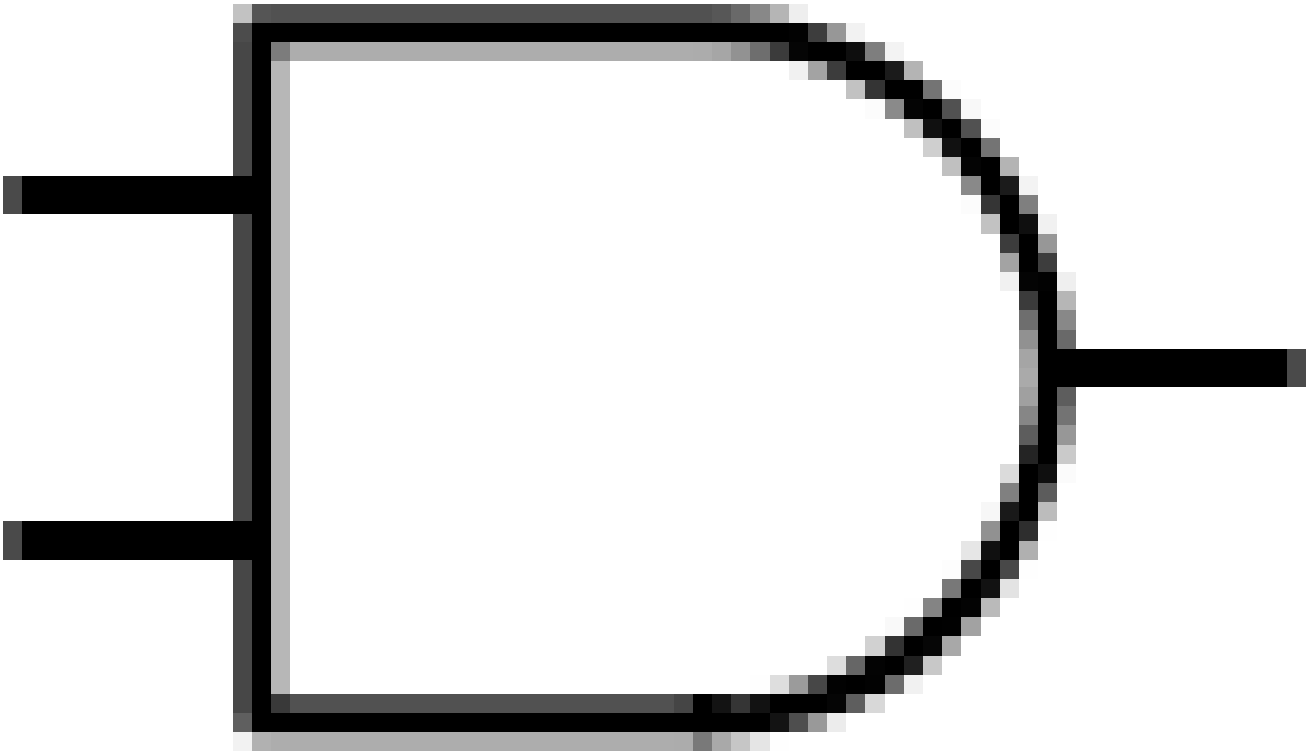Question 4:

What is the output of the AND gate with inputs 1, 1?



Options:


1. 1

2. 0

Correct Answer: 1

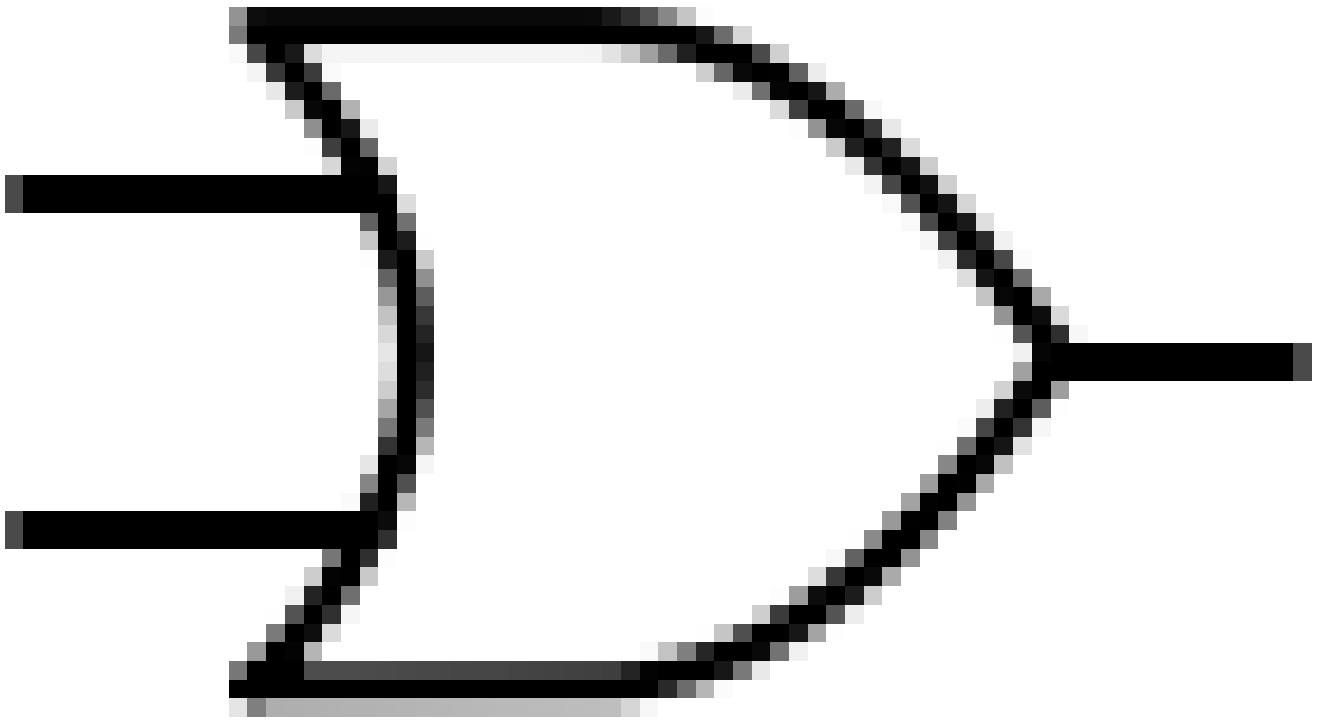Question 5:

What is the output of the OR gate with inputs 0, 0?



Options:

1. 1

2. 0


Correct Answer: 0

Question 6:

Are these two circuits equivalent?

Expression 1: $(c \text{ xnor } b)$

Expression 2: $(c \text{ xnor } b)$

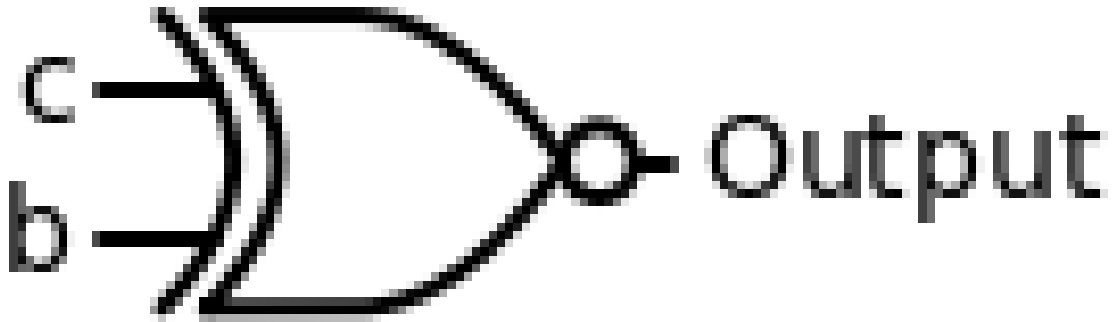


Options:

1. Yes
2. No

Correct Answer: yes

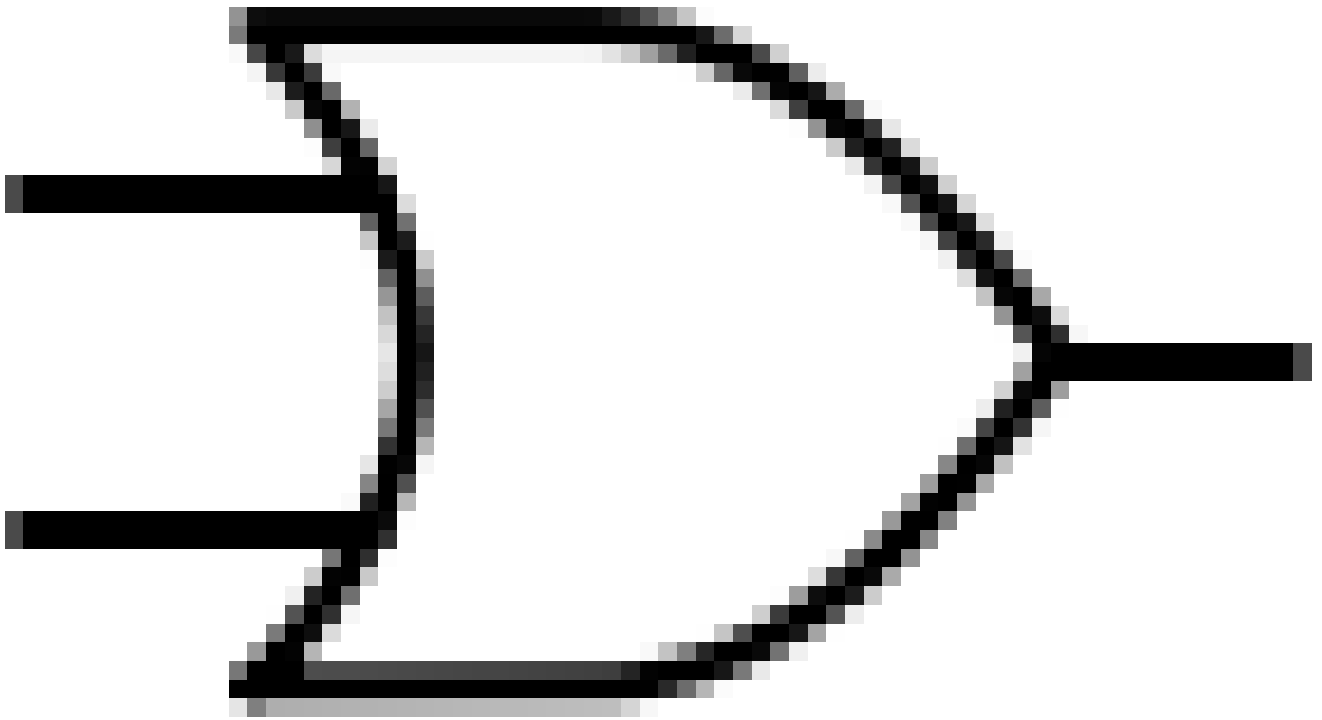Question 7:

What is the output of the OR gate with inputs 0, 0?



Options:

1. 0

2. 1


Correct Answer: 0


Question 8:

Are these two circuits equivalent?

Expression 1: $((b \text{ and } a) \text{ nor } (a \text{ nand } b)) \text{ and } ((b \text{ xnor } c) \text{ xor } (c \text{ xor } b))$

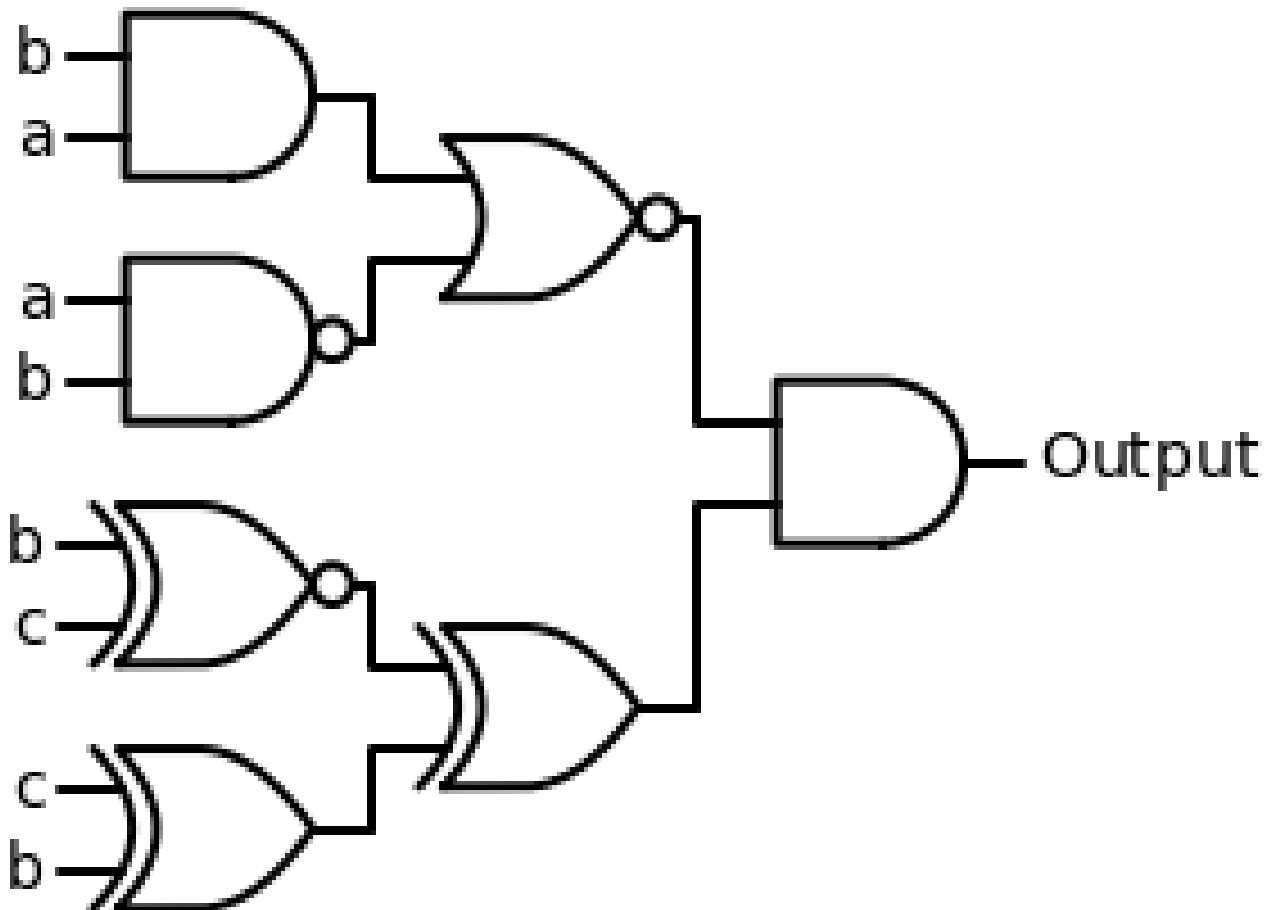Expression 2: $((b \text{ and } a) \text{ nor } (a \text{ nand } b)) \text{ and } ((b \text{ xnor } c) \text{ xor } (c \text{ xor } b))$



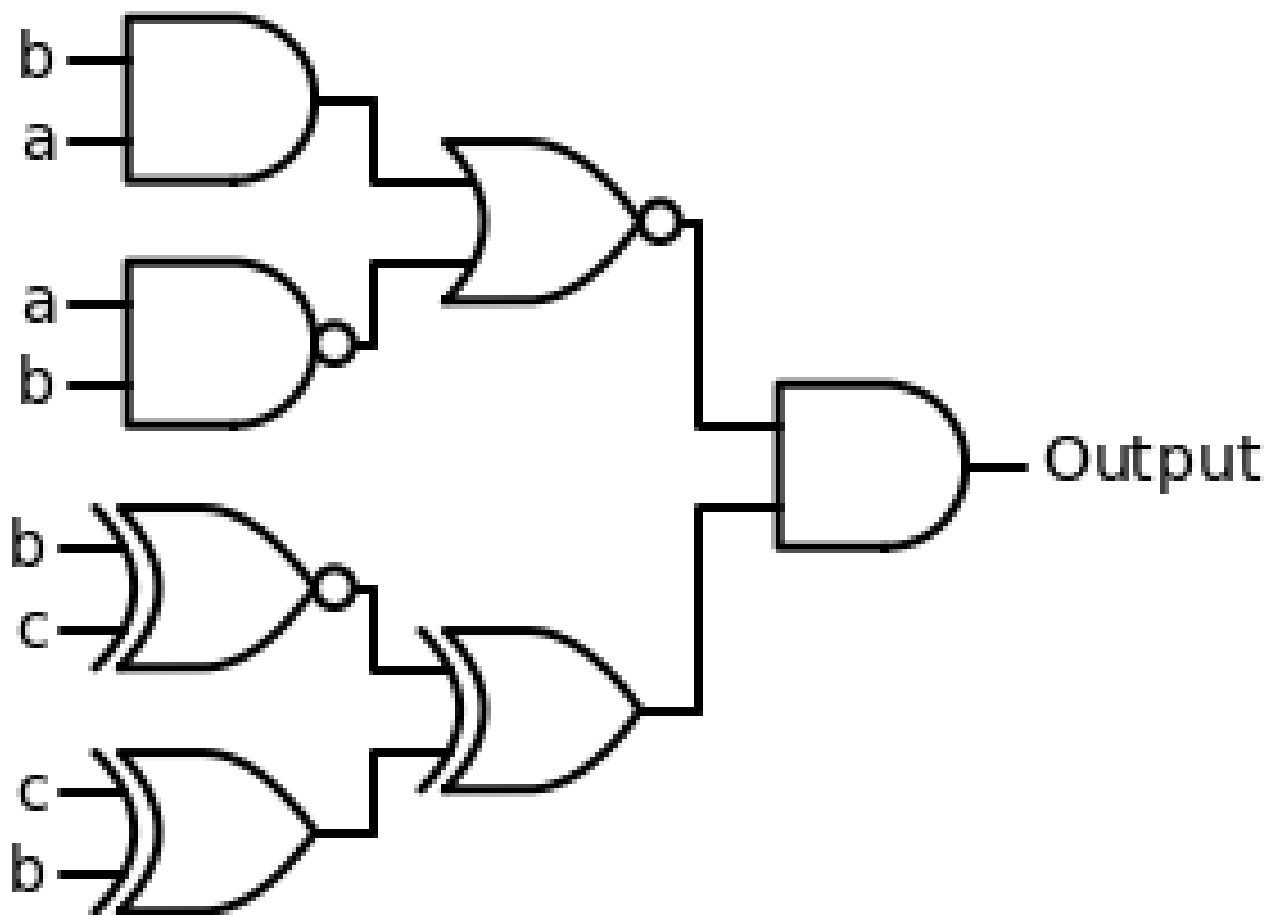

Options:

1. Yes
2. No



Correct Answer: yes

Question 9:

Are these two circuits equivalent?

Expression 1: $((c \text{ nor } b) \text{ nand } (\text{not } b)) \text{ nand } ((b \text{ and } a) \text{ or } (b \text{ nand } a))$

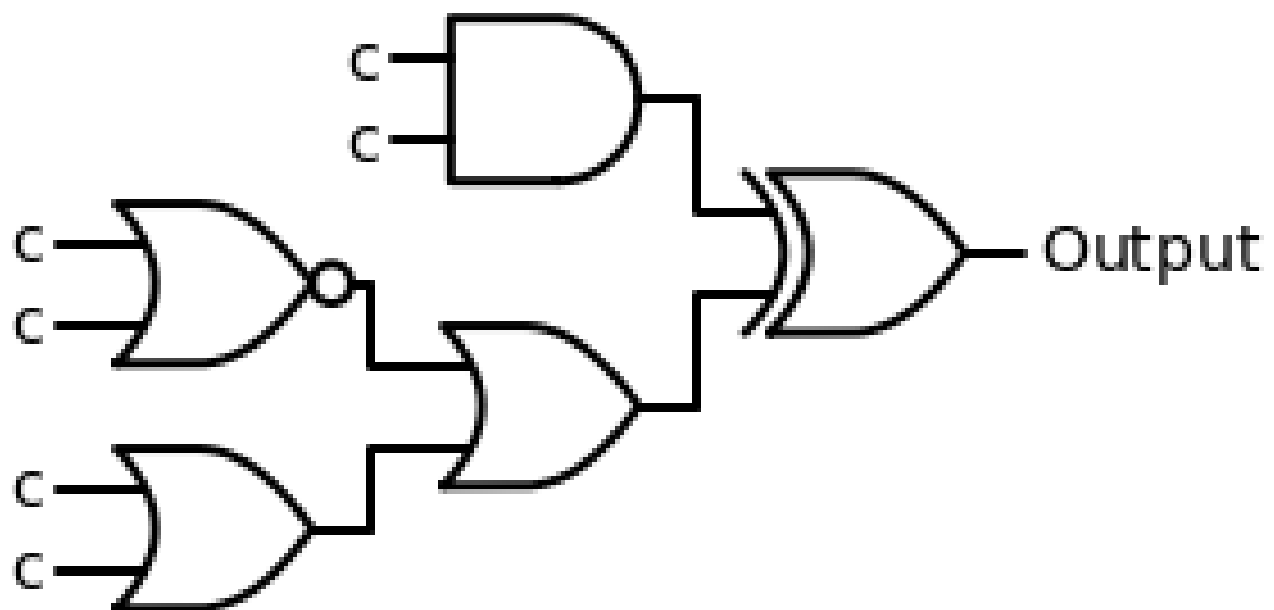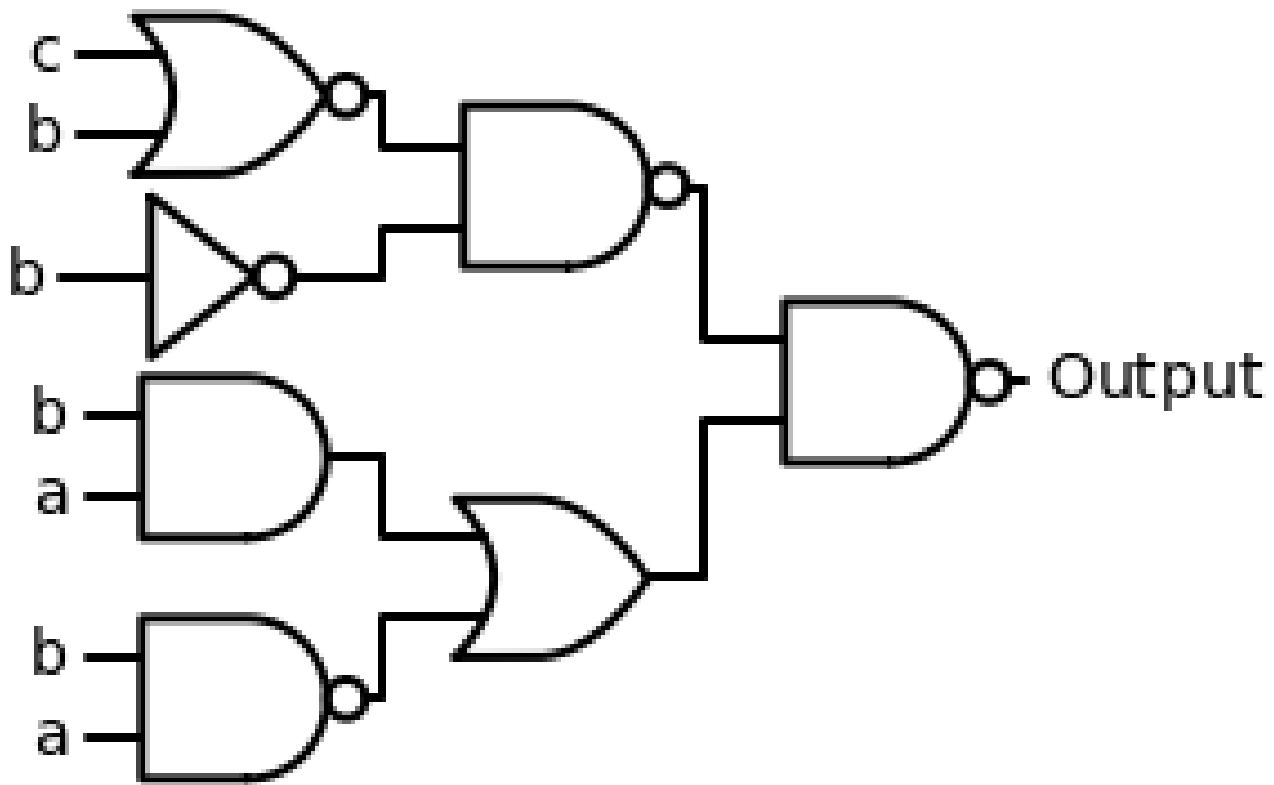Expression 2: $((\text{not } (c \text{ nand } c)) \text{ xor } ((c \text{ nor } c) \text{ or } (c \text{ or } c)))$



Options:

1. Yes

2. No


Correct Answer: no


Question 10:

Are these two circuits equivalent?

Expression 1: $((a \text{ or } b) \text{ xnor } (b \text{ nor } c)) \text{ nand } ((c \text{ nor } b) \text{ nand } (b \text{ xnor } c))$

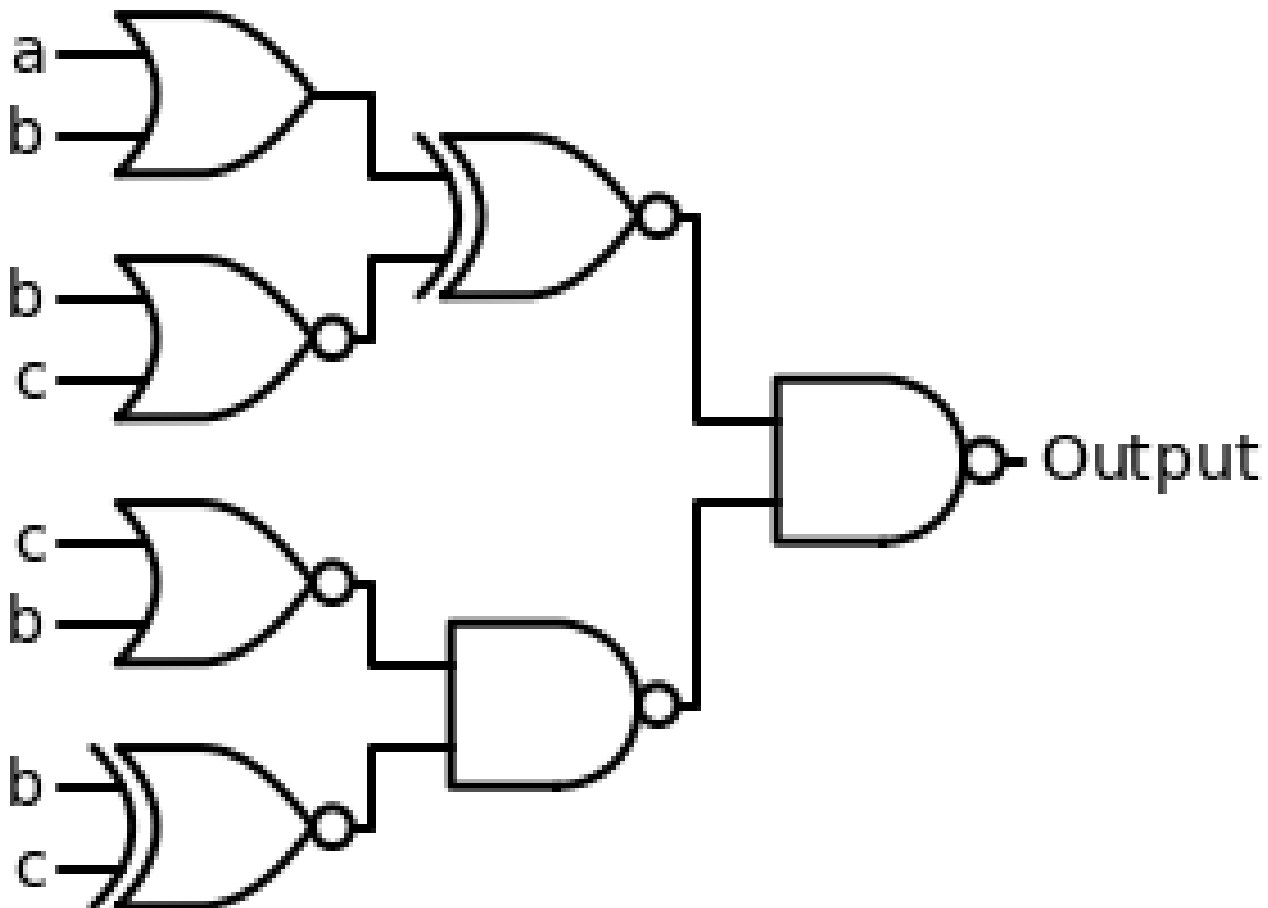Expression 2: $((a \text{ xor } c) \text{ nor } (\text{not } a)) \text{ xnor } ((c \text{ xnor } c) \text{ nor } (b \text{ and } b))$



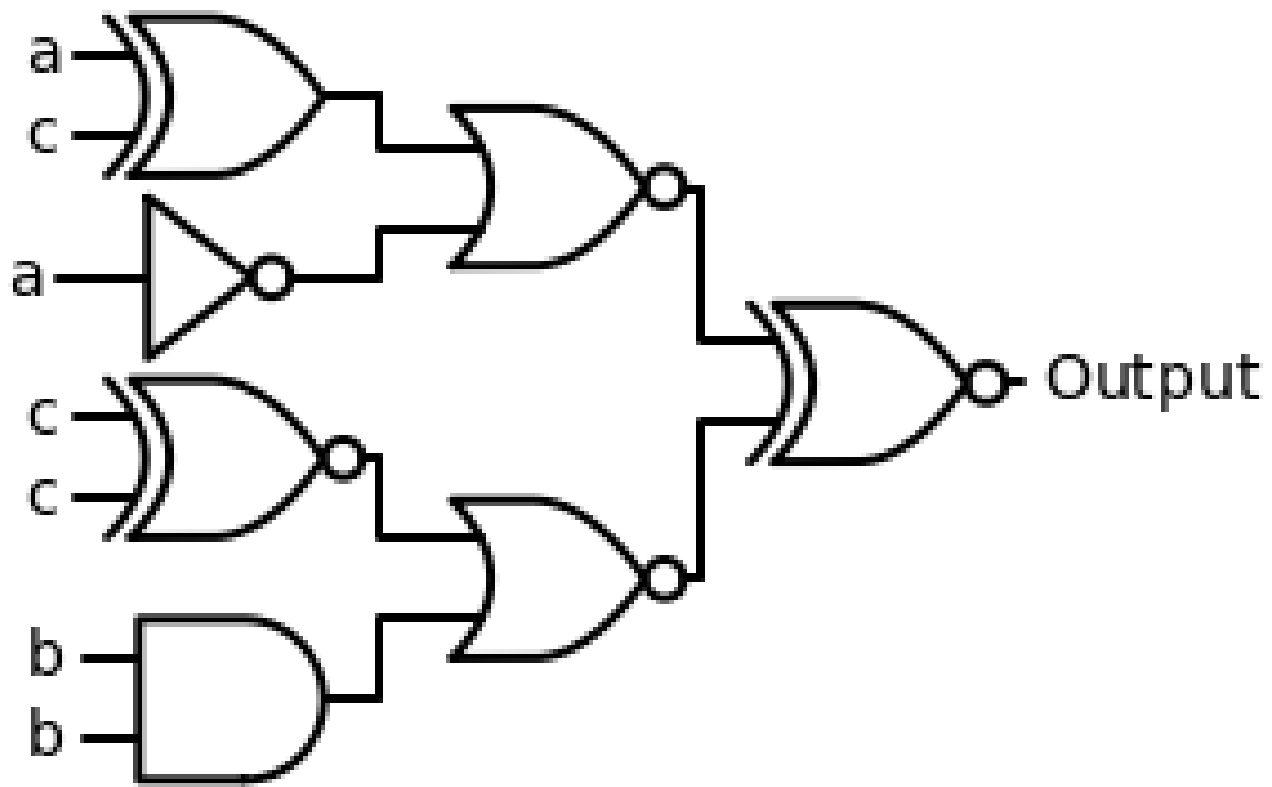


Options:

1. Yes
2. No

Correct Answer: no

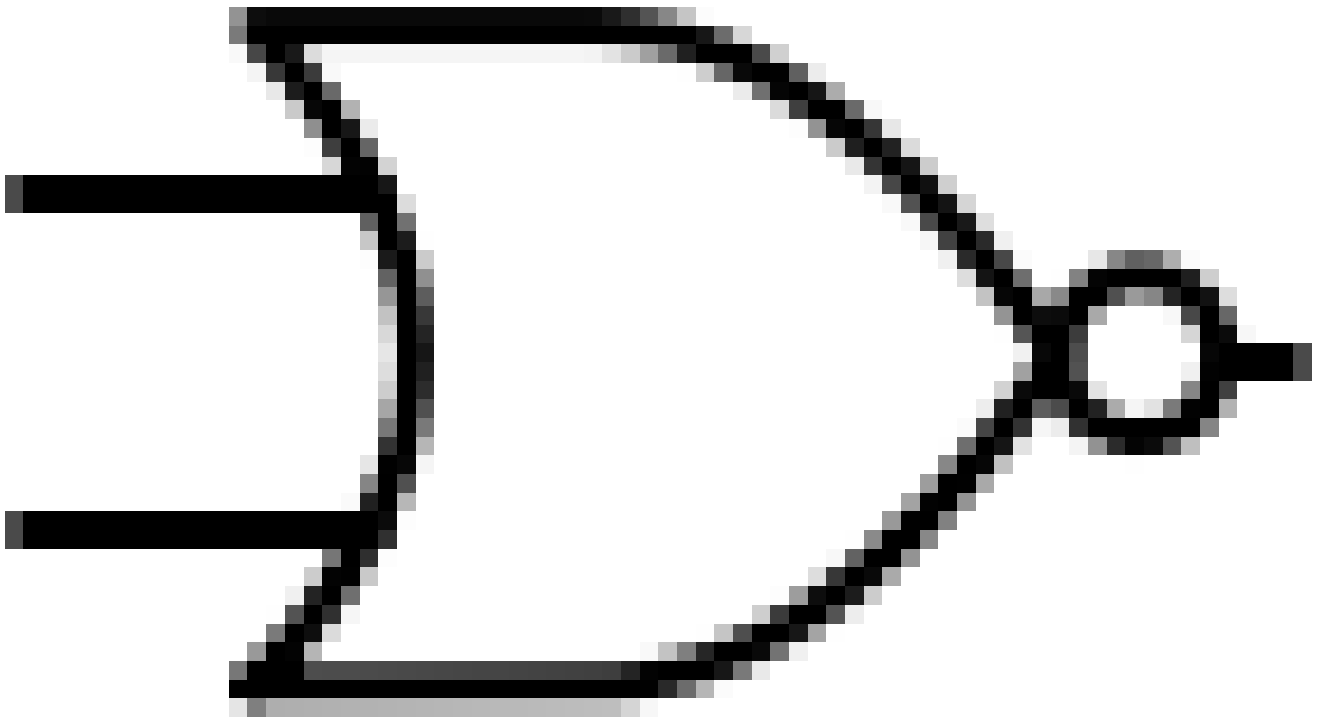Question 11:

What is the output of the NOR gate with inputs 1, 1?



Options:

1. 0

2. 1


Correct Answer: 0

Question 12:

Are these two circuits equivalent?

Expression 1: $(c \text{ nand } b)$

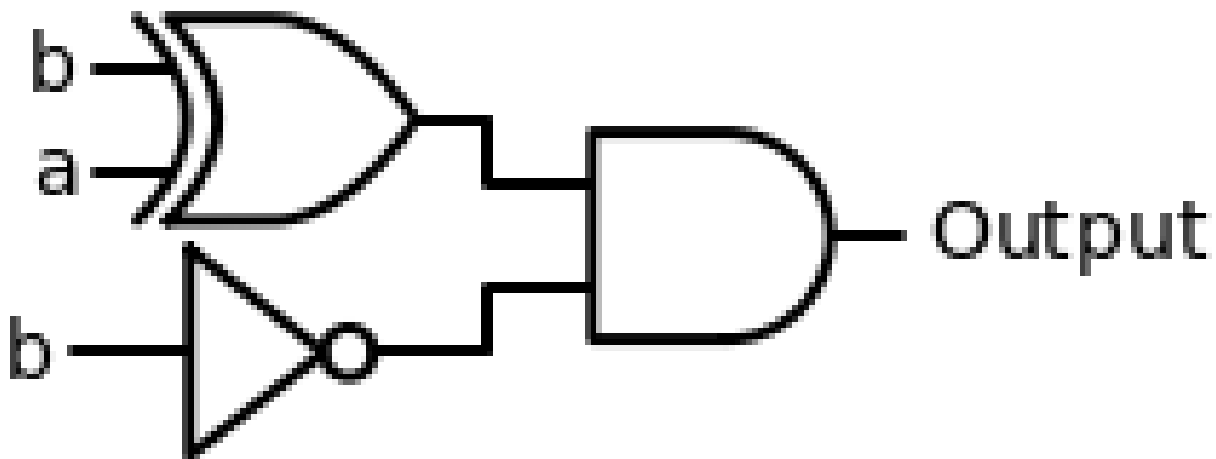Expression 2: $((b \text{ xor } a) \text{ and } (\text{not } b))$



Options:

1. Yes
2. No



Correct Answer: no

Question 13:

Are these two circuits equivalent?

Expression 1: $((b \text{ and } b) \text{ xnor } (a \text{ nor } b))$

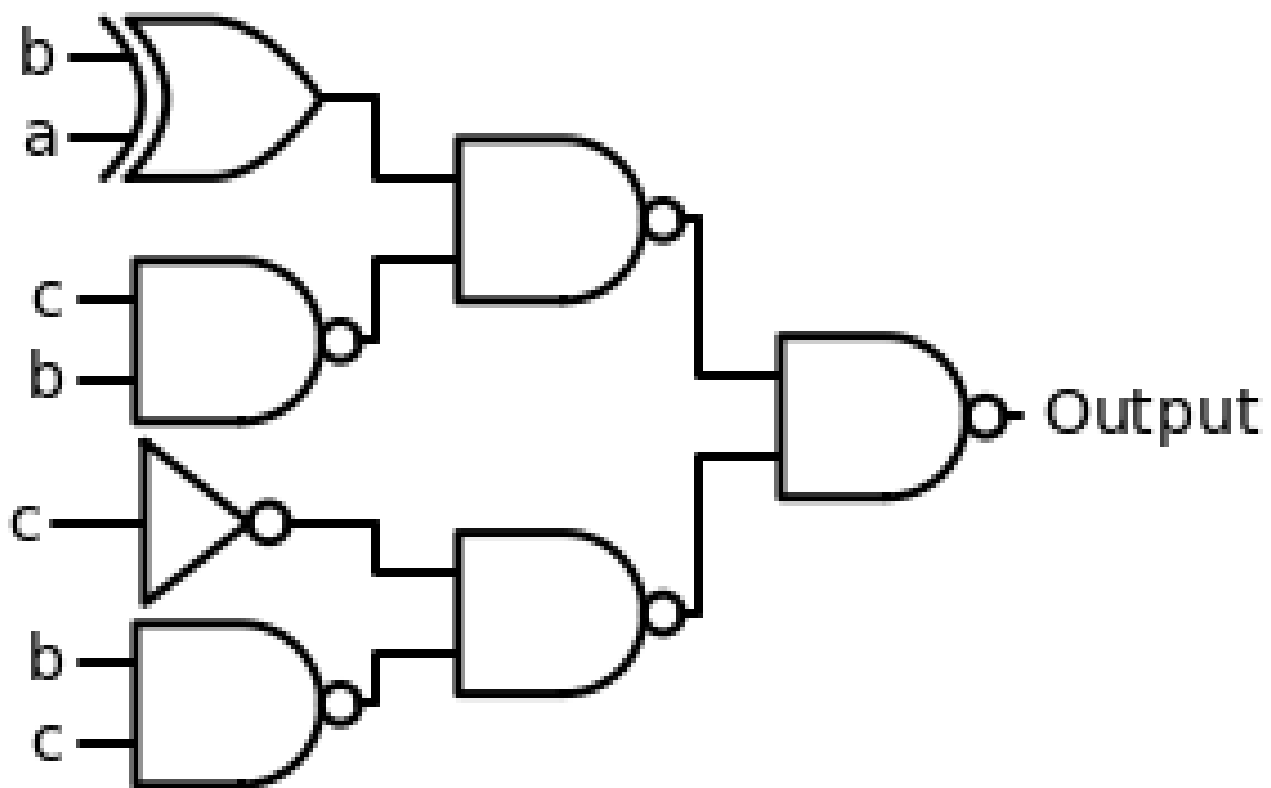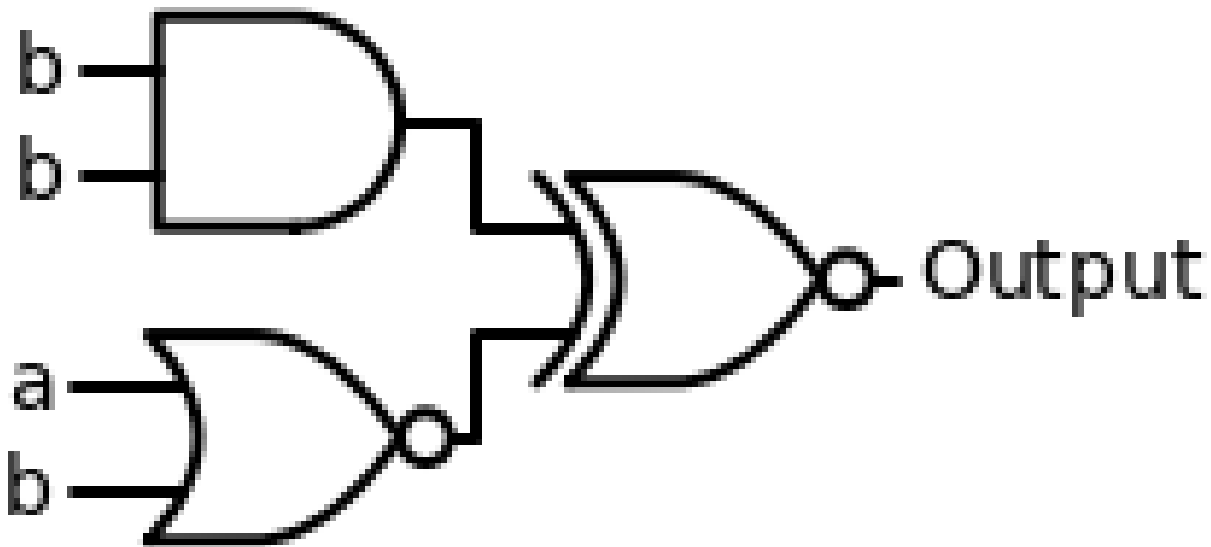Expression 2: $((b \text{ xor } a) \text{ nand } (c \text{ nand } b)) \text{ nand } ((\text{not } c) \text{ nand } (b \text{ nand } c))$



Options:


1. Yes

2. No

Correct Answer: no

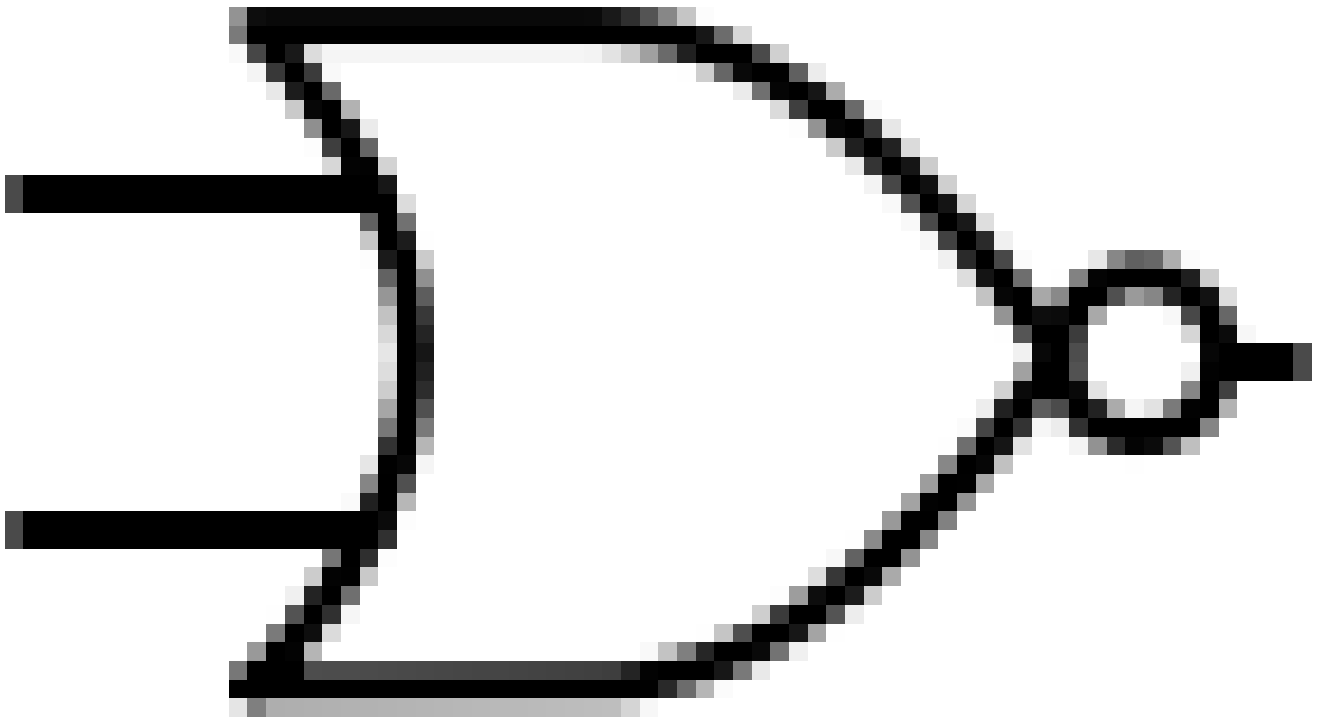Question 14:

What is the output of the NOR gate with inputs 1, 1?



Options:


1. 0

2. 1

Correct Answer: 0

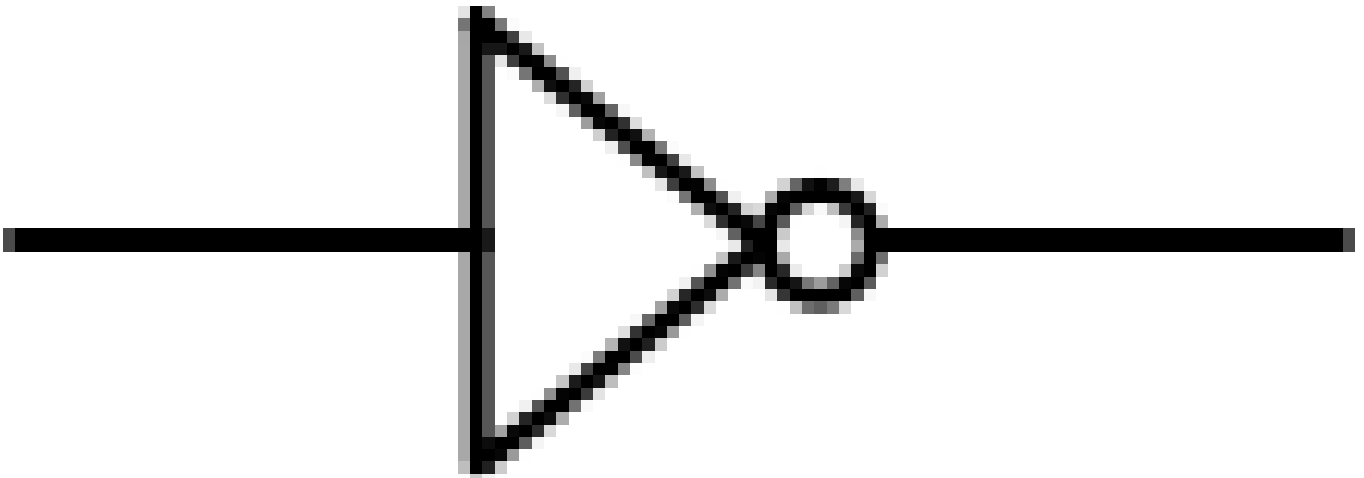Question 15:

What is the output of the NOT gate with input 1?



Options:


1. 1

2. 0

Correct Answer: 0

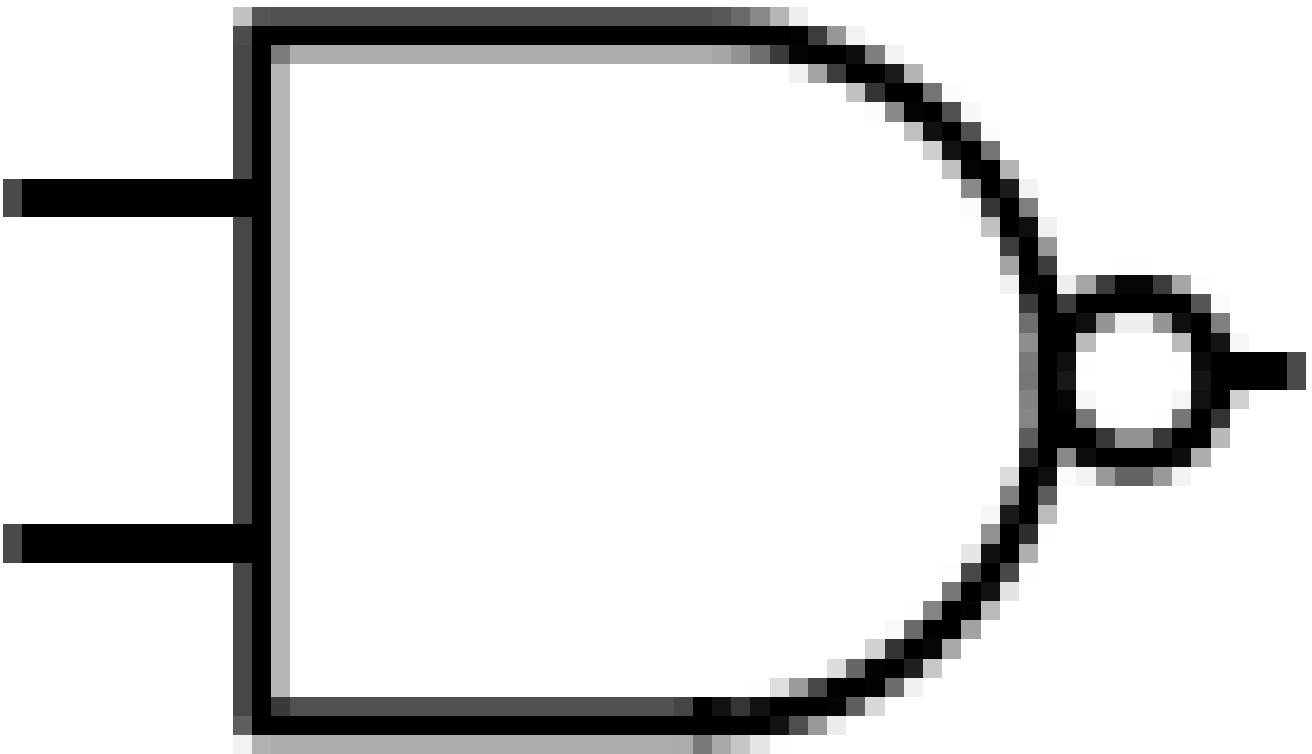Question 16:

What is the output of the NAND gate with inputs 0, 0?



Options:

1. 1

2. 0



Correct Answer: 1

Question 17:

Are these two circuits equivalent?

Expression 1: $((\text{not } b) \text{ nand } (a \text{ nor } a))$

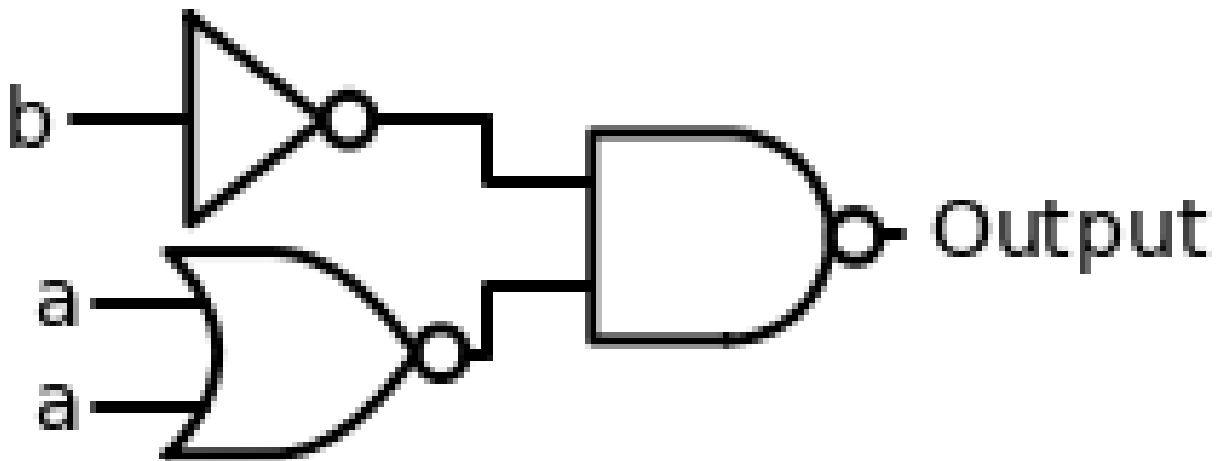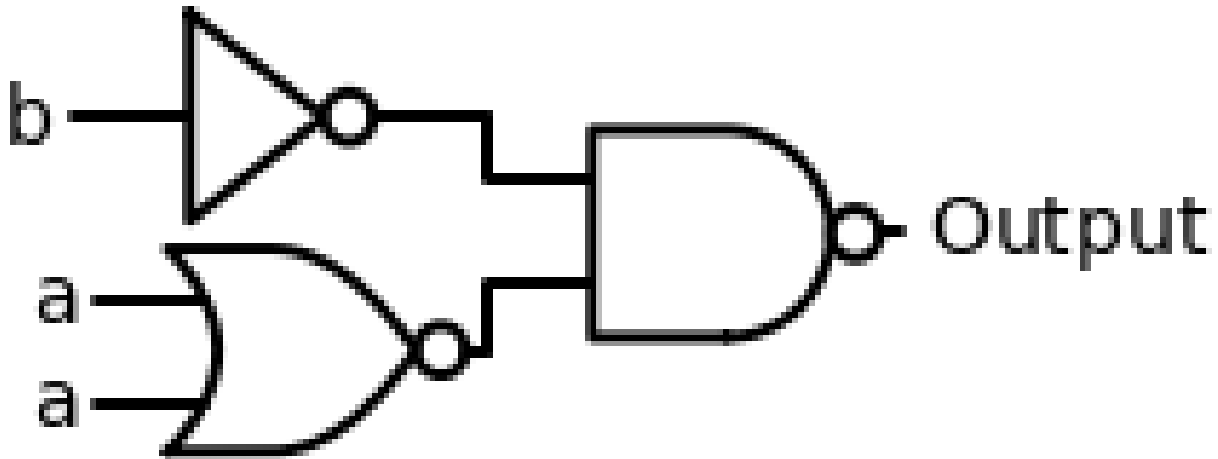Expression 2: $((\text{not } b) \text{ nand } (a \text{ nor } a))$




Options:

1. Yes
2. No

Correct Answer: yes

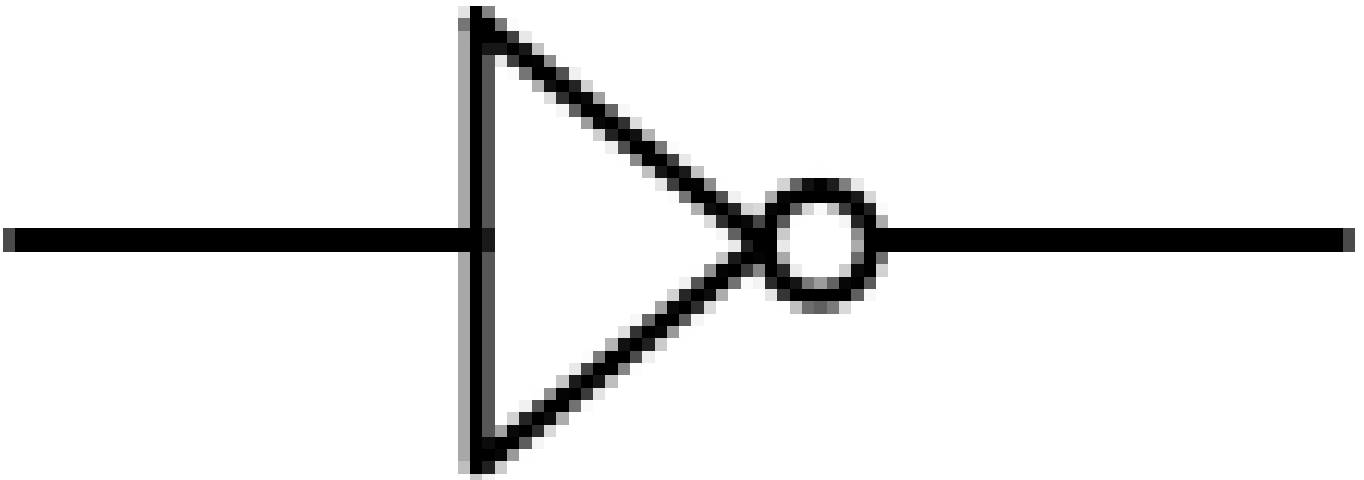Question 18:

What is the output of the NOT gate with input 0?



Options:


1. 1

2. 0

Correct Answer: 1

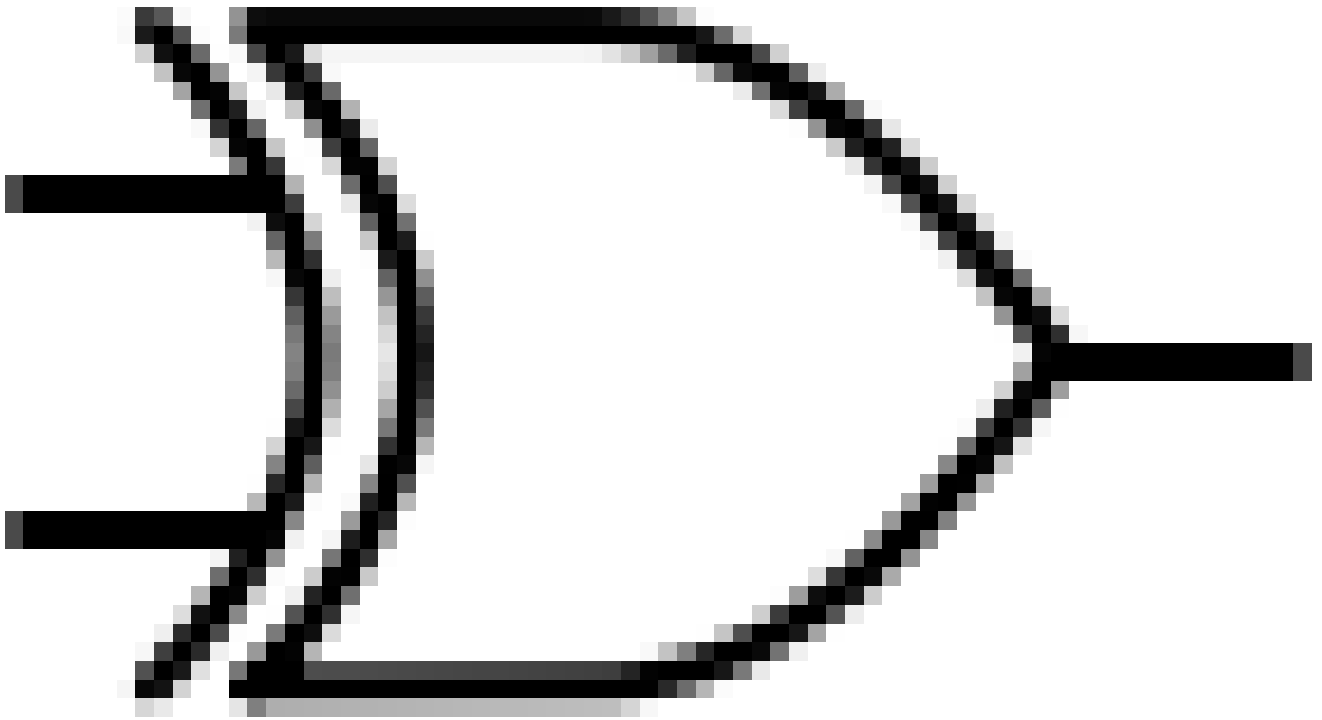Question 19:

What is the output of the XOR gate with inputs 0, 0?



Options:


1. 0

2. 1

Correct Answer: 0

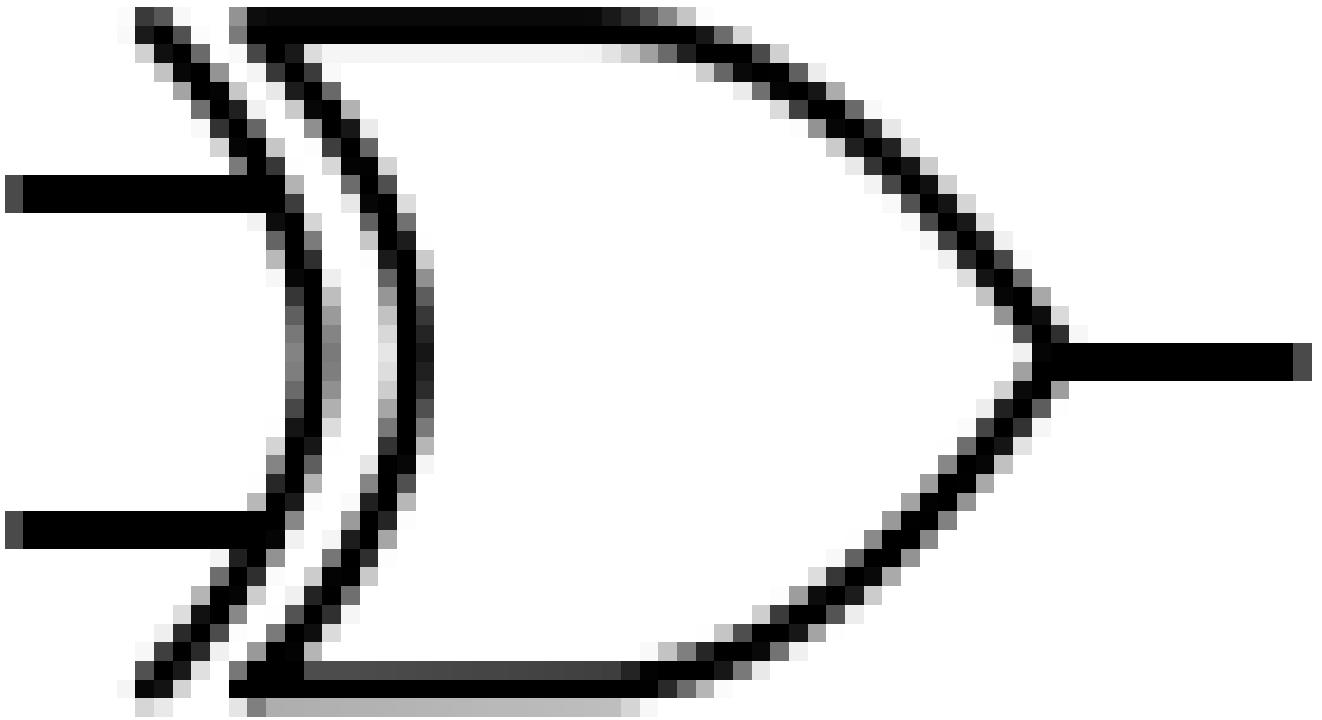Question 20:

What is the output of the XOR gate with inputs 0, 0?



Options:

1. 1

2. 0



Correct Answer: 0

Question 21:

Are these two circuits equivalent?

Expression 1: $((c \text{ xor } b) \text{ or } (c \text{ and } c))$

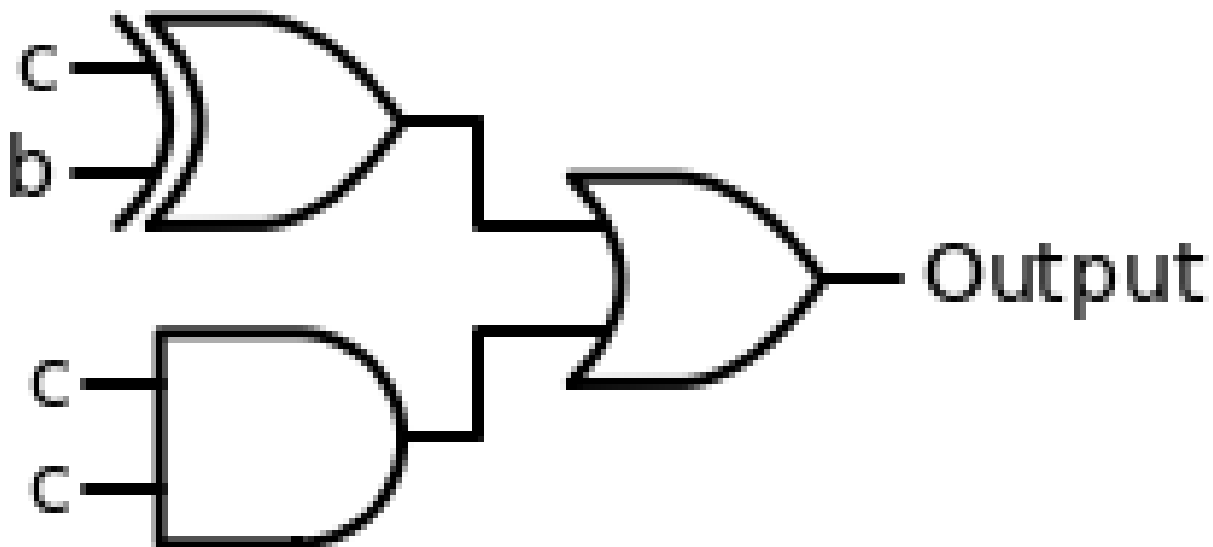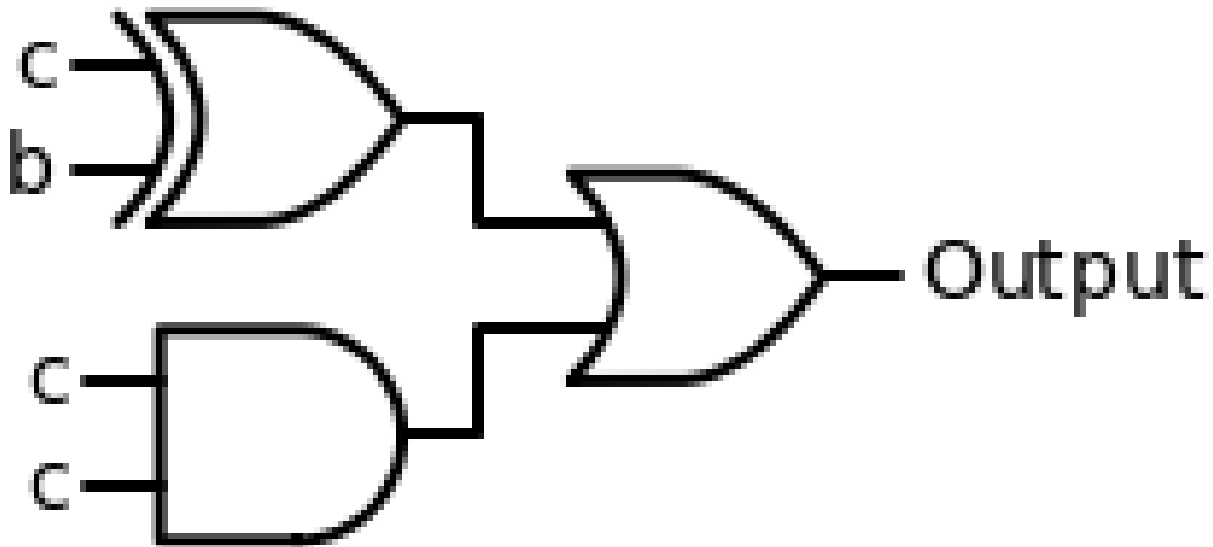Expression 2: $((c \text{ xor } b) \text{ or } (c \text{ and } c))$



Options:

1. Yes
2. No



Correct Answer: yes

Question 22:

Are these two circuits equivalent?

Expression 1: $(c \text{ xor } b)$

Expression 2: $(b \text{ and } c)$

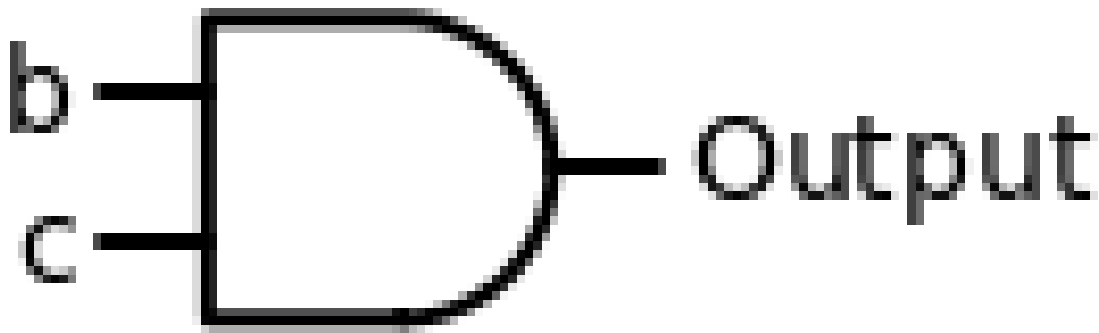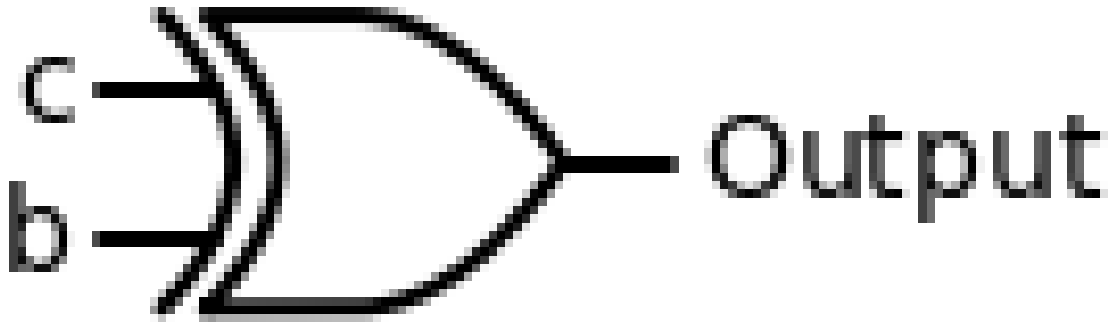

Options:

1. Yes
2. No



Correct Answer: no

Question 23:

Are these two circuits equivalent?

Expression 1: $((c \text{ nand } a) \text{ xnor } (\text{not } c))$

Expression 2: $(b \text{ and } b)$

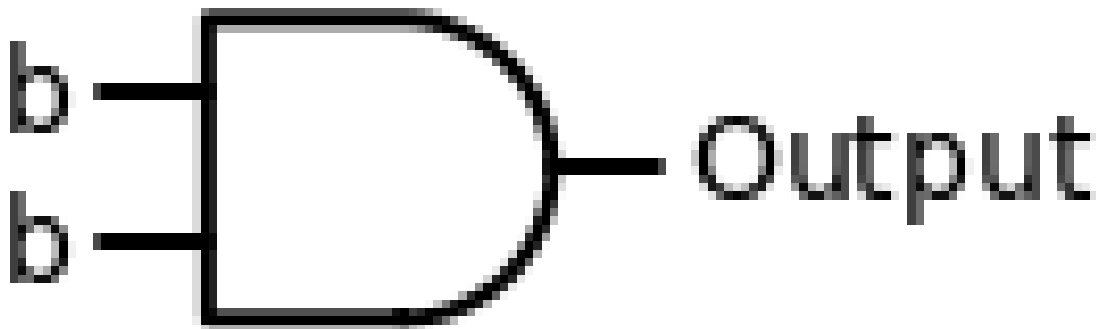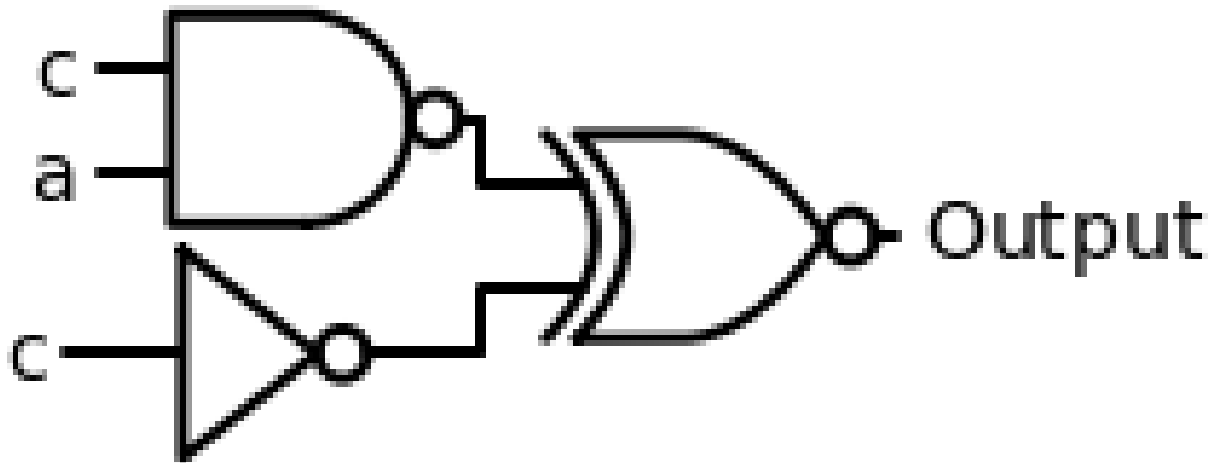

Options:

1. Yes
2. No


Correct Answer: no


Question 24:

Are these two circuits equivalent?

Expression 1: $((\text{not } c) \text{ xor } (b \text{ nand } a)) \text{ xor } ((b \text{ and } a) \text{ or } (\text{not } a))$

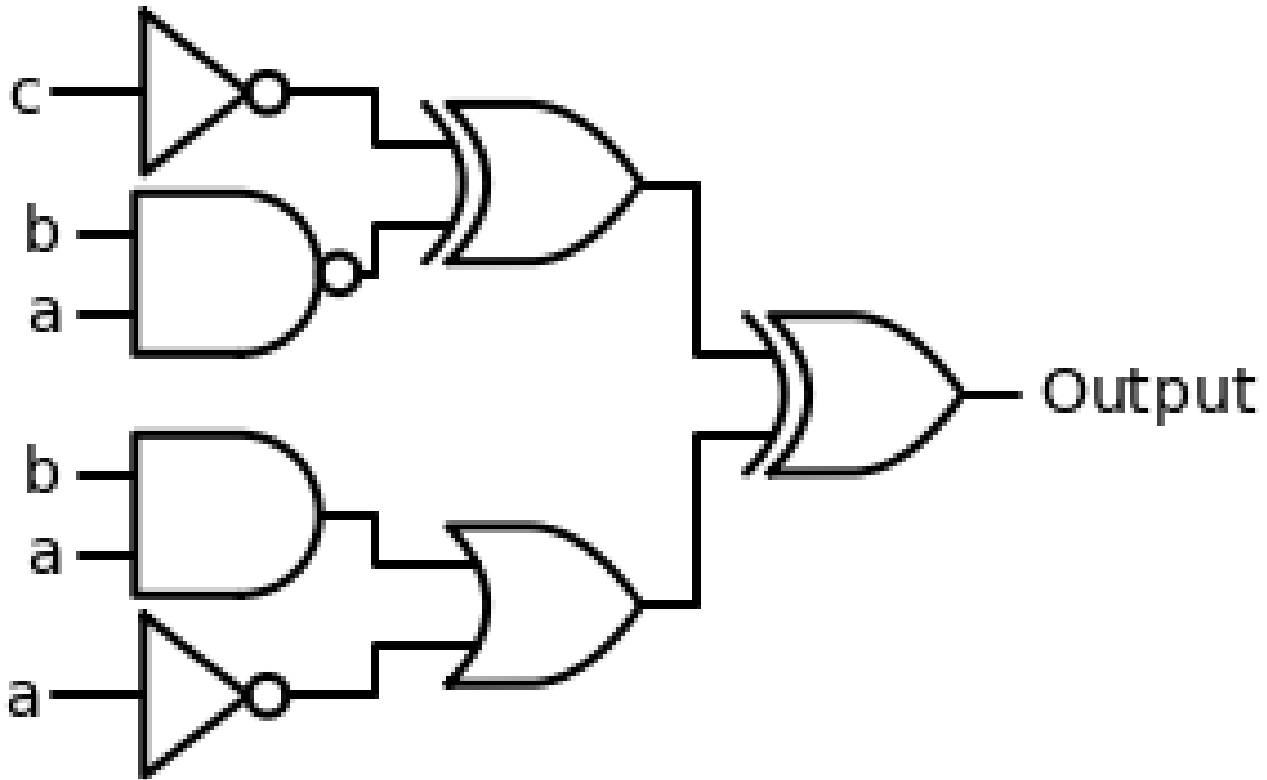Expression 2: $((\text{not } c) \text{ xor } (b \text{ nand } a)) \text{ xor } ((b \text{ and } a) \text{ or } (\text{not } a))$



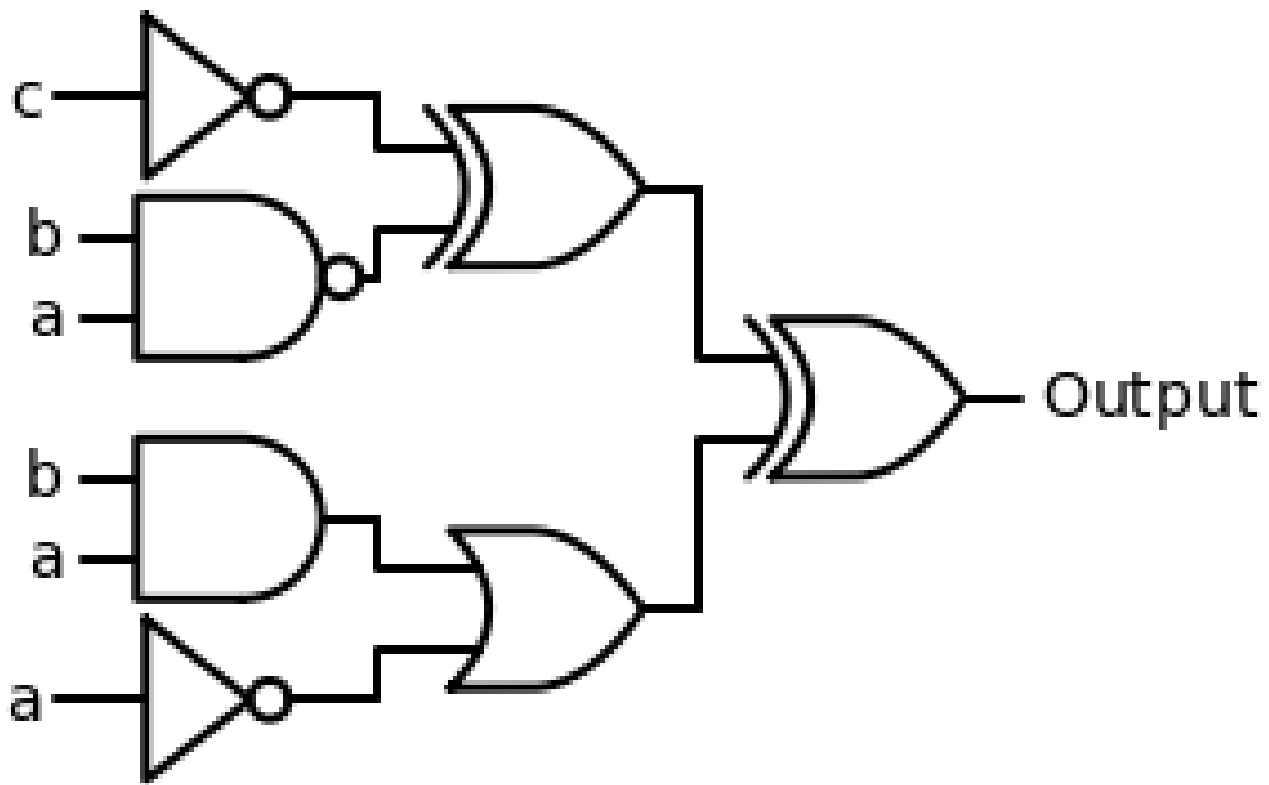


Options:

1. Yes
2. No

Correct Answer: yes

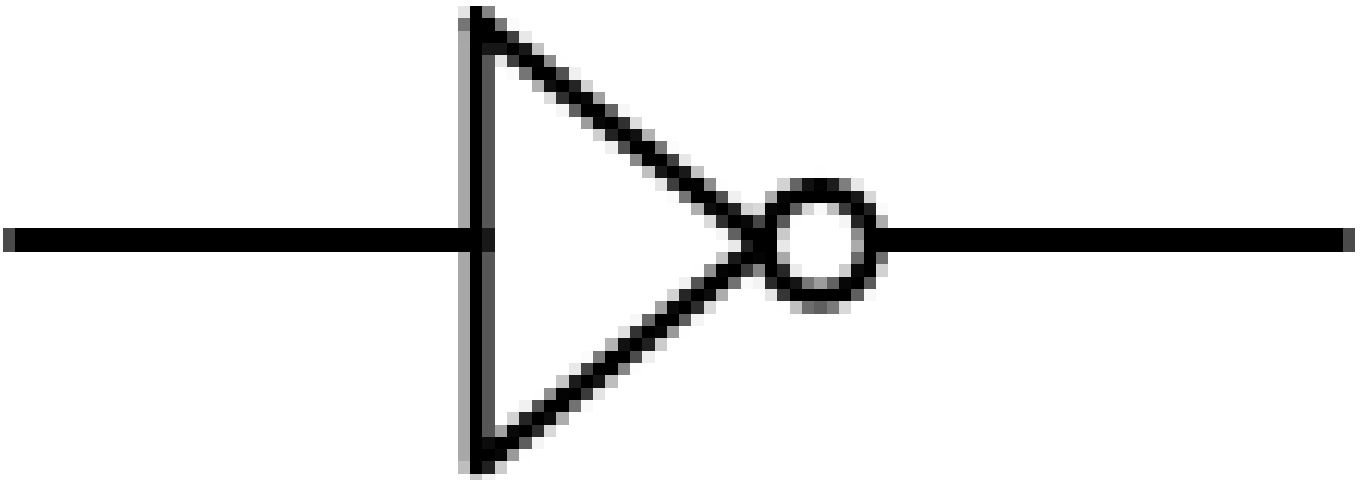Question 25:

What is the output of the NOT gate with input 1?



Options:


1. 0

2. 1

Correct Answer: 0

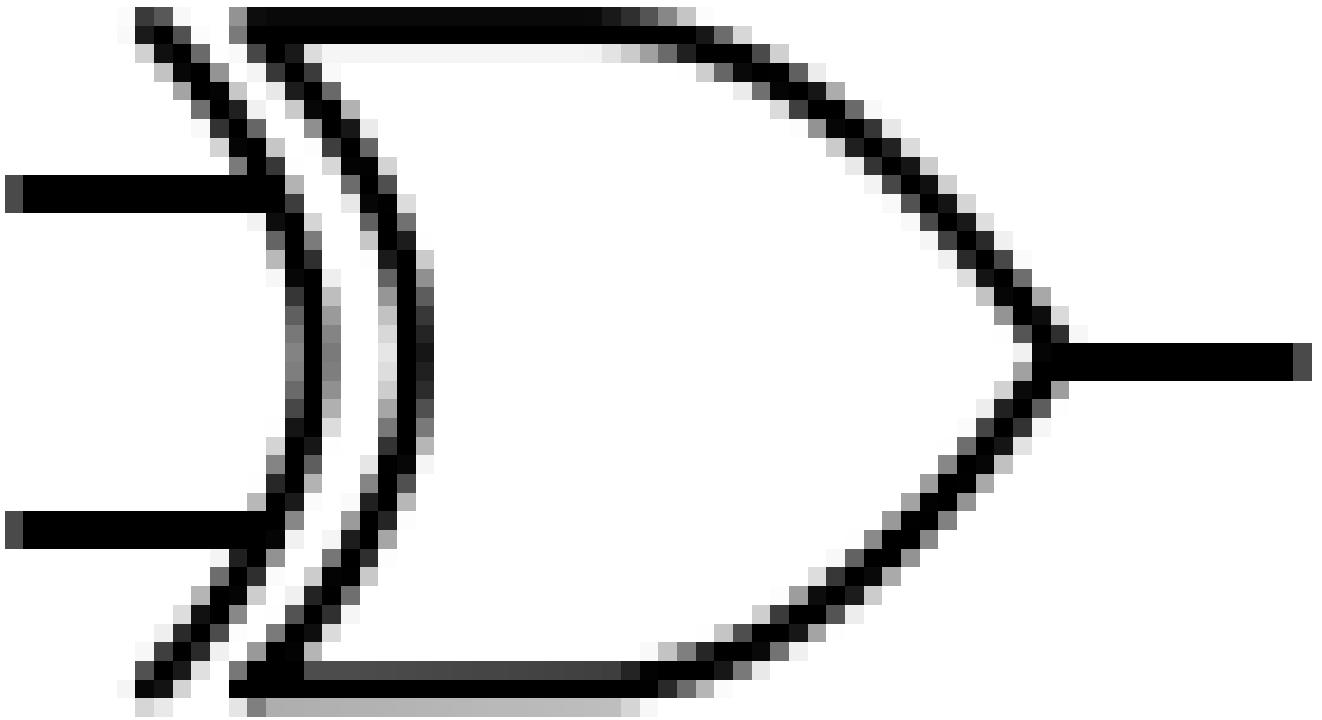Question 26:

What is the output of the XOR gate with inputs 0, 0?



Options:


1. 1

2. 0

Correct Answer: 0

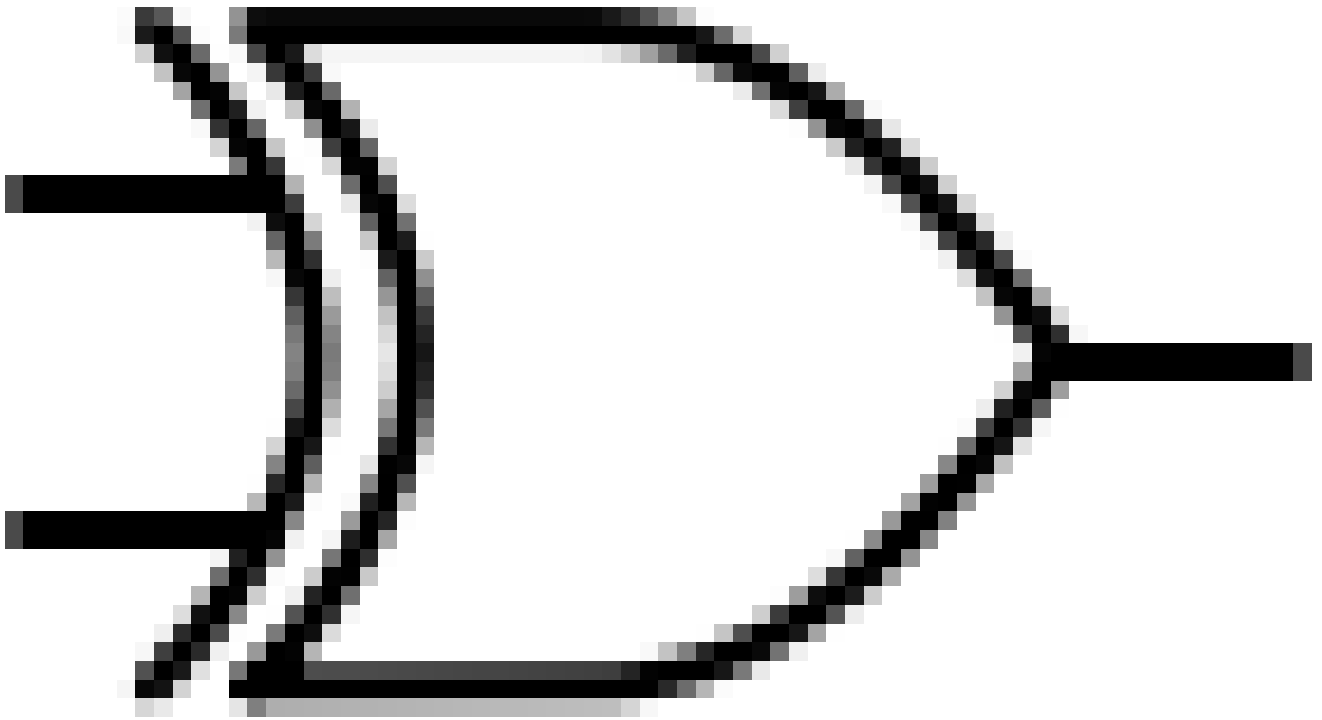Question 27:

What is the output of the XOR gate with inputs 0, 0?



Options:


1. 1

2. 0

Correct Answer: 0

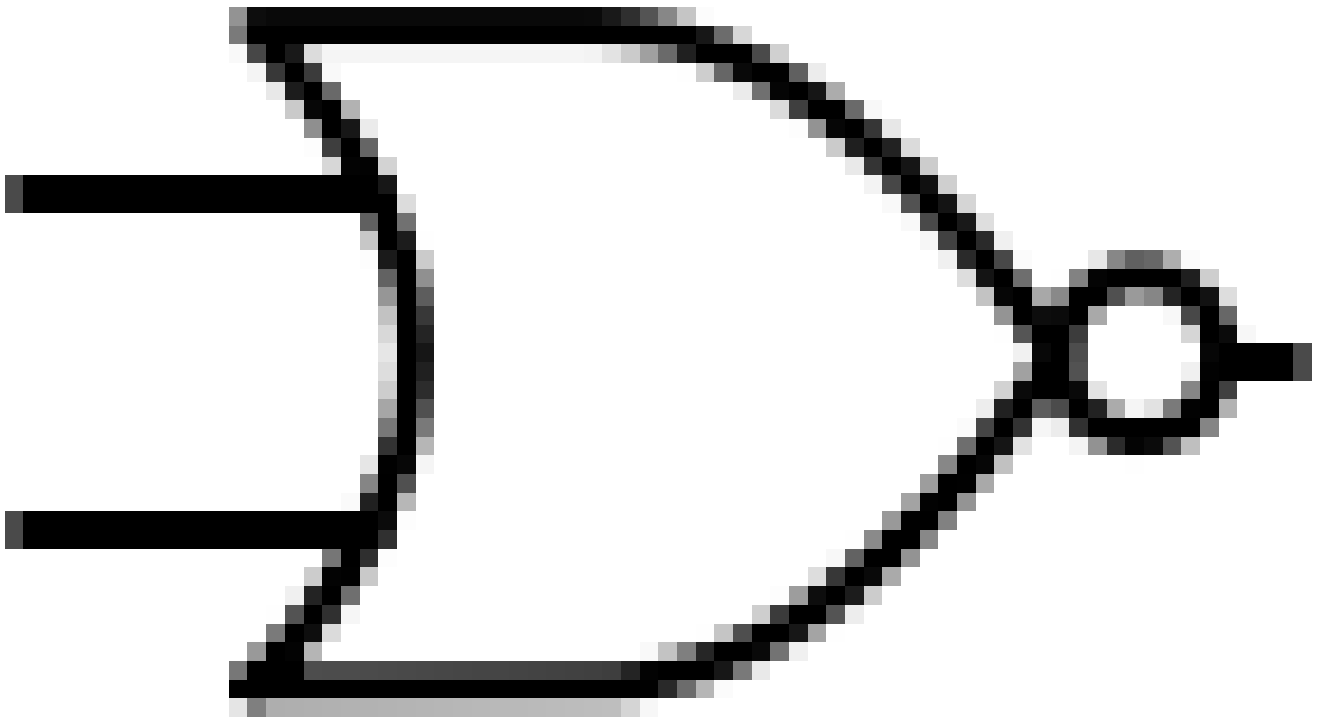Question 28:

What is the output of the NOR gate with inputs 0, 0?



Options:

1. 0

2. 1



Correct Answer: 1

Question 29:

Are these two circuits equivalent?

Expression 1: $((\text{not } a) \text{ and } (c \text{ nor } b))$

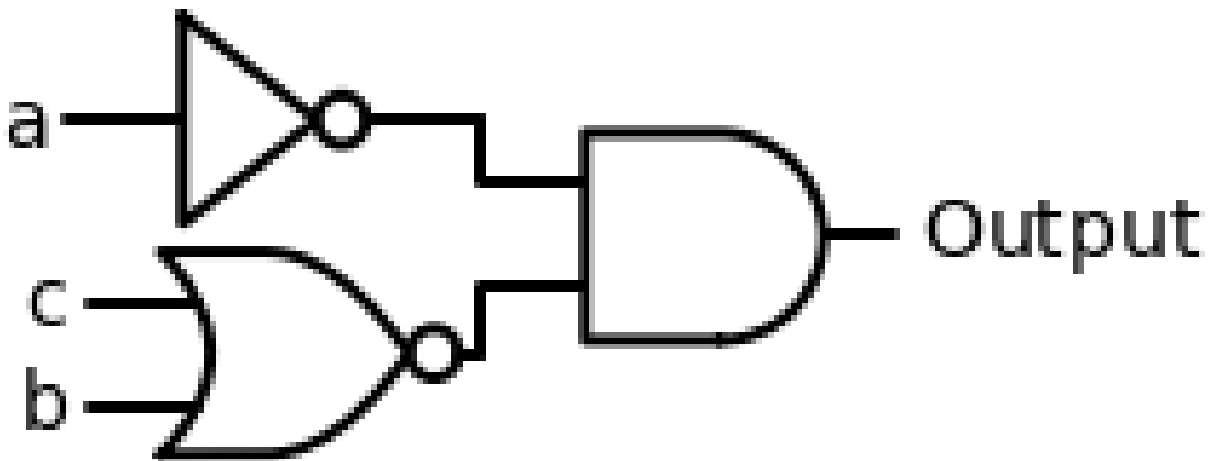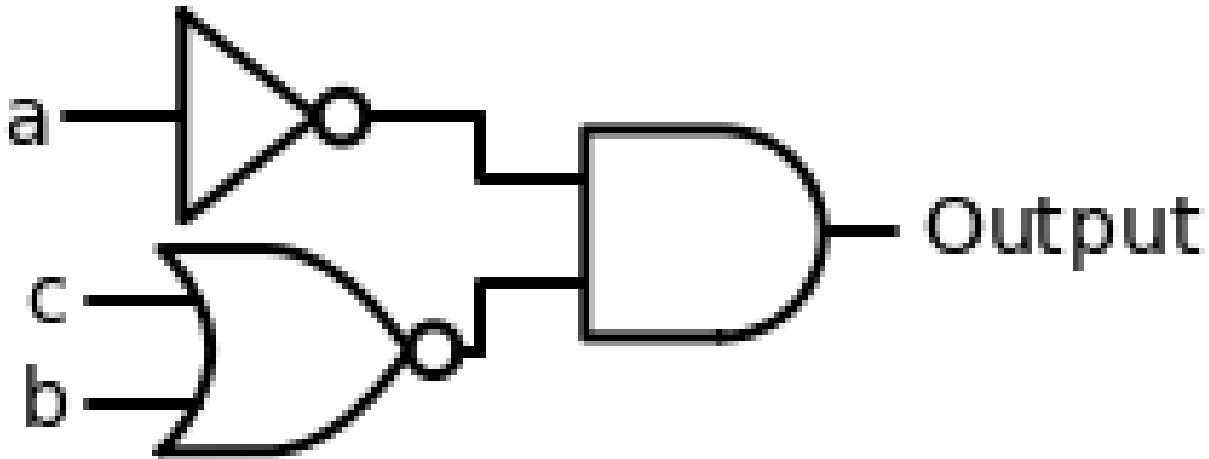Expression 2: $((\text{not } a) \text{ and } (c \text{ nor } b))$



Options:

1. Yes
2. No



Correct Answer: yes

Question 30:

Are these two circuits equivalent?

Expression 1: $((a \text{ xor } c) \text{ nor } (b \text{ and } a))$

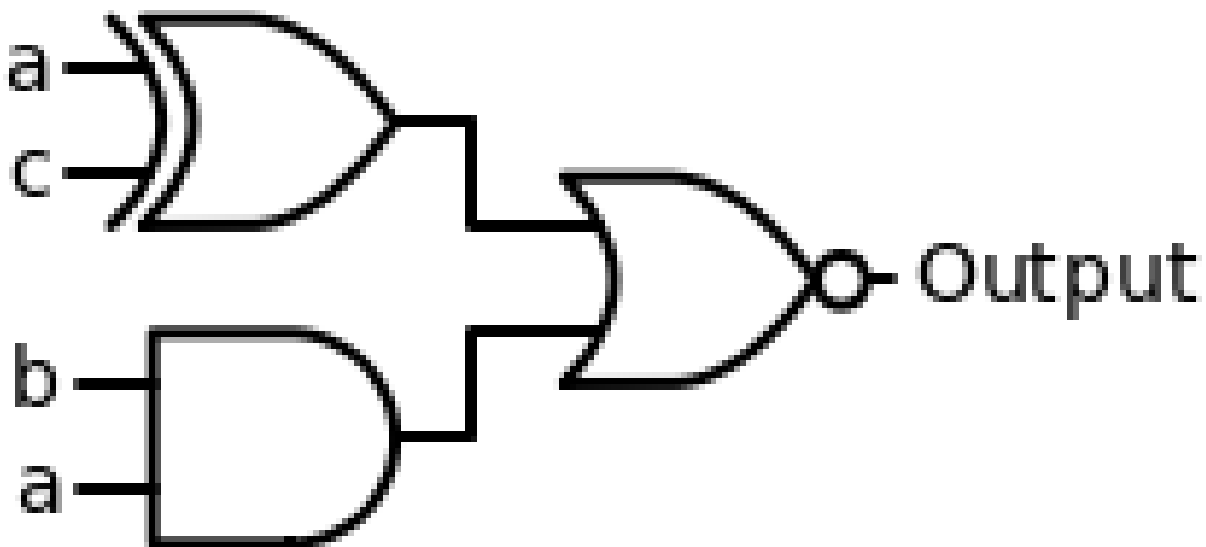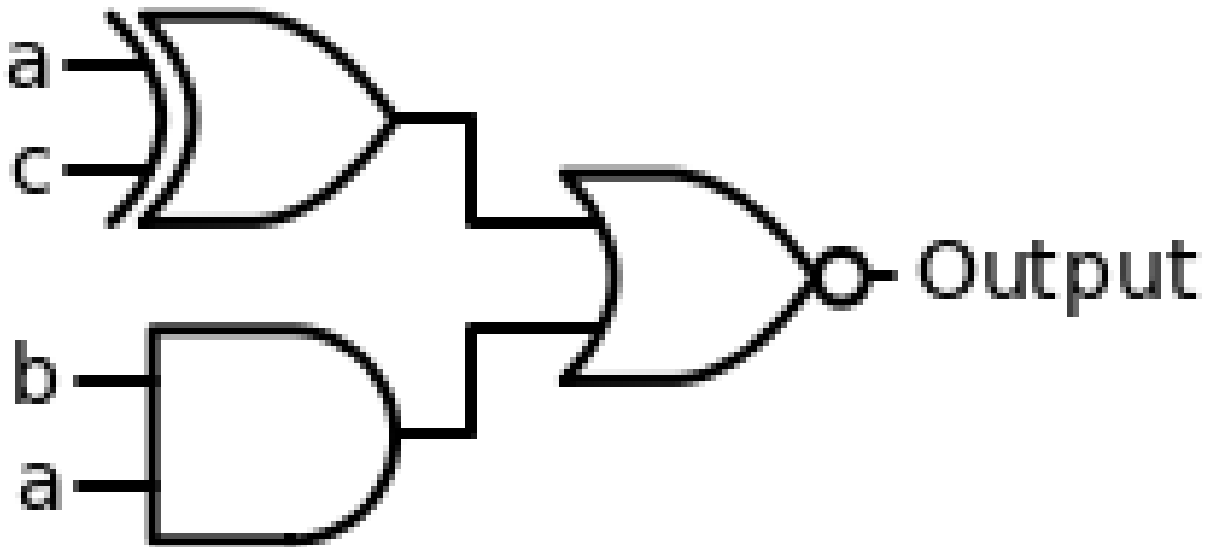Expression 2: $((a \text{ xor } c) \text{ nor } (b \text{ and } a))$




Options:

1. Yes
2. No

Correct Answer: yes

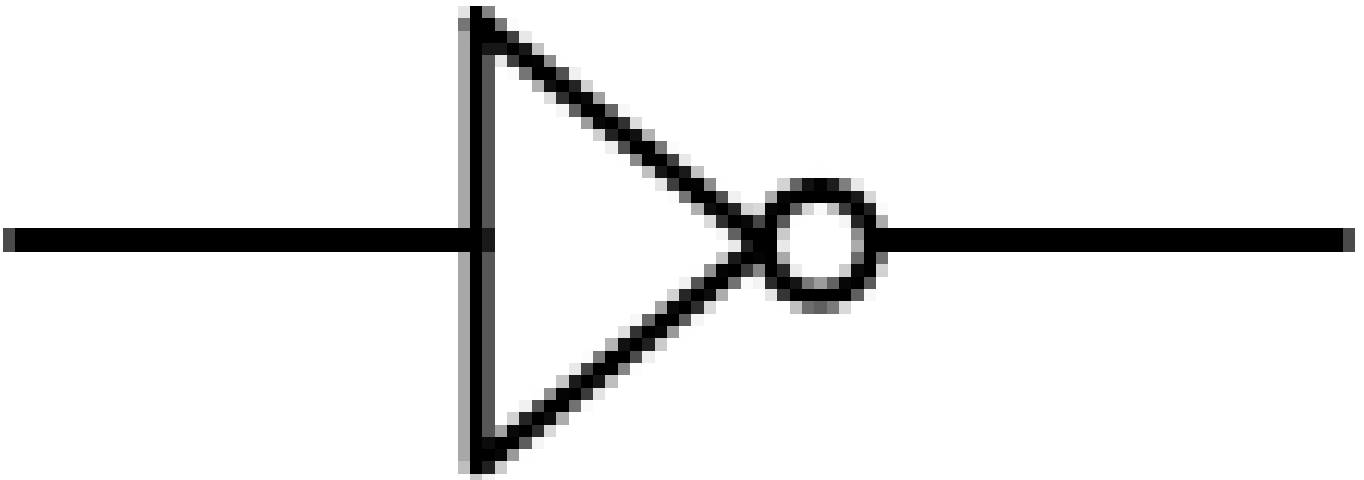Question 31:

What is the output of the NOT gate with input 0?



Options:

1. 1

2. 0



Correct Answer: 1

Question 32:

Are these two circuits equivalent?

Expression 1: $(\text{not } ((b \text{ nor } a) \text{ or } (a \text{ and } a)))$

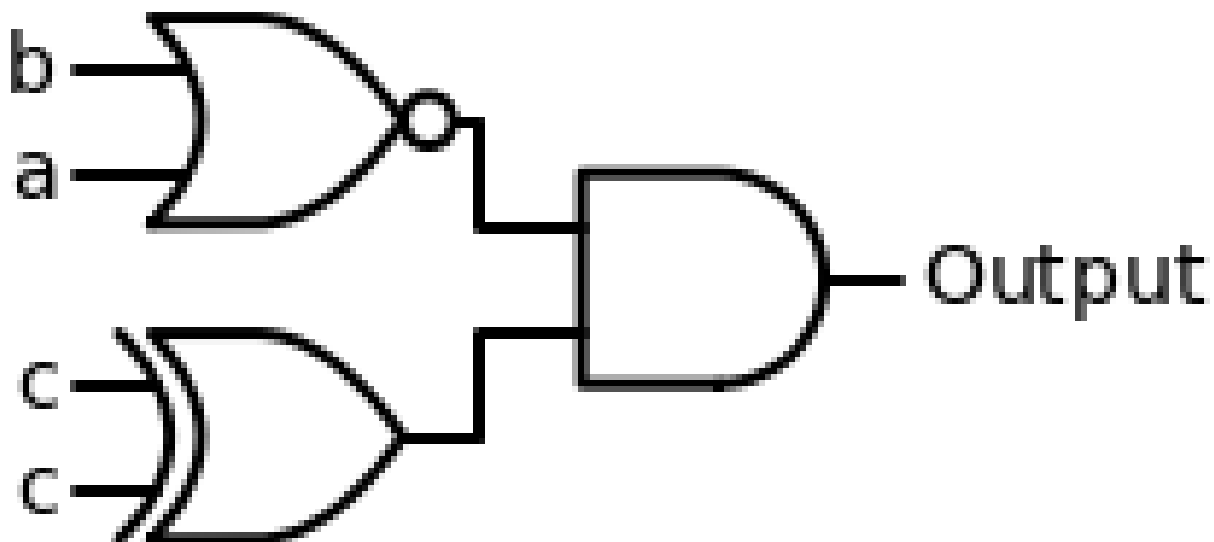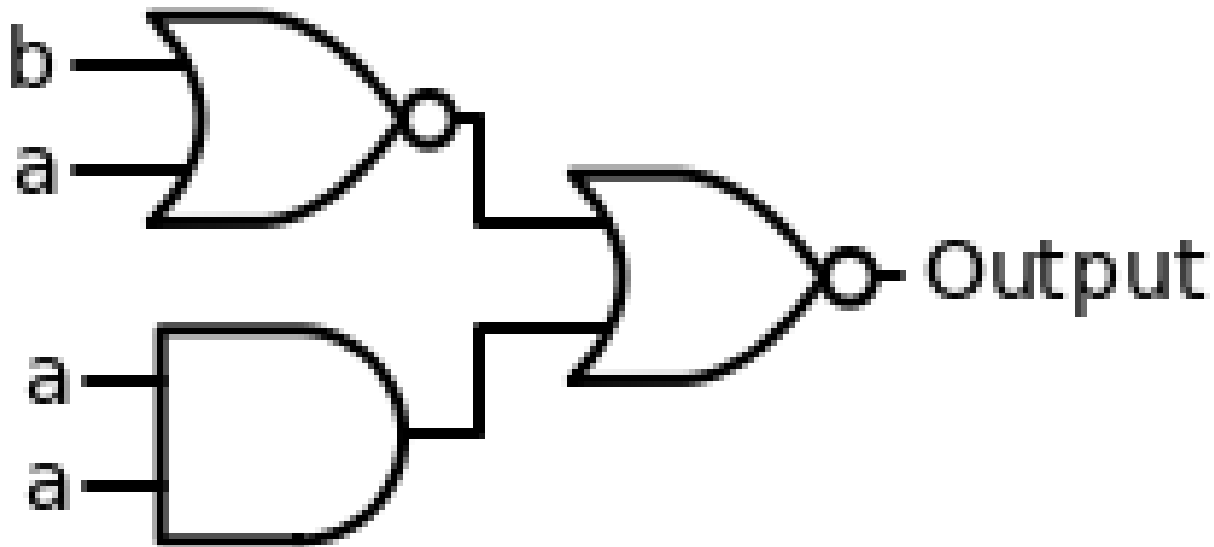Expression 2: $((b \text{ nor } a) \text{ and } (c \text{ xor } c))$




Options:

1. Yes
2. No

Correct Answer: no

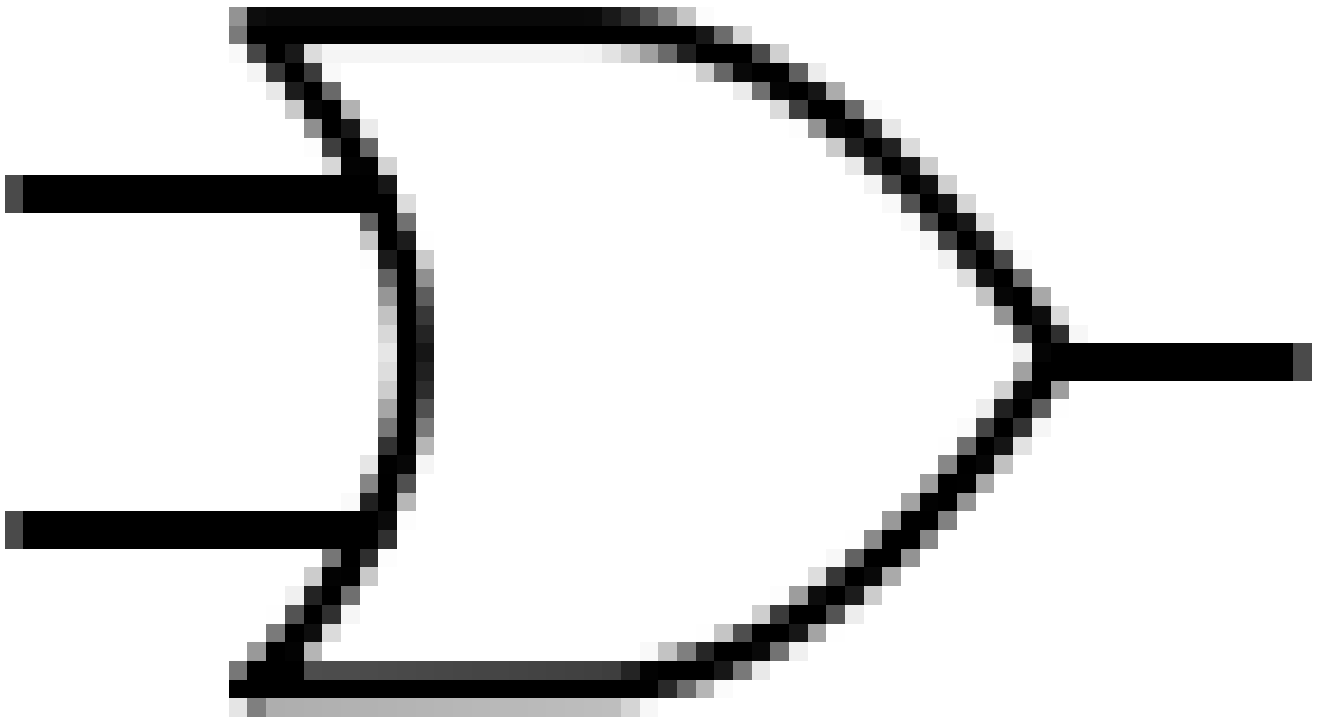Question 33:

What is the output of the OR gate with inputs 1, 1?



Options:

1. 1

2. 0



Correct Answer: 1

Question 34:

Are these two circuits equivalent?

Expression 1: (a and c)

Expression 2: (b and b)

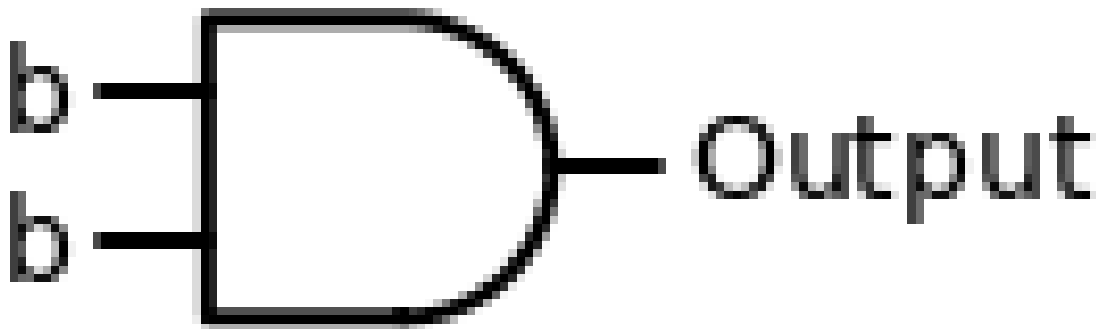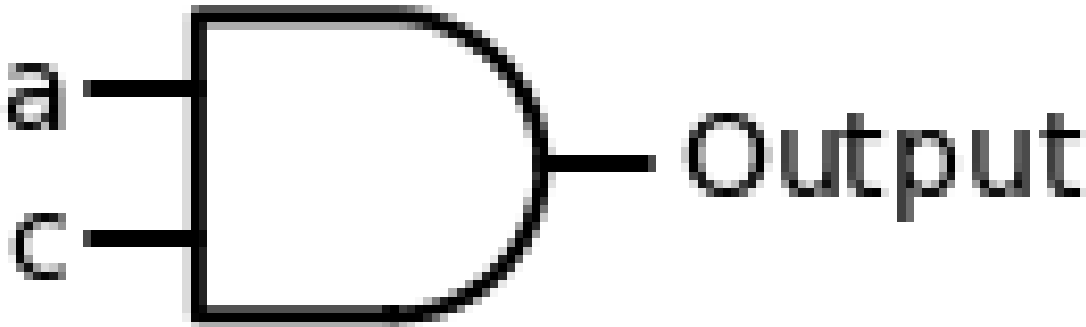

Options:

1. Yes
2. No



Correct Answer: no

Question 35:

Are these two circuits equivalent?

Expression 1: $(a \text{ xor } a)$

Expression 2: $(b \text{ or } b)$

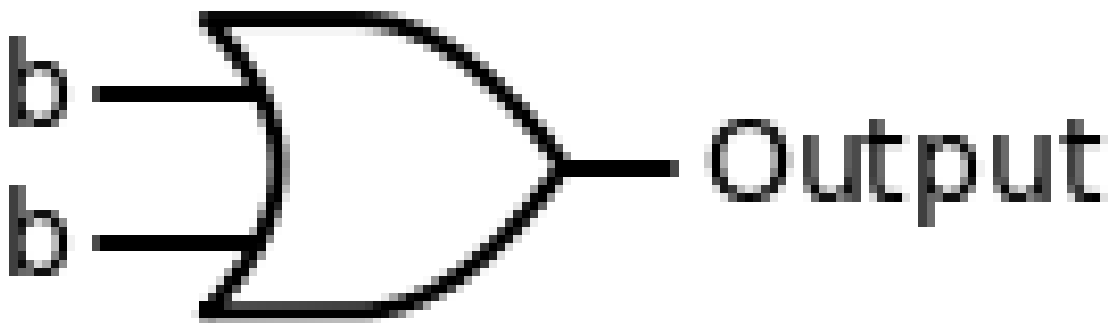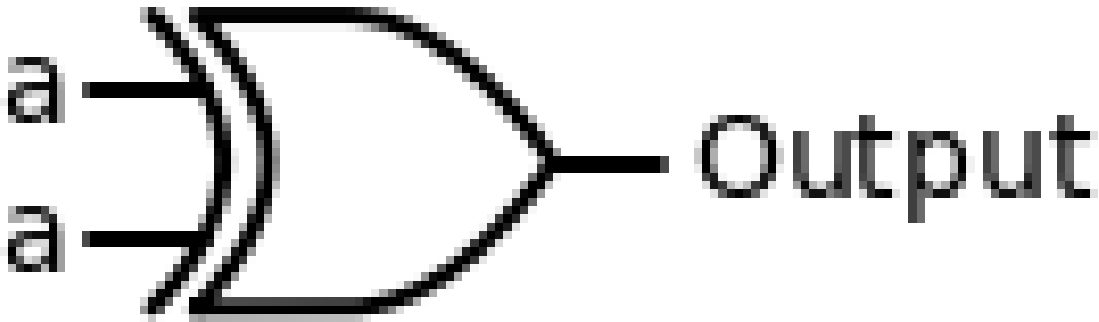

Options:

1. Yes
2. No


Correct Answer: no


Question 36:

Are these two circuits equivalent?

Expression 1: $((b \text{ nor } a) \text{ or } (b \text{ nor } a)) \text{ and } ((a \text{ nor } a) \text{ or } (b \text{ xnor } a))$

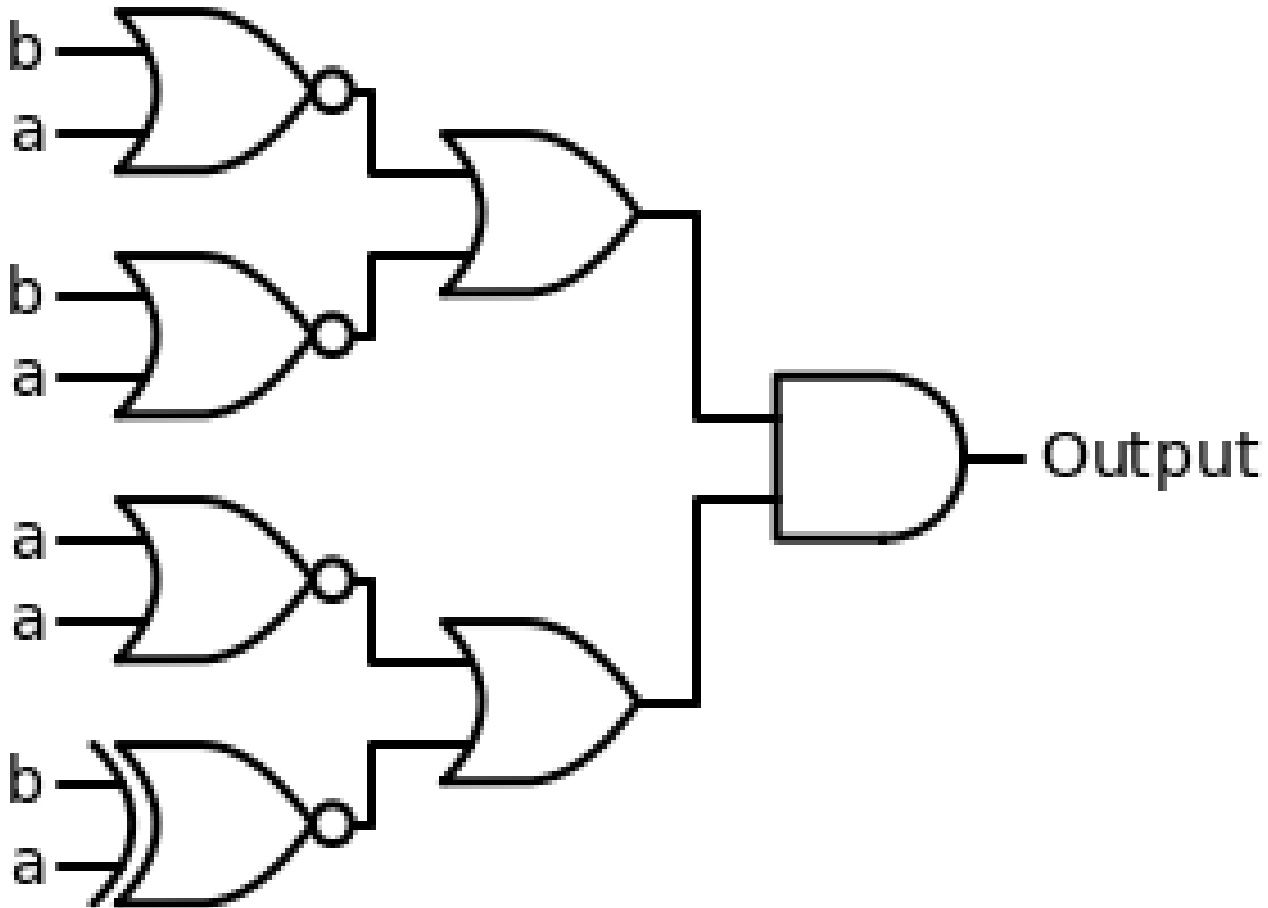Expression 2: $((b \text{ nor } a) \text{ or } (b \text{ nor } a)) \text{ and } ((a \text{ nor } a) \text{ or } (b \text{ xnor } a))$



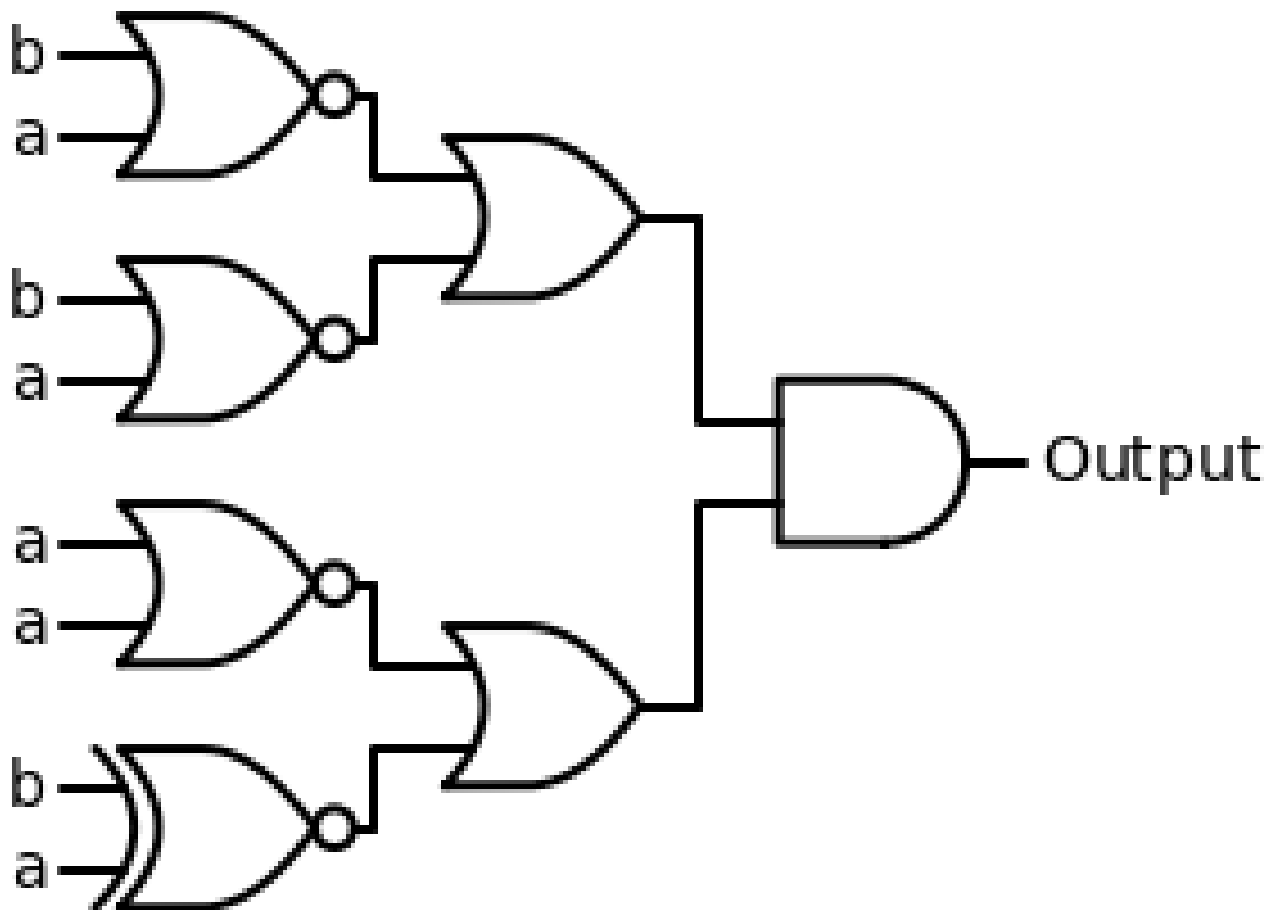

Options:

1. Yes
2. No



Correct Answer: yes

Question 37:

Are these two circuits equivalent?

Expression 1: $((\text{not } (c \text{ xnor } b)) \text{ or } (\text{not } (a \text{ nor } a)))$

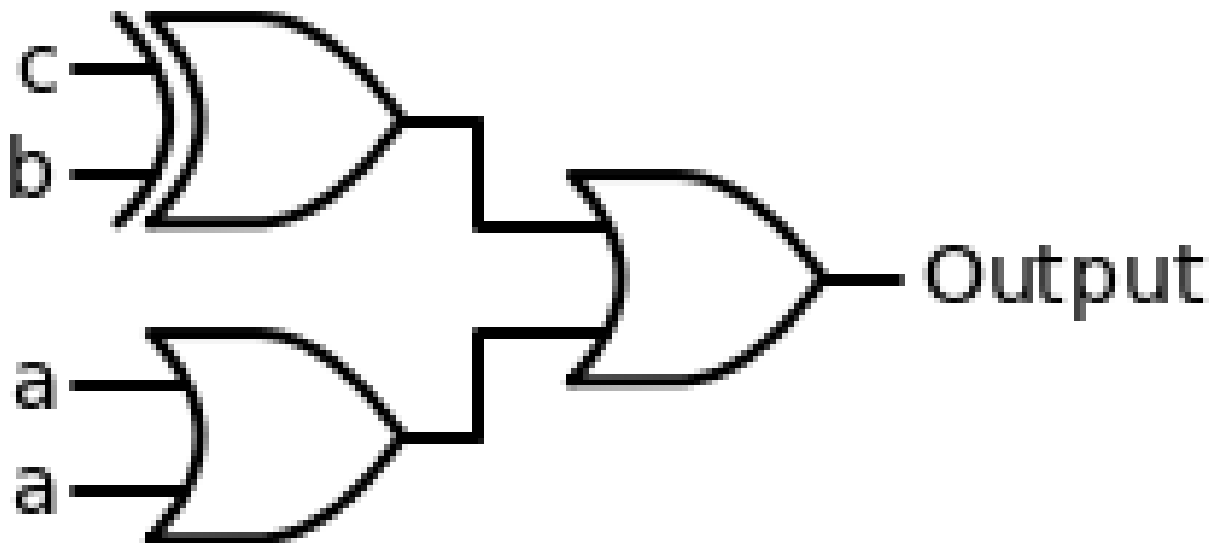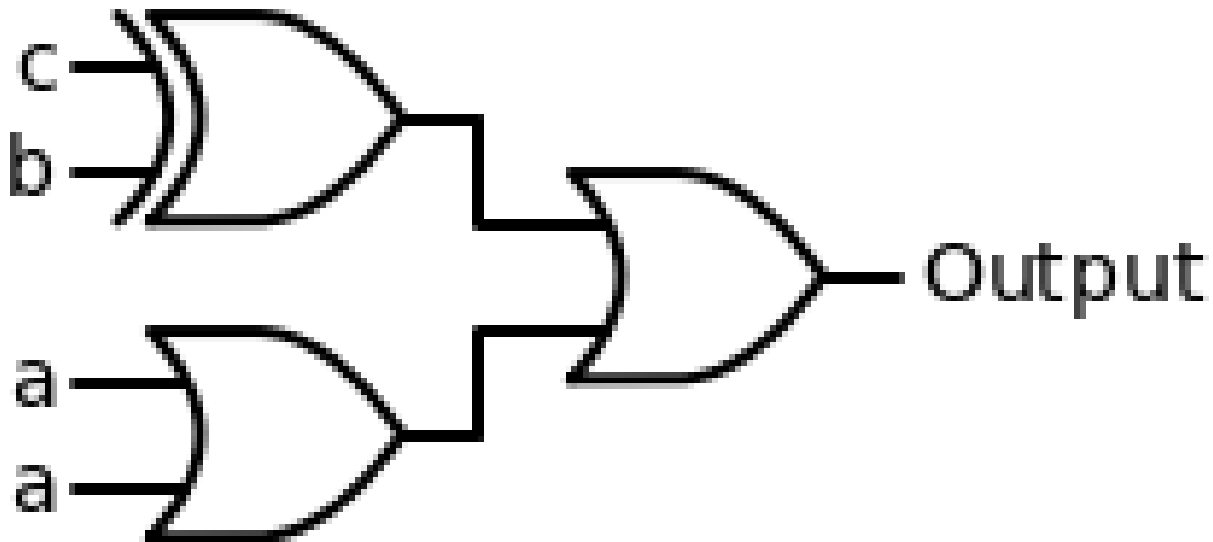Expression 2: $((\text{not } (c \text{ xnor } b)) \text{ or } (\text{not } (a \text{ nor } a)))$




Options:

1. Yes
2. No

Correct Answer: yes

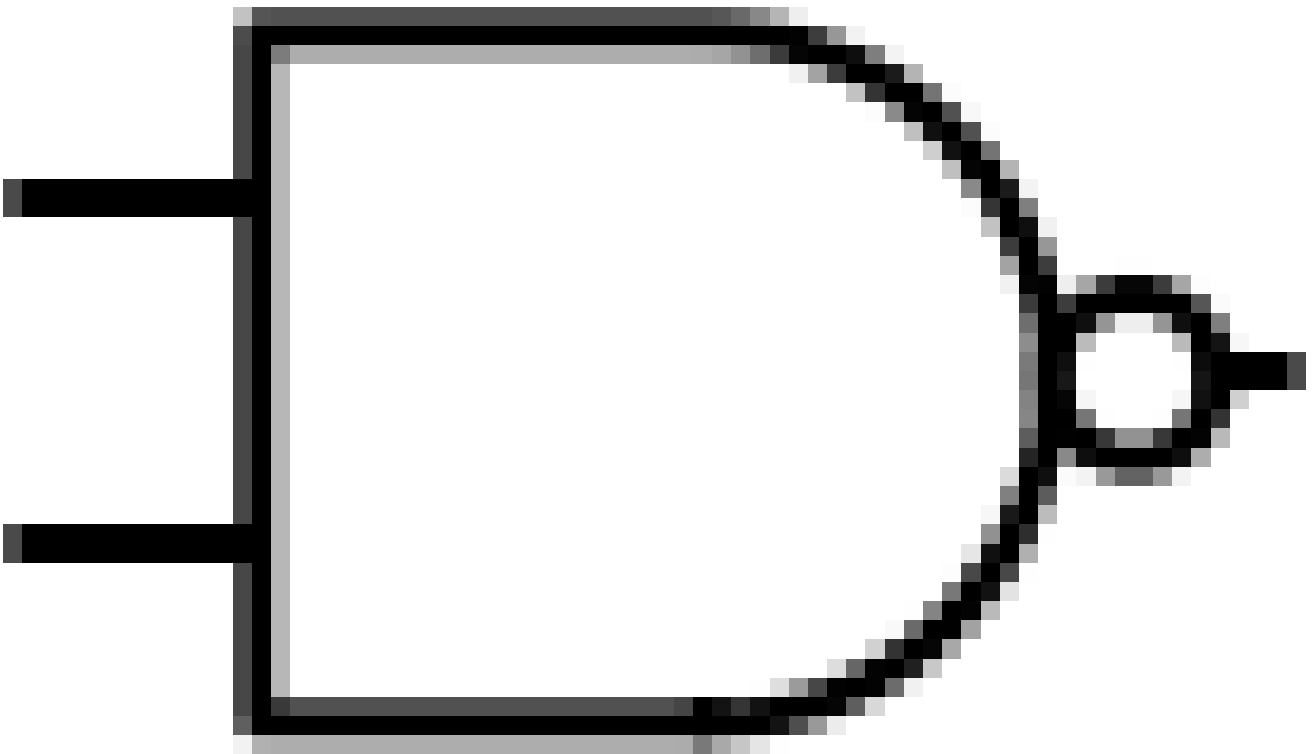Question 38:

What is the output of the NAND gate with inputs 0, 1?



Options:

1. 0

2. 1



Correct Answer: 1

Question 39:

Are these two circuits equivalent?

Expression 1: $(a \text{ xor } c)$

Expression 2: $(a \text{ xor } c)$

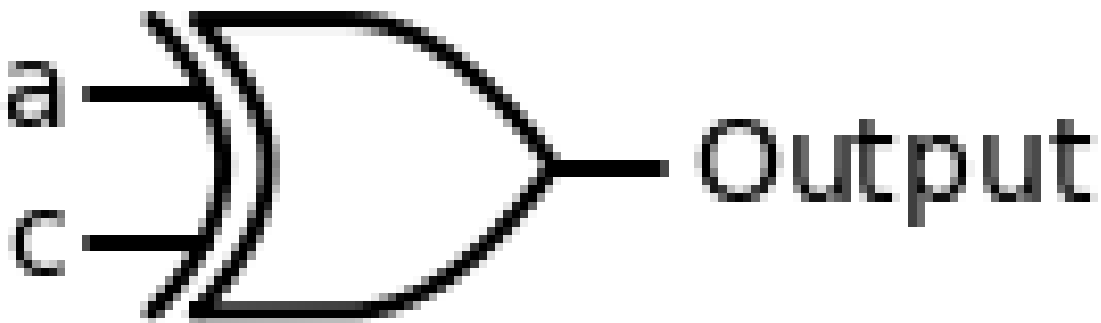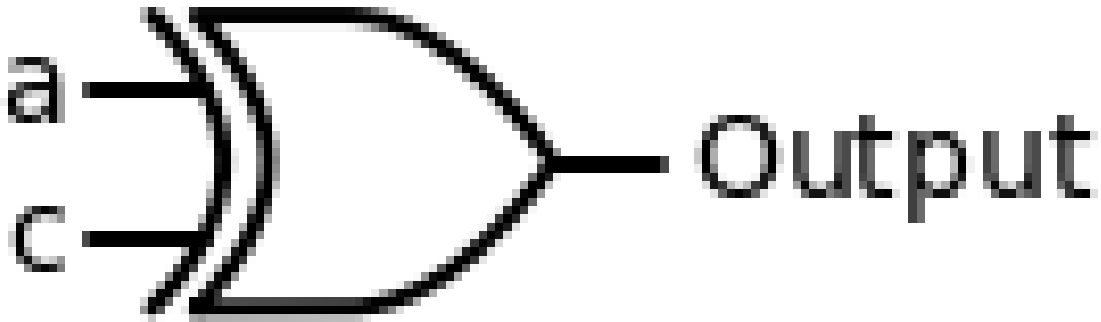


Options:

1. Yes
2. No

Correct Answer: yes

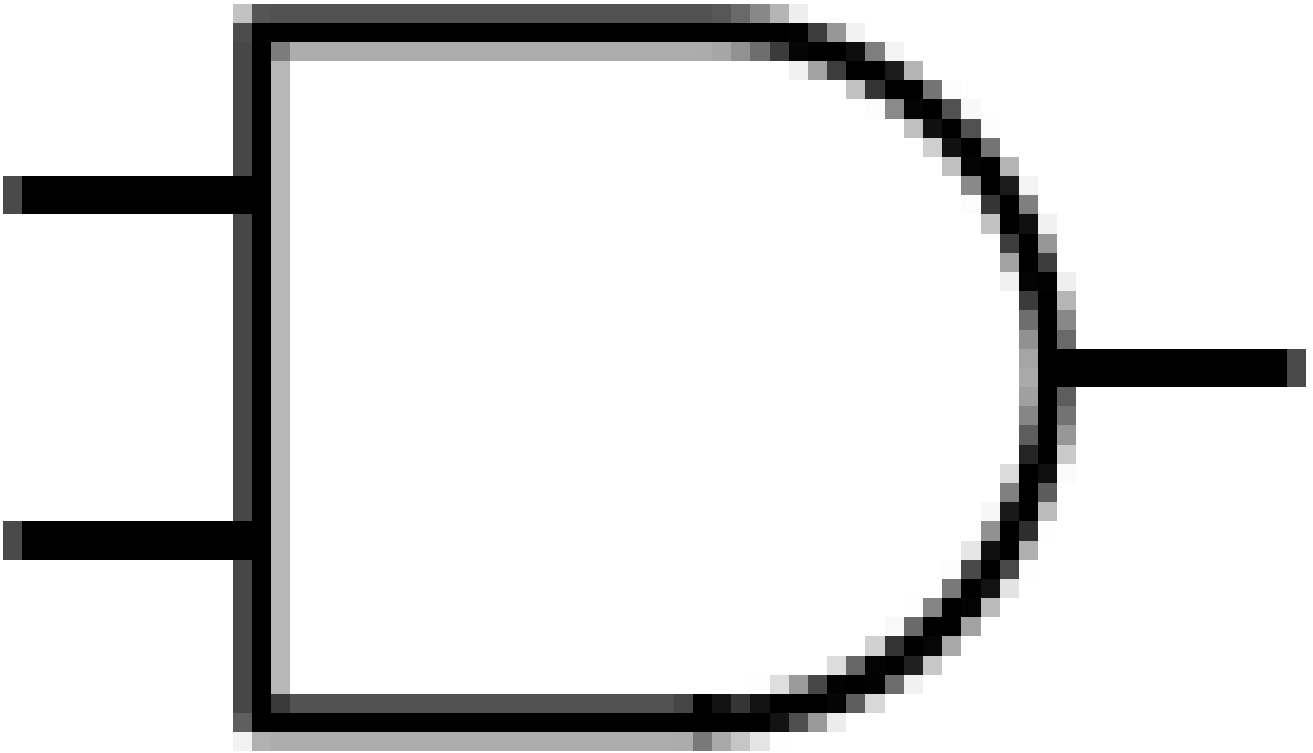Question 40:

What is the output of the AND gate with inputs 1, 0?



Options:

1. 0

2. 1



Correct Answer: 0

Question 41:

Are these two circuits equivalent?

Expression 1: $((a \text{ nor } b) \text{ nor } (\text{not } a))$

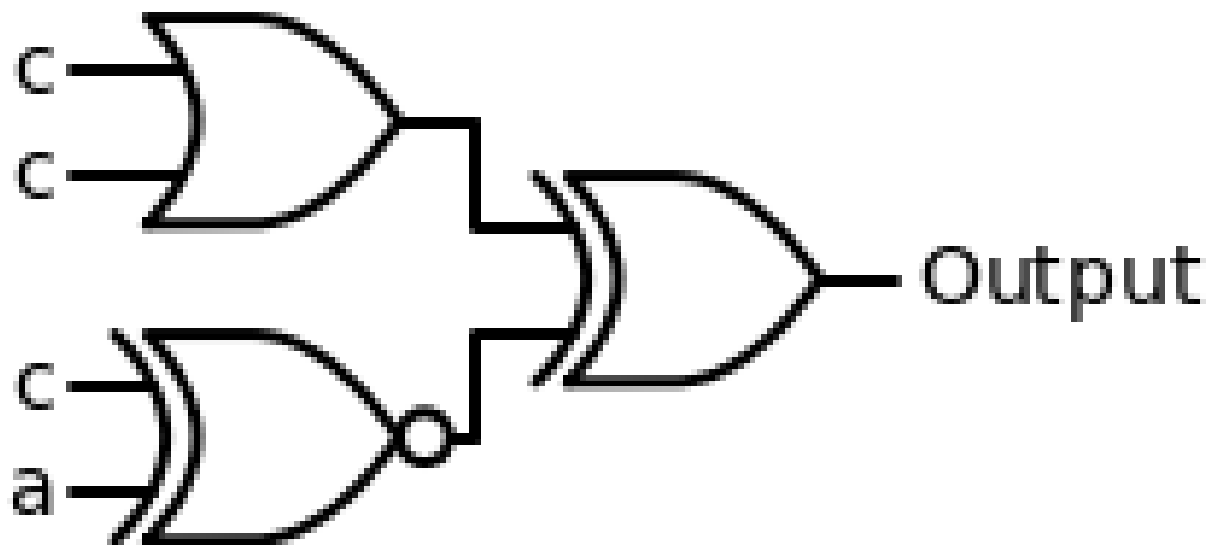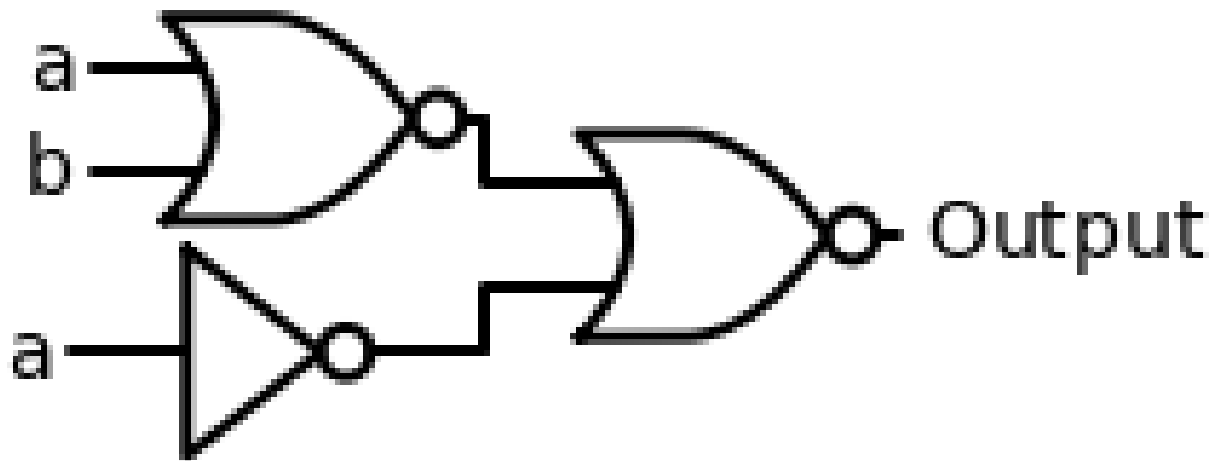Expression 2: $((c \text{ or } c) \text{ xor } (c \text{ xnor } a))$




Options:

1. Yes
2. No

Correct Answer: no

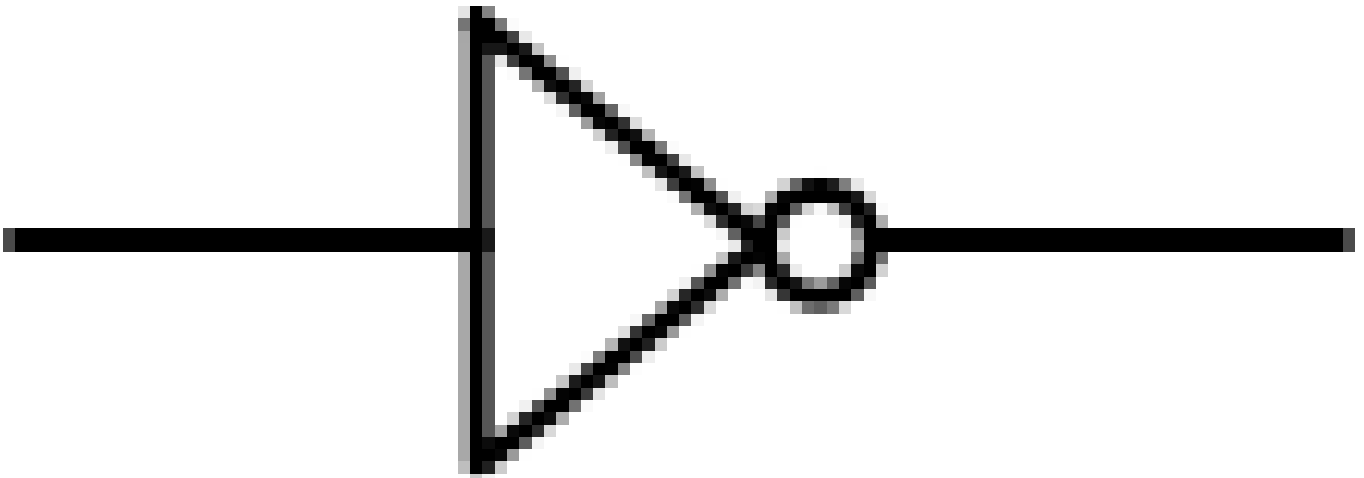Question 42:

What is the output of the NOT gate with input 1?



Options:

1. 1

2. 0



Correct Answer: 0

Question 43:

Are these two circuits equivalent?

Expression 1: $((b \text{ xnor } c) \text{ nand } (a \text{ or } c))$

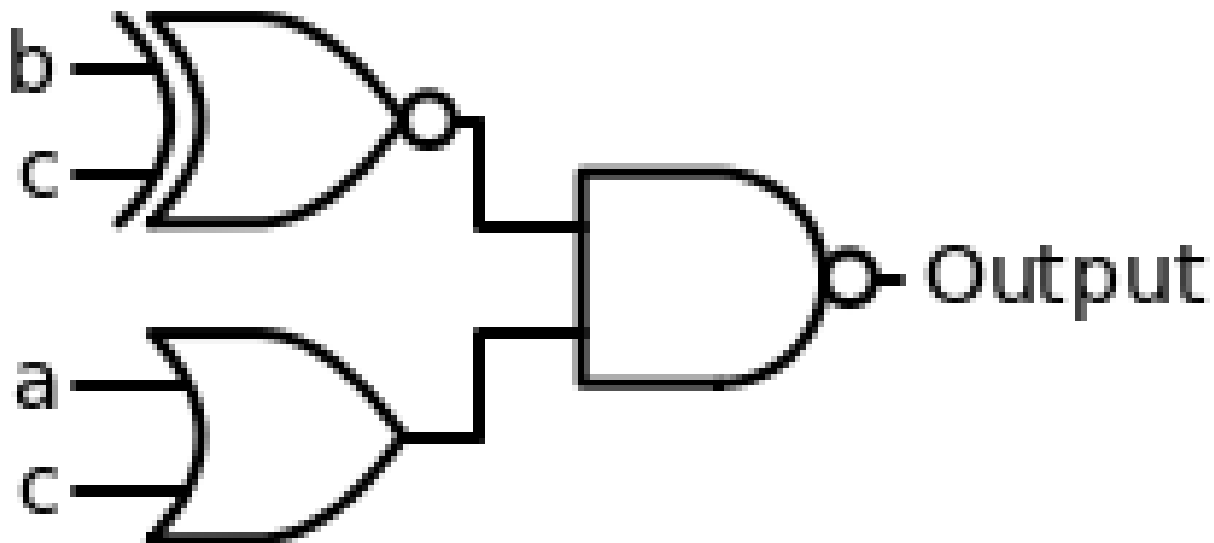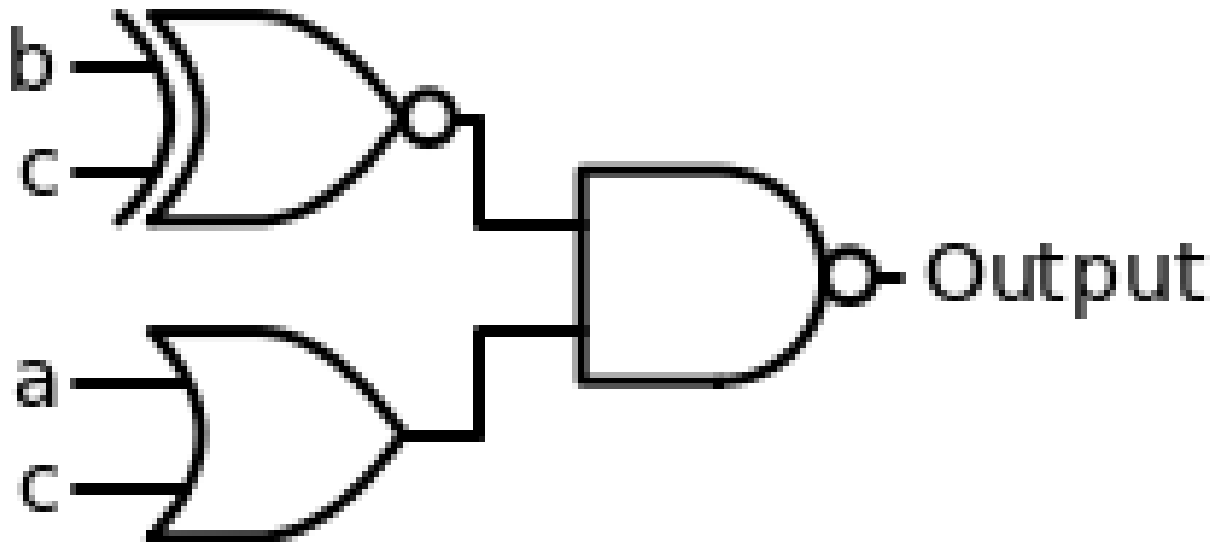Expression 2: $((b \text{ xnor } c) \text{ nand } (a \text{ or } c))$



Options:

1. Yes
2. No



Correct Answer: yes

Question 44:

Are these two circuits equivalent?

Expression 1: (not a)

Expression 2: (not b)

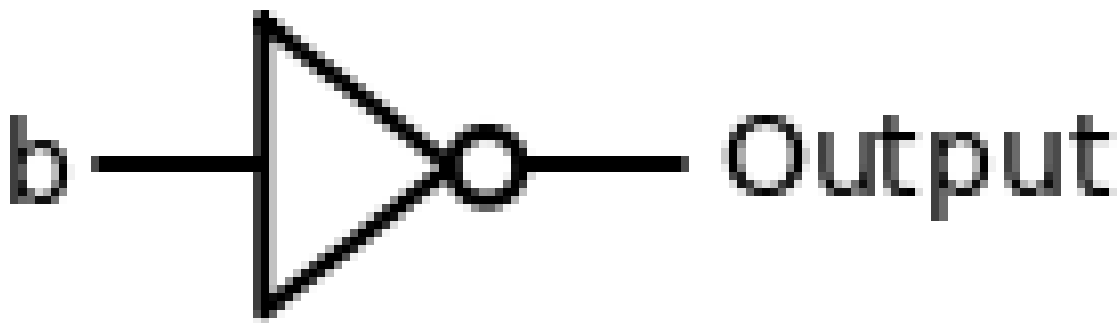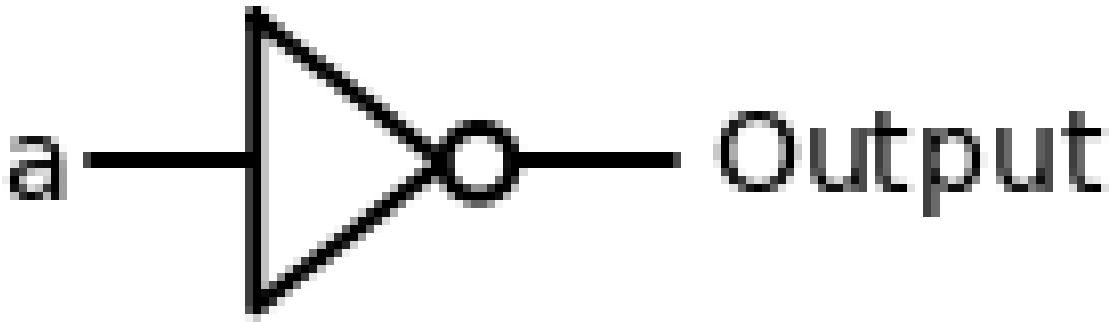


Options:

1. Yes
2. No

Correct Answer: no

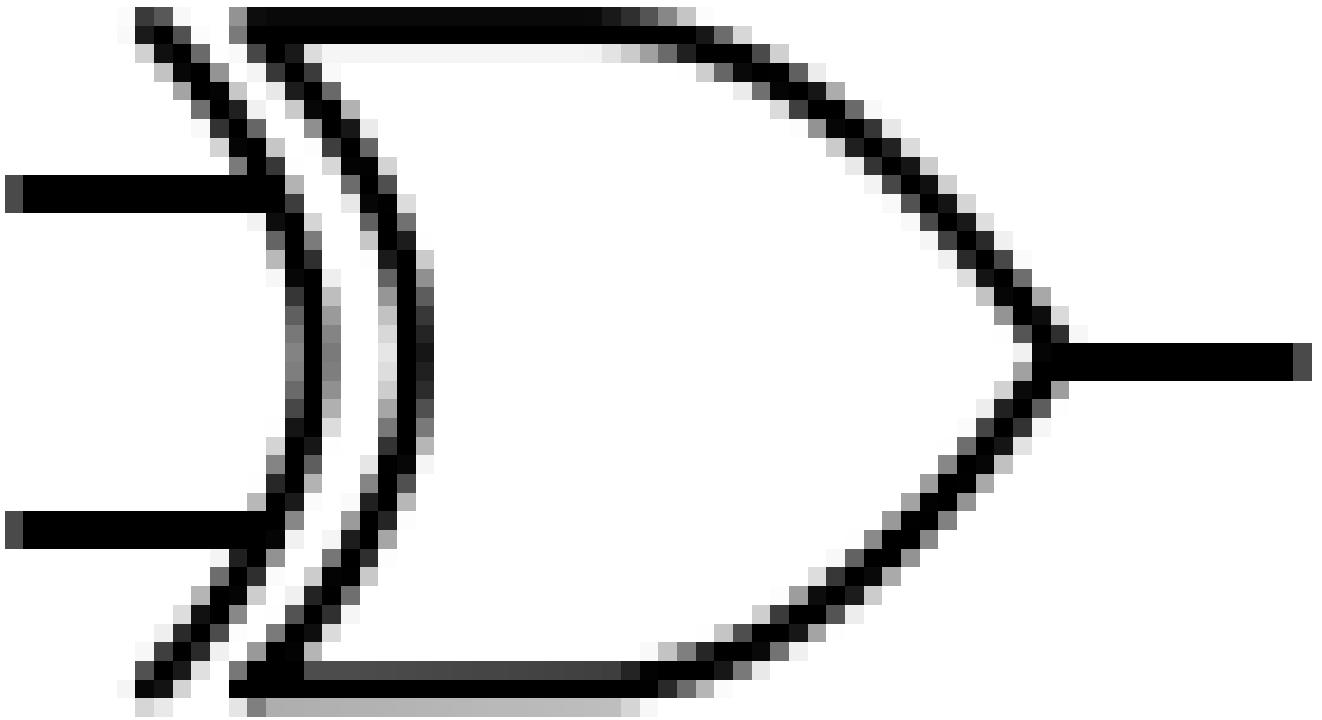Question 45:

What is the output of the XOR gate with inputs 1, 1?



Options:

1. 1

2. 0



Correct Answer: 0

Question 46:

Are these two circuits equivalent?

Expression 1: $(\text{not } ((c \text{ and } c) \text{ and } (a \text{ xor } b)))$

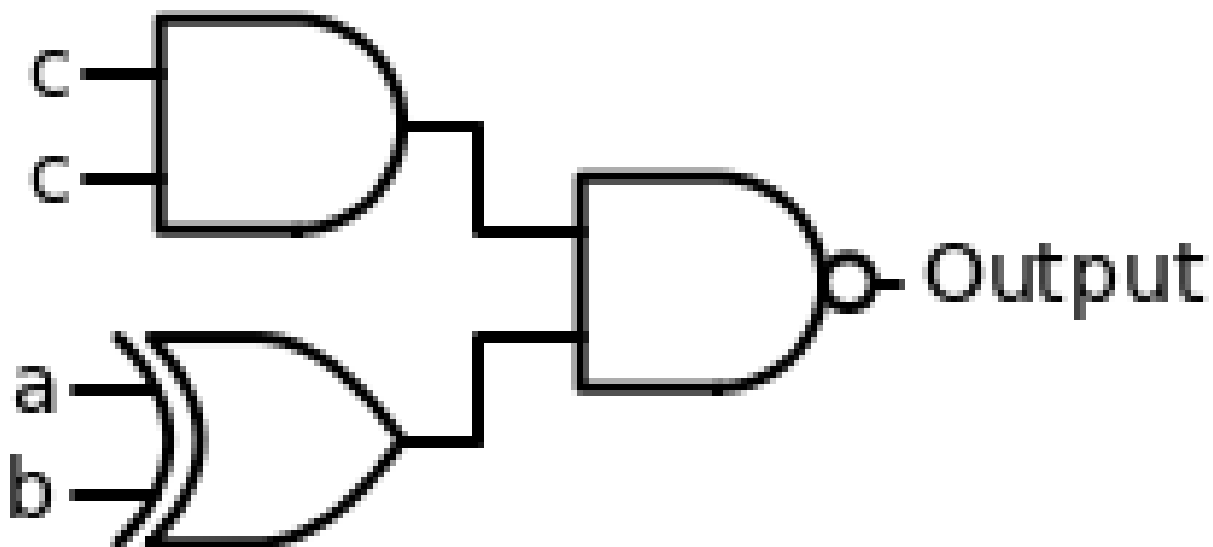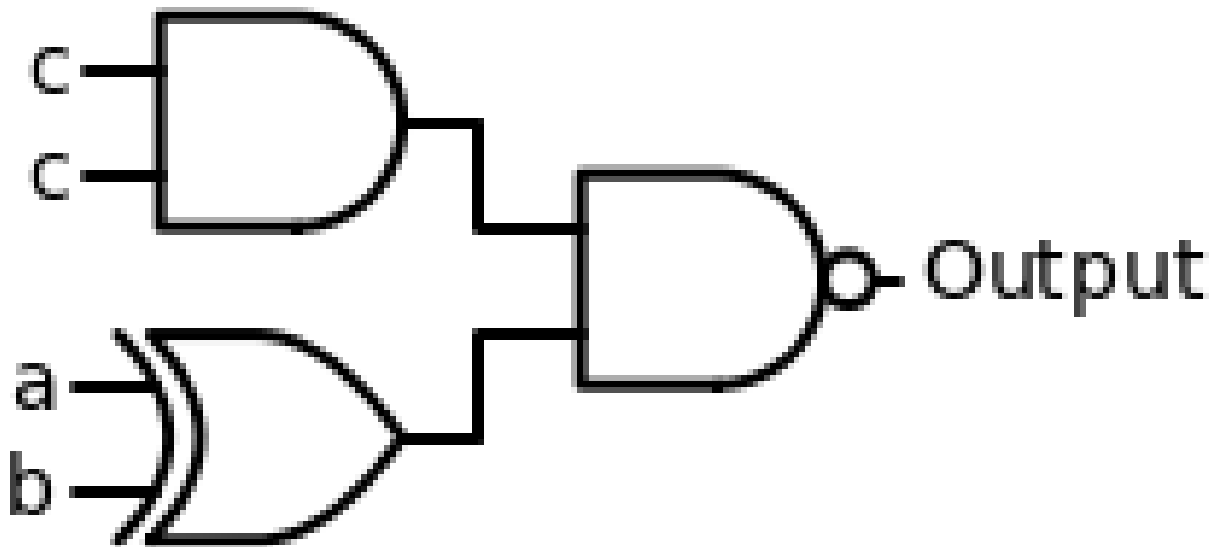Expression 2: $(\text{not } ((c \text{ and } c) \text{ and } (a \text{ xor } b)))$



Options:

1. Yes

2. No

Correct Answer: yes

Question 47:

Are these two circuits equivalent?

Expression 1: $(c \text{ nor } c)$

Expression 2: $(c \text{ nor } c)$



Options:

1. Yes

2. No


Correct Answer: yes

Question 48:

Are these two circuits equivalent?

Expression 1: $((a \text{ or } a) \text{ xor } (\text{not } b)) \text{ xor } ((a \text{ nor } a) \text{ xor } (a \text{ nor } a))$

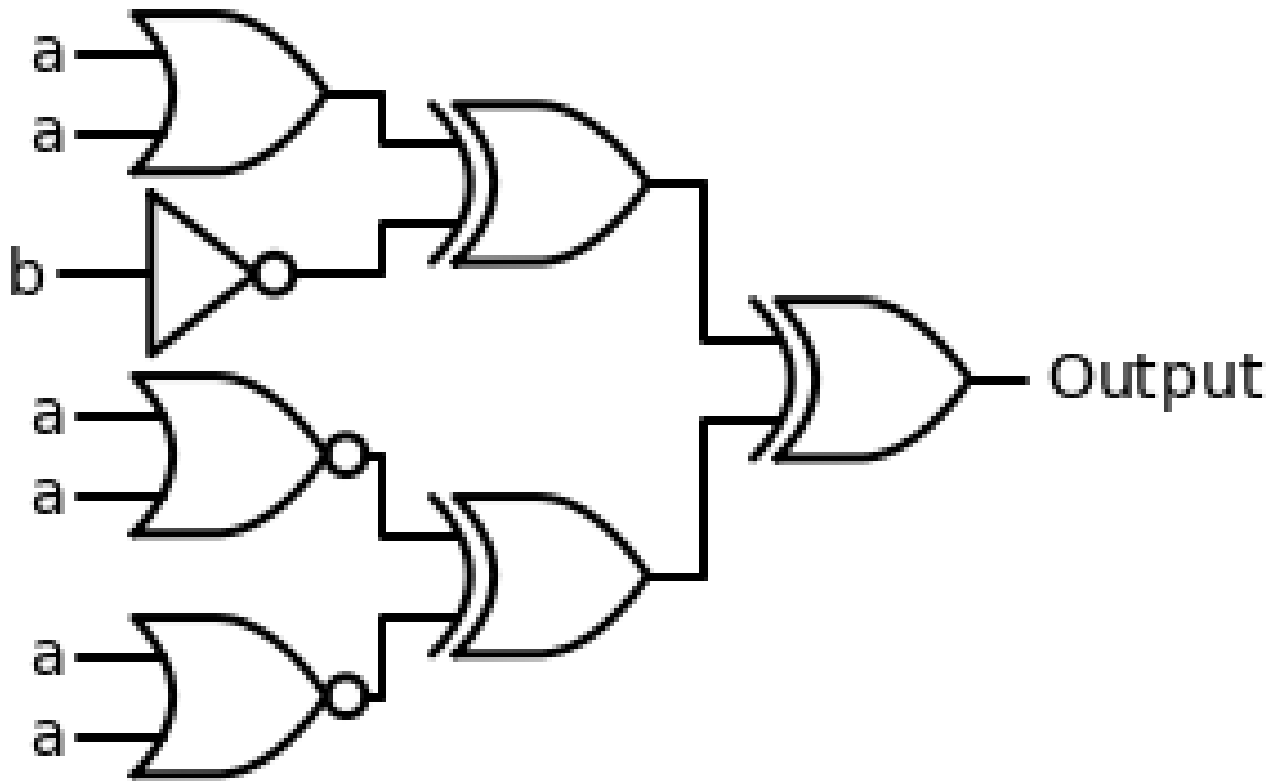Expression 2: $(\text{not } (b \text{ and } a))$



Options:

1. Yes
2. No



Correct Answer: no

Question 49:

Are these two circuits equivalent?

Expression 1: (a and a)

Expression 2: (a and a)

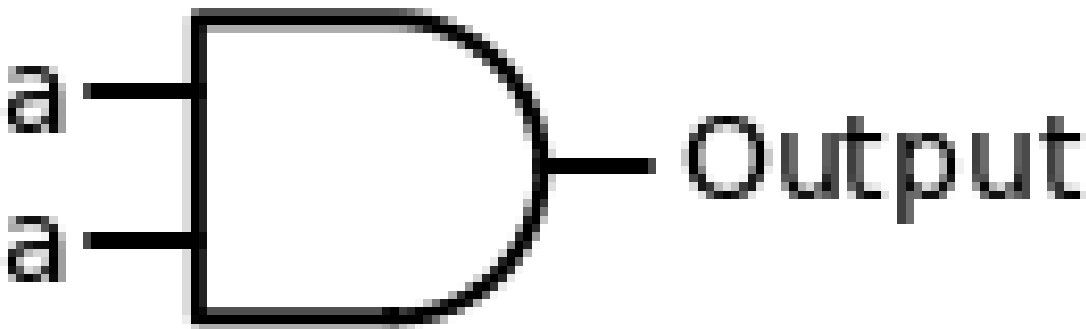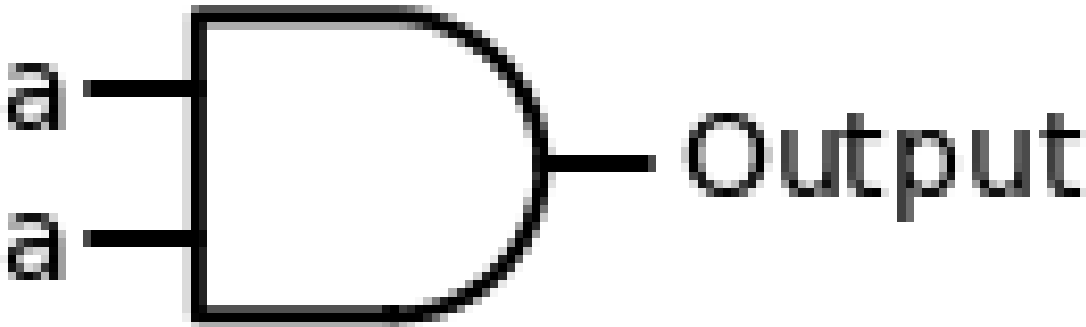

Options:

1. Yes
2. No

Correct Answer: yes