


Question 1:

What is the output of the NAND gate with inputs 1, 0?

Options:

1. 0

2. 1

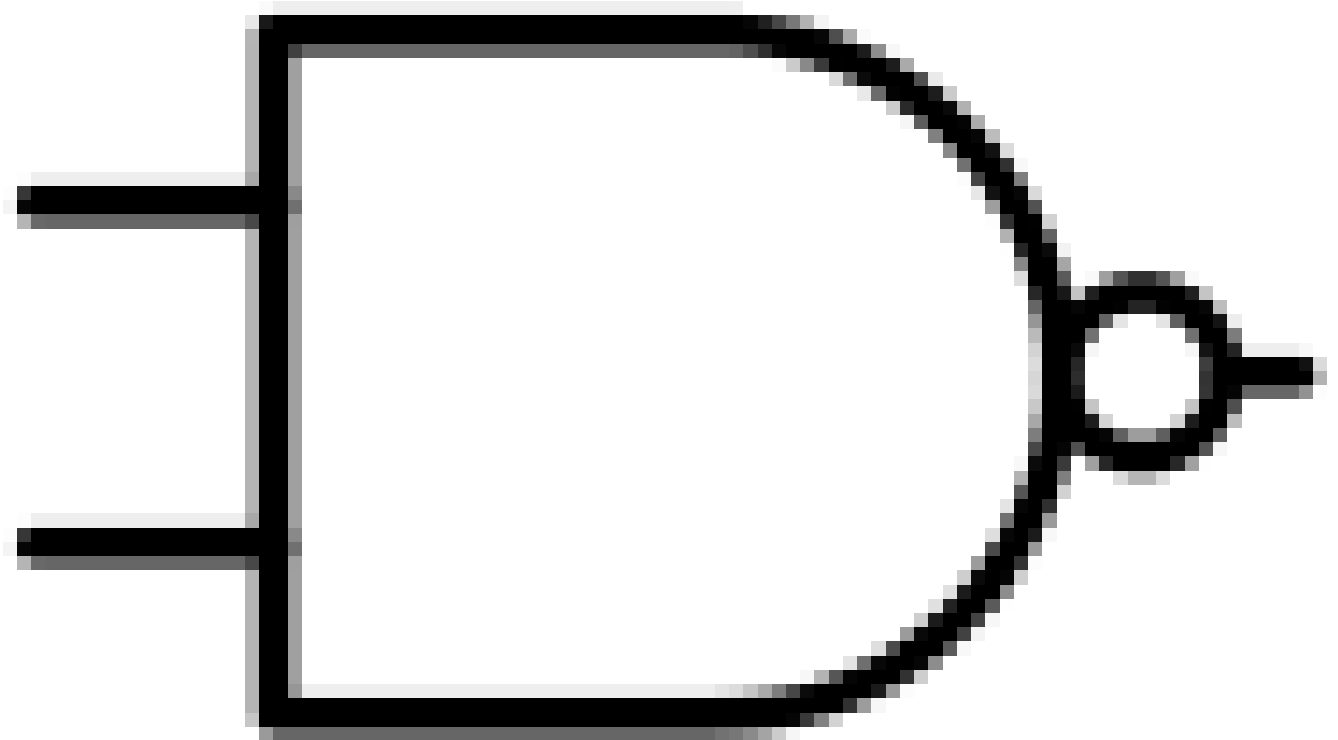

Correct Answer: 1


Question 2:

What is the output of the NOT gate with input 1?

Options:

1. 0

2. 1

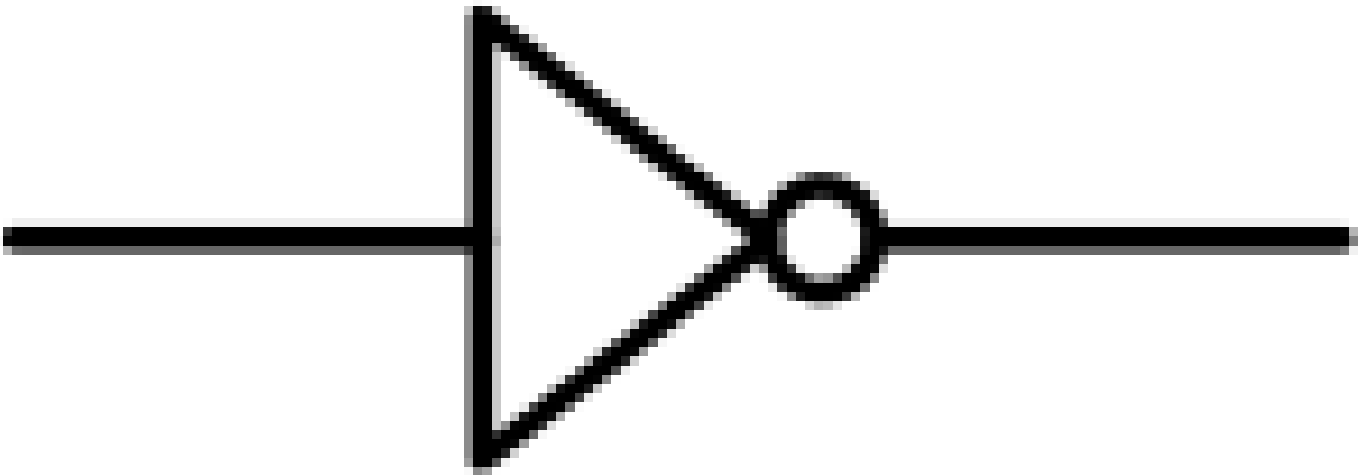

Correct Answer: 0

Question 3:



Are these two circuits equivalent?

Expression 1: $(\text{not } (a \text{ xnor } b))$

Expression 2: $(\text{not } (\text{not } c))$

Options:

1. Yes
2. No

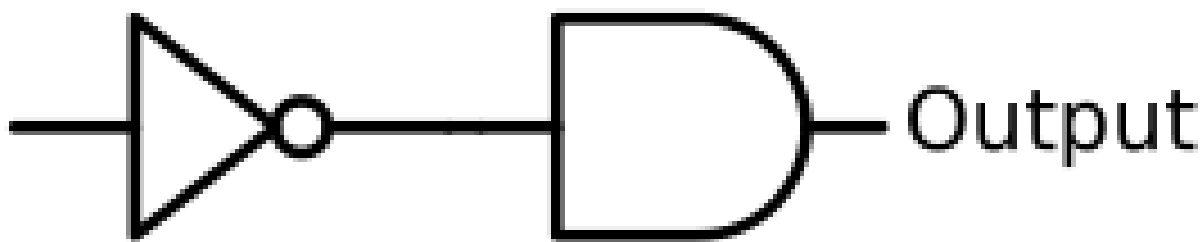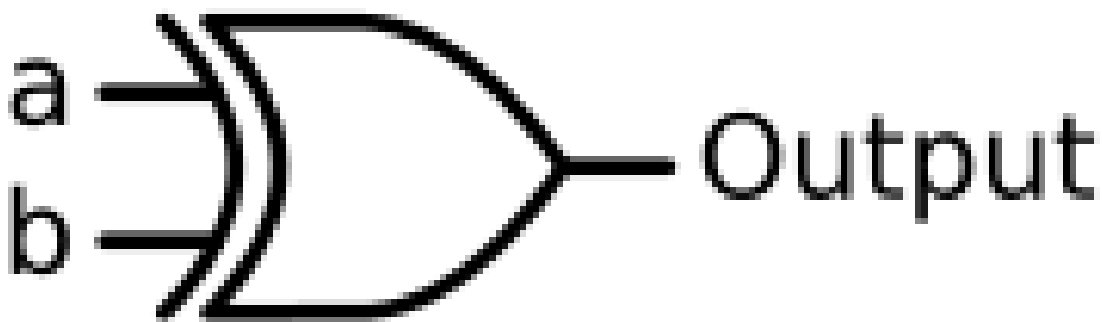

Correct Answer: no

Question 4:

Are these two circuits equivalent?



Expression 1: (not a)

Expression 2: (not a)

Options:

1. Yes

2. No

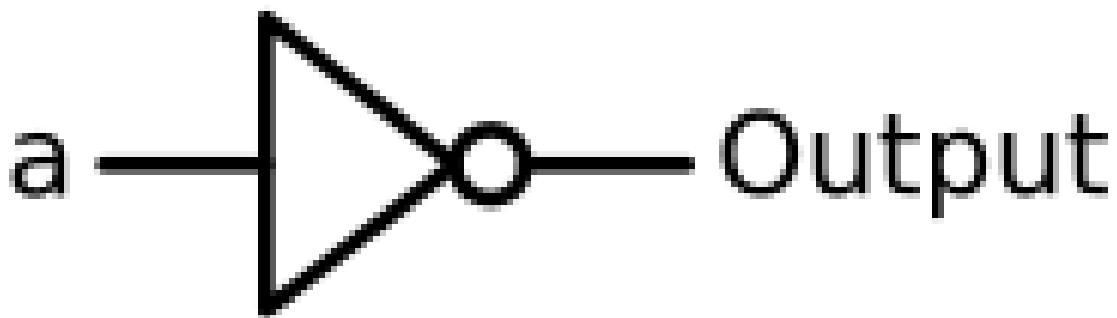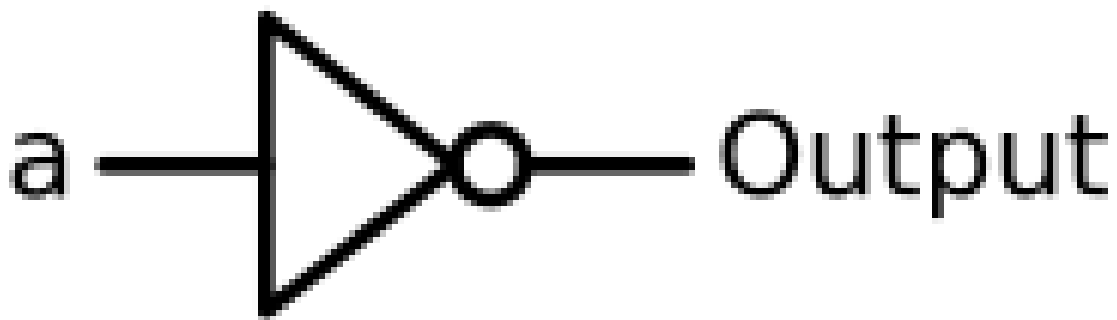

Correct Answer: yes


Question 5:

What is the output of the AND gate with inputs 1, 1?

Options:

1. 1

2. 0

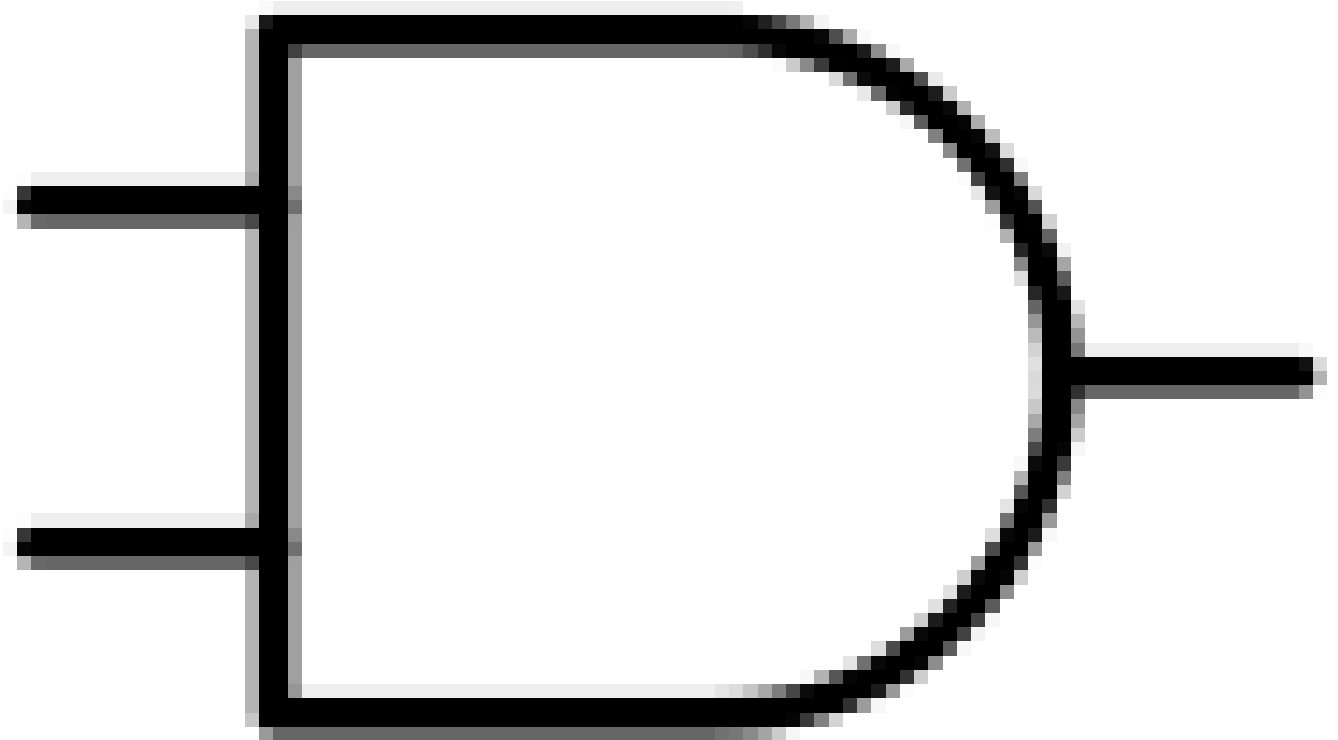

Correct Answer: 1

Question 6:


Are these two circuits equivalent?

Expression 1: $((c \text{ or } c) \text{ and } (b \text{ xor } c))$

Expression 2: $((a \text{ xnor } b) \text{ nand } (a \text{ xnor } c))$

Options:

1. Yes
2. No

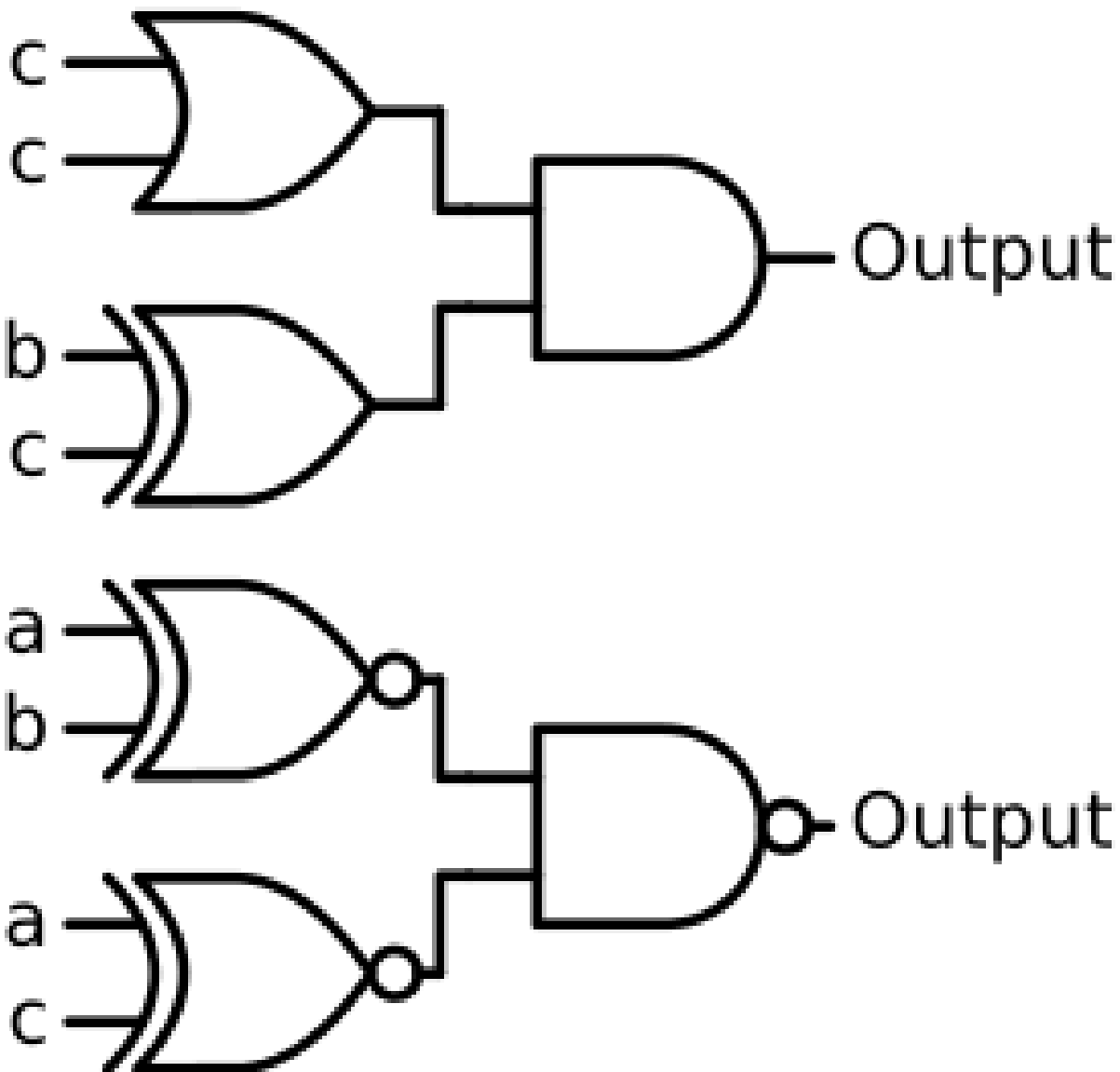

Correct Answer: no

Question 7:



Are these two circuits equivalent?

Expression 1: (b or c)

Expression 2: (not ((a xor a) nor (c nor b)))

Options:

1. Yes
2. No

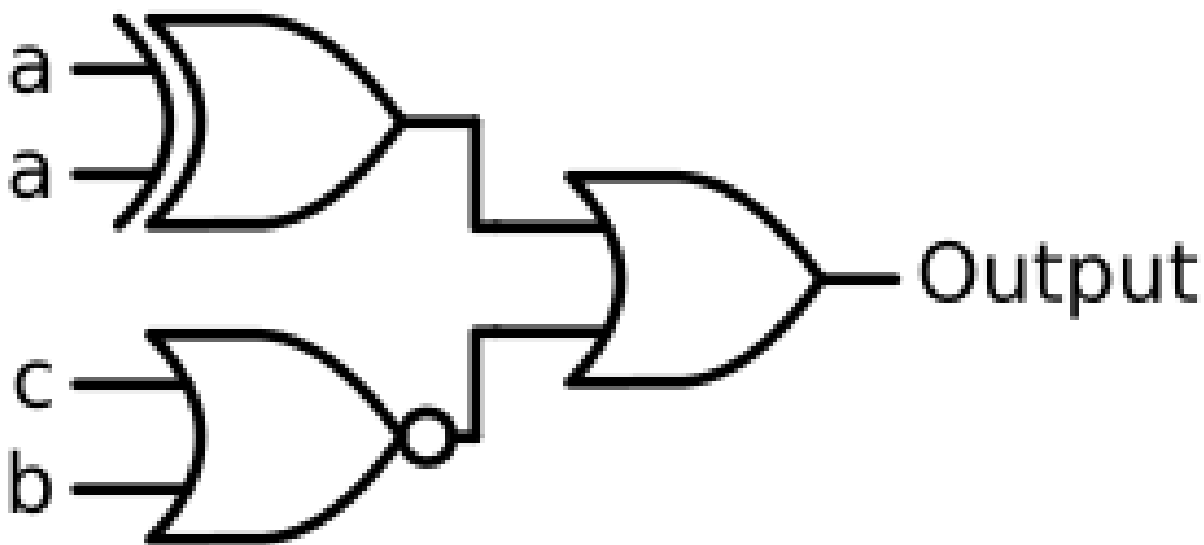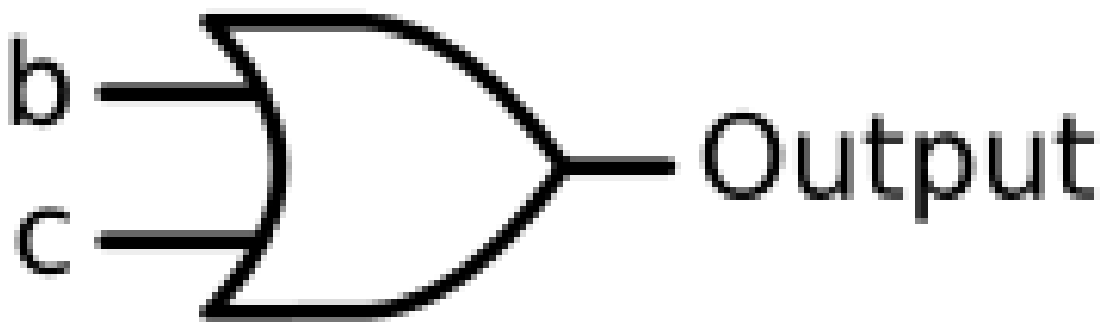

Correct Answer: no


Question 8:

What is the output of the XOR gate with inputs 1, 0?

Options:

1. 1

2. 0

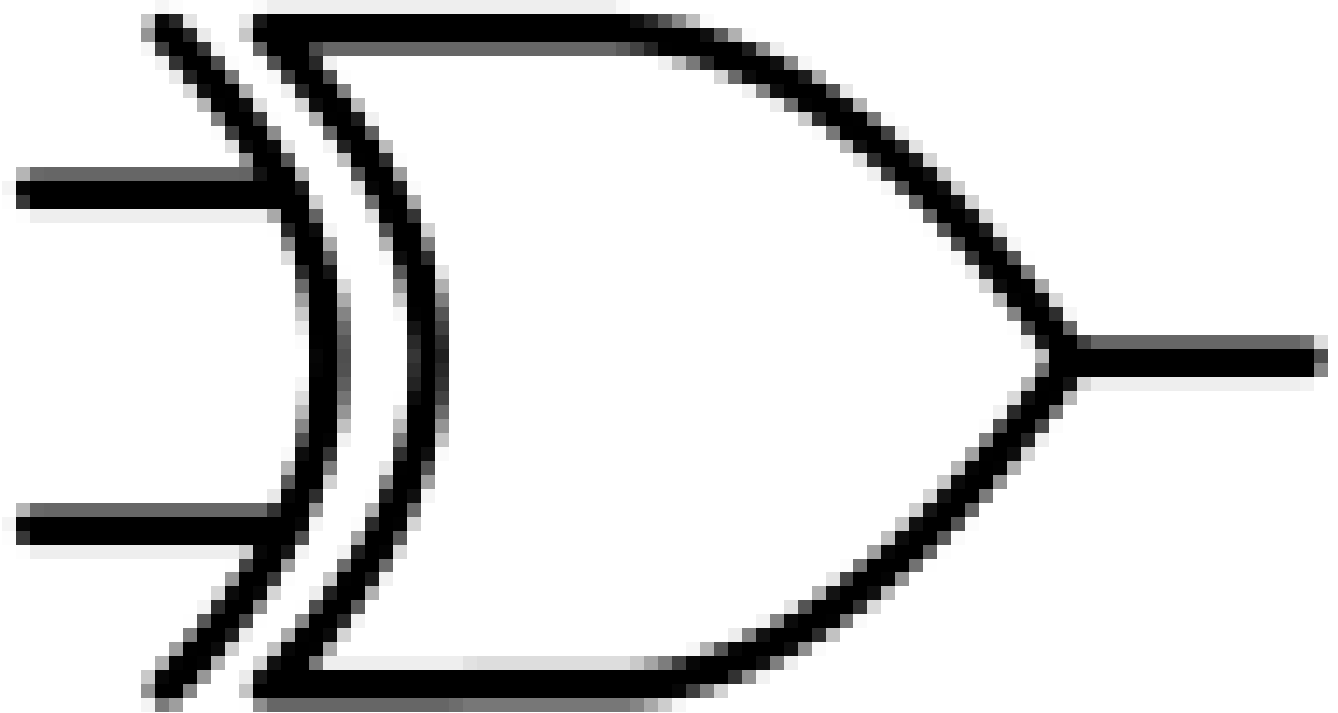

Correct Answer: 1

Question 9:



Are these two circuits equivalent?

Expression 1: $(c \text{ nor } c)$

Expression 2: $((b \text{ xnor } a) \text{ or } (a \text{ and } b)) \text{ nand } ((\text{not } b) \text{ or } (c \text{ and } b))$

Options:

1. Yes
2. No

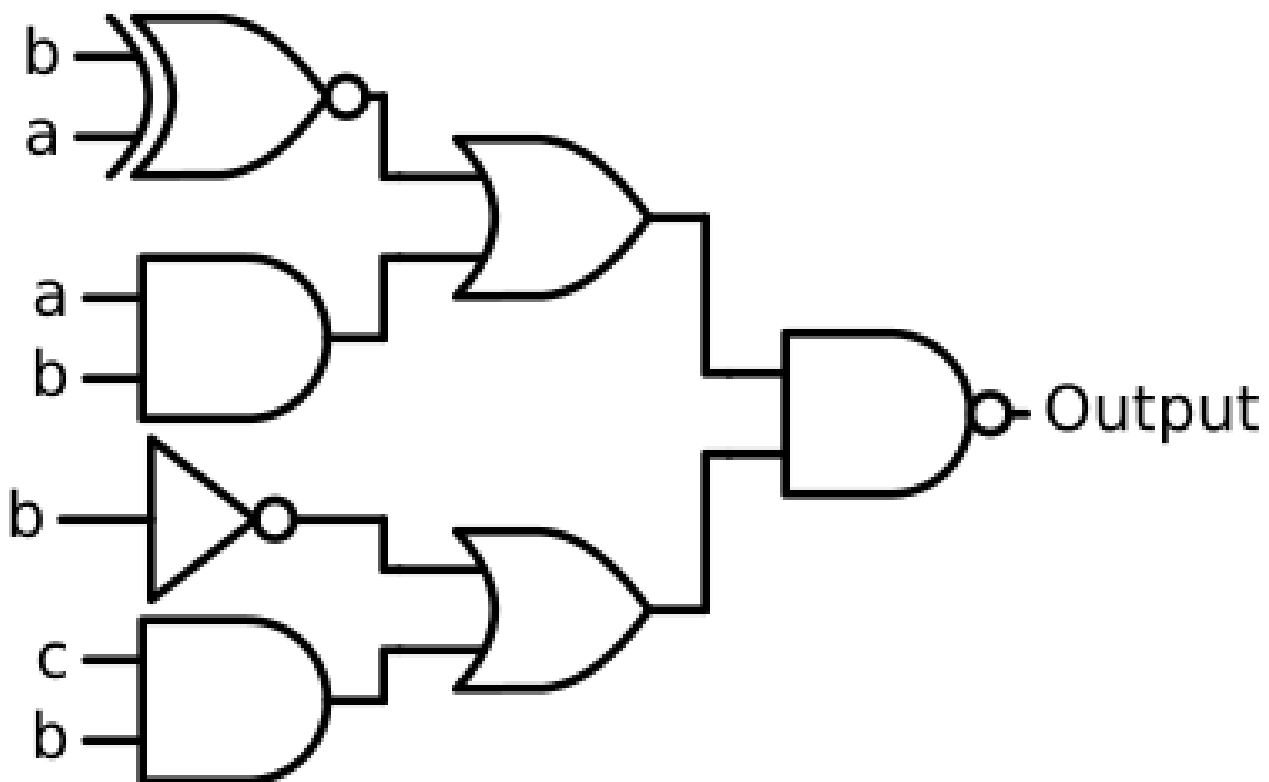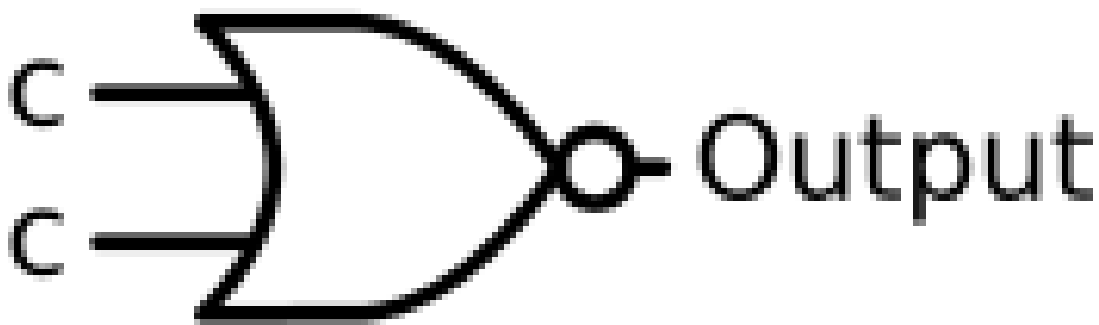

Correct Answer: no


Question 10:

What is the output of the OR gate with inputs 1, 1?

Options:

1. 1

2. 0

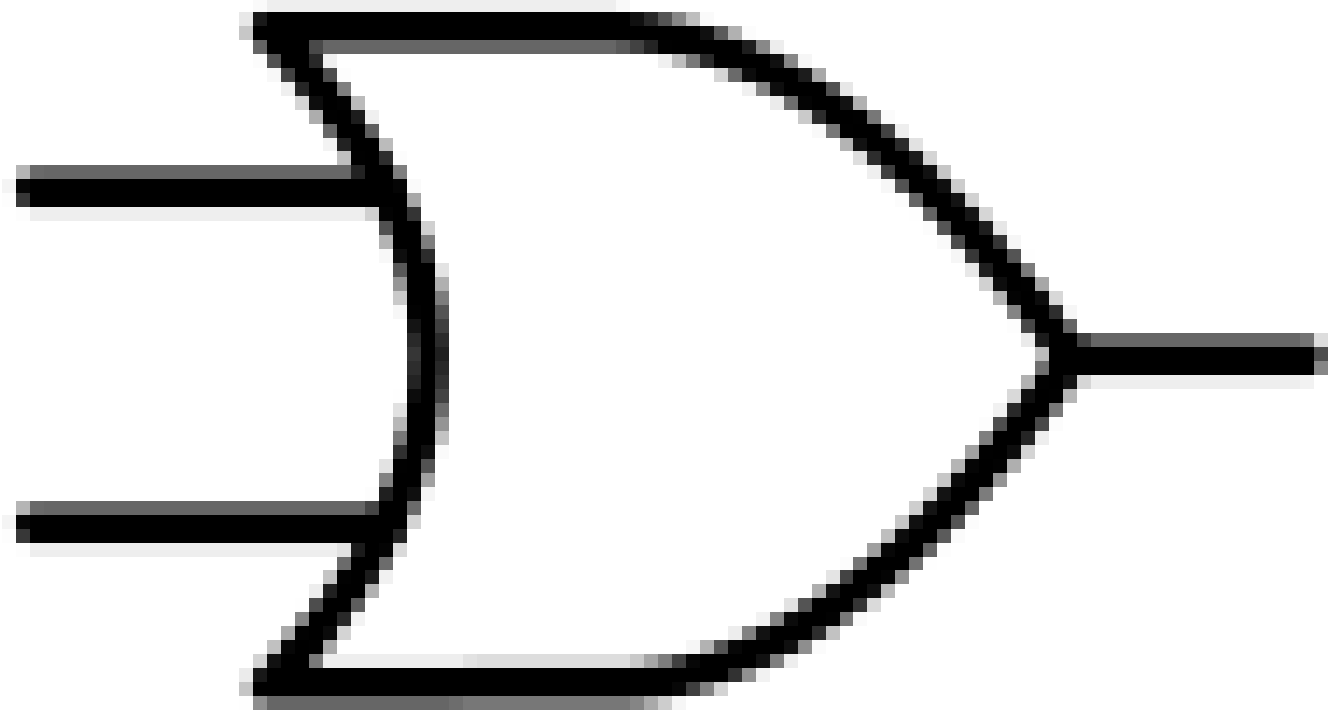

Correct Answer: 1