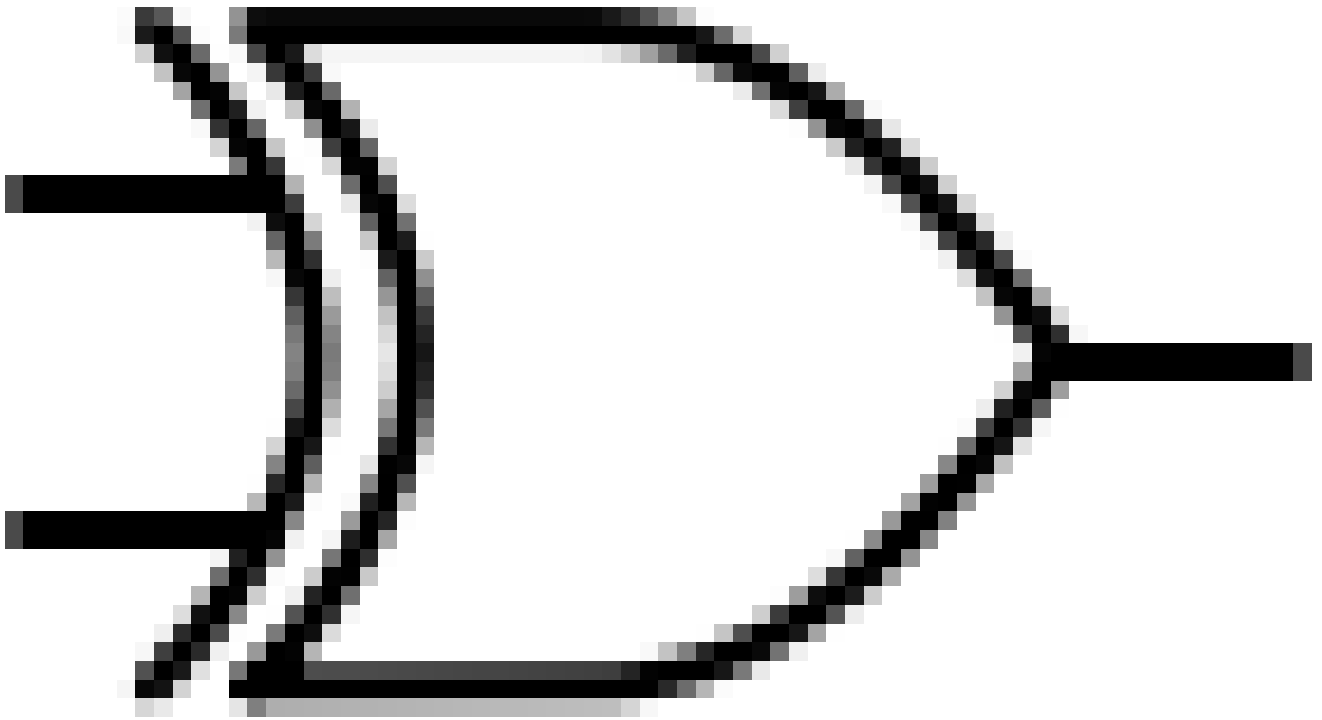


### Question 1:

What is the output of the XOR gate with inputs 0, 0?



Options:


1. 0

2. 1

Correct Answer: 0
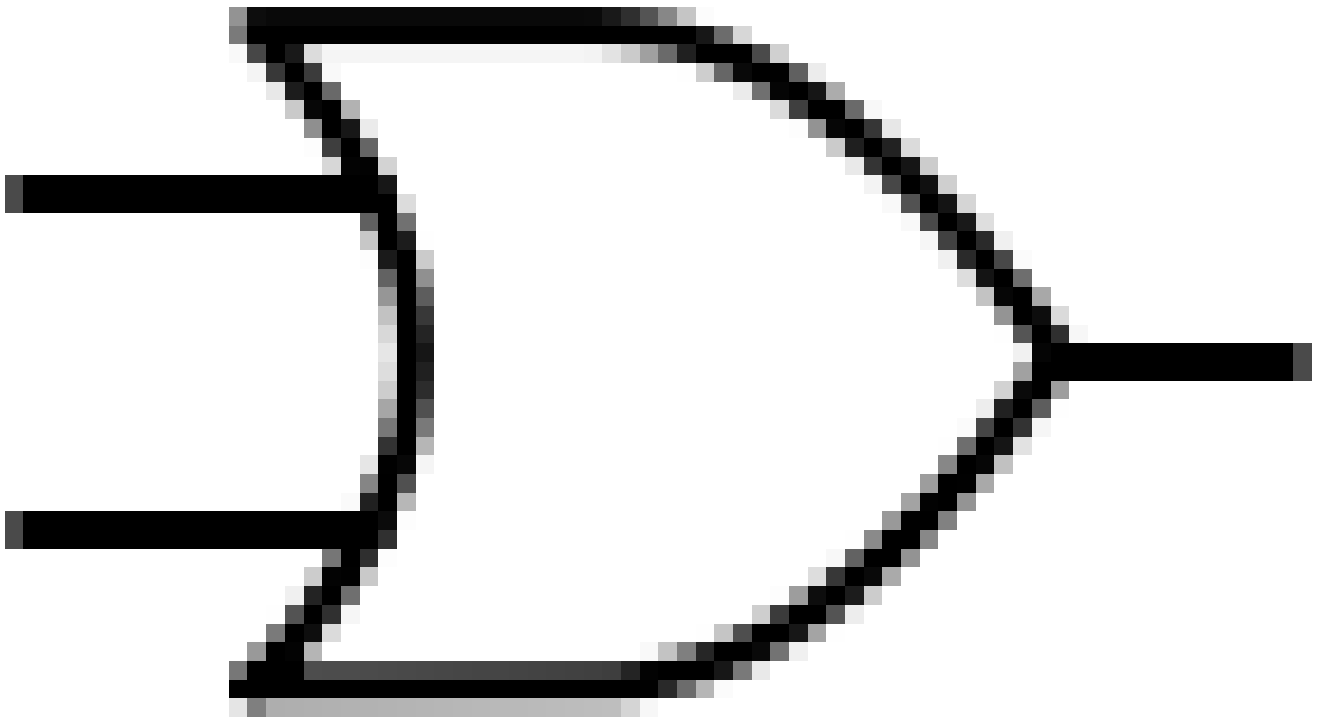
## Question 2:

What is the output of the OR gate with inputs 1, 0?



Options:


1. 1

2. 0

Correct Answer: 1
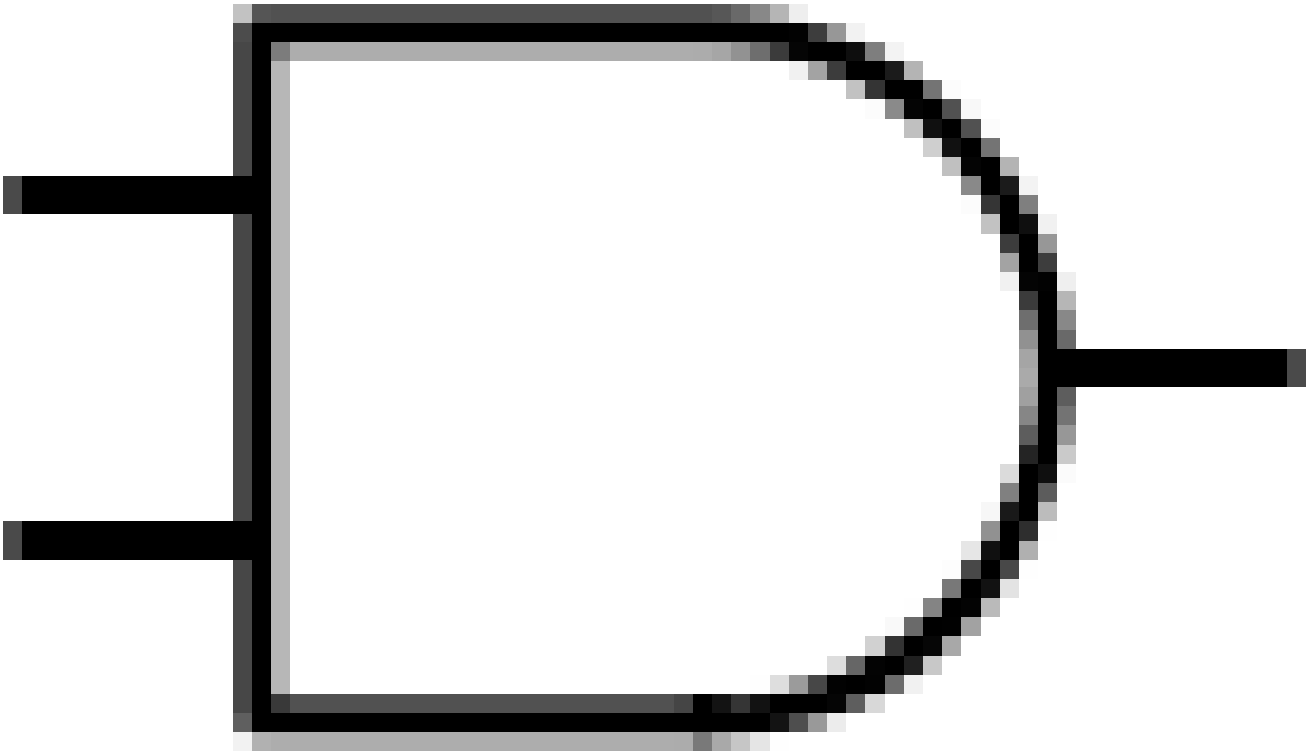
### Question 3:

What is the output of the AND gate with inputs 0, 0?



Options:


1. 0

2. 1

Correct Answer: 0
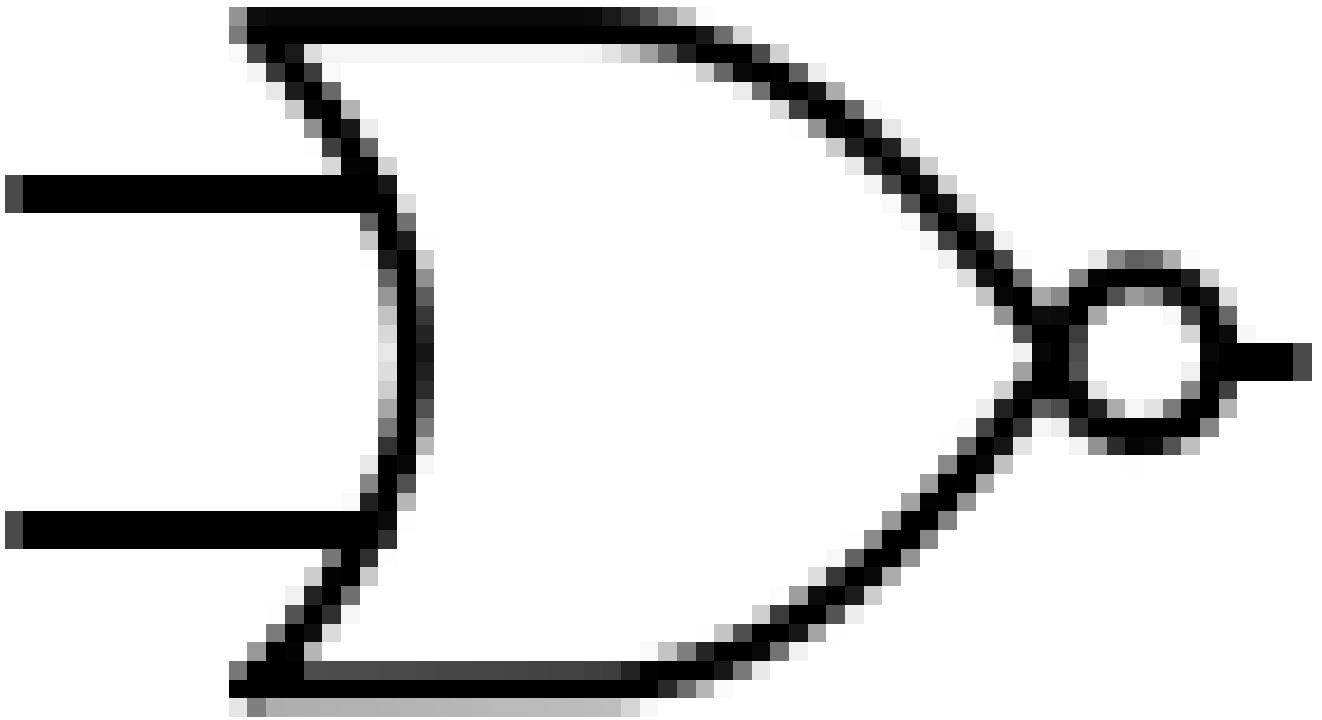
#### Question 4:

What is the output of the NOR gate with inputs 1, 1?



Options:


1. 1

2. 0

Correct Answer: 0

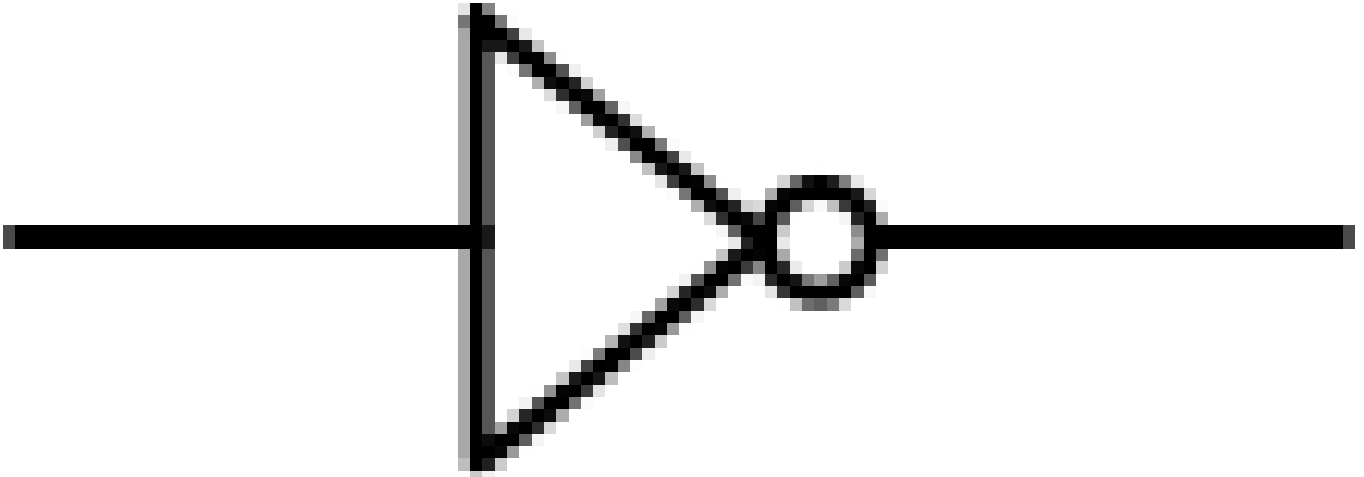Question 5:

What is the output of the NOT gate with input 0?



Options:

1. 1

2. 0



Correct Answer: 1

Question 6:

Are these two circuits equivalent?

Expression 1:  $(c \text{ xnor } a)$

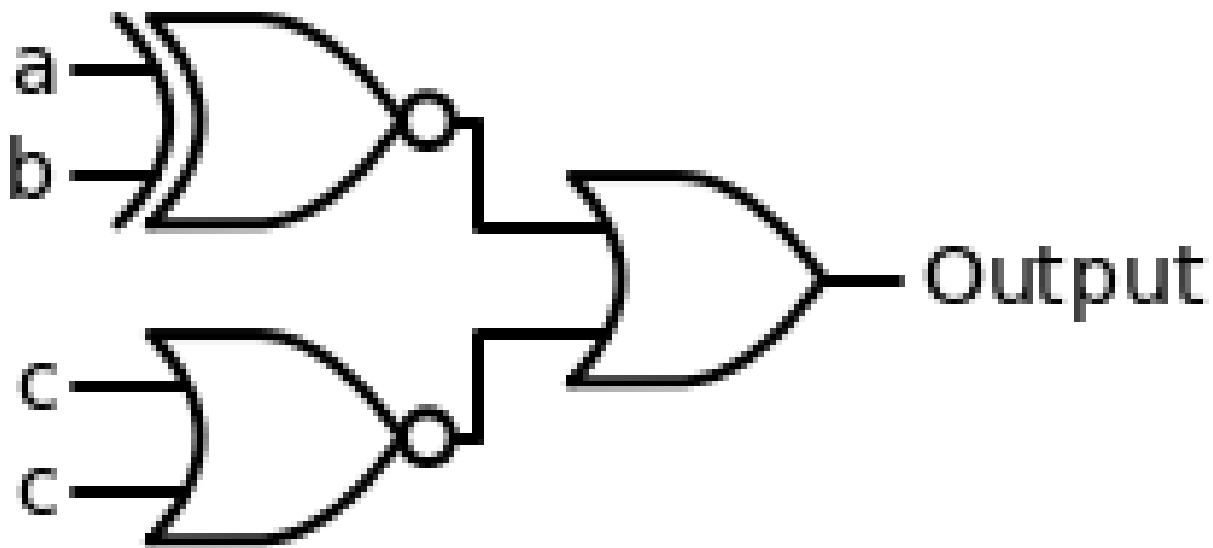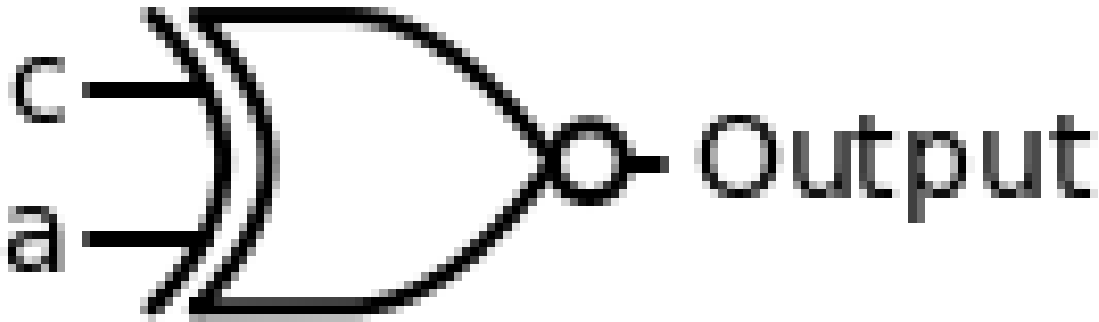Expression 2:  $((\text{not } (a \text{ xor } b)) \text{ or } (\text{not } (c \text{ or } c)))$



Options:

1. Yes
2. No



Correct Answer: no

Question 7:

Are these two circuits equivalent?

Expression 1:  $((a \text{ or } a) \text{ xor } (c \text{ and } b))$

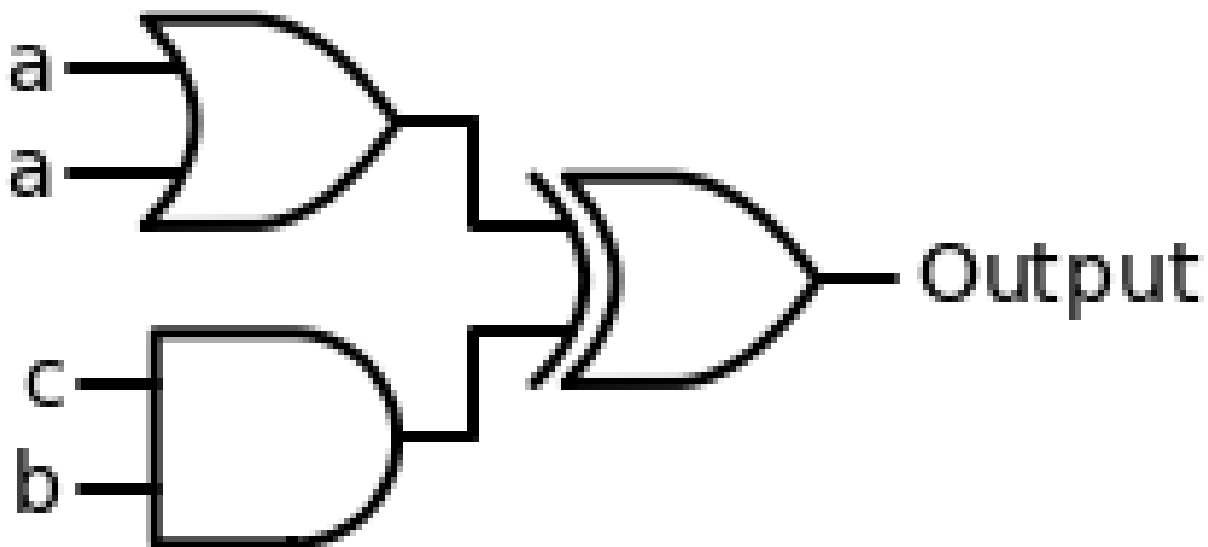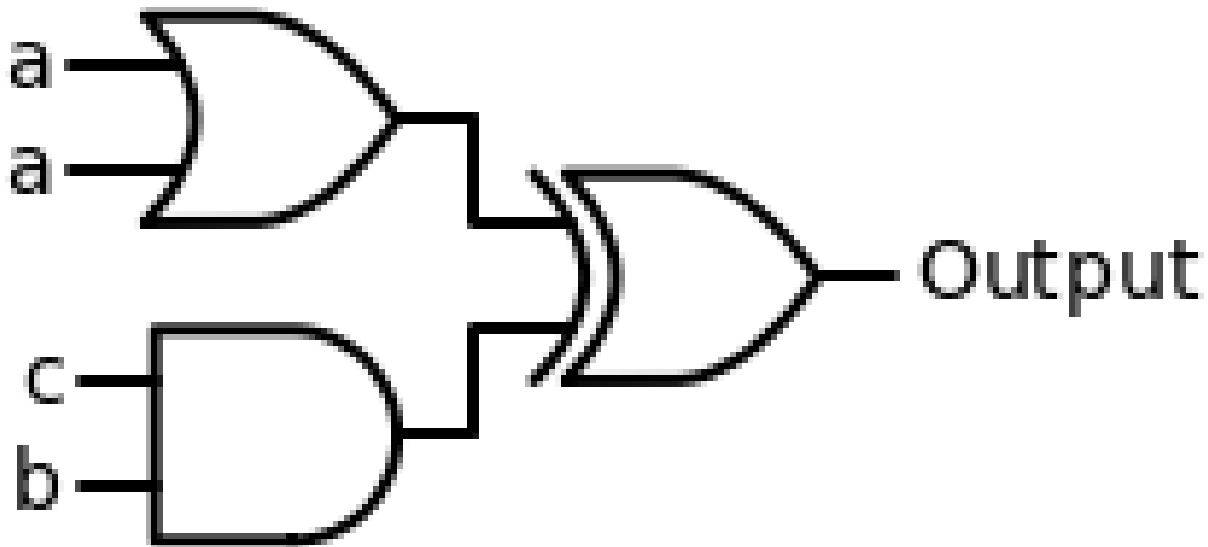Expression 2:  $((a \text{ or } a) \text{ xor } (c \text{ and } b))$



Options:

1. Yes
2. No

Correct Answer: yes





Question 8:

Are these two circuits equivalent?

Expression 1: (a or c)

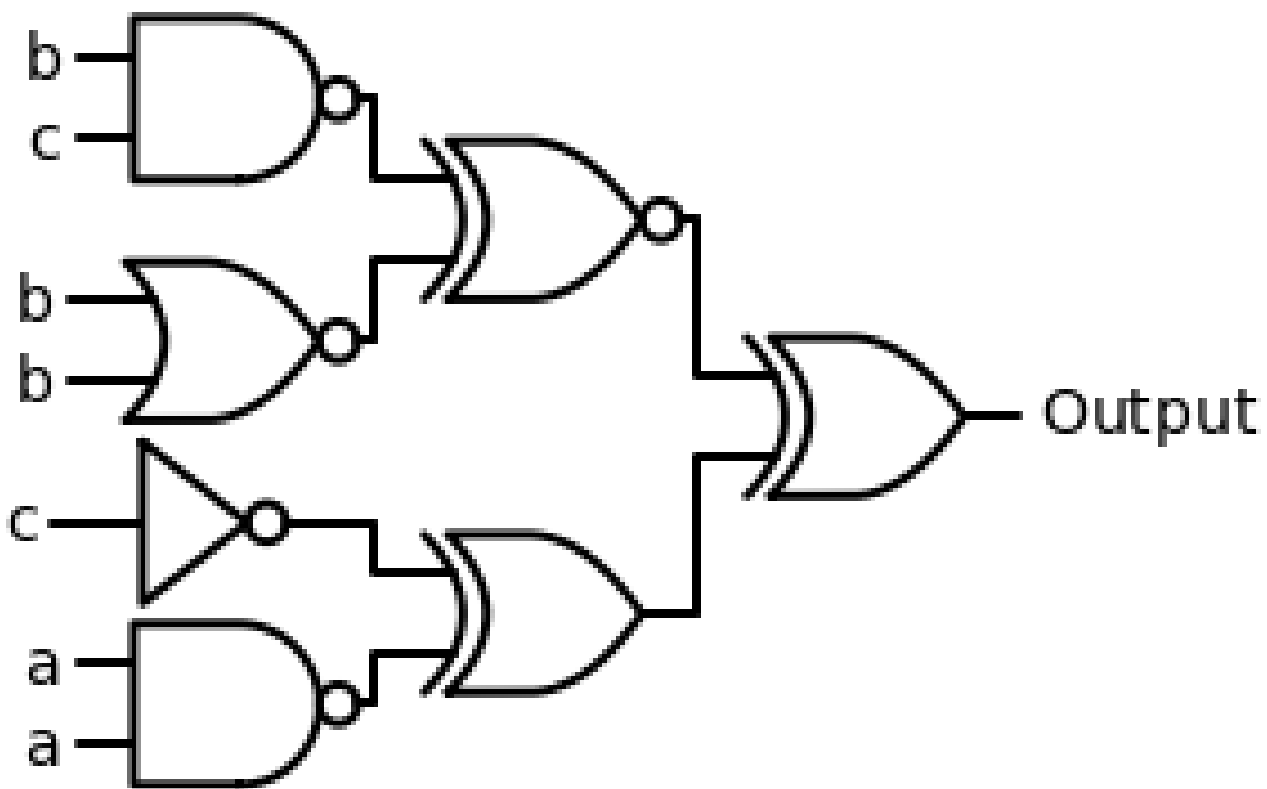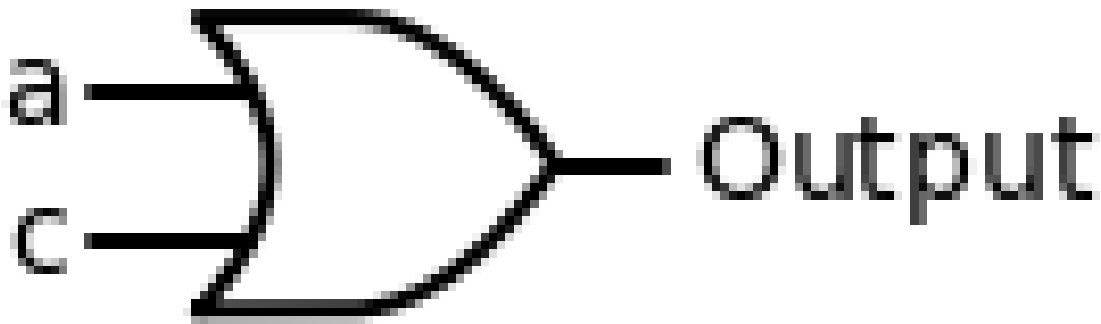Expression 2: (((b nand c) xnor (b nor b)) xor ((not c) xor (a nand a)))




Options:

1. Yes
2. No

Correct Answer: no
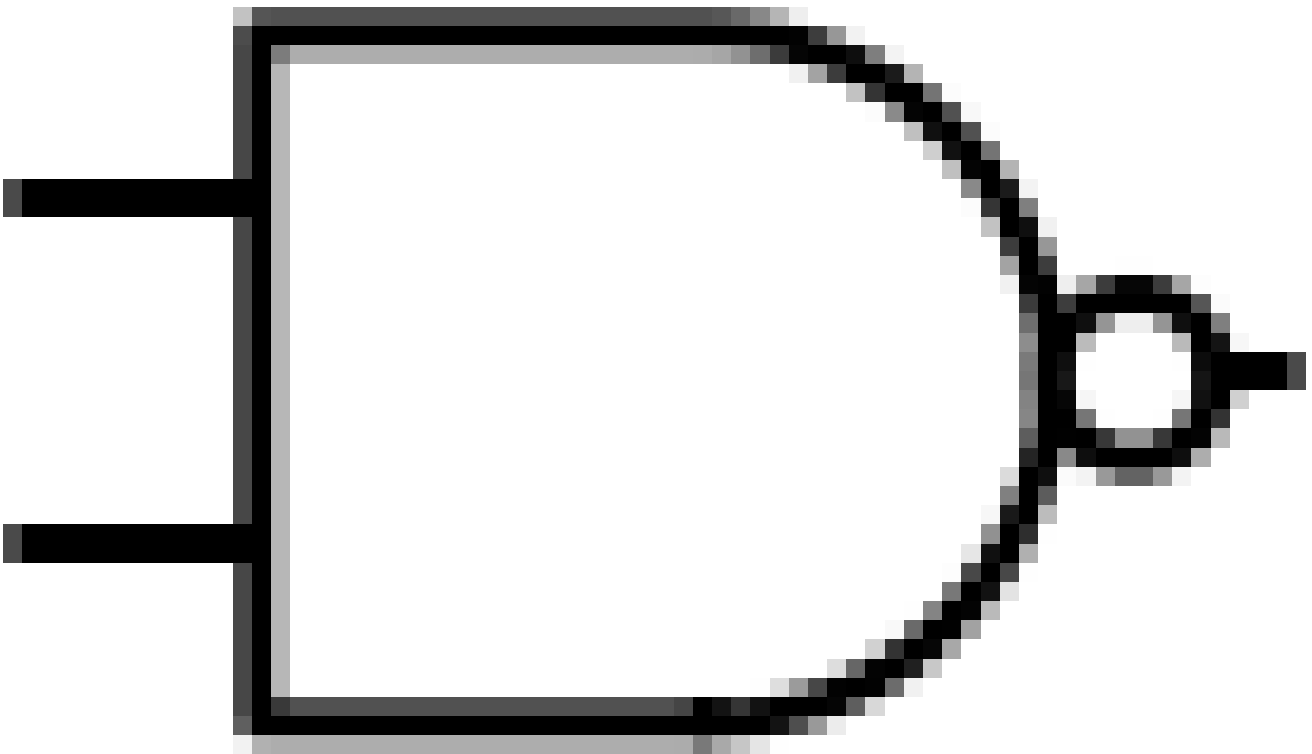
### Question 9:

What is the output of the NAND gate with inputs 0, 0?



Options:

1. 0

2. 1


Correct Answer: 1

Question 10:

Are these two circuits equivalent?

Expression 1:  $((\text{not } c) \text{ and } (b \text{ xor } c)) \text{ xor } ((a \text{ xnor } a) \text{ nand } (\text{not } a))$

Expression 2:  $(b \text{ nand } b)$

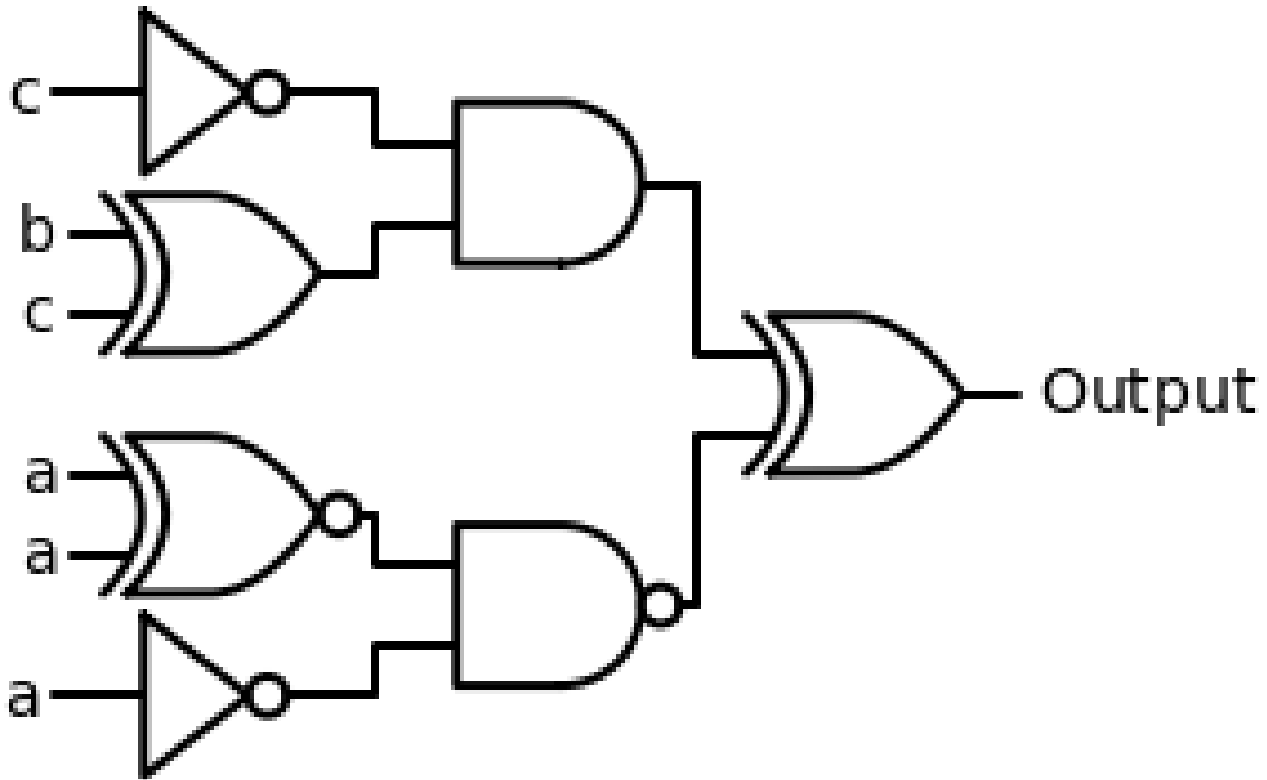

Options:

1. Yes
2. No

Correct Answer: no