

Question 1:

Are these two circuits equivalent?

Expression 1: $(a \text{ nor } c)$

Expression 2: $(b \text{ nand } a)$



Options:

1. Yes
2. No



Correct Answer: no

Question 2:

Are these two circuits equivalent?

Expression 1: $(\text{not } (a \text{ nand } c))$

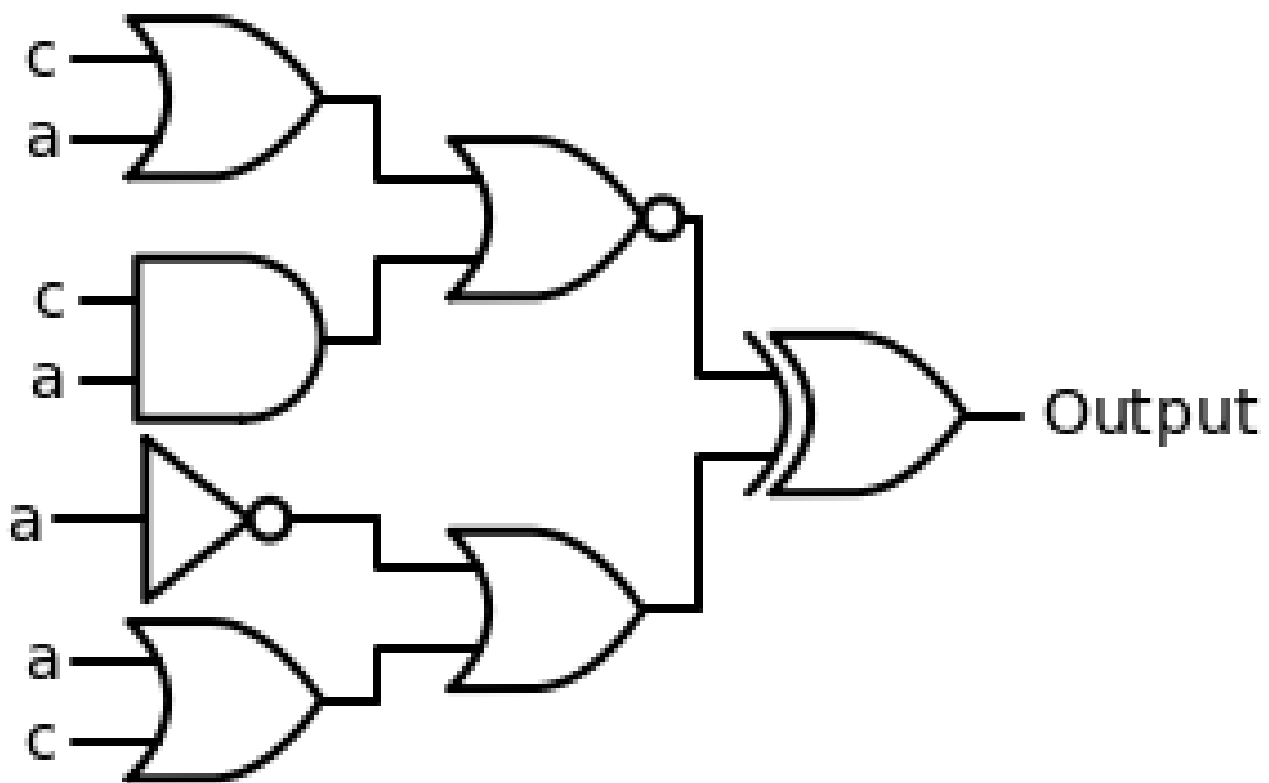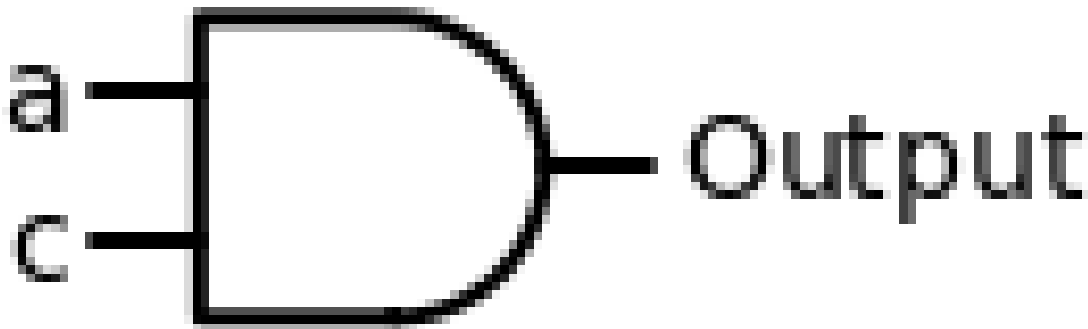Expression 2: $((c \text{ or } a) \text{ nor } (c \text{ and } a)) \text{ xor } ((\text{not } a) \text{ or } (a \text{ or } c))$




Options:

1. Yes
2. No

Correct Answer: no

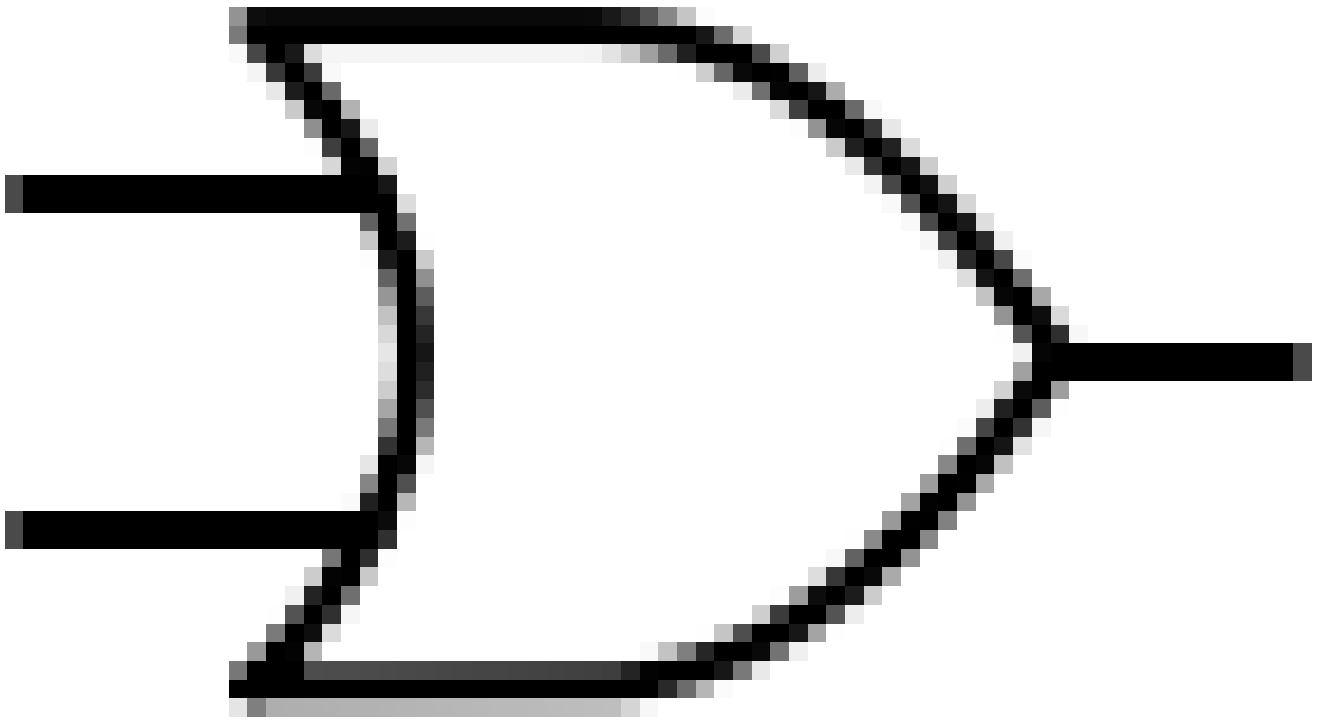Question 3:

What is the output of the OR gate with inputs 1, 0?



Options:

1. 0

2. 1



Correct Answer: 1

Question 4:

Are these two circuits equivalent?

Expression 1: $((c \text{ xnor } c) \text{ xor } (a \text{ or } a))$

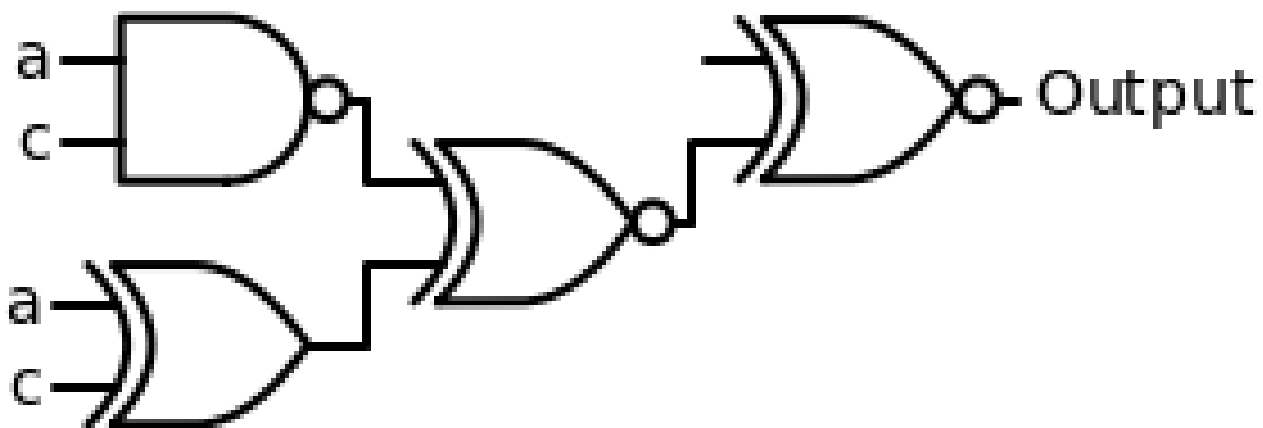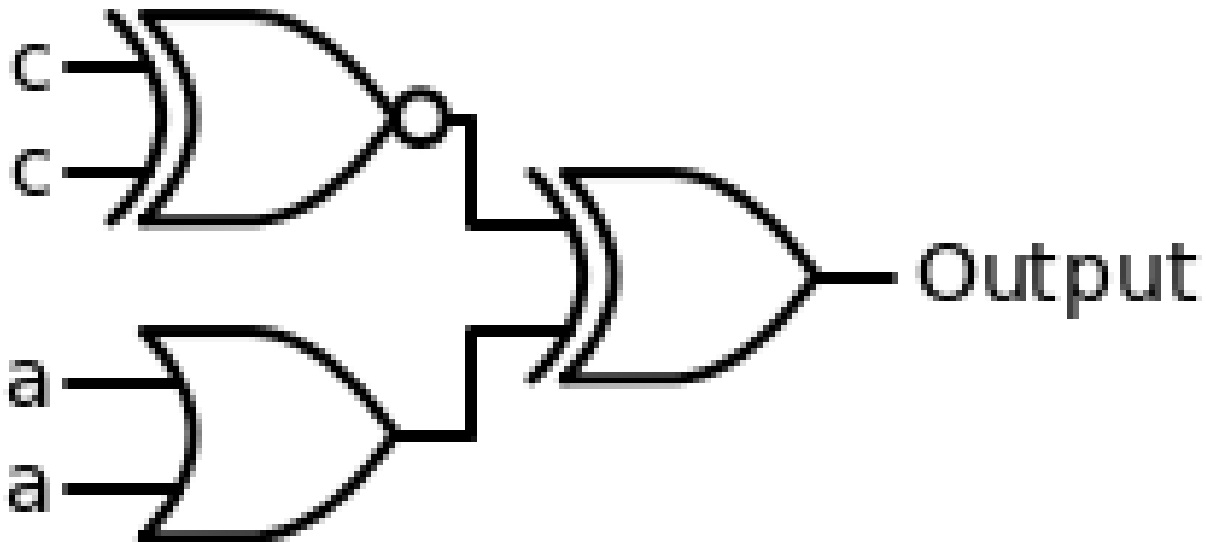Expression 2: $((\text{not } (\text{not } a)) \text{ xnor } ((a \text{ nand } c) \text{ xnor } (a \text{ xor } c)))$




Options:

1. Yes
2. No

Correct Answer: no

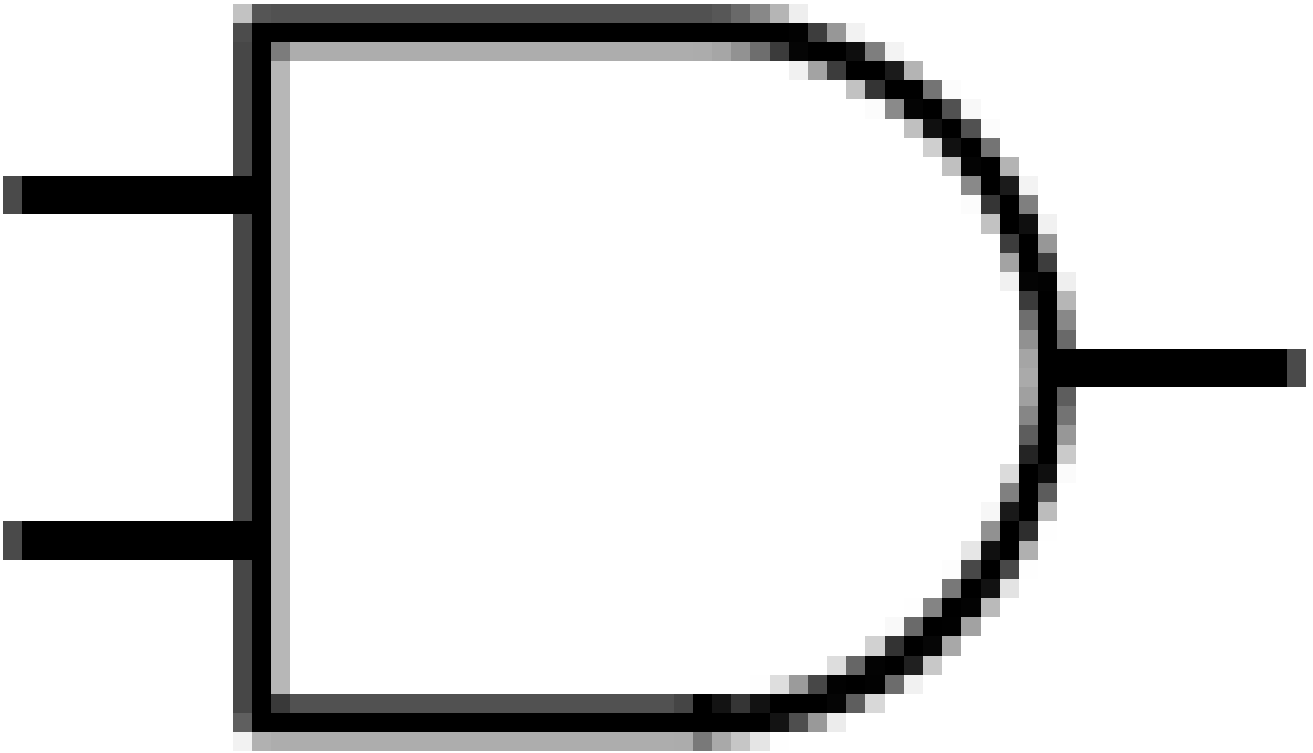Question 5:

What is the output of the AND gate with inputs 1, 1?



Options:


1. 0

2. 1

Correct Answer: 1

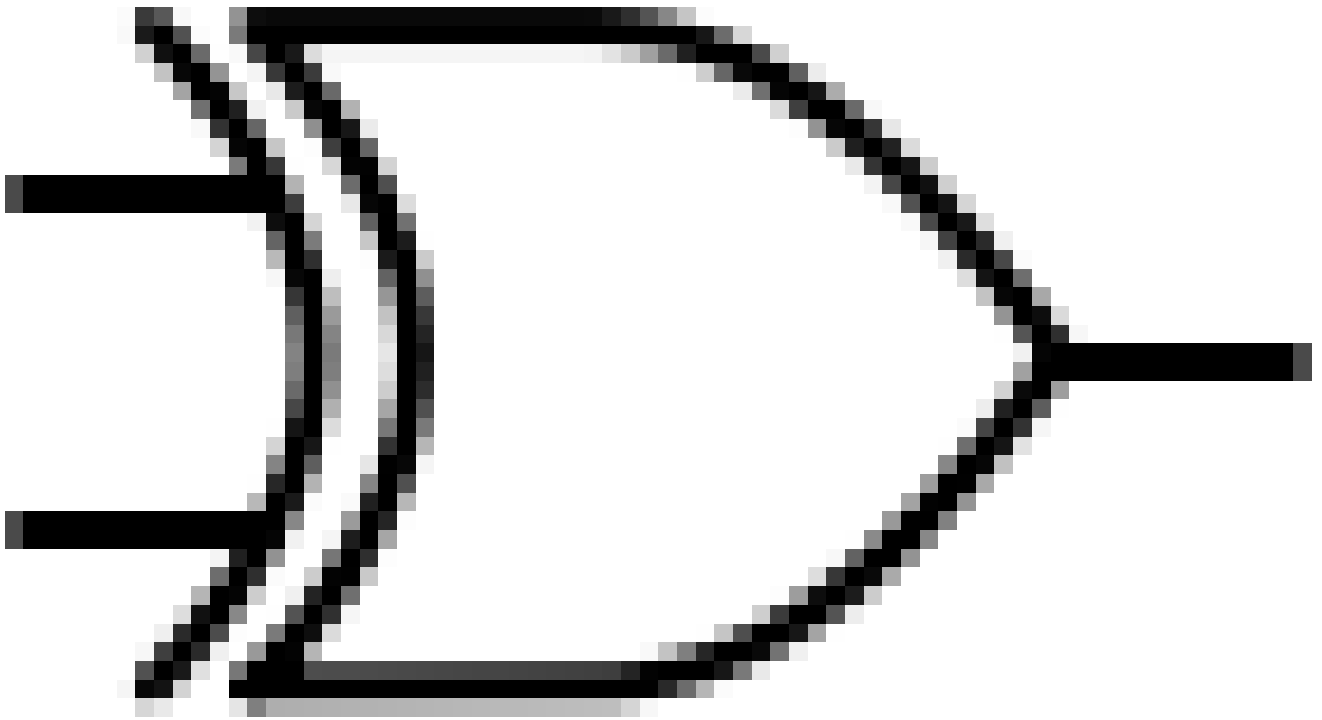Question 6:

What is the output of the XOR gate with inputs 0, 0?



Options:

1. 0

2. 1



Correct Answer: 0

Question 7:

Are these two circuits equivalent?

Expression 1: (c and c)

Expression 2: (b nor b)

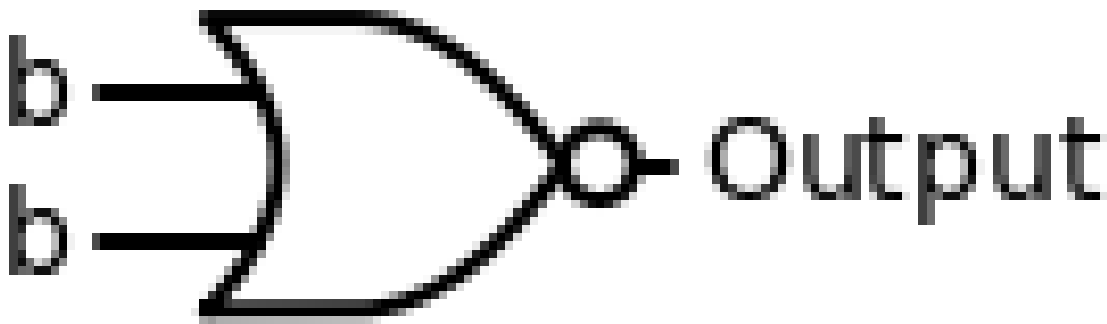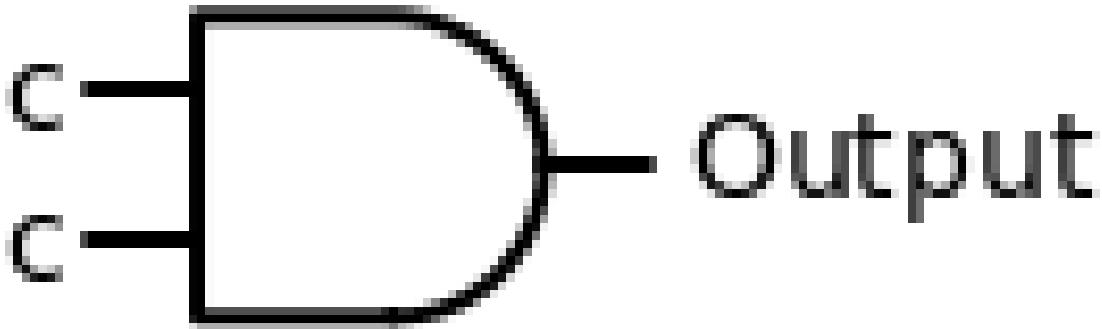


Options:

1. Yes
2. No

Correct Answer: no

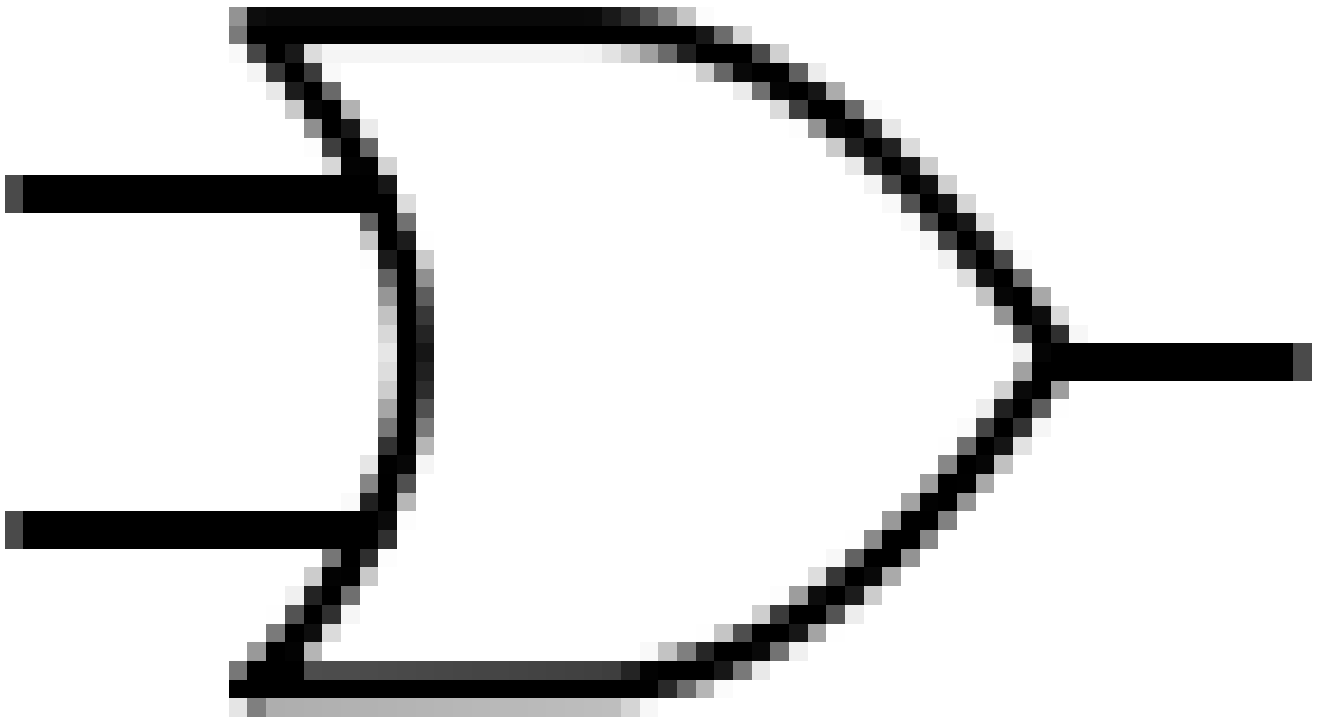Question 8:

What is the output of the OR gate with inputs 1, 1?



Options:


1. 0

2. 1

Correct Answer: 1

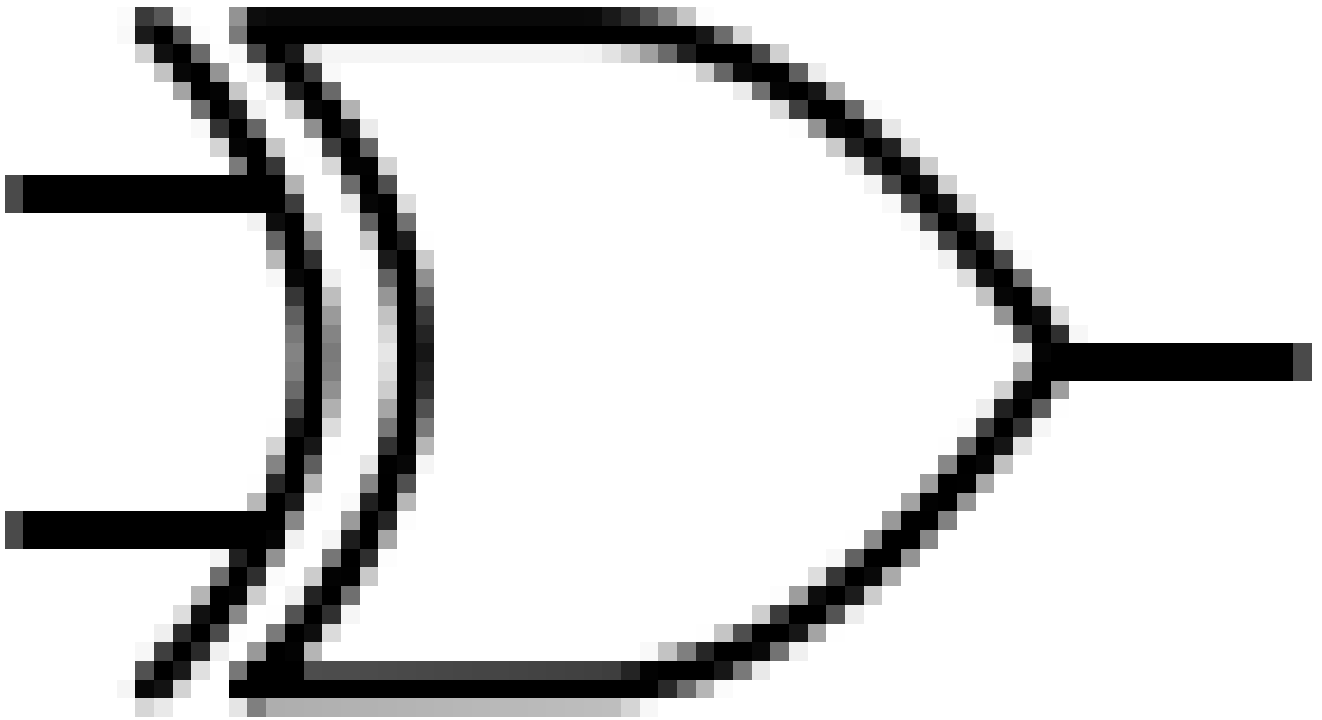Question 9:

What is the output of the XOR gate with inputs 0, 0?



Options:

1. 0

2. 1



Correct Answer: 0

Question 10:

Are these two circuits equivalent?

Expression 1: $((a \text{ xnor } a) \text{ or } (b \text{ and } c))$

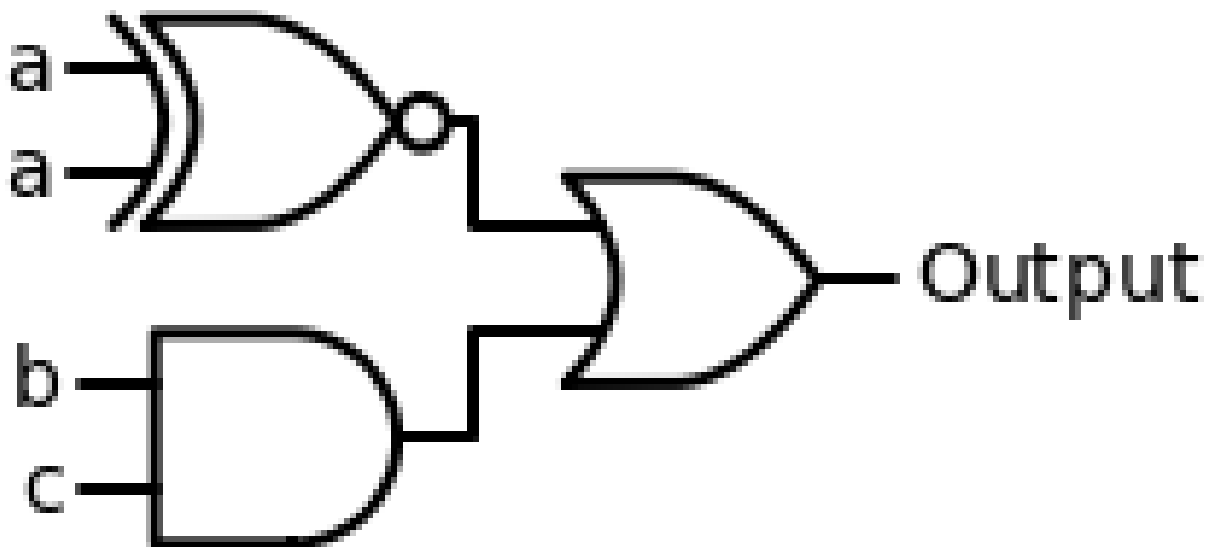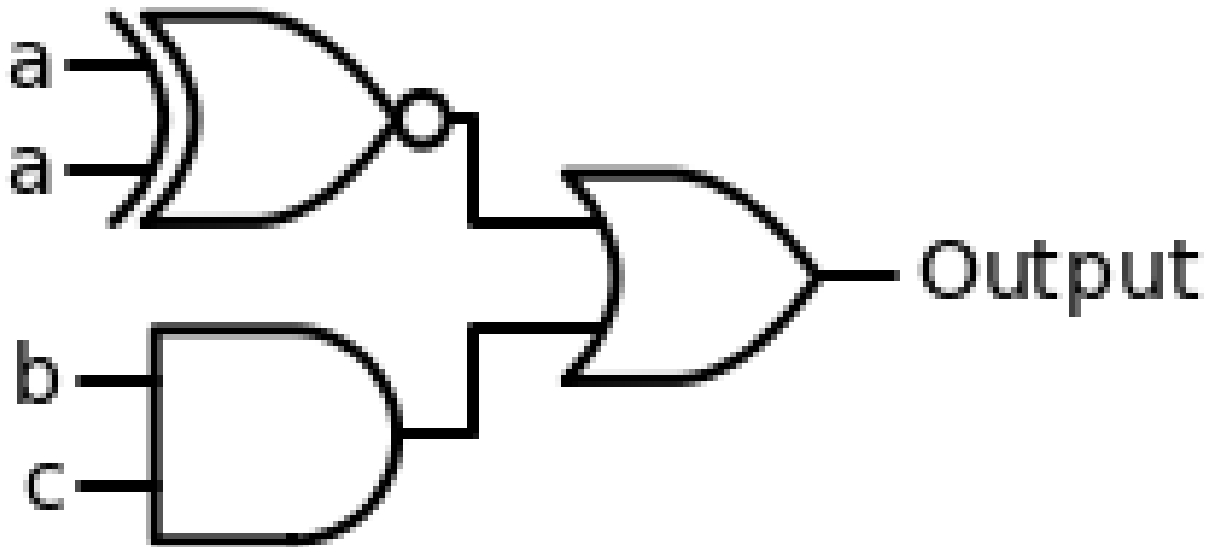Expression 2: $((a \text{ xnor } a) \text{ or } (b \text{ and } c))$



Options:

1. Yes
2. No



Correct Answer: yes

Question 11:

Are these two circuits equivalent?

Expression 1: (a and b)

Expression 2: (a and b)

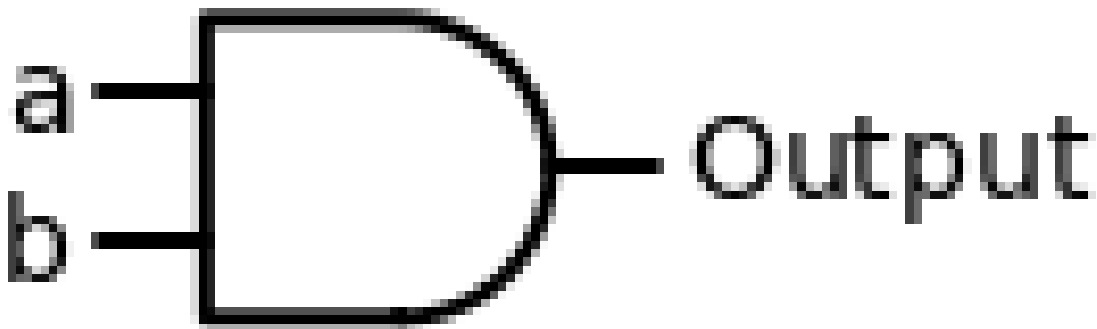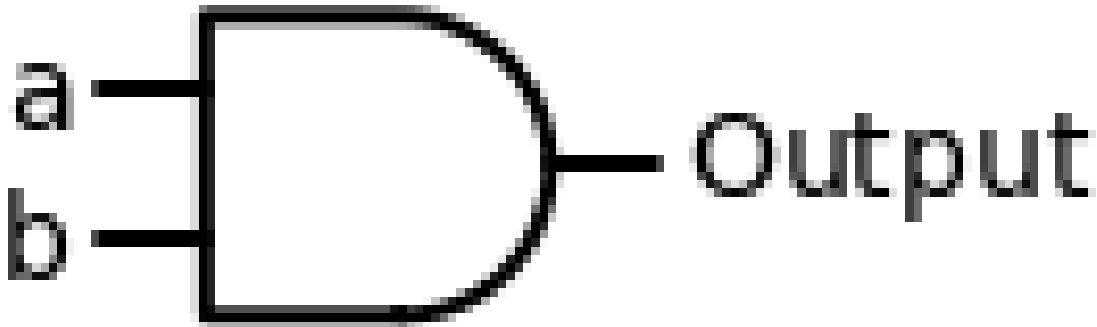

Options:

1. Yes
2. No


Correct Answer: yes

Question 12:

Are these two circuits equivalent?

Expression 1: $(b \text{ nand } c)$

Expression 2: $(\text{not } b)$

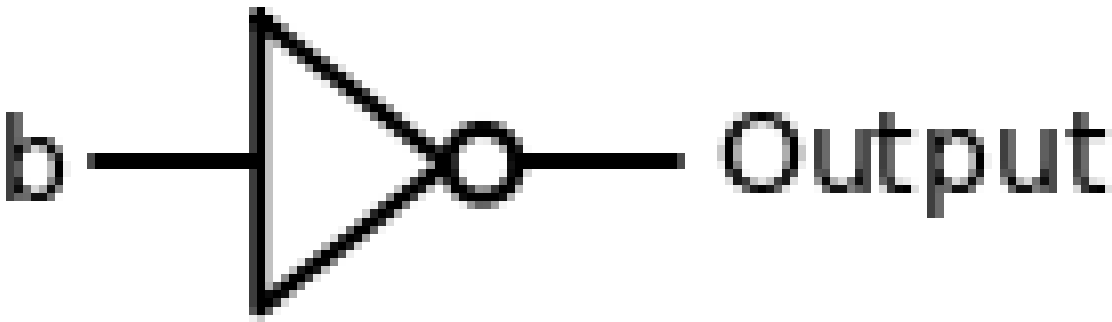


Options:

1. Yes
2. No

Correct Answer: no

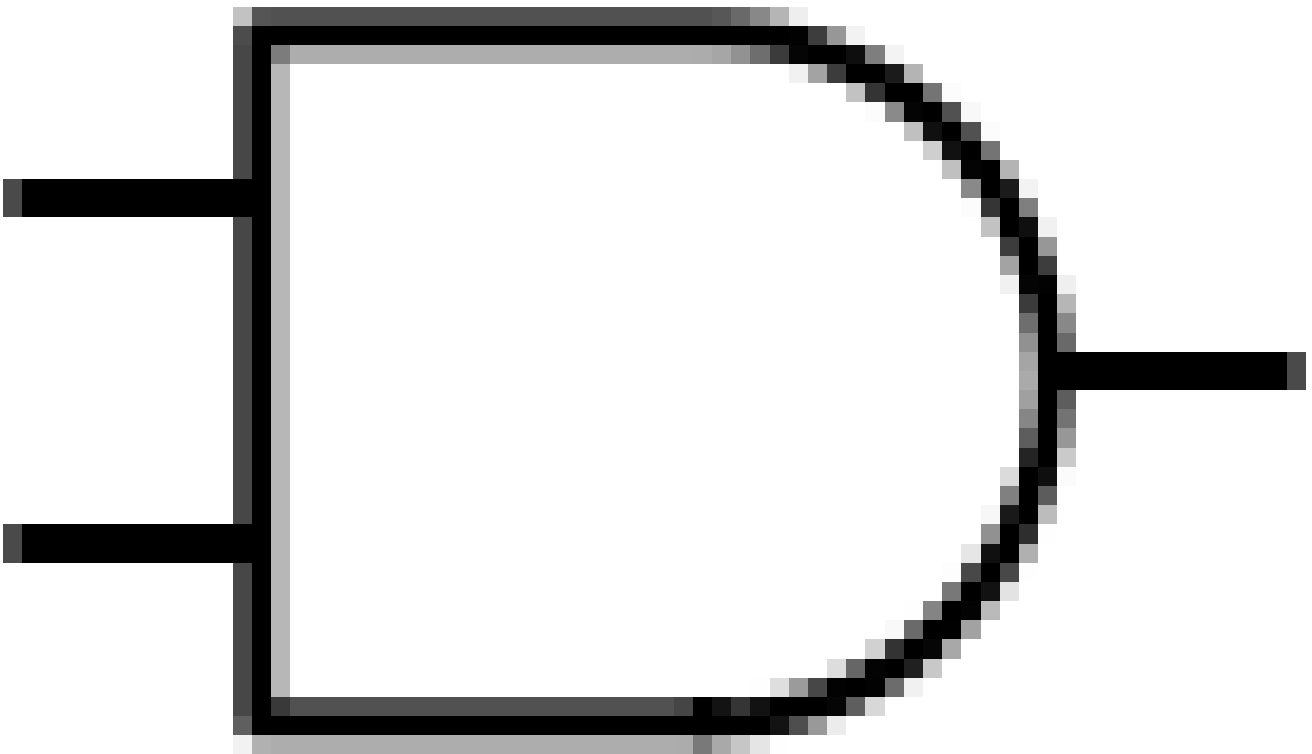Question 13:

What is the output of the AND gate with inputs 0, 0?



Options:


1. 0

2. 1

Correct Answer: 0

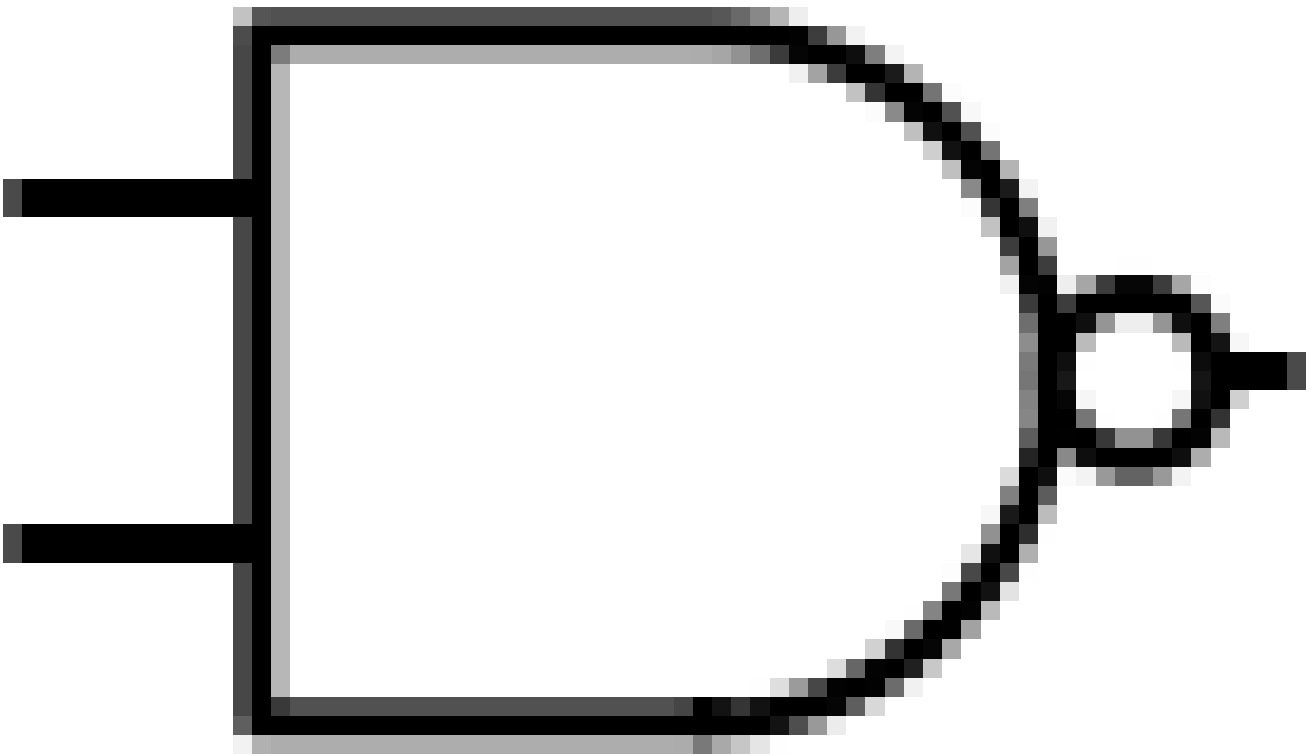Question 14:

What is the output of the NAND gate with inputs 1, 1?



Options:


1. 0

2. 1

Correct Answer: 0

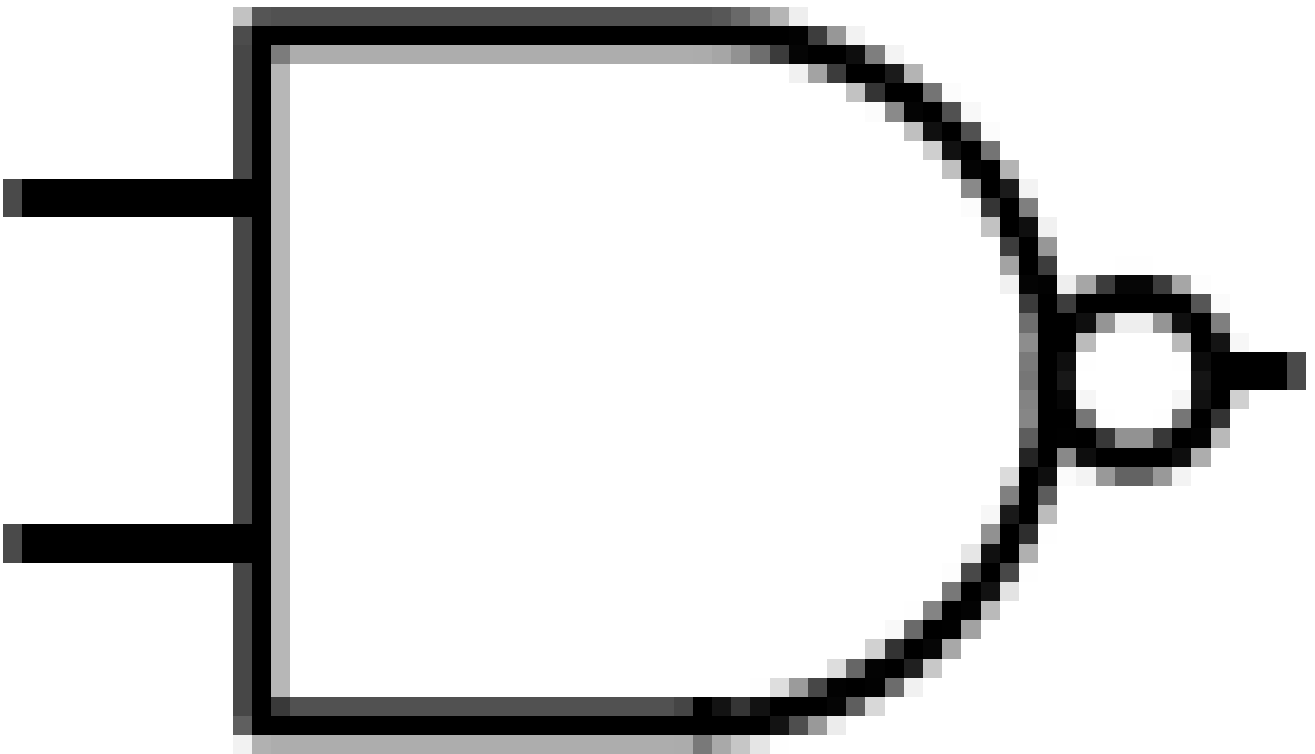Question 15:

What is the output of the NAND gate with inputs 0, 1?



Options:


1. 0

2. 1

Correct Answer: 1

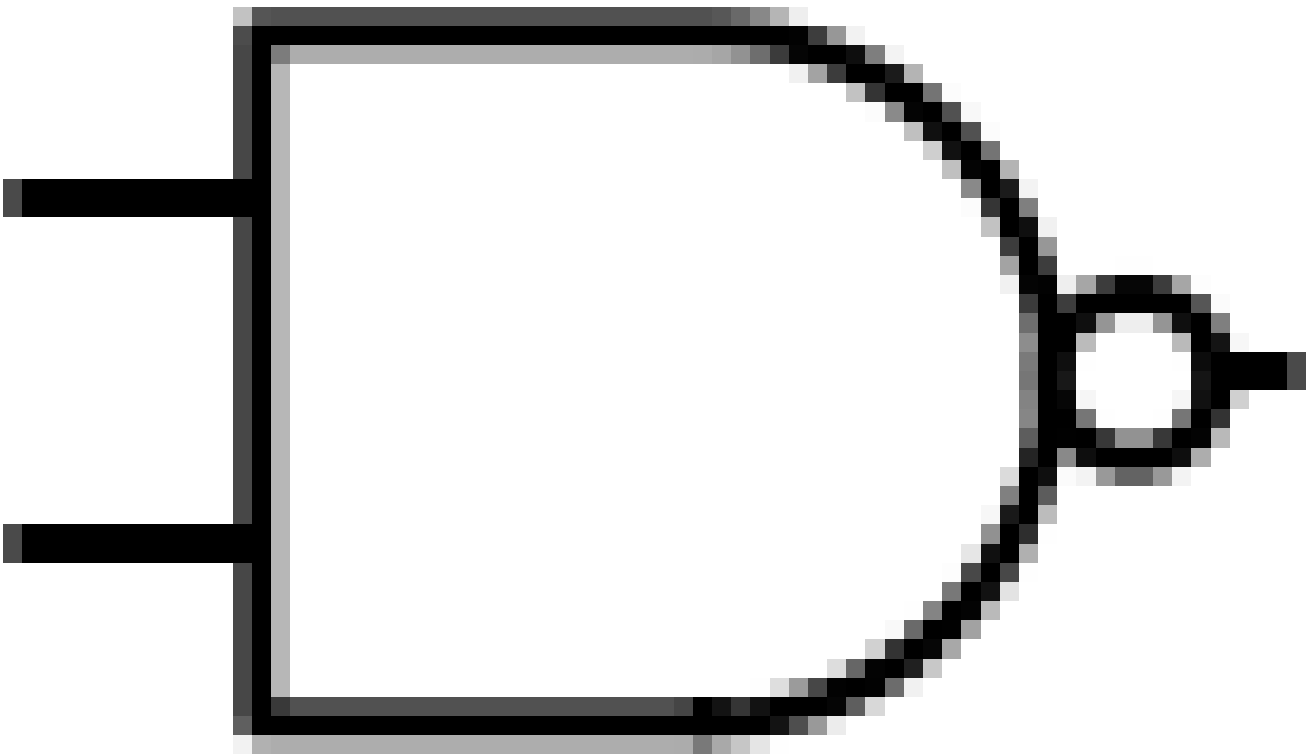Question 16:

What is the output of the NAND gate with inputs 0, 0?



Options:


1. 1

2. 0

Correct Answer: 1

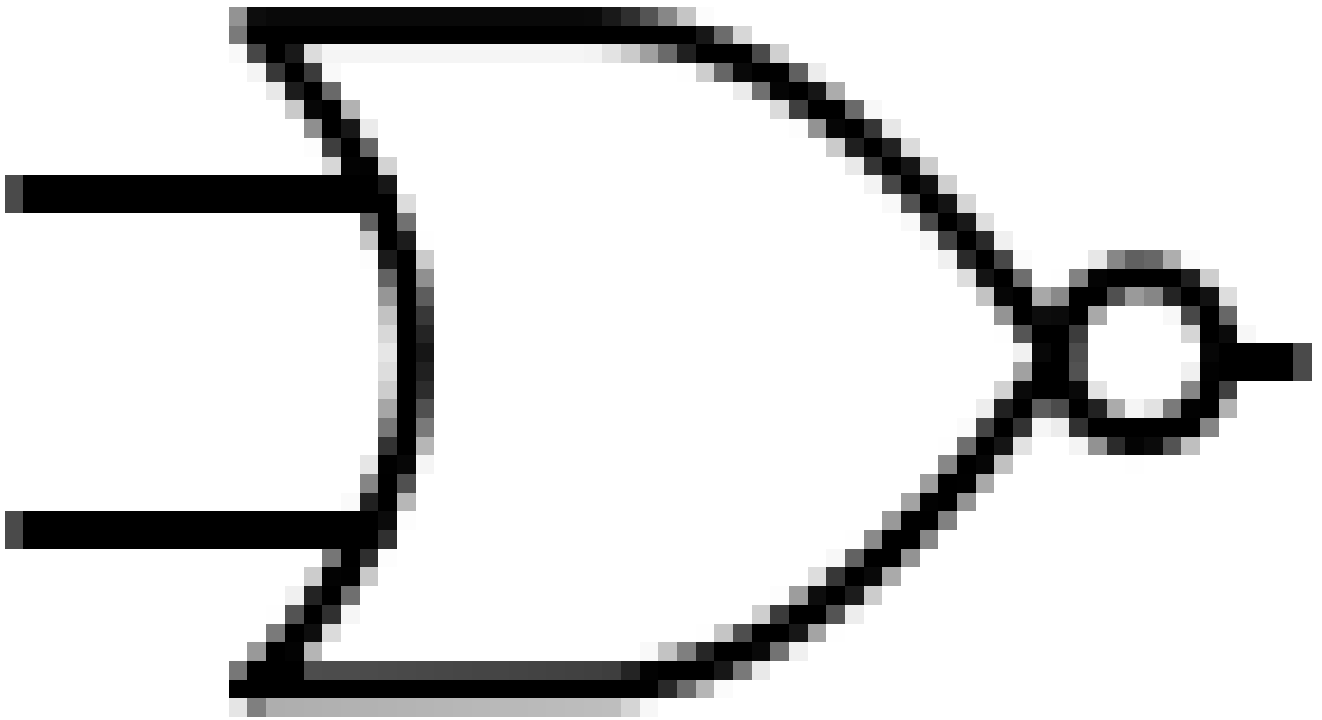Question 17:

What is the output of the NOR gate with inputs 1, 0?



Options:

1. 0

2. 1



Correct Answer: 0

Question 18:

Are these two circuits equivalent?

Expression 1: (not a)

Expression 2: (not a)

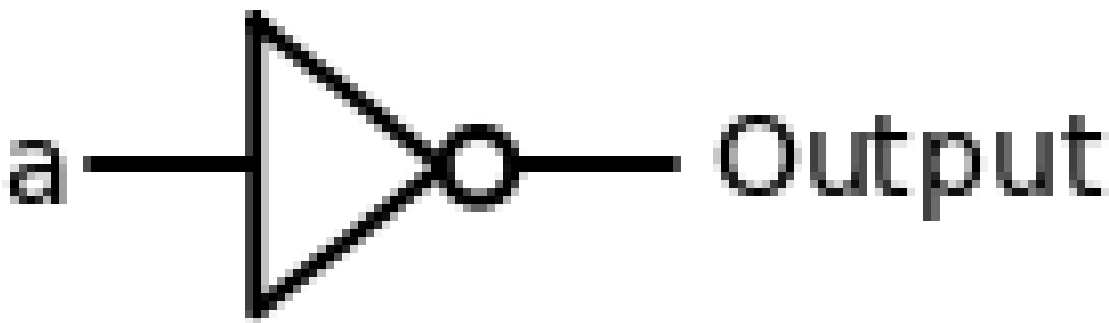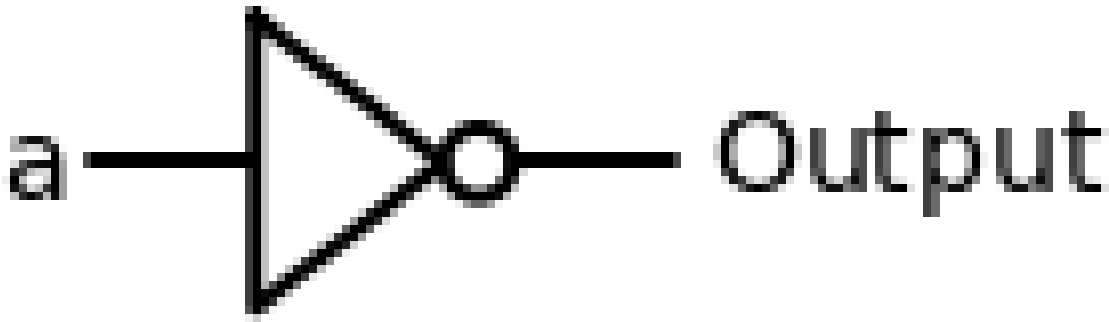

Options:

1. Yes

2. No



Correct Answer: yes

Question 19:

Are these two circuits equivalent?

Expression 1: (not a)

Expression 2: ((c or b) and (c nor a))

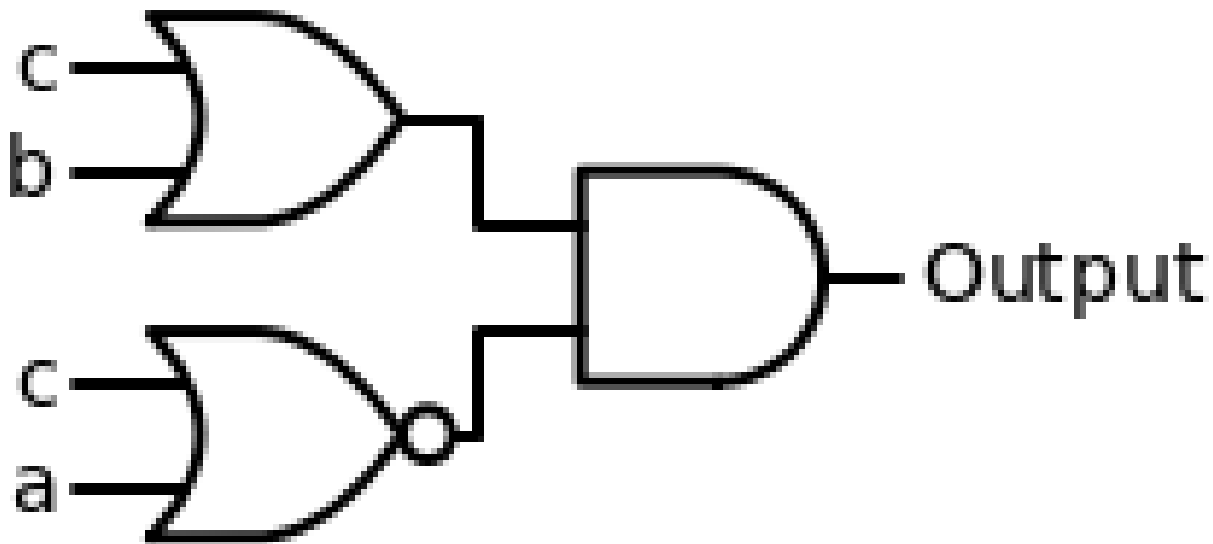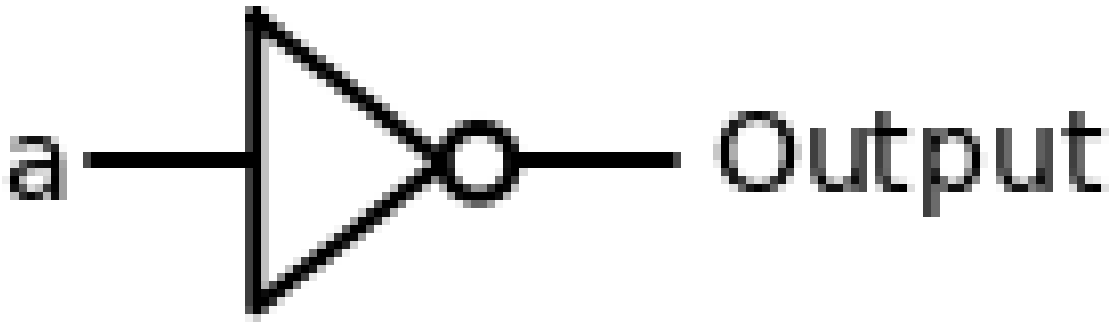


Options:

1. Yes
2. No

Correct Answer: no

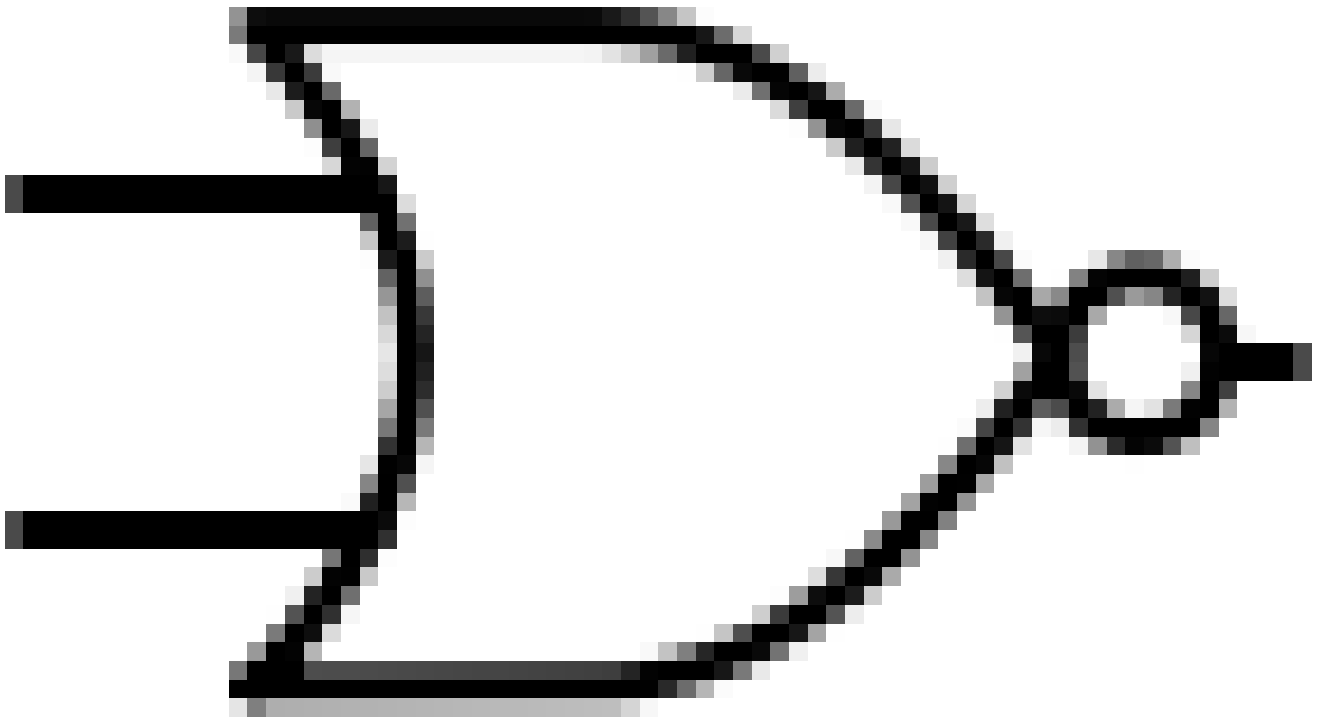Question 20:

What is the output of the NOR gate with inputs 1, 0?



Options:

1. 1

2. 0


Correct Answer: 0

Question 21:

Are these two circuits equivalent?

Expression 1: $(a \text{ nand } b)$

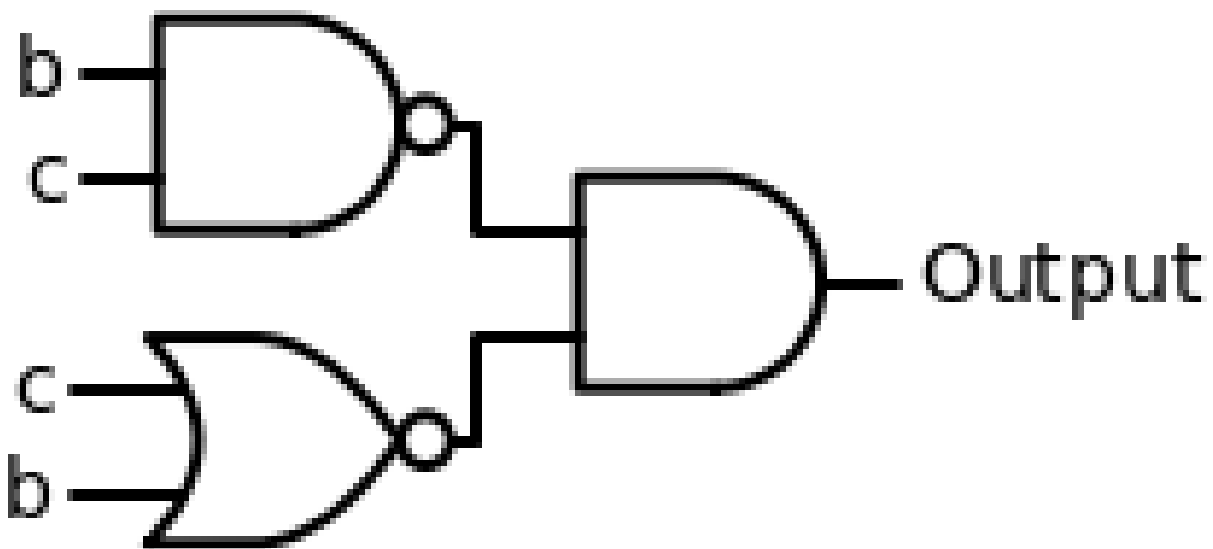Expression 2: $((b \text{ nand } c) \text{ and } (c \text{ nor } b))$



Options:

1. Yes
2. No



Correct Answer: no

Question 22:

Are these two circuits equivalent?

Expression 1: $((a \text{ nor } a) \text{ nand } (c \text{ and } a))$

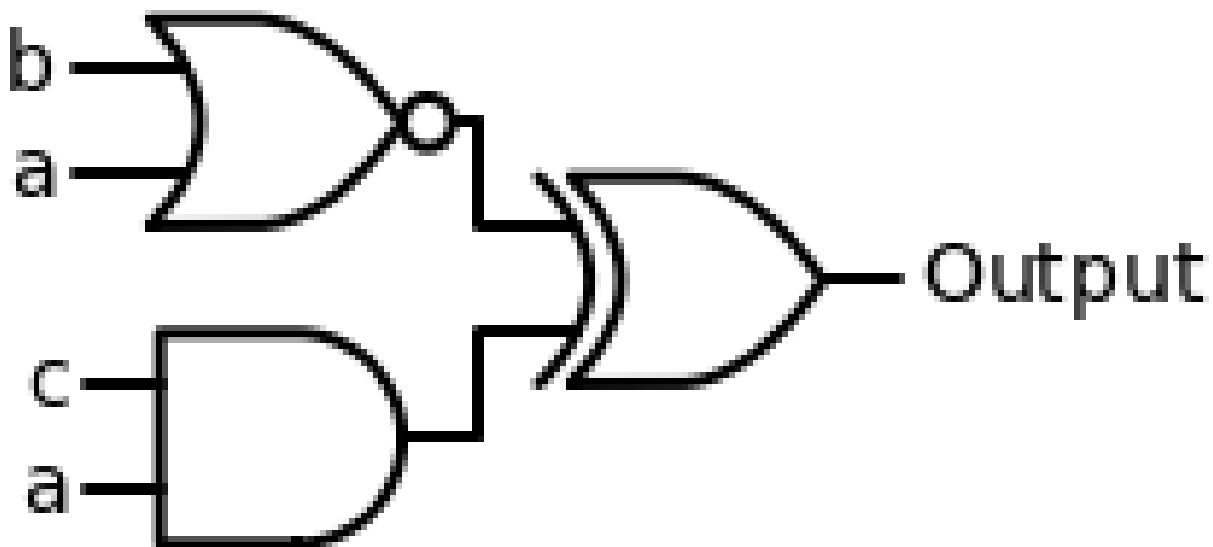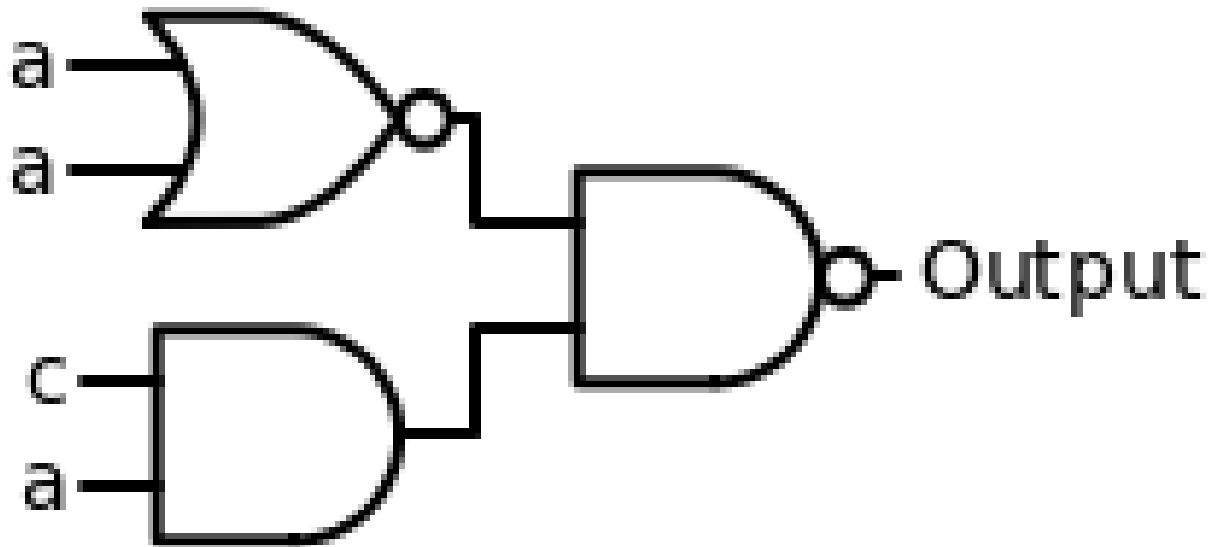Expression 2: $((b \text{ nor } a) \text{ xor } (c \text{ and } a))$




Options:

1. Yes
2. No

Correct Answer: no

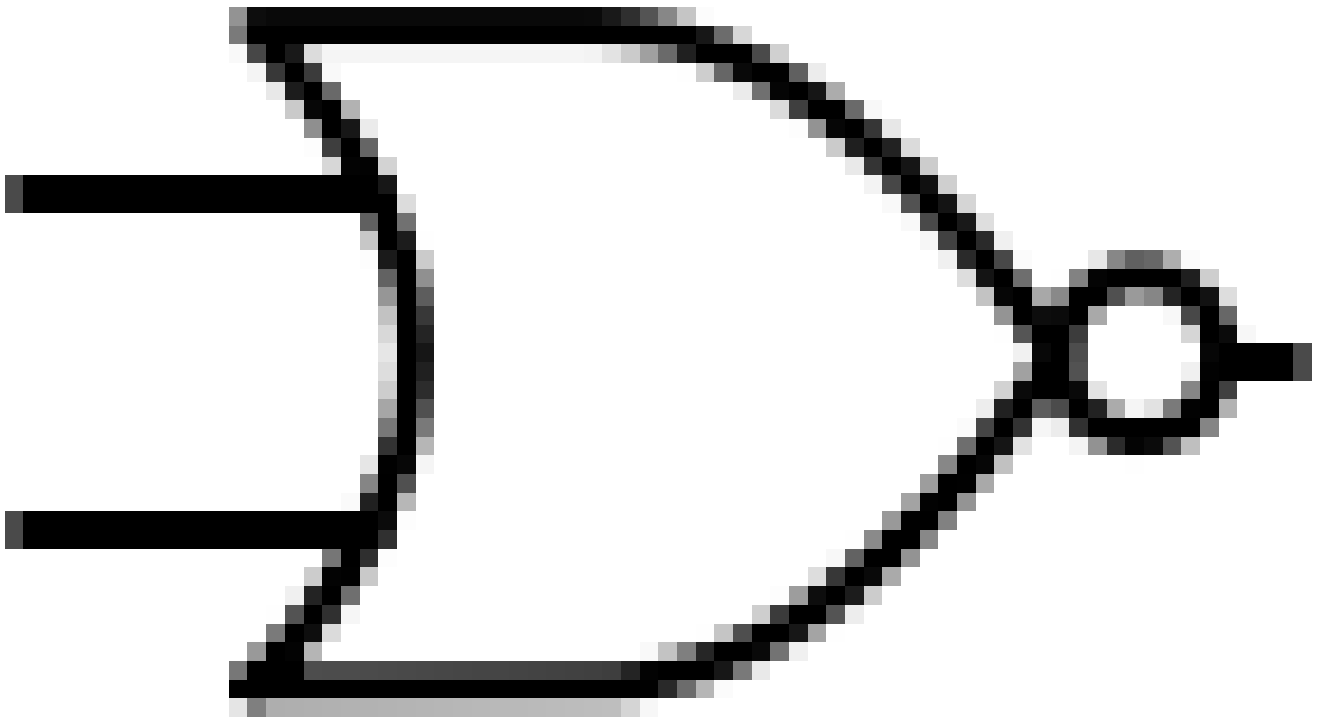Question 23:

What is the output of the NOR gate with inputs 0, 0?



Options:


1. 0

2. 1

Correct Answer: 1

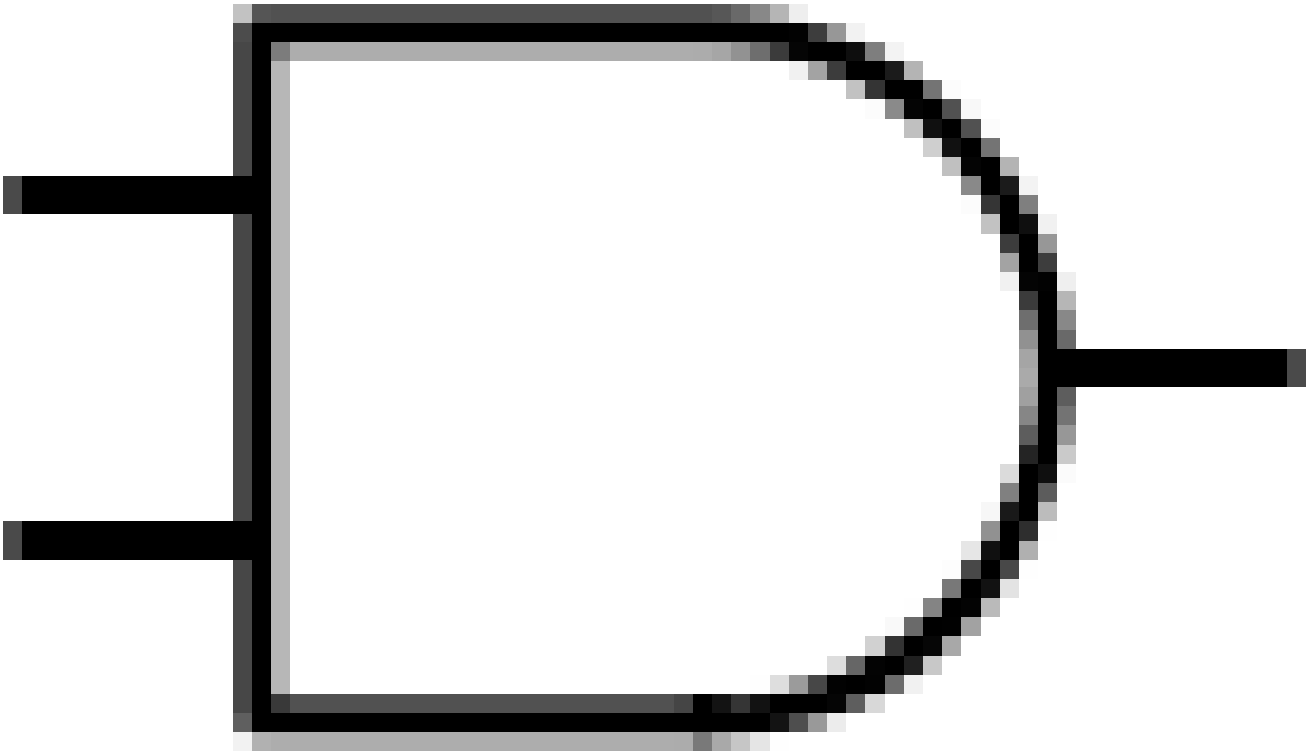Question 24:

What is the output of the AND gate with inputs 0, 1?



Options:

1. 1

2. 0


Correct Answer: 0

Question 25:

Are these two circuits equivalent?

Expression 1: (not c)

Expression 2: (c xnor a)

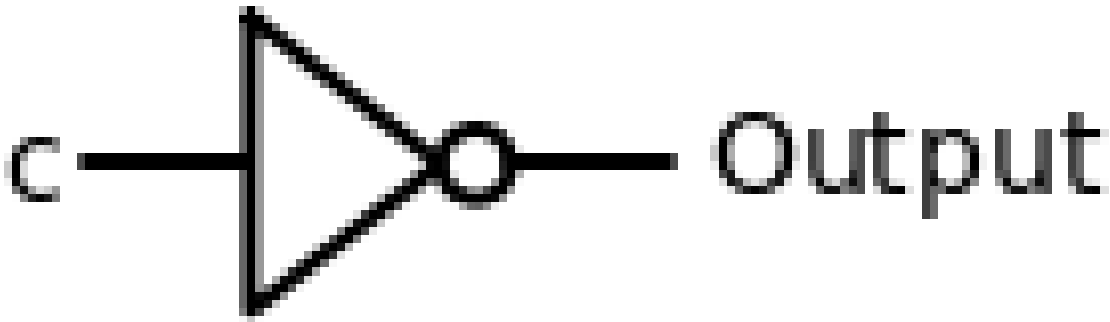

Options:

1. Yes
2. No

Correct Answer: no

Question 26:

Are these two circuits equivalent?

Expression 1: $(a \text{ nand } c)$

Expression 2: $(a \text{ nand } c)$




Options:

1. Yes
2. No

Correct Answer: yes

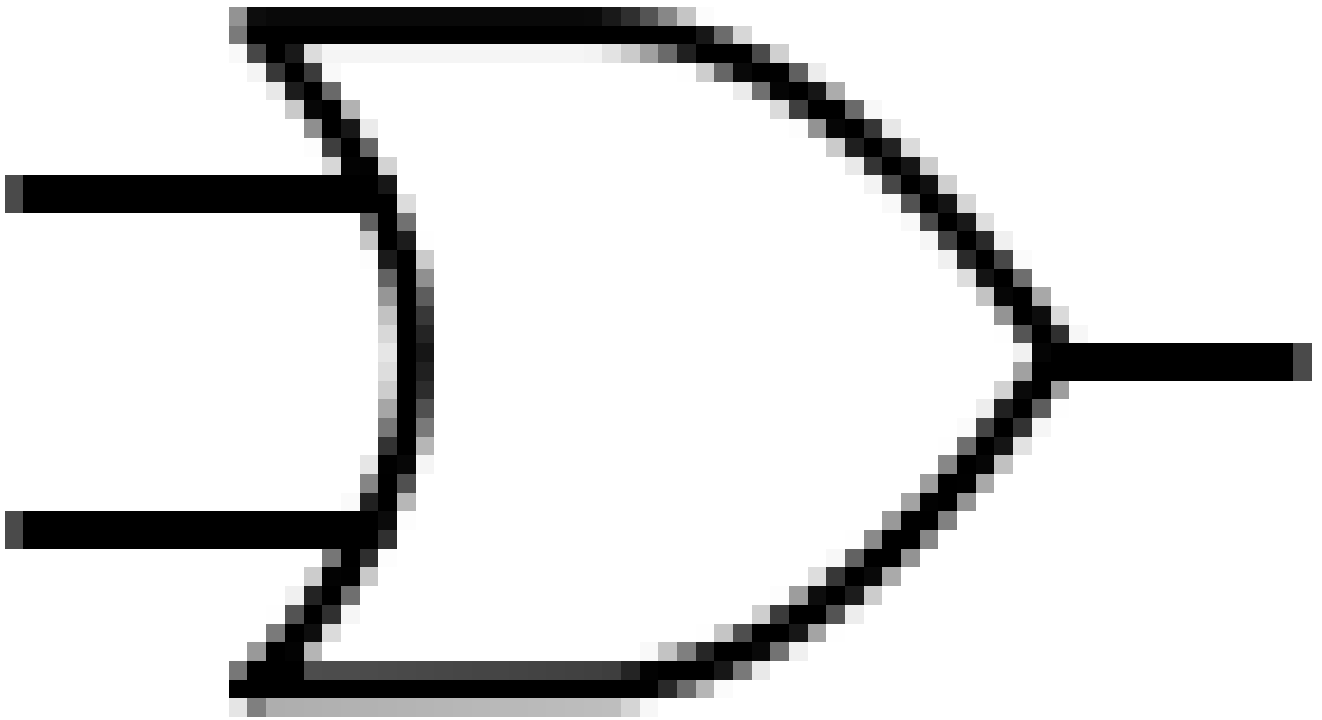Question 27:

What is the output of the OR gate with inputs 1, 1?



Options:

1. 0

2. 1


Correct Answer: 1


Question 28:

Are these two circuits equivalent?

Expression 1: $((a \text{ and } b) \text{ xnor } (a \text{ xor } a)) \text{ nor } ((c \text{ or } b) \text{ and } (a \text{ xnor } a))$

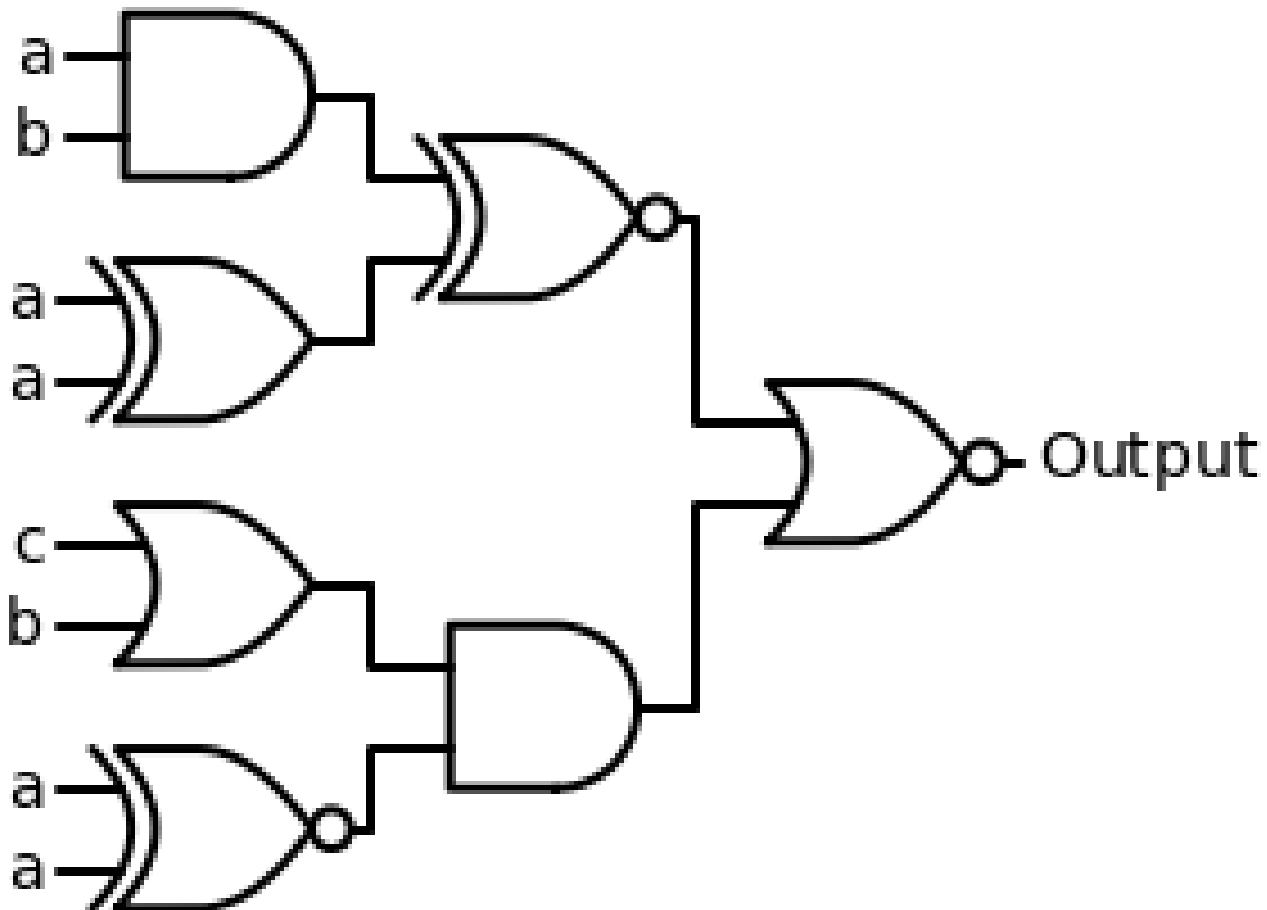Expression 2: $((a \text{ and } b) \text{ xnor } (a \text{ xor } a)) \text{ nor } ((c \text{ or } b) \text{ and } (a \text{ xnor } a))$



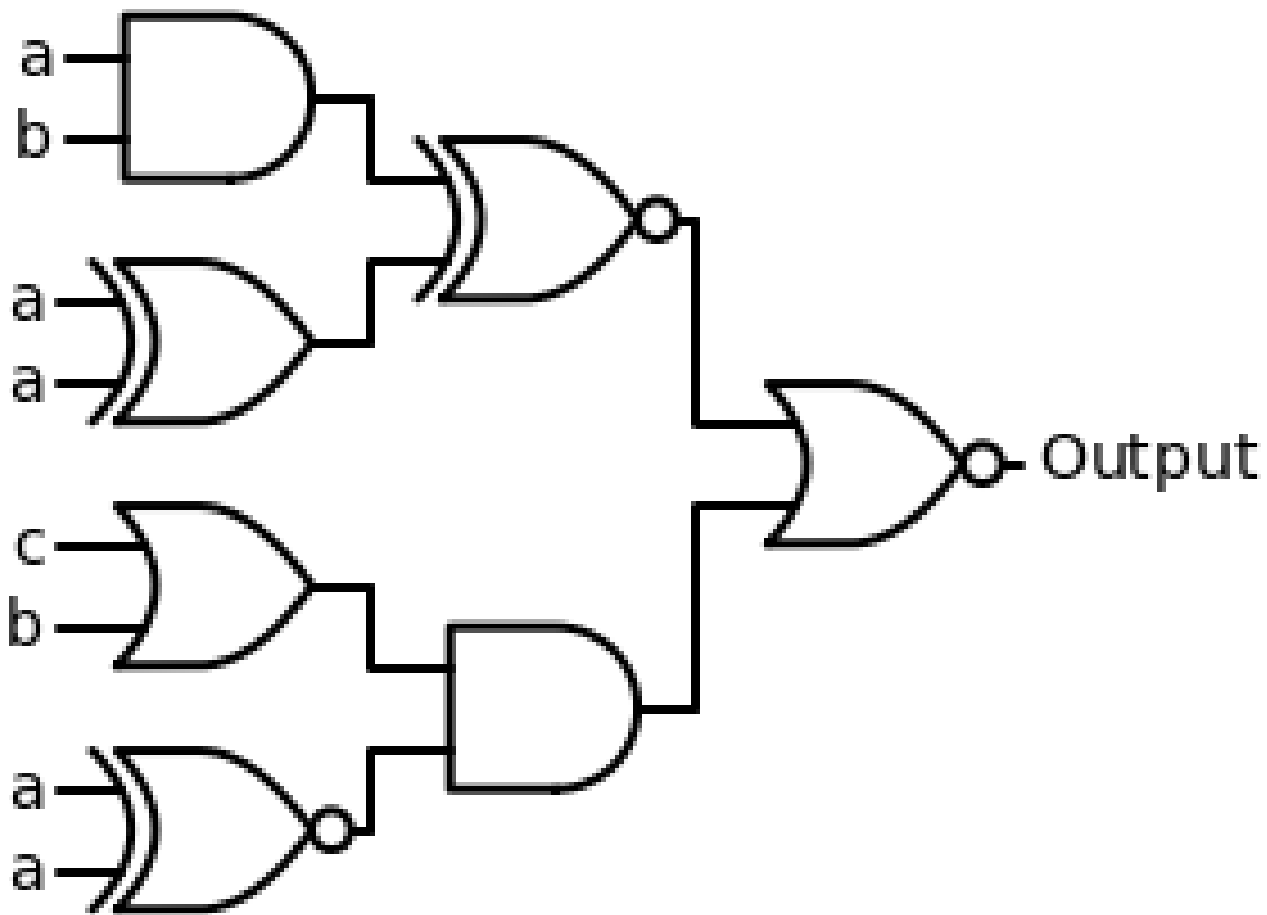


Options:

1. Yes
2. No

Correct Answer: yes

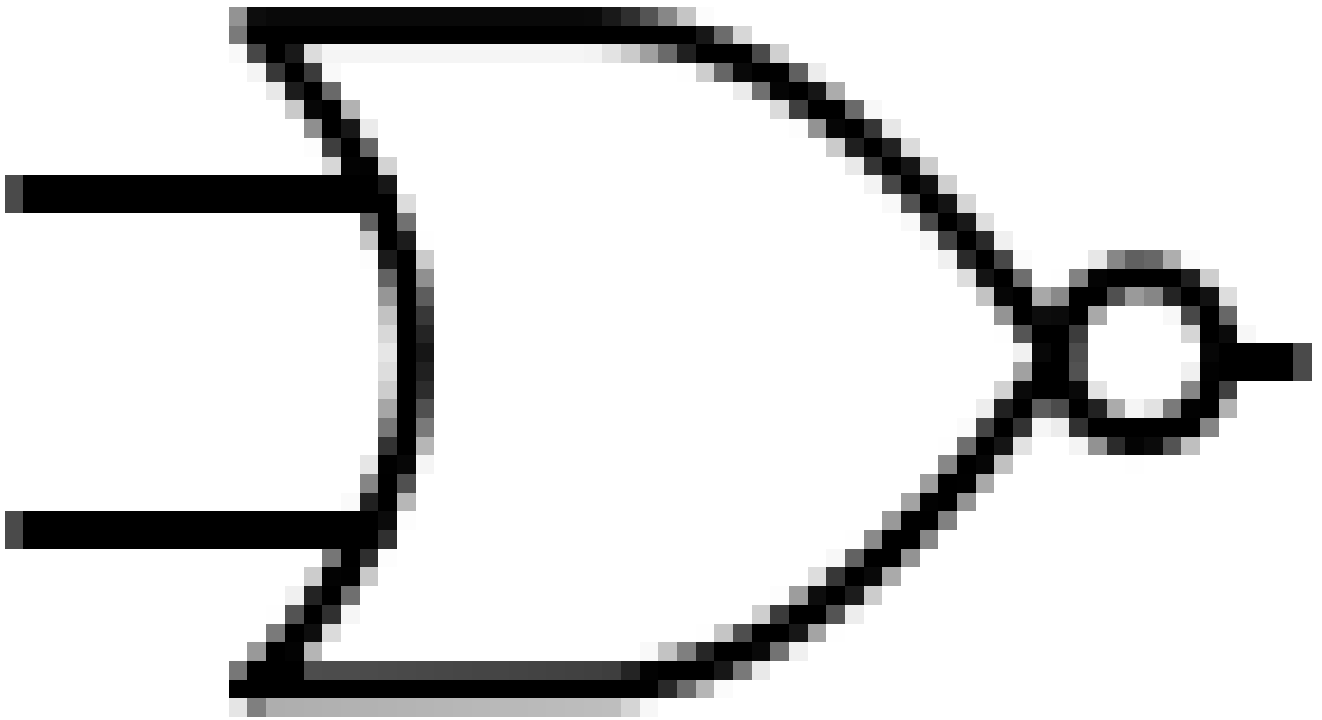Question 29:

What is the output of the NOR gate with inputs 0, 1?



Options:

1. 1

2. 0


Correct Answer: 0

Question 30:

Are these two circuits equivalent?

Expression 1: (b and c)

Expression 2: (c xnor c)

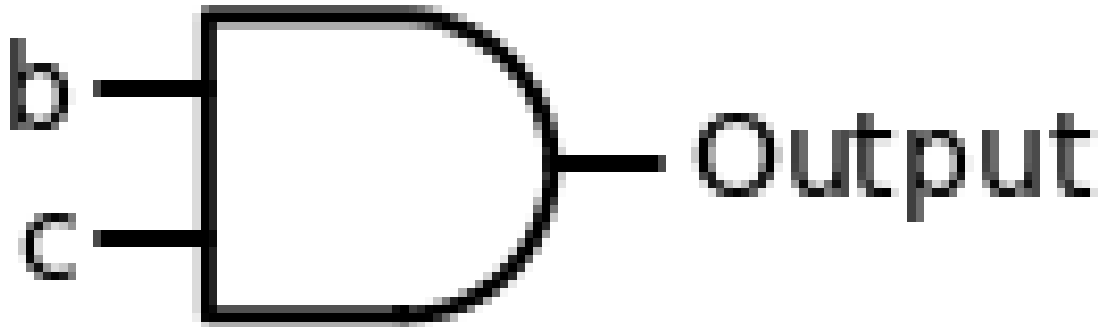


Options:

1. Yes
2. No

Correct Answer: no

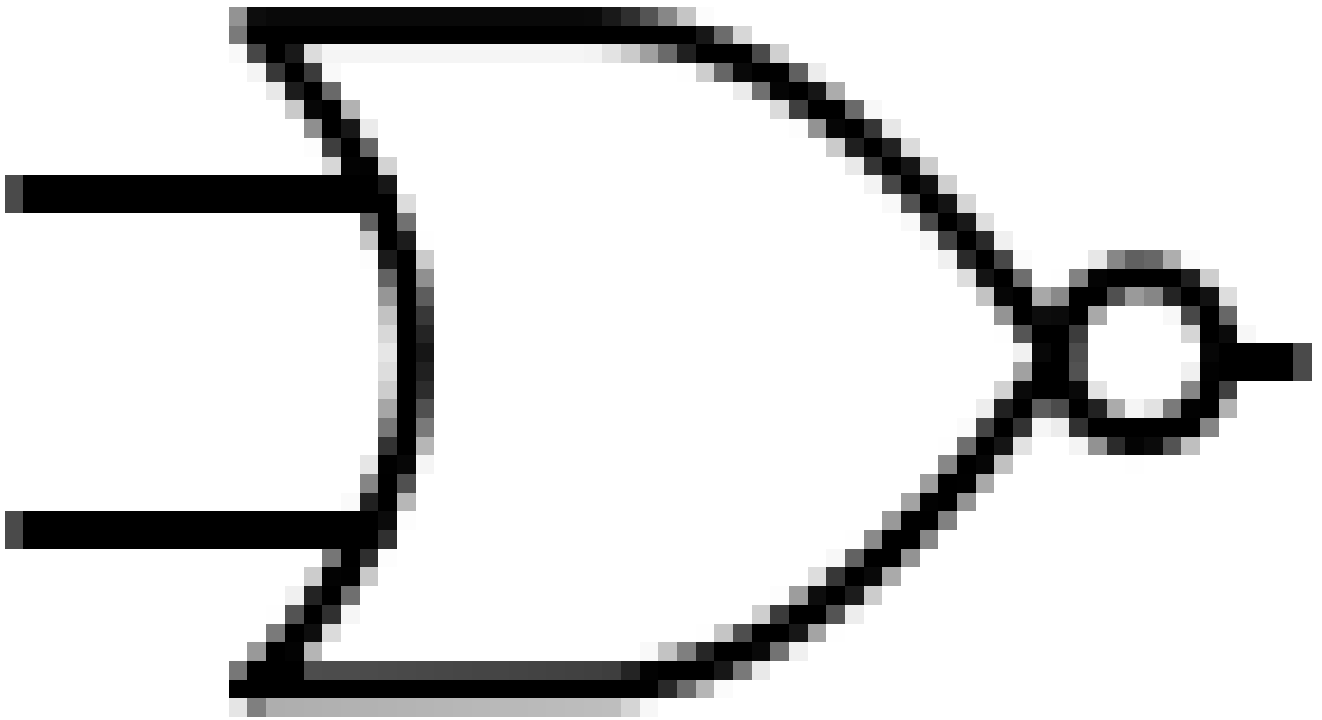Question 31:

What is the output of the NOR gate with inputs 0, 0?



Options:


1. 0

2. 1

Correct Answer: 1

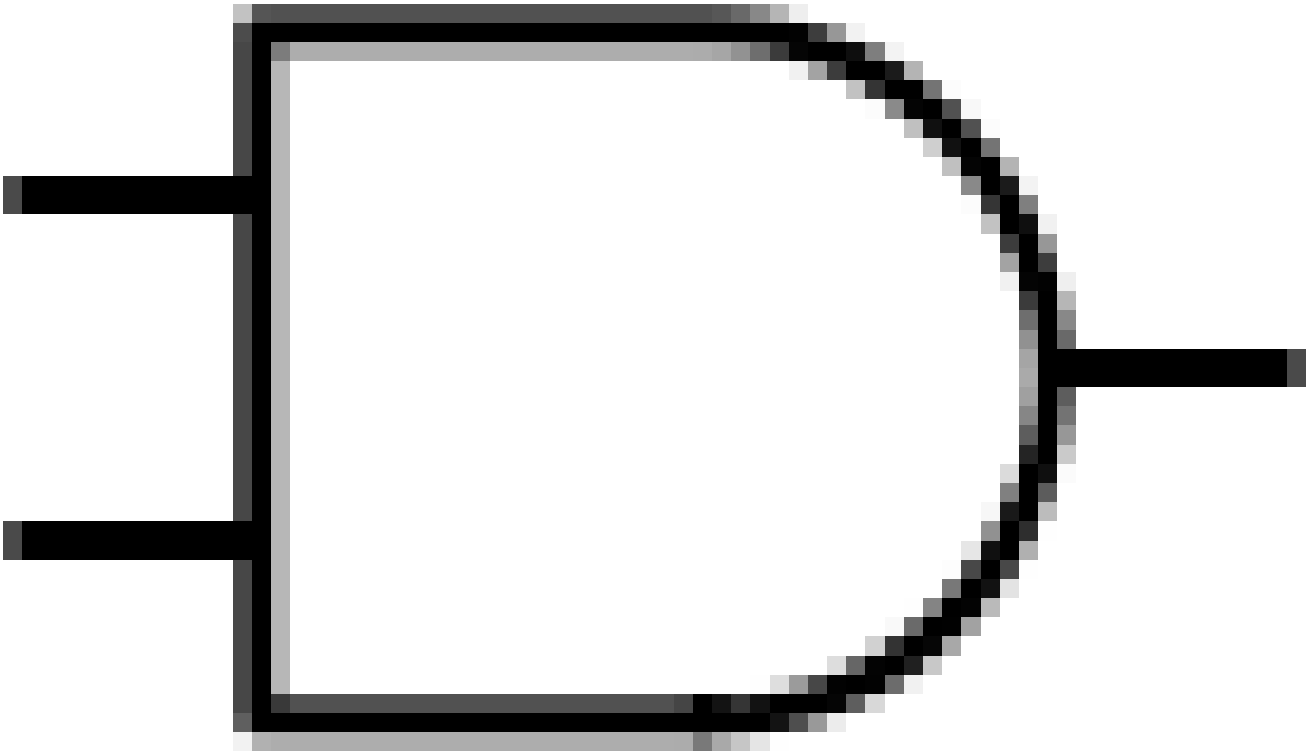Question 32:

What is the output of the AND gate with inputs 1, 0?



Options:


1. 0

2. 1

Correct Answer: 0

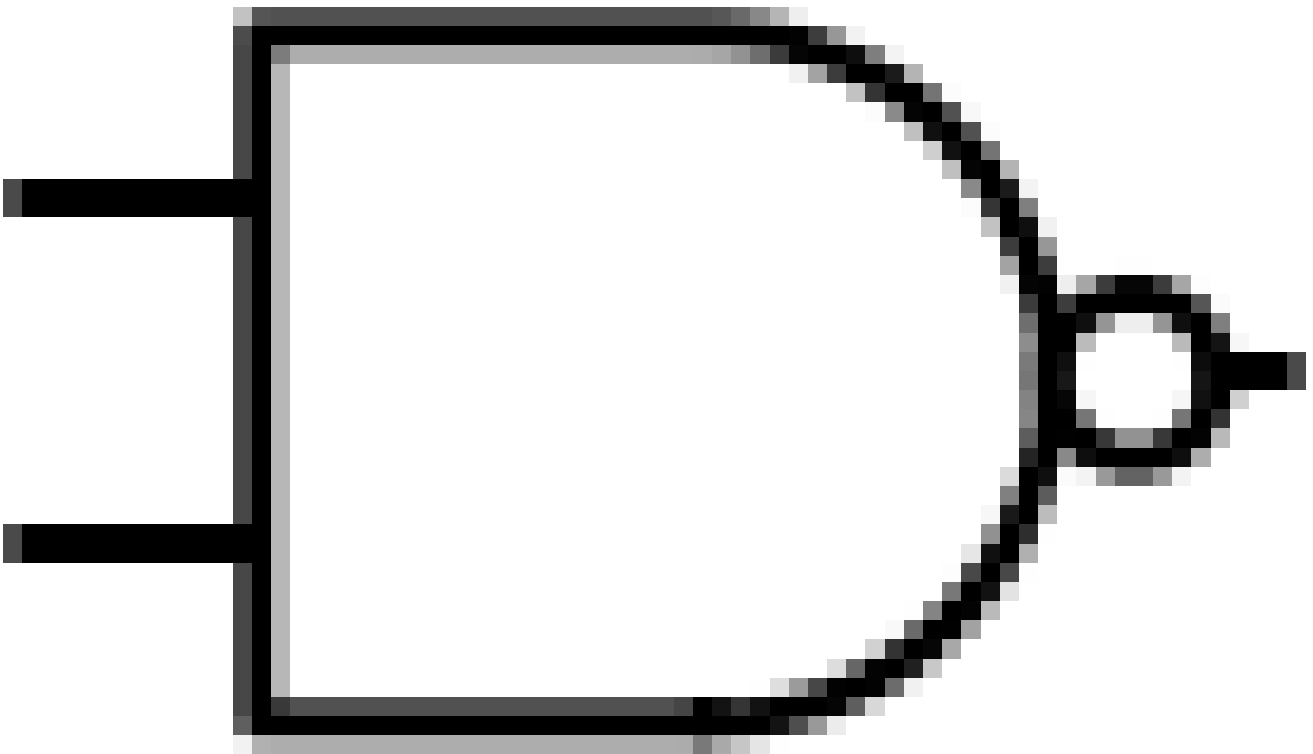Question 33:

What is the output of the NAND gate with inputs 1, 0?



Options:

1. 1

2. 0



Correct Answer: 1

Question 34:

Are these two circuits equivalent?

Expression 1: $((a \text{ or } c) \text{ and } (a \text{ or } a))$

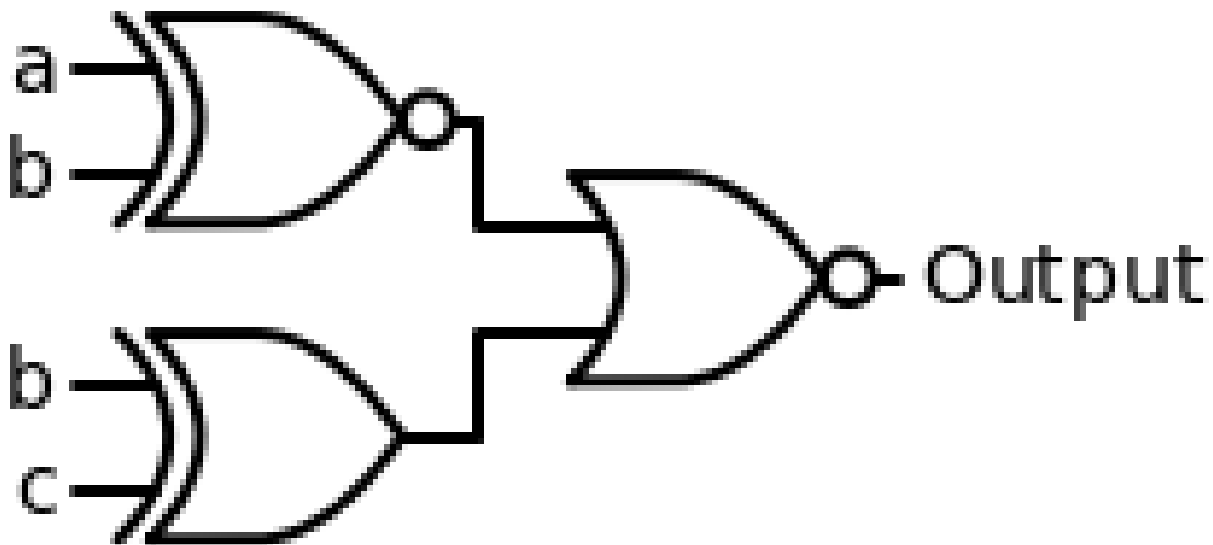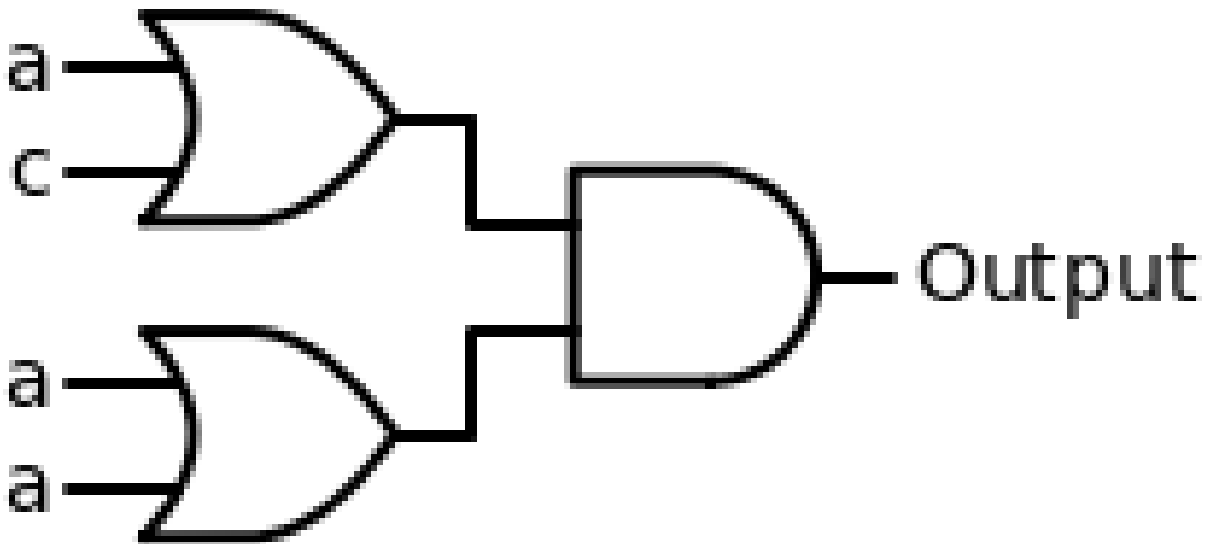Expression 2: $((a \text{ xnor } b) \text{ nor } (b \text{ xor } c))$



Options:

1. Yes
2. No


Correct Answer: no


Question 35:

Are these two circuits equivalent?

Expression 1: $((c \text{ nor } a) \text{ xnor } (b \text{ nor } a)) \text{ xnor } ((b \text{ or } c) \text{ xnor } (a \text{ xnor } a))$

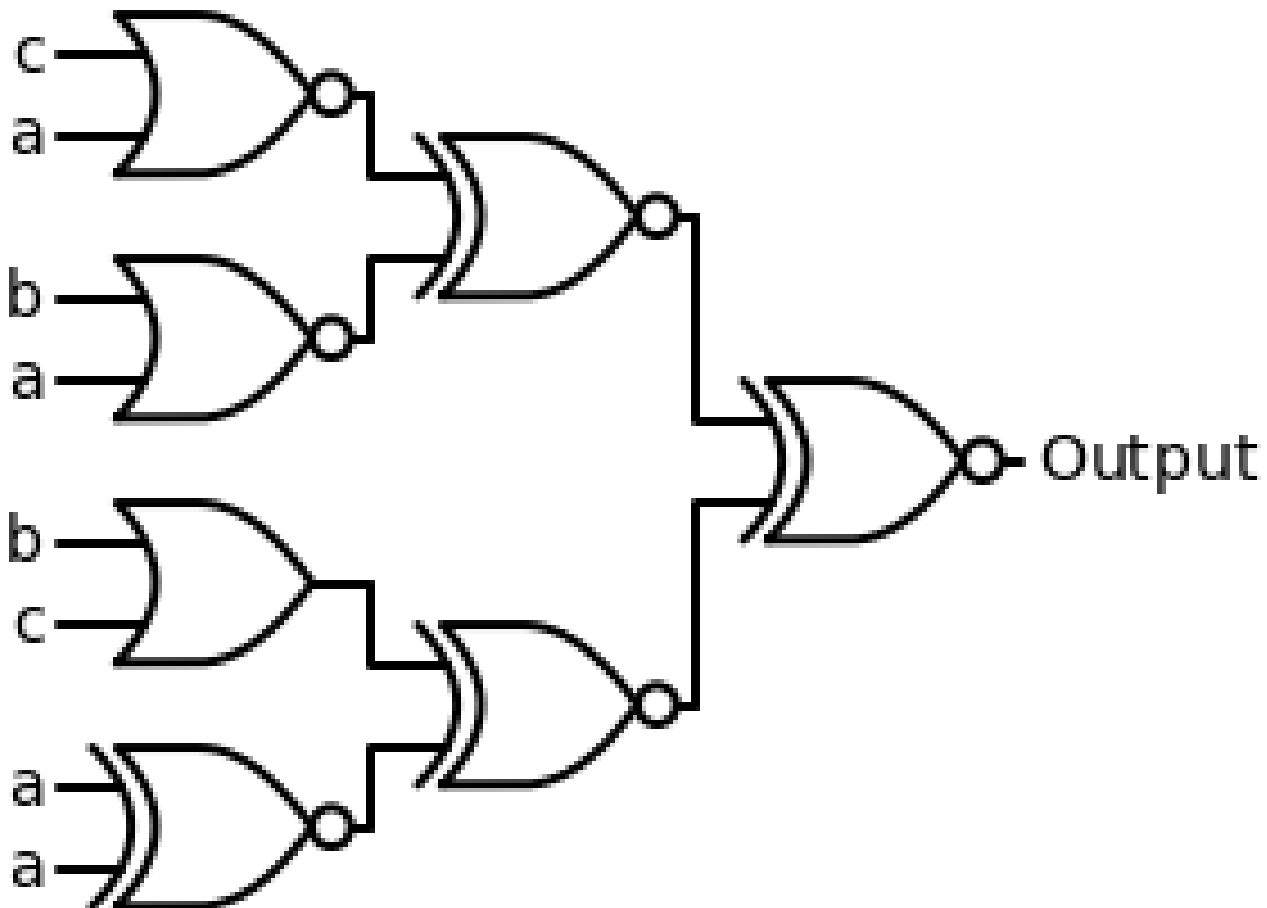Expression 2: $((b \text{ nor } a) \text{ xnor } (c \text{ and } b)) \text{ nand } ((a \text{ nor } c) \text{ xor } (a \text{ xor } b))$



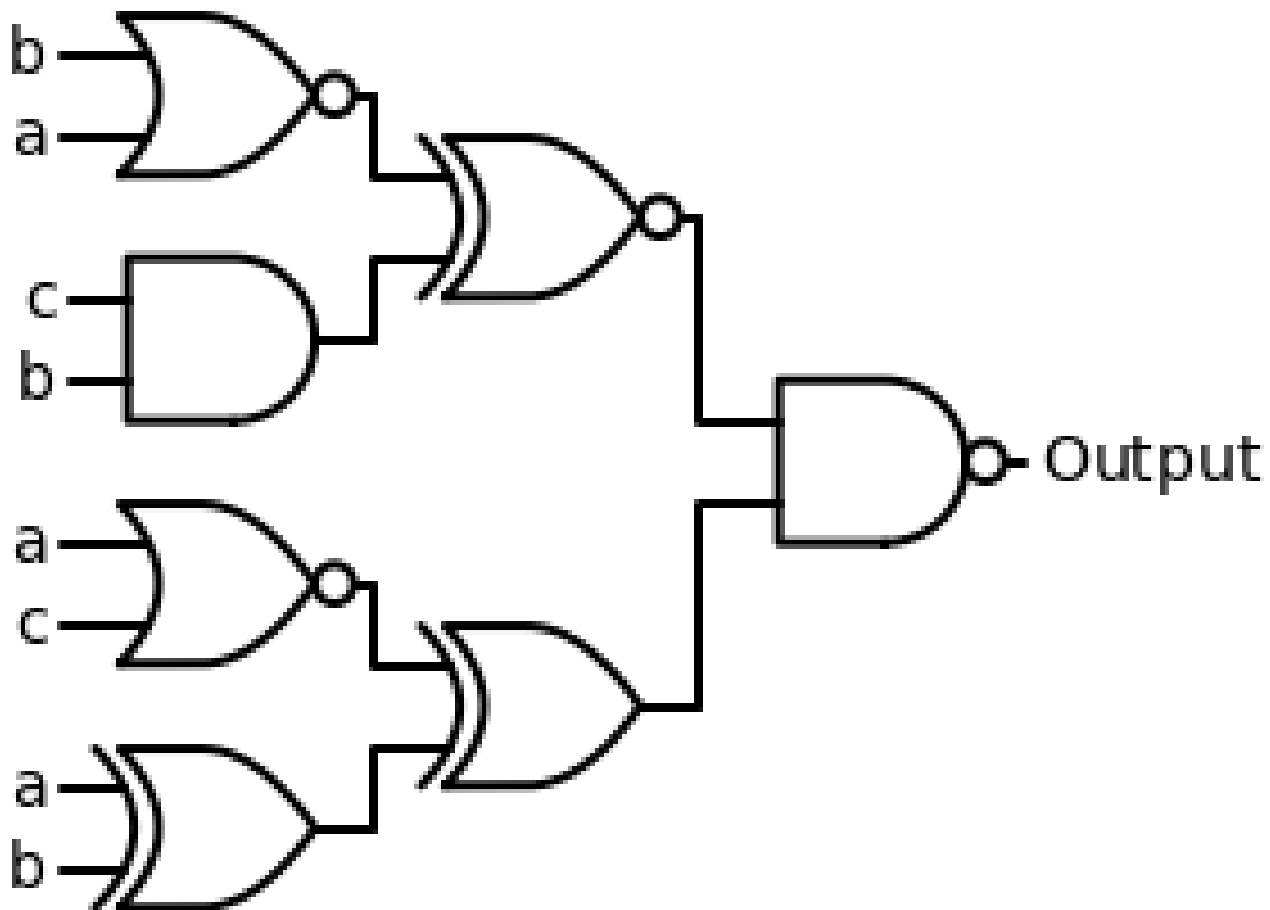


Options:

1. Yes
2. No

Correct Answer: no

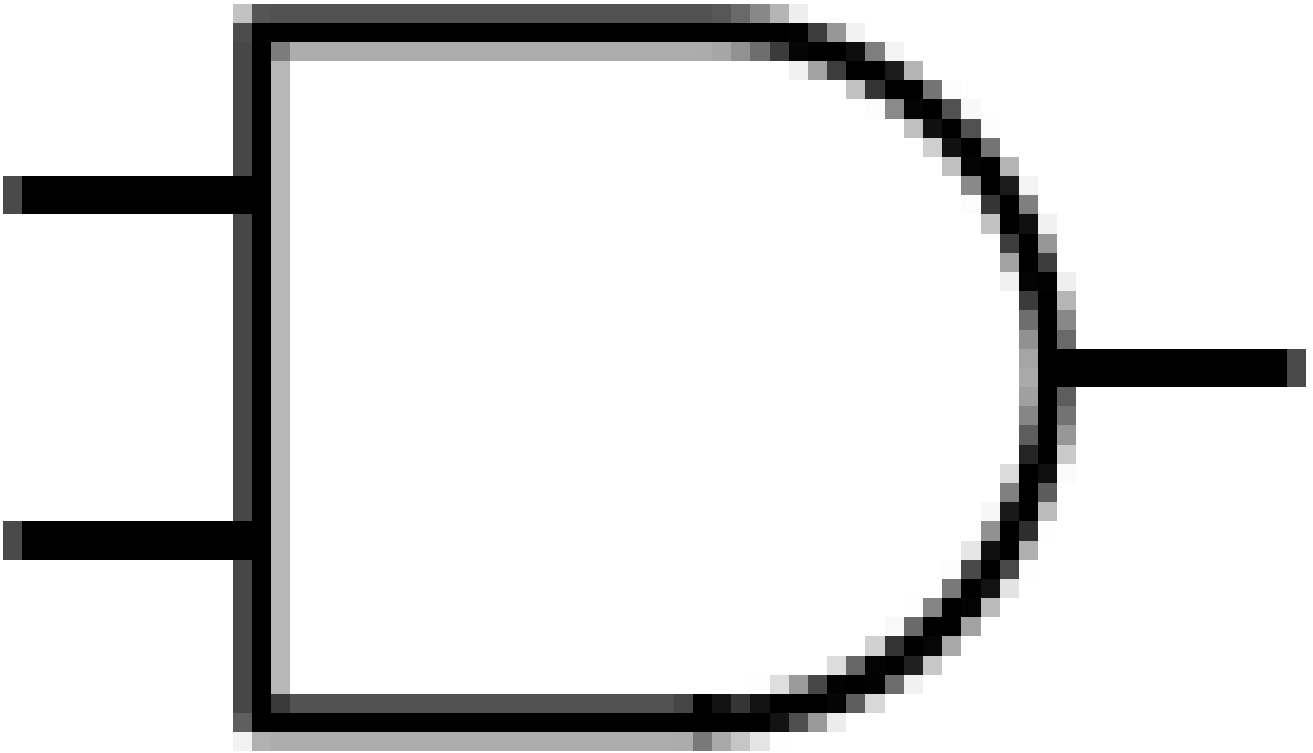Question 36:

What is the output of the AND gate with inputs 0, 0?



Options:


1. 0

2. 1

Correct Answer: 0

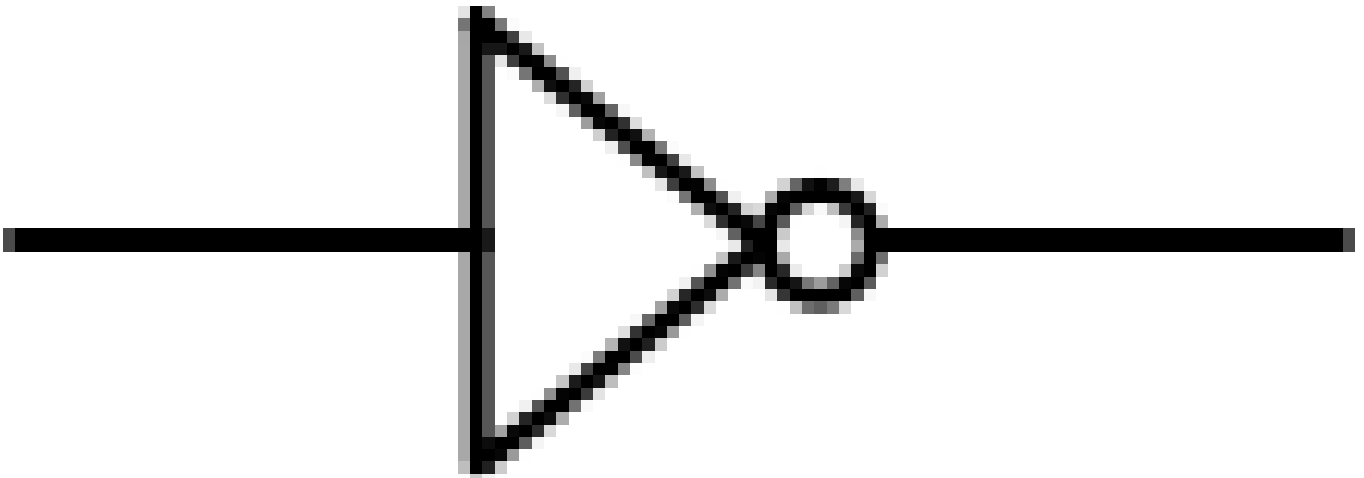Question 37:

What is the output of the NOT gate with input 0?



Options:

1. 0

2. 1



Correct Answer: 1

Question 38:

Are these two circuits equivalent?

Expression 1: (not b)

Expression 2: (c nor b)

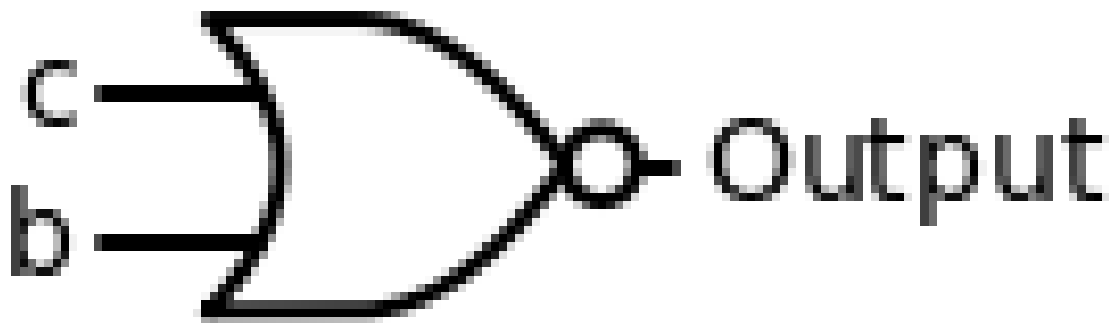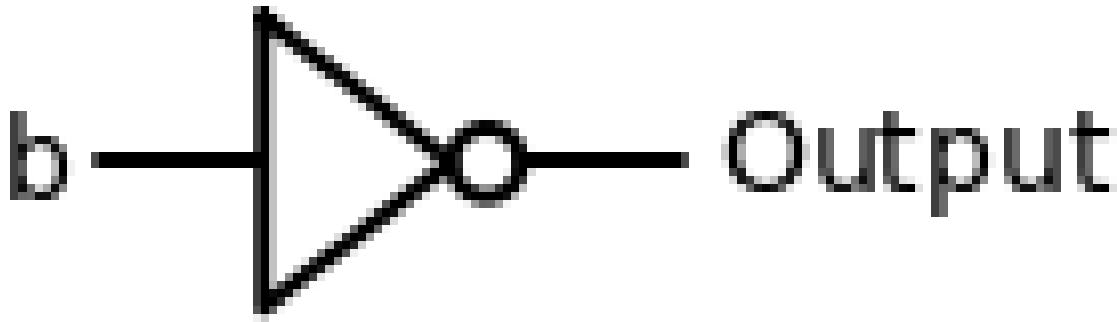

Options:

1. Yes
2. No



Correct Answer: no

Question 39:

Are these two circuits equivalent?

Expression 1: (b and c)

Expression 2: ((b xnor c) and (c or a))

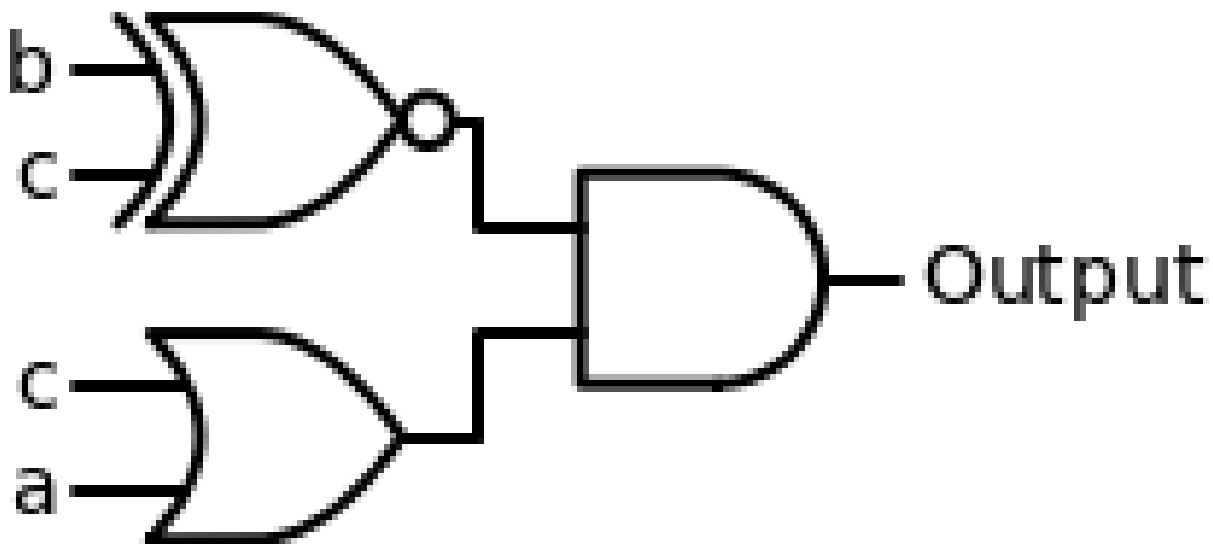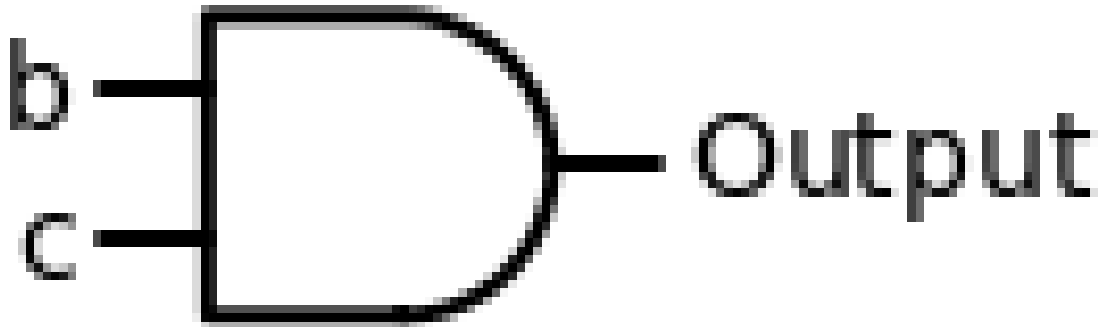


Options:

1. Yes
2. No

Correct Answer: no

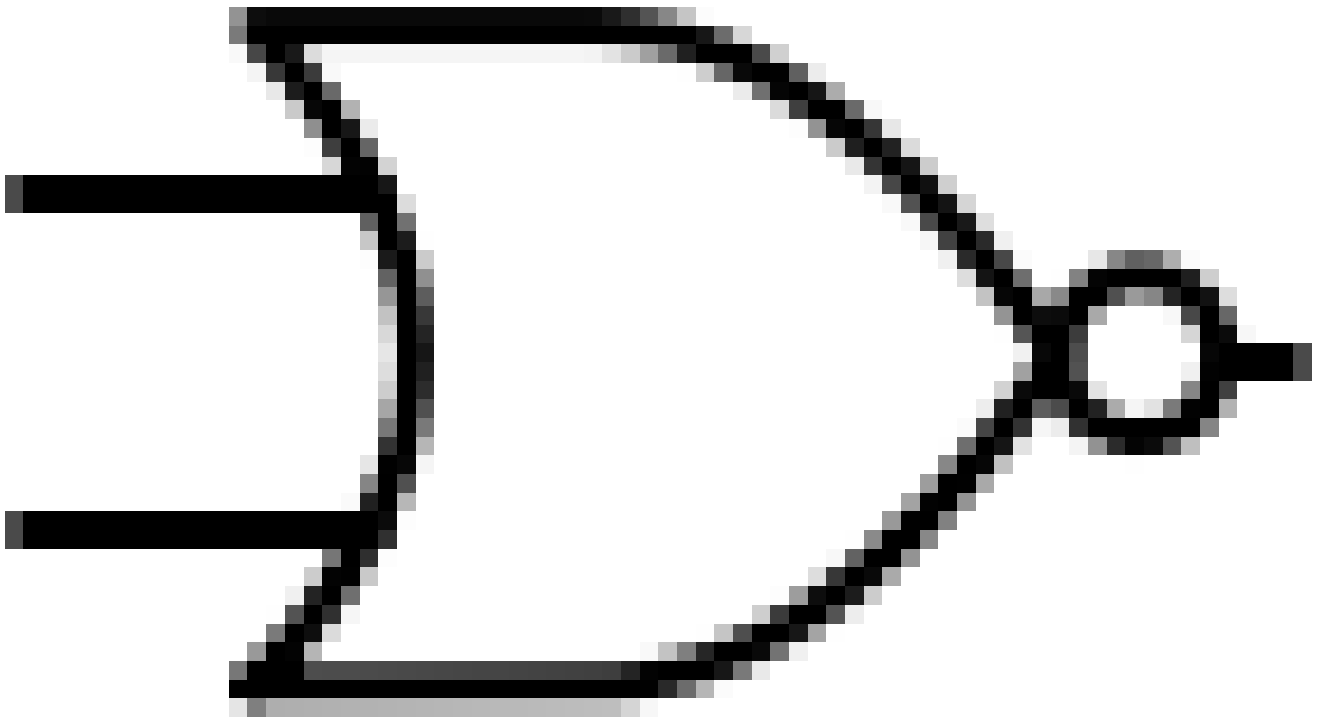Question 40:

What is the output of the NOR gate with inputs 0, 0?



Options:

1. 0

2. 1

Correct Answer: 1