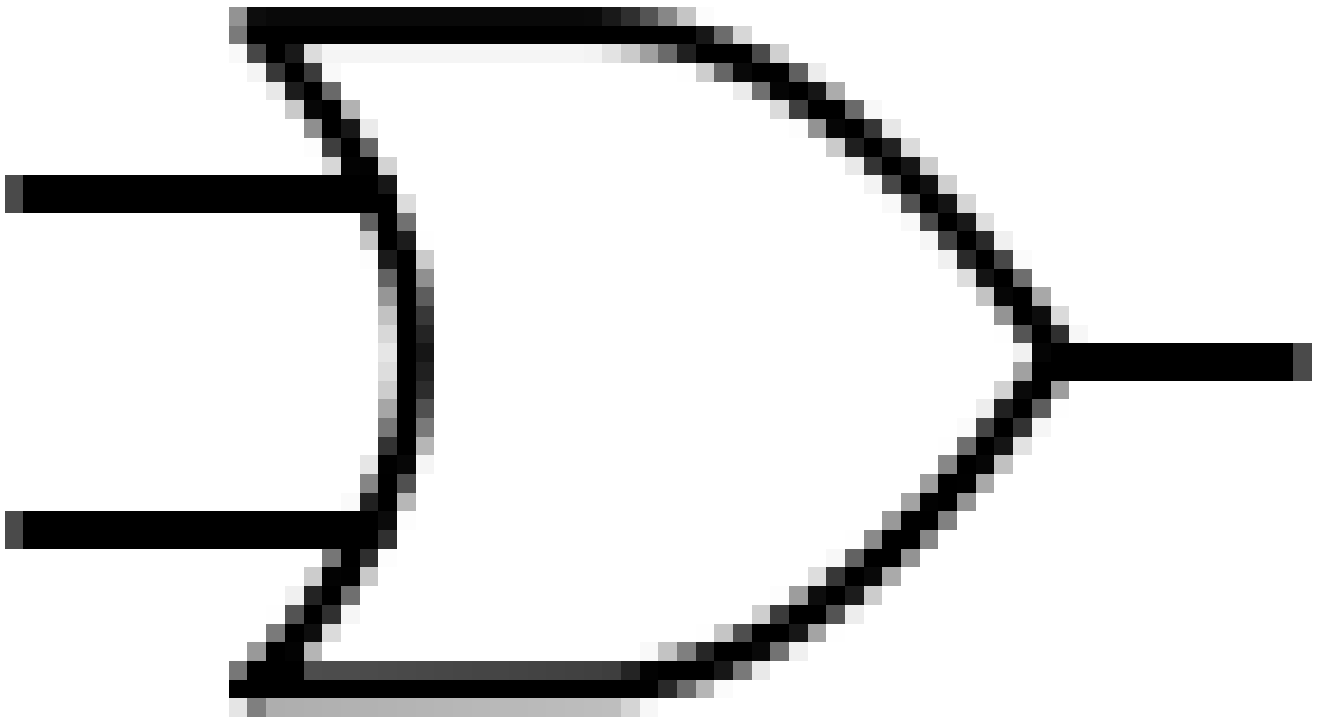


### Question 1:

What is the output of the OR gate with inputs 0, 1?



Options:

1. 1

2. 0



Correct Answer: 1

Question 2:

Are these two circuits equivalent?

Expression 1:  $((c \text{ xnor } a) \text{ nand } (b \text{ and } c))$

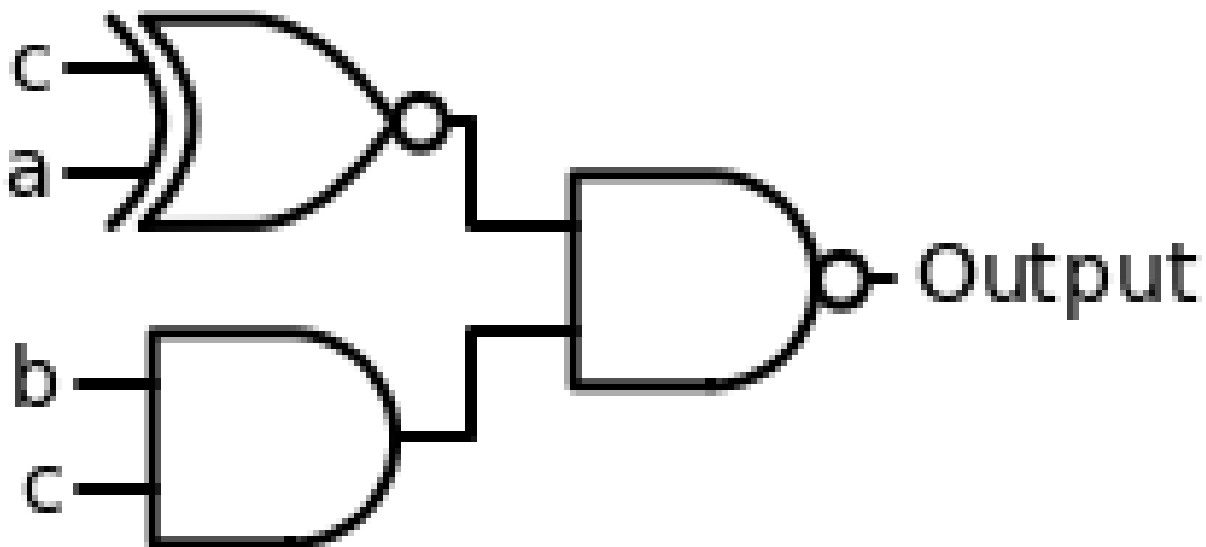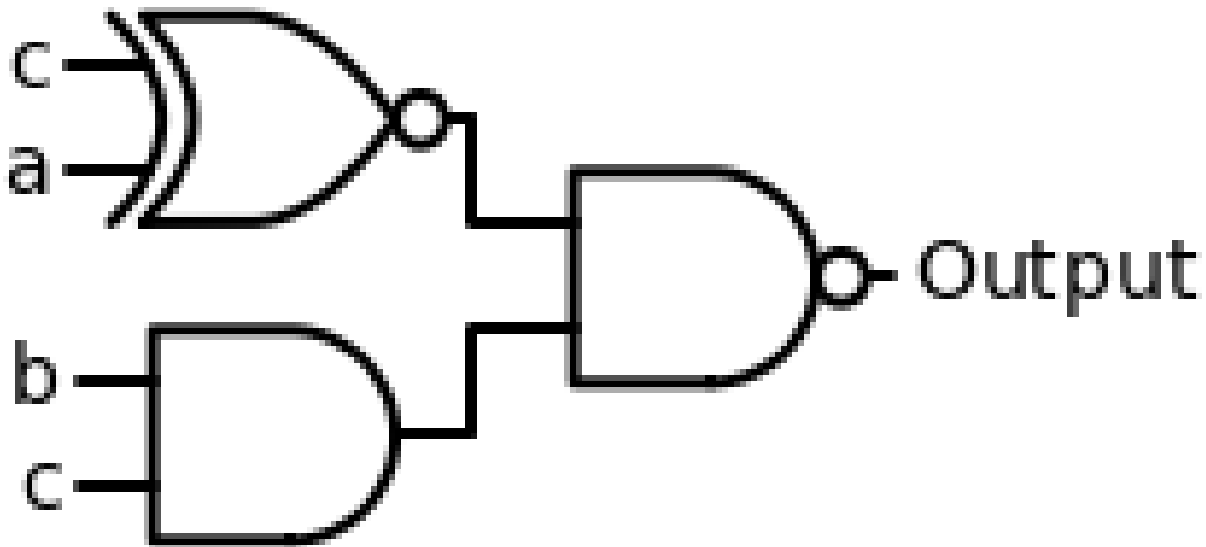Expression 2:  $((c \text{ xnor } a) \text{ nand } (b \text{ and } c))$




Options:

1. Yes
2. No

Correct Answer: yes
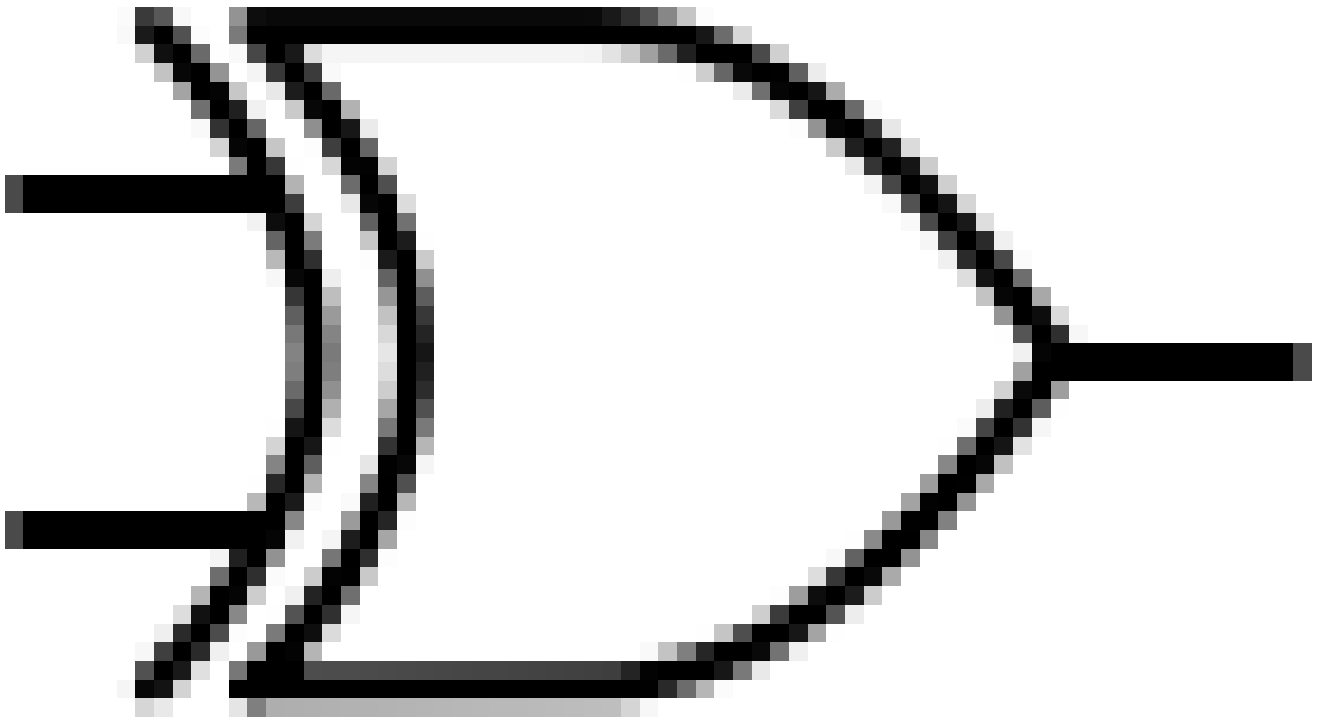
### Question 3:

What is the output of the XOR gate with inputs 0, 1?



Options:

1. 0

2. 1

Correct Answer: 1